



Introduction & Motivation

CPEN 230 – Introduction to Digital Logic


Digital Abstraction

Abstraction = hiding details when they are not important
Abstraction helps to manage complexity

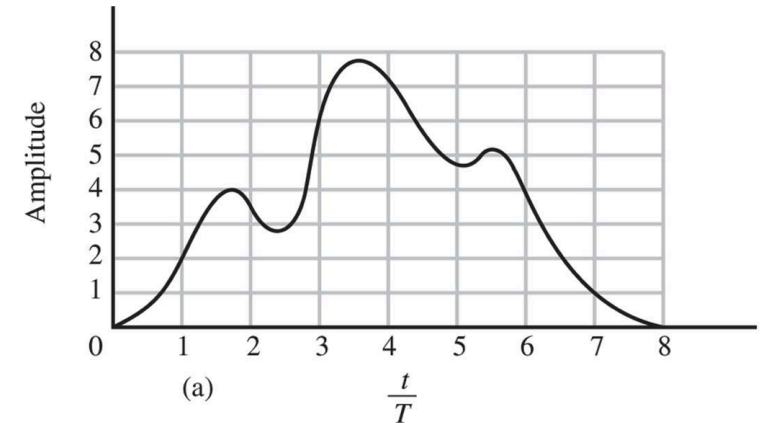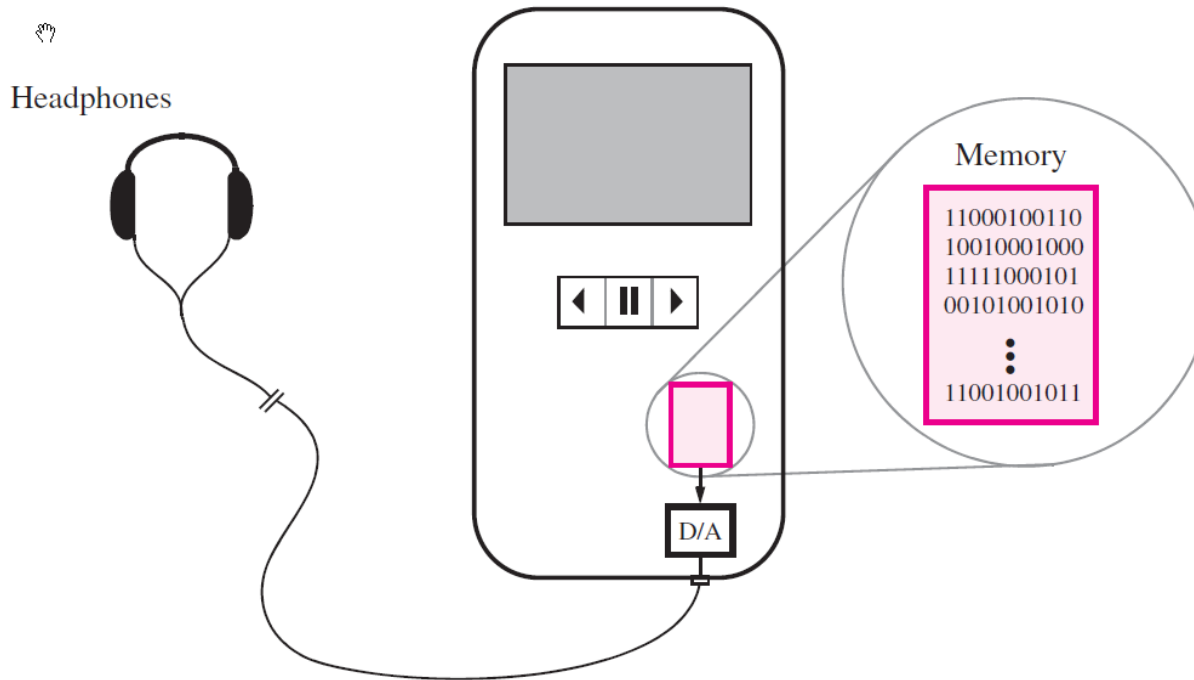- The world is “digital” with analog at the edges



(a) analog signal

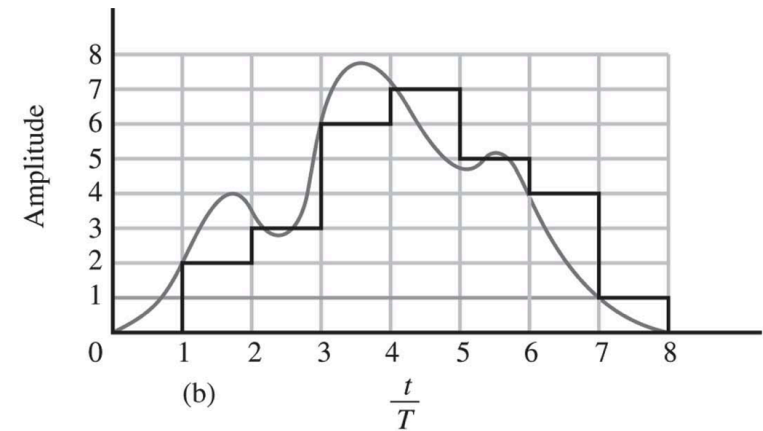

(b) digital signal

Common Applications

- Desktop Computers
- Notebooks
- Smartphones
- Embedded Systems



CPEN 230
Digital Logic

CPEN 231
Microcontrollers

EENG 406
Integrated
Circuits

EENG 412
Digital Controls

CPEN 342
Embedded
Systems


CPEN 430
Digital Systems
Design

EENG 422
Digital
Communications


CPEN/CPSC 431
Computer
Architecture

EENG 424
Digital Signal
Processing


Moore's Law

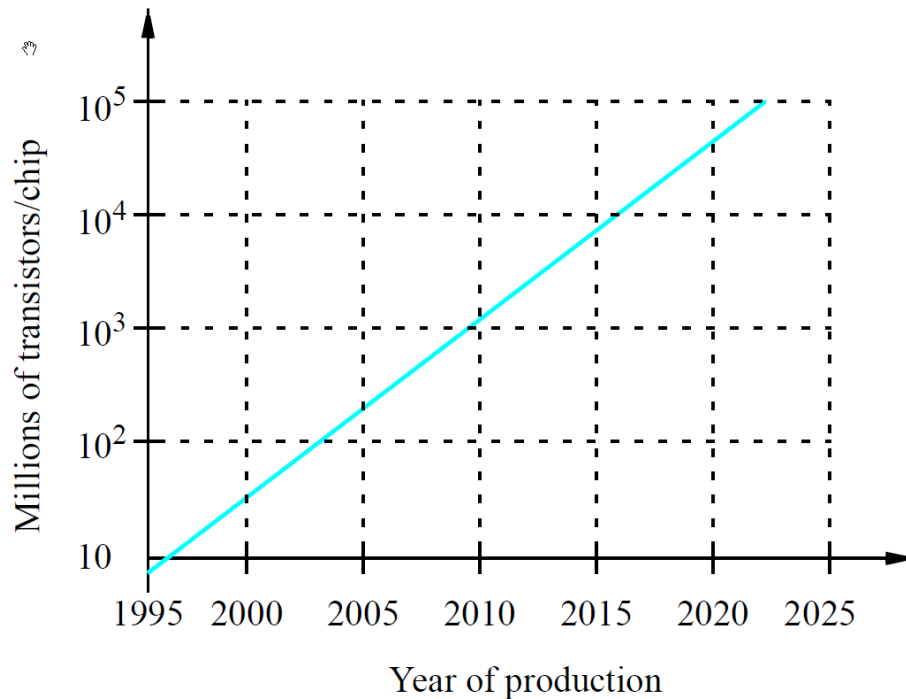

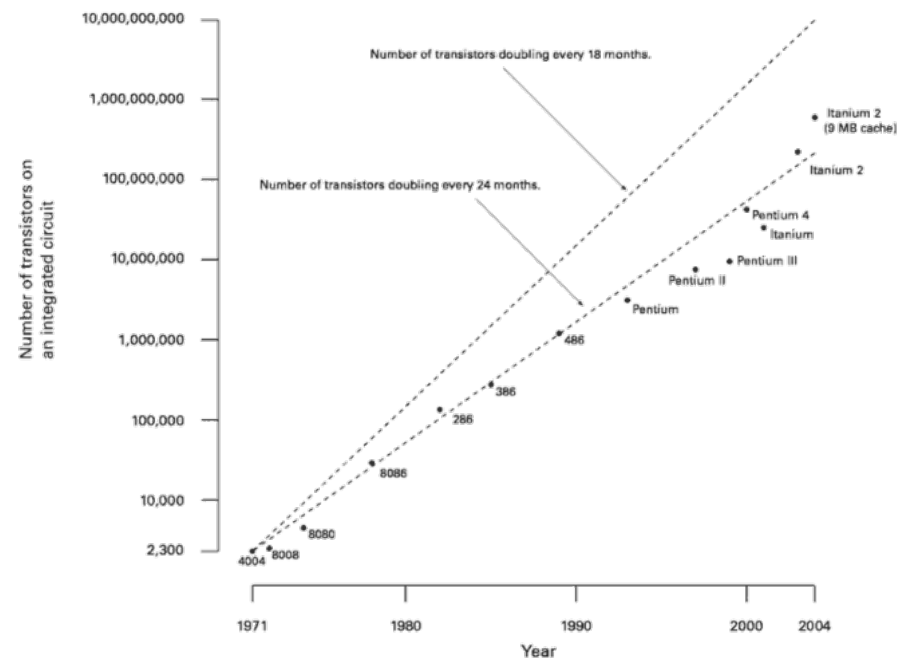An estimate of the maximum number of transistors per chip over time.



Enabling Technology

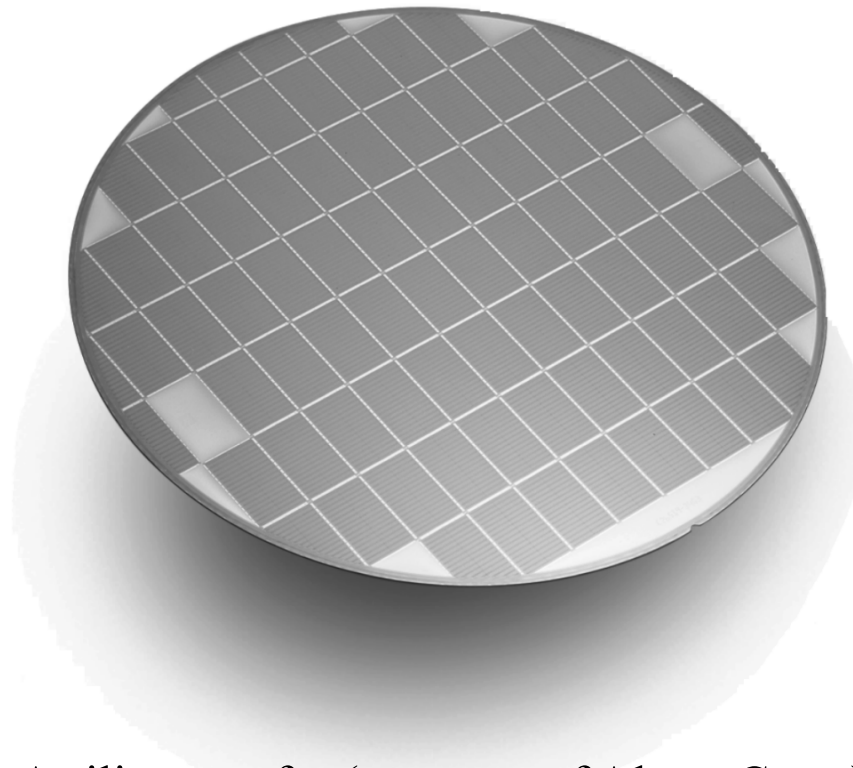

A silicon wafer (courtesy of Altera Corp.).

- The focus of this class is on digital circuits: i.e. the interconnection of logic gates

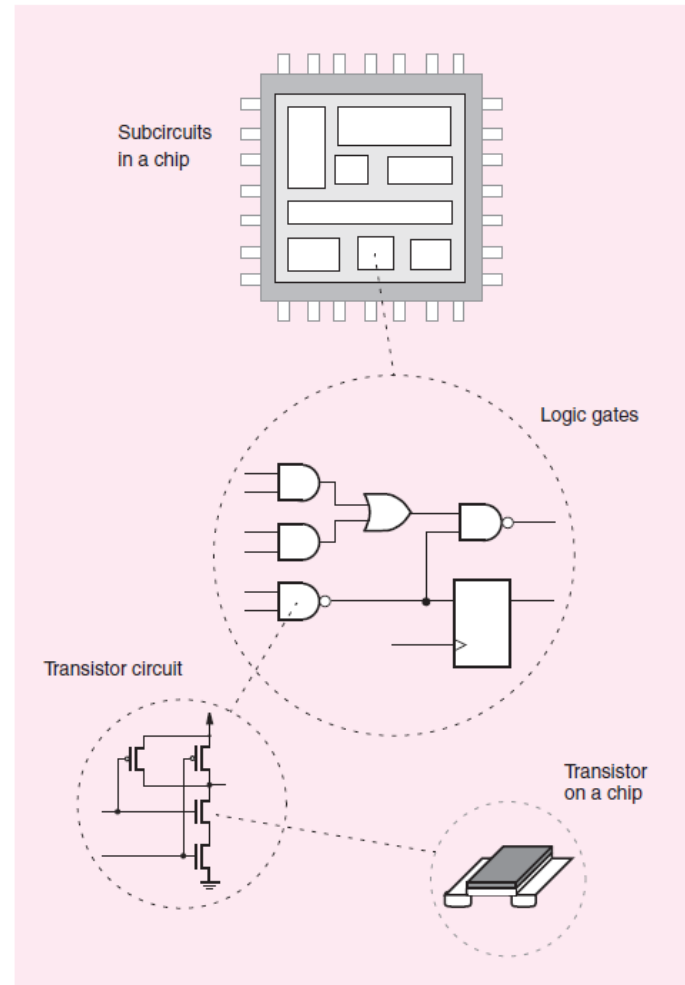



Figure 1.4 A digital hardware system (Part b).



An example of chip (CPU)

CAD Tools

Typical FPGA HDL-based Flow

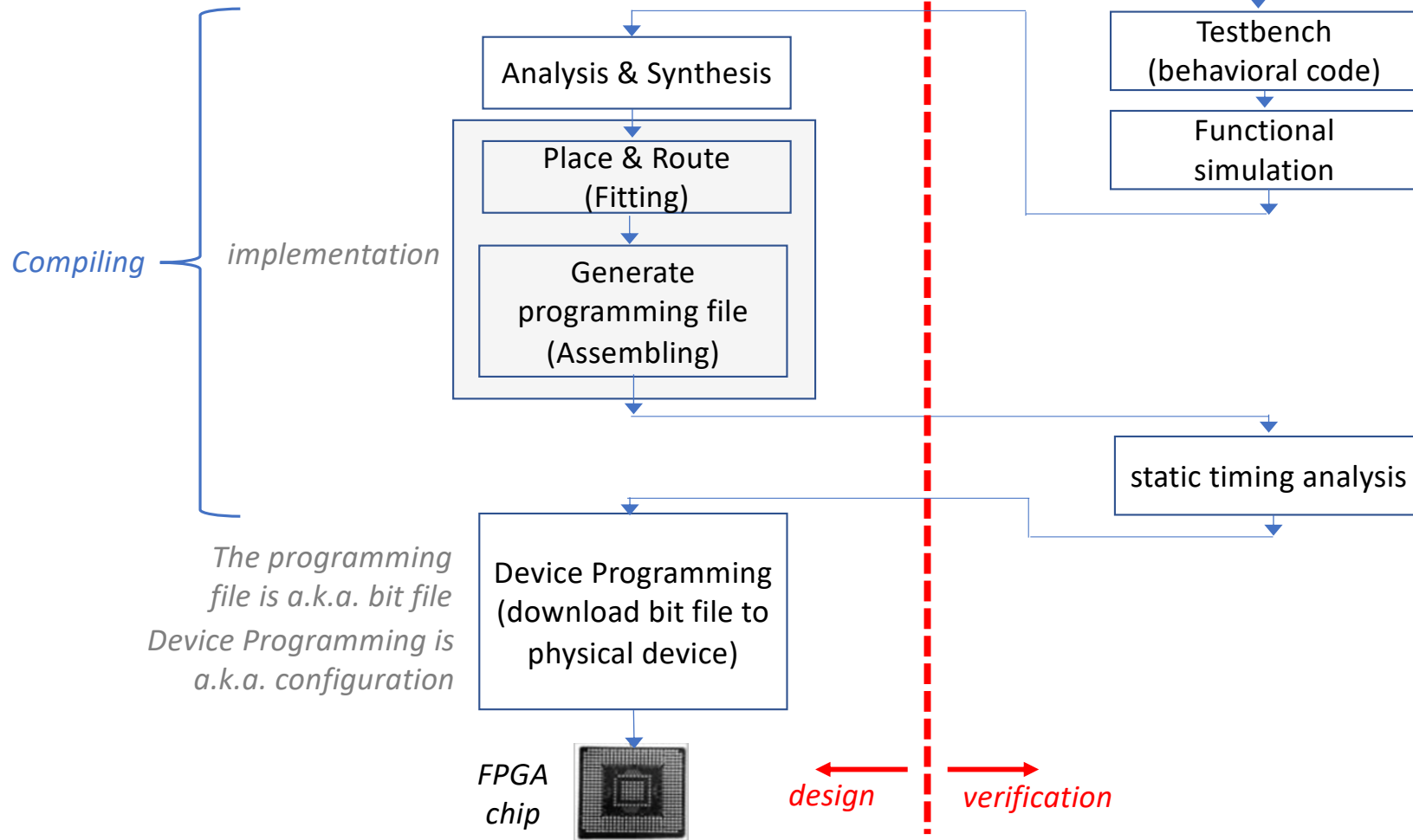

CAD Tools

The flow is iterative!


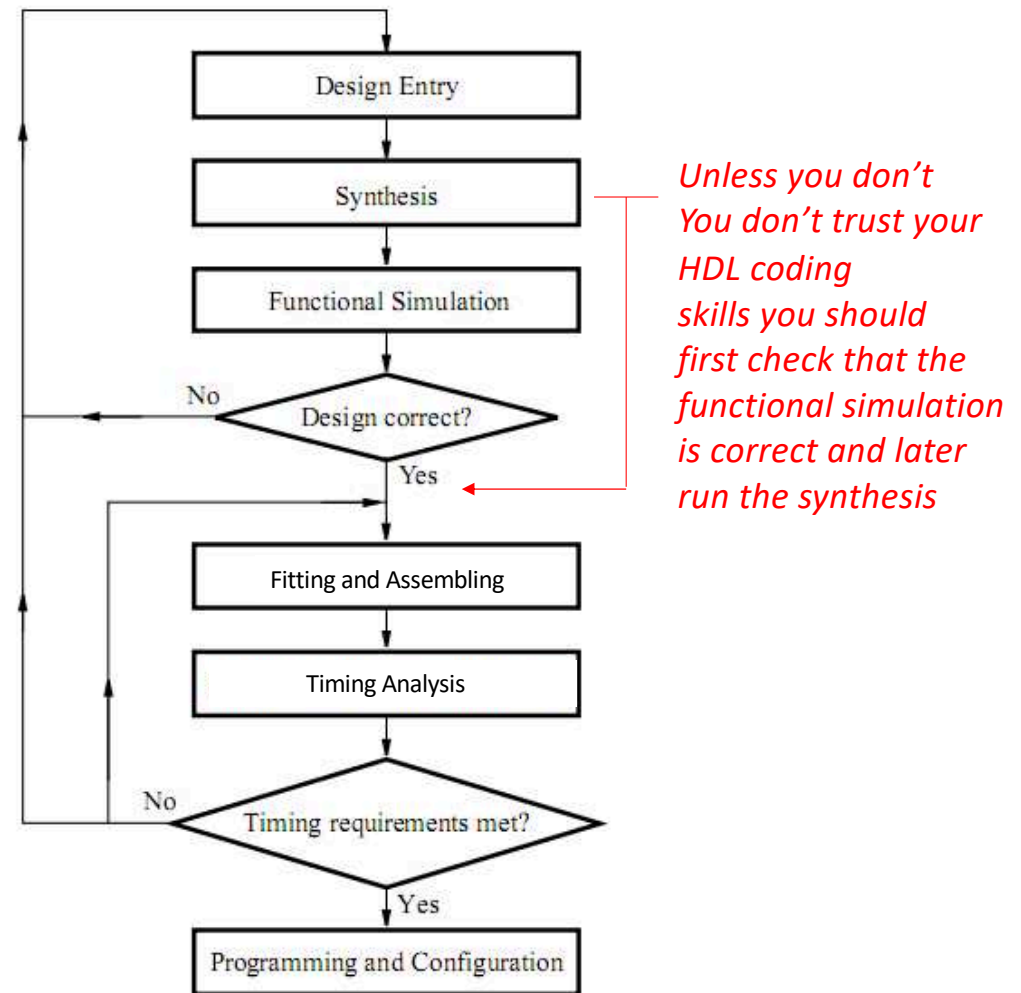


Figure 1. Typical CAD flow.

 

An FPGA (Field Programmable Gate Array) board.




Digital Abstraction

Key idea:

assume we have only two voltage levels


(i.e., assume binary signals)

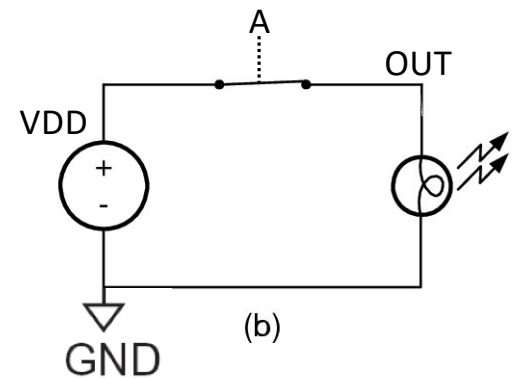  - $VDD \leftrightarrow 1 \leftrightarrow H$
- $GND \leftrightarrow 0 \leftrightarrow L$





Binary Waveforms

 
Assume we have a switch that when the control signal x is at VDD ($x=1$) the switch closes and when x is at GND ($x=0$) the switch opens



  $x = \text{input variable}$ $y = \text{output variable}$




(a) Simple connection to a battery

 

(b) Using a ground connection as the return path

Binary digits (bits)

 

If we “slice” the amplitude of our analog signal in 8 values, we need 3 binary signals (i.e. 3 bits) to represent it ($8 = 2^3$).

Decimal number	Binary code
0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111
8	1000
9	1001
10	1010
11	1011
12	1100
13	1101
14	1110
15	1111

Number Systems

$$num = \sum_{k=0}^{N-1} d_k R^k$$

Decimal numbers

1's column
10's column
100's column
1000's column

$$5374_{10} = 5 \times 10^3 + 3 \times 10^2 + 7 \times 10^1 + 4 \times 10^0$$

five thousands three hundreds seven tens four ones

Binary numbers


1's column
2's column
4's column
8's column

$$1101_2 = 1 \times 2^3 + 1 \times 2^2 + 0 \times 2^1 + 1 \times 2^0 = 13_{10}$$

one eight one four no two one one

Digital Abstraction:

Voltage ranges of binary signals

 



The building blocks of a digital circuit are called logic gates

$AND = \cdot = \vee = \cap = \&$



$OR = + = \vee = \cup = |$

$NOT = ' = - = \sim = !$


The three Basic Logic gates

  

(a) AND gates

  

(b) OR gates

 


(c) NOT gate

A digital circuit is a “network” of logic gates (i.e. a bunch of logic gates wired together)

The Basic Logic Gates: AND, OR, NOT


AND

 

$$Y = AB$$

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1


OR

 

$$Y = A + B$$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

NOT

 


$$Y = \overline{A}$$


A	Y
0	1
1	0

These three basic components are all you need to build any possible logic circuit you want


AND, OR, NOT

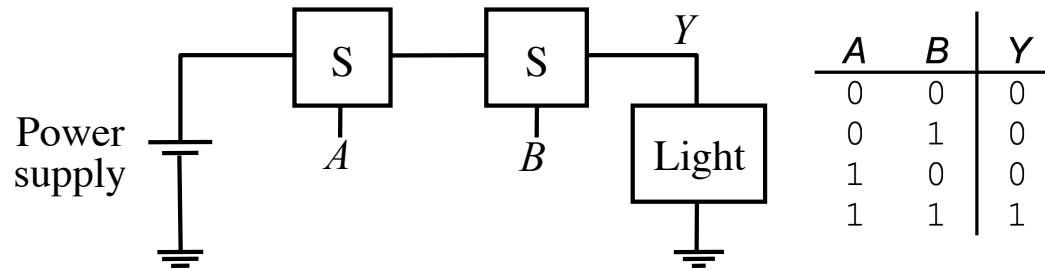

 (a) The logical AND function (series connection)



 
(b) The logical OR function (parallel connection)



(c) The logical NOT function

<i>A</i>	<i>Y</i>
0	1
1	0

 
More Logic Gates: NAND, NOR, and BUFFER (inverting AND, OR, and NOT)



It turns out that instead of using the three basic gates (AND, OR, NOT) you can build any logic circuit you want also by using only NAND gates or only NOR gates

More Logic Gates: XOR, XNOR


XOR

 

$$Y = A \oplus B$$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

XNOR

 


$$Y = \overline{A \oplus B}$$


A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

Beneath the Digital Abstraction



... there are transistors

 

Example: $V_{DD} = 5V$, $GND = 0V$

 

(a)

  

(b)


 


FIGURE 1.11


Inverter schematic

(a) and symbol

(b) $Y = \bar{A}$

 


(a)

 


(b)

FIGURE 1.12 2-input NAND gate schematic (a) and symbol (b) $Y = \overline{A \cdot B}$

 


(a)

FIGURE 1.16 2-input NOR gate schematic (a) and symbol (b) $Y = \overline{A + B}$

 


(b)


General CMOS Logic Gate

 

Logic Levels and Noise Margins

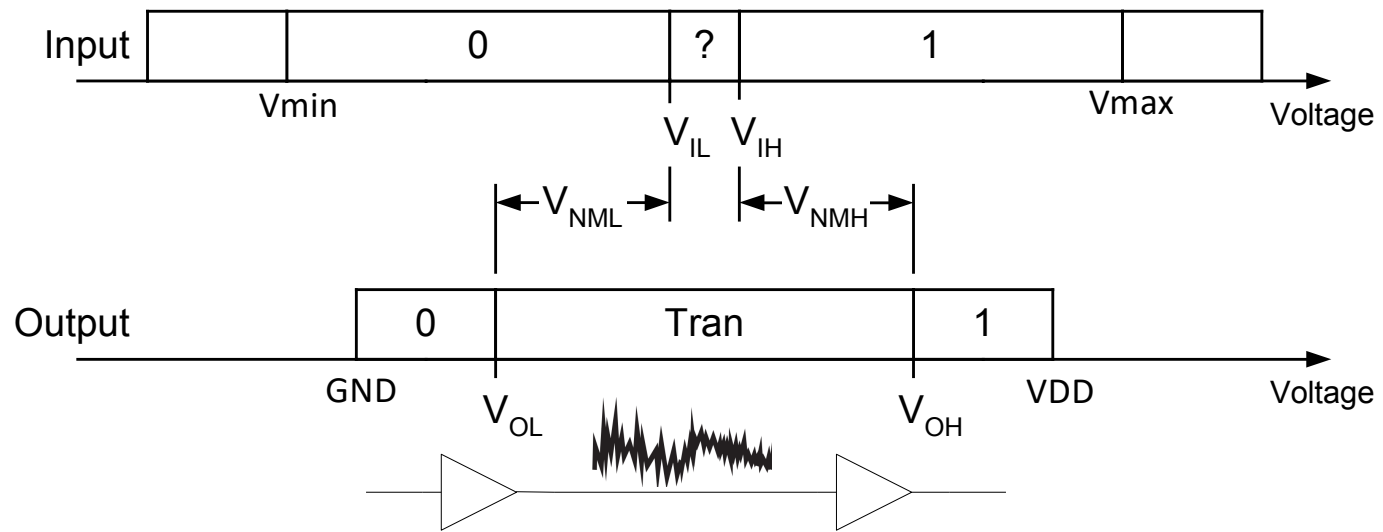


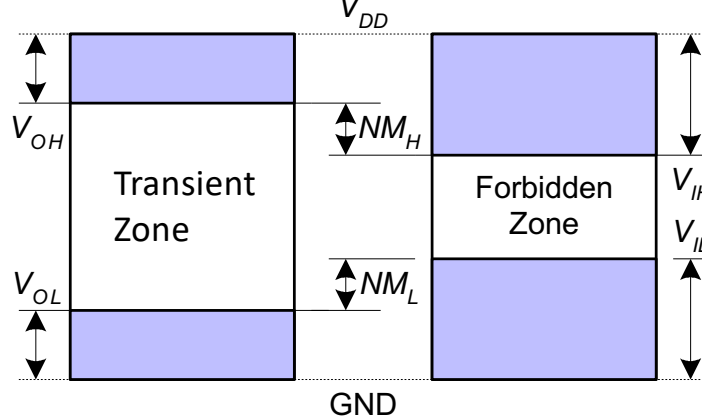
Output Characteristics Input Characteristics





Digital gates are restoring

  if Noise added to Input < Noise Margin
we get the correct value at output






DC Transfer Characteristics

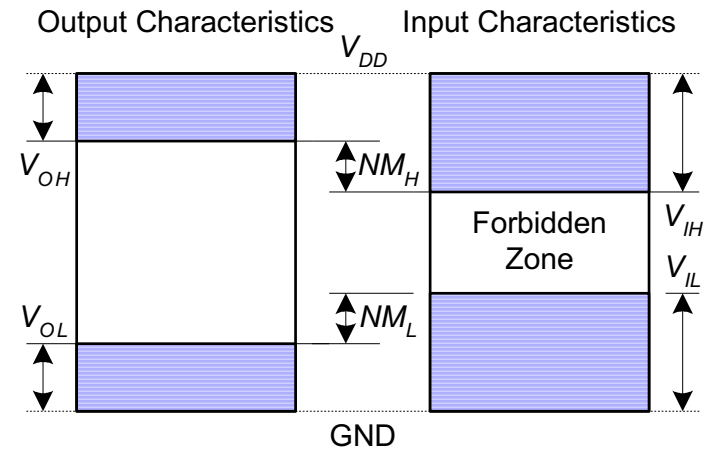 

If gain < 1 the noise superimposed to a given level gets "attenuated"

VDD Scaling

 

- In 1970's and 1980's, $V_{DD} = 5\text{ V}$

- V_{DD} has dropped
 - Save power

$$P_d = \alpha \cdot C_L \cdot f_{clk} \cdot V_{DD}^2$$

- 3.3 V, 2.5 V, 1.8 V, 1.5 V, 1.2 V, 1.0 V, ...
 - Be careful connecting chips with different supply voltages

Logic Family Examples

Logic Family	V_{DD}	V_{IL}	V_{IH}	V_{OL}	V_{OH}
TTL	5 (4.75 - 5.25)	0.8	2.0	0.4	2.4
CMOS	5 (4.5 - 6)	1.35	3.15	0.33	3.84
LVTTL	3.3 (3 - 3.6)	0.8	2.0	0.4	2.4
LVC MOS	3.3 (3 - 3.6)	0.9	1.8	0.36	2.7

Bits, Bytes, Nibbles, Words, ...

Bits

10010110
└─┘ └─┘
most least
significant significant
bit bit

Bytes & Nibbles

byte
└──────────┘
10010110
└──┘
nibble

Bytes

CEBF9AD7
└─┘ └─┘
most least
significant significant
byte byte

??

Hexadecimal Numbers










Hex Digit	Decimal Equivalent	Binary Equivalent
0	0	0000
1	1	0001
2	2	0010
3	3	0011
4	4	0100
5	5	0101
6	6	0110
7	7	0111
8	8	1000
9	9	1001
A	10	1010
B	11	1011
C	12	1100
D	13	1101
E	14	1110
F	15	1111

Next Time

- Types of logic circuits:
combinational circuits vs. sequential circuits
- Types of Integrated Circuits (ICs)
- Boolean Algebra

Combinational --> NOT Combinatorial


Common 74xx-series logic gates

         

Boolean Algebra

CPEN 230 – Introduction to Digital Logic


Review

 



- Binary (or Boolean or Digital or Logic) Signal (or Variable)



 - Fundamental Logic Functions (or Operations or Gates)



  These tables we are using to show the behavior of the logic functions are called *TRUTH TABLES*




Review

Precedence of basic operations:


- Parenthesis
- NOT
- AND
- OR

Review


A typical CAD Flow

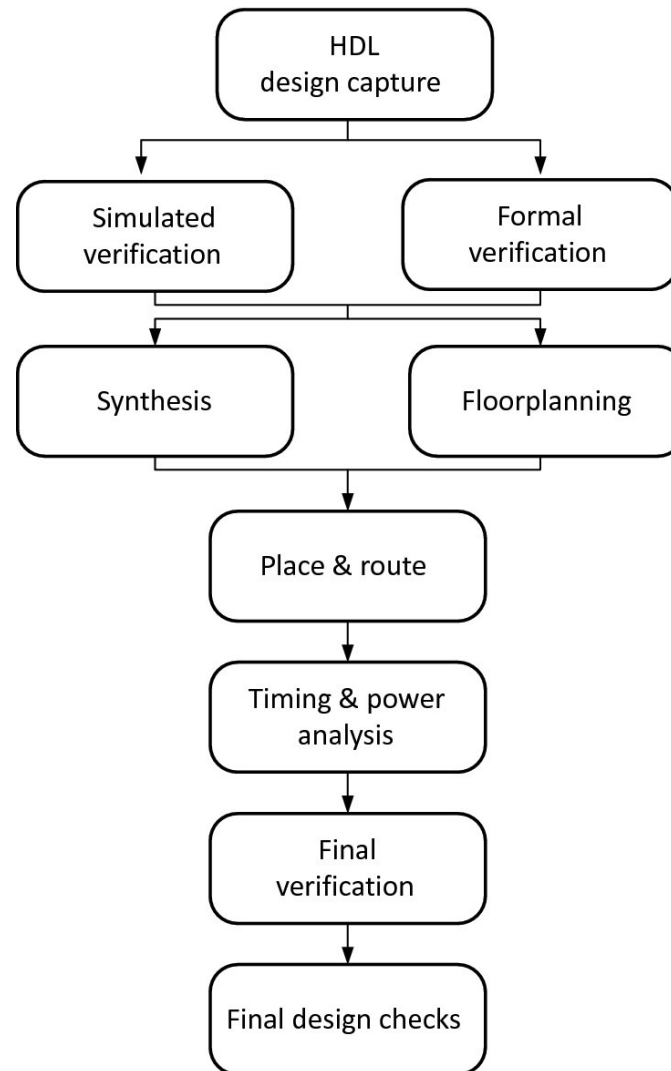

 AND and OR gates can have more than two inputs



Example

 


Think about the switch structure


Example

A	B	C	$Y=A+B+C$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

A	B	C	$Y=A \cdot B \cdot C$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

 


Think about switch structure

 

“Composite” Boolean Functions (or Expressions)

 - All Boolean Functions are formed by applying the basic operations to one or more variables or constants




A	B	C	$Y = A \cdot B' + C$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1


“Composite” Logic Functions: another example

- So far we have seen 4 ways to express Logic Functions:

 - Switches
- Equations (= expressions)
- Truth Tables
in general for N input variables
the truth table has 2^N rows
(there are 2^N combinations)



- Gates

 

x_3	x_2	x_1	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

- There is a fifth way called Karnaugh-maps (coming soon!)

Analysis and Synthesis of Logic Functions


Analysis

Given a logic function, determine its behavior

Synthesis

Given a desired behavior, design the logic function that implements it

Analysis of Logic Functions (1)

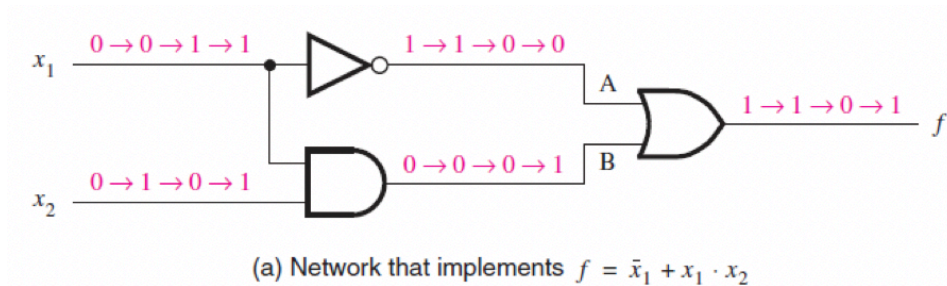


$$A = \bar{x}_1 \quad B = x_1 \cdot x_2$$


$x_1 x_2$	$f = A + B$
0 0	1
0 1	1
1 0	0
1 1	1

(b) Truth Table


A	B
1	0
1	0
0	0
0	1

 

Analysis of Logic Functions (2)

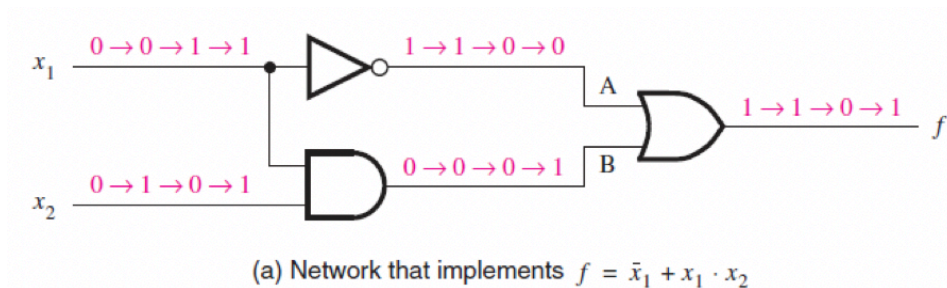

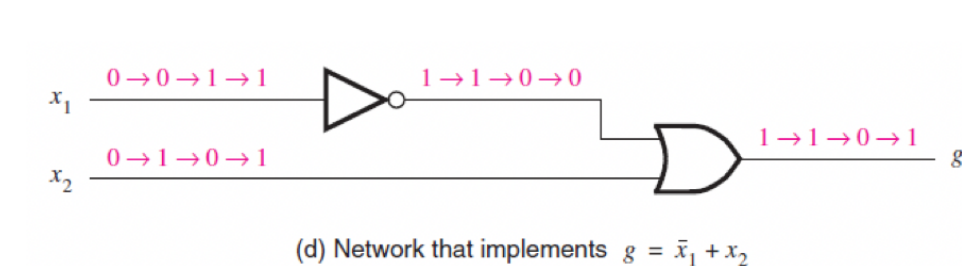
*f and g behave exactly the same !
f and g are equivalent, but ...
g is less "expensive" than f*




It would be nice to have some systematic method to find out the less "expensive" implementation of a given logic function !

Types of Logic Circuits

 - Combinational Circuits: the output values depend only on the present value of the inputs and not on past values.




 - Sequential Circuits: the outputs depend on both the present and past input values




As a consequence, combinational circuits are “memory less”, while sequential circuits requires storage elements (latches or flip-flops).

 To build storage elements we need a “feedback loop”





PCBs and Integrated Circuits

 


- DIP = dual Inline Package
- SMD = Surface Mount Devices
- PLCC = Plastic Leaded Chip Carrier
- LQFP = Low-Profile Quad Flat Package
- PQFP = Plastic Quad Flat Package
- TQFP = Thin Quad Flat package
- FBGA = Fine-Pitch Ball Grid Array
- PGA = Pin Grid Array

  
- Standard ICs
- Programmable ICs
- Application Specific ICs



Standard Chips (e.g. 7400-series)

 

(a) Dual-inline package

 


(b) Structure of 7404 chip

Implementation Example using Standard Chips

An implementation
of $f = x_1x_2 + \bar{x}_2x_3$


Limitations of 7400
series standard chips:

 1. The function provided by each chip is fixed
2. Each chip only contains a few logic gates



Programmable Logic Devices

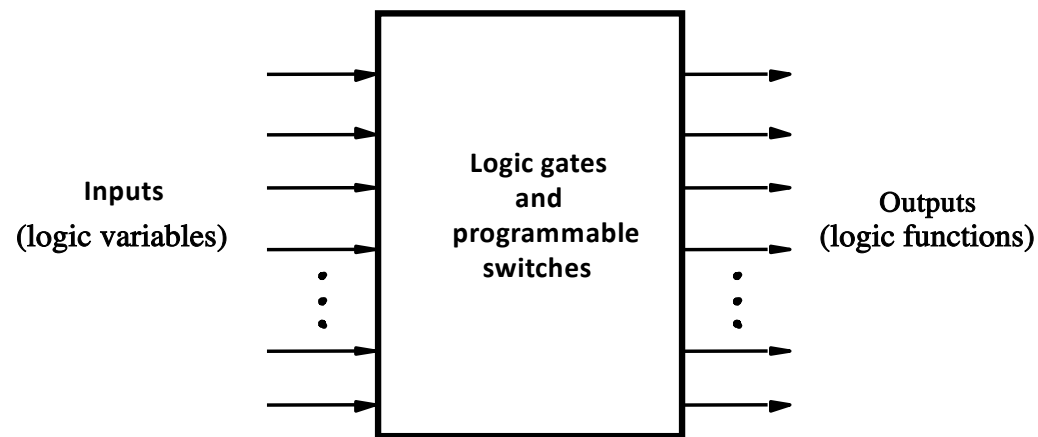- **Programmable Logic Devices** – chips that contain relatively large amounts of logic circuits with a structure that is not fixed (the structure can be customized)




Programmable logic device as a black box

Types of Programmable Logic Devices



- There are several types of Programmable Logic Devices commercially available:
 - Programmable Logic Array (PLA)
 - Programmable Array Logic (PAL)
 - Complex Programmable Logic Devices (CPLDs)
 - Field-Programmable Gate Arrays (FPGA)
- Logic circuit elements in programmable logic devices can be **customized** (that is programmed) through the use of CAD tools

FPGA's internal fabric

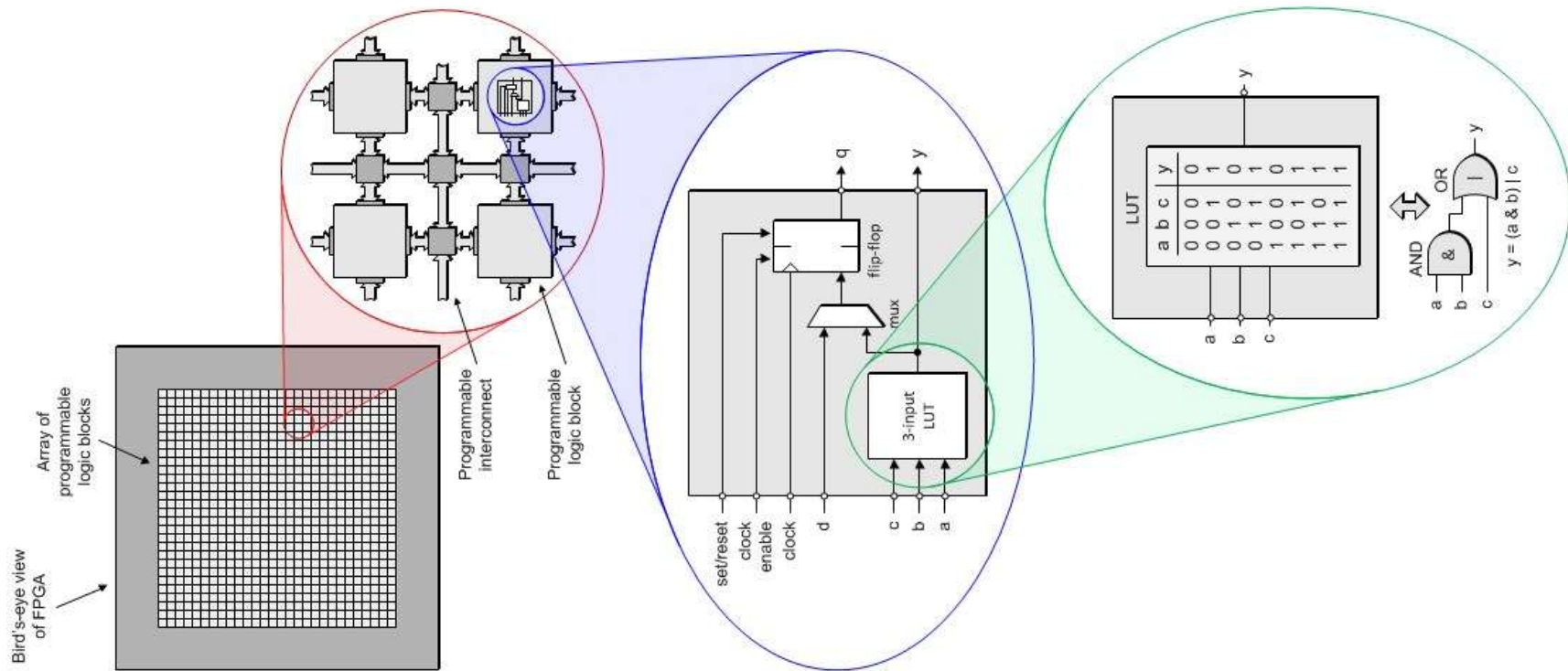- Both the basic logic cells (LUT) and the interconnections are programmable





Manipulating the Basic Boolean Functions

  

a b	a' b'	a' + b'
0 0	1 1	1
0 1	1 0	1
1 0	0 1	1
1 1	0 0	0

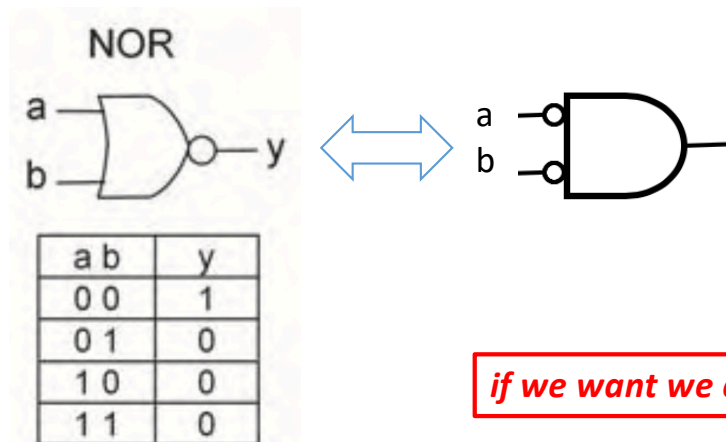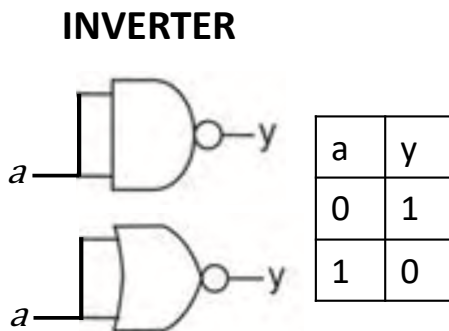if we want we can use NAND gates for everything !



a b	a' b'	a' * b'
0 0	1 1	1
0 1	1 0	0
1 0	0 1	0
1 1	0 0	0

if we want we can use NOR gates for everything !

Boolean Algebra

Objective:

Systematic way of manipulating Boolean expression

- One-Variable Theorems

$x \cdot 1 = x$	$x + 0 = x$
$x \cdot 0 = 0$	$x + 1 = 1$
$x \cdot x = x$	$x + x = x$
$x \cdot x' = 0$	$x + x' = 1$
$(x')' = x$	

Boolean Algebra

- Two and Three-Variable Theorems

$x + x \cdot y = x$	$x \cdot (x + y) = x$
$x \cdot y + x \cdot y' = x$	$(x + y)(x + y') = x$
$(x \cdot y)' = x' + y'$	$(x + y)' = x' \cdot y'$
$x \cdot y = y \cdot x$	$x + y = y + x$
$(x \cdot y) \cdot z = x \cdot (y \cdot z)$	$(x + y) + z = x + (y + z)$
$x \cdot (y + z) = x \cdot y + x \cdot z$	$x + (y \cdot z) = (x + y) \cdot (x + z)$
$x' \cdot y + x \cdot z = x' \cdot y + x \cdot z + y \cdot z$	$(x' + y)(x + z) = (x' + y)(x + z)(y + z)$

absorption (a.k.a. covering)

combining

De Morgan

commutative

associative

distributive

consensus (muxing)

- Duality Principle

If a Boolean function f is true then the dual function f_D is also true.

The dual of a logic function f is the function f_D derived from f by swapping "+" with "·", "·" with "+", "0" with "1" and "1" with "0".


Boolean Algebra

- N-Variable Theorems

$(x_1 + x_2 + x_3 + \dots + x_N)' = x_1' \cdot x_2' \cdot x_3' \cdot \dots \cdot x_N'$	De Morgan Theorem
$(x_1 \cdot x_2 \cdot x_3 \cdot \dots \cdot x_N)' = x_1' + x_2' + x_3' + \dots + x_N'$	
$f(x_1, x_2, x_3, \dots, x_N) = x_1' \cdot f(0, x_2, x_3, \dots, x_N) + x_1 \cdot f(1, x_2, x_3, \dots, x_N)$	Shannon Expansion Theorem
$f(x_1, x_2, x_3, \dots, x_N) = [x_1' + f(1, x_2, x_3, \dots, x_N)] \cdot [x_1 + f(0, x_2, x_3, \dots, x_N)]$	

DeMorgan Theorem:

 
The **complement** of the **product** is the **sum** of the **complements**.



$$Y = \overline{A \cdot B} = \bar{A} + \bar{B}$$

Dual:

 The **complement** of the **sum** is the **product** of the **complements**.





$$Y = \overline{A + B} = \bar{A} \cdot \bar{B}$$



Next Time

- Standard Form Representations of Logic Functions:
 - SOP
 - POS
 - min terms
 - max terms

Consensus (a practical perspective)

 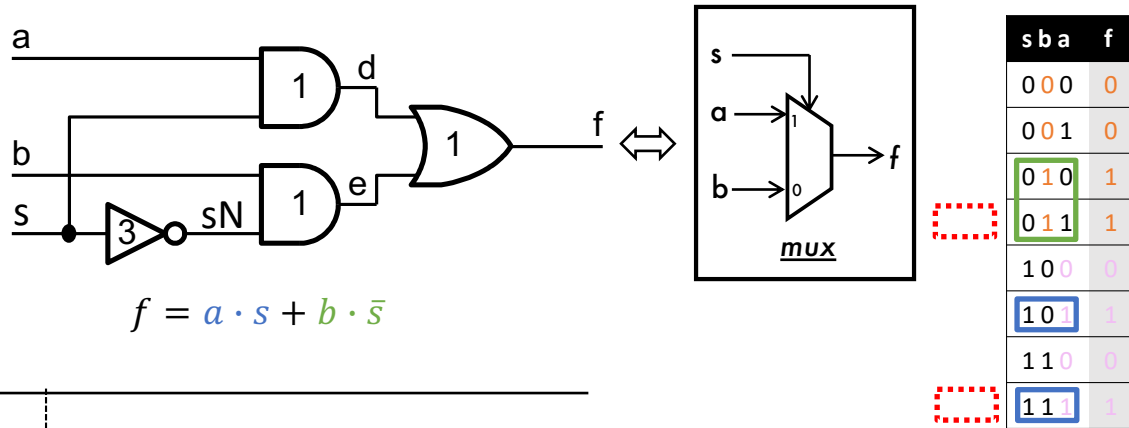

There is a "Glitch"
Static-1 hazard

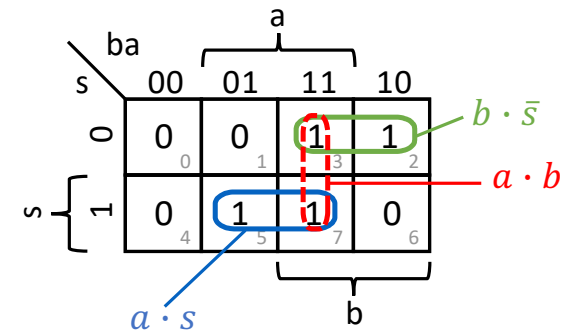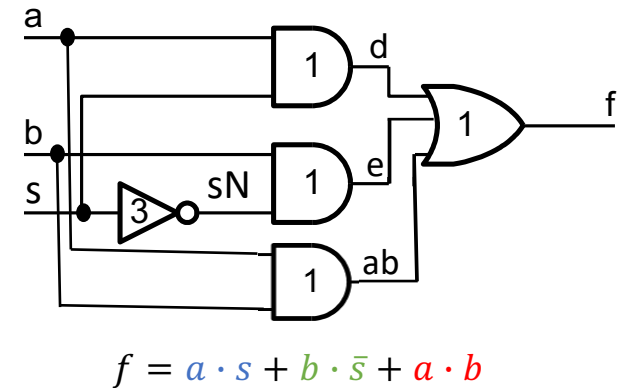

Example. Prove Combining Theorem

$$x \cdot y + x \cdot y' = x \cdot (y + y') = x \cdot 1 = x$$

$$(x + y) \cdot (x + y') = x \cdot x + x \cdot y + x \cdot y' + y \cdot y' = x + x \cdot (y + y') + 0 = x + x \cdot 1 + 0 = x$$

Example. Prove Absorption Theorem


$$x + x \cdot y = x \cdot (y + y') + x \cdot y = x \cdot y + x \cdot y' + x \cdot y = x \cdot y + x \cdot y' = x$$

$$x \cdot (x + y) = x \cdot x + x \cdot y = x + x \cdot y = x \cdot (y + y') + x \cdot y = x \cdot y + x \cdot y' + x \cdot y = x \cdot y + x \cdot y' = x$$

Example. Prove Following Property

x y	f
0 0	0
0 1	1
1 0	1
1 1	1

OR

 

P1: $x + \bar{x} \cdot y = x + y$ <-- Very easy to see from truth table or if we notice that it is a mux

P1.D: $x \cdot (\bar{x} + y) = x \cdot y$ (not so easy using equations)

Since P1 is not so easy to prove it may be a property worth remembering !
Let's call it "Simplification" Theorem.

= complement
of missing term(s)







↔ In other words remember that $f = \overline{\overline{f}}$

$$P1 \rightarrow x + x'y = x(y + y') + x'y = xy + xy' + x'y = (x'y')' = (x + y)'' = x + y$$

$$P1.D \rightarrow x \cdot (x' + y) = x \cdot x' + x \cdot y = 0 + x \cdot y = x \cdot y$$

De Morgan

      An addition tool to gain insight into a logic equation is to use Venn Diagrams from set theory



$$x + x'y = x + y$$

How to Prove ?

- **Method 1:** Perfect induction
- **Method 2:** Use other theorems and axioms to simplify the equation
 - Make one side of the equation look like the other

What does Perfect Induction mean ?

- Despite the “fancy” name this is the most obvious solution
- Also called: **proof by exhaustion**
- Check every possible input value
- If two expressions produce the same value for every possible input combination, the expressions are equal

Standard Forms

CPEN 230 – Introduction to Digital Logic

Review: Boolean Algebra

One-Variable Theorems

$x \cdot 1 = x$	$x + 0 = x$
$x \cdot 0 = 0$	$x + 1 = 1$
$x \cdot x = x$	$x + x = x$
$x \cdot x' = 0$	$x + x' = 1$
$(x')' = x$	

Two and Three- Variable Theorems

$x + x \cdot y = x$	$x \cdot (x + y) = x$
$x \cdot y + x \cdot y' = x$	$(x + y)(x + y') = x$
$x + x' \cdot y = x + y$	$x \cdot (x' + y) = x \cdot y$
$(x \cdot y)' = x' + y'$	$(x + y)' = x' \cdot y'$
$x \cdot y = y \cdot x$	$x + y = y + x$
$(x \cdot y) \cdot z = x \cdot (y \cdot z)$	$(x + y) + z = x + (y + z)$
$x \cdot (y + z) = x \cdot y + x \cdot z$	$x + (y \cdot z) = (x + y) \cdot (x + z)$
$x' \cdot y + x \cdot z = x' \cdot y + x \cdot z + y \cdot z$	$(x' + y)(x + z) = (x' + y)(x + z)(y + z)$

absorption (a.k.a. covering)

combining

“simplification”

De Morgan

commutative

associative

distributive

consensus (muxing)

Review: Boolean Algebra

Duality Principle

If a Boolean function f is true then the dual function f_D is also true. The dual of a logic function f is the function f_D derived from f by swapping "+" with "·", "·" with "+", "0" with "1" and "1" with "0".

N-Variable Theorems

$(x_1 + x_2 + x_3 + \cdots + x_N)' = x_1' \cdot x_2' \cdot x_3' \cdot \cdots \cdot x_N'$	De Morgan Theorem
$(x_1 \cdot x_2 \cdot x_3 \cdot \cdots \cdot x_N)' = x_1' + x_2' + x_3' + \cdots + x_N'$	
$f(x_1, x_2, x_3, \dots, x_N) = x_1' \cdot f(0, x_2, x_3, \dots, x_N) + x_1 \cdot f(1, x_2, x_3, \dots, x_N)$	Shannon Expansion Theorem
$f(x_1, x_2, x_3, \dots, x_N) = [x_1' + f(1, x_2, x_3, \dots, x_N)] \cdot [x_1 + f(0, x_2, x_3, \dots, x_N)]$	

Truth Tables: min-terms and max-terms

For an N-input function a truth table has 2^N rows (= 2^N minterms = 2^N maxterms)

Row #	$x_2 x_1 x_0$	f	Minterm	Maxterm
0	000		$m_0 = \overline{x_2} \cdot \overline{x_1} \cdot \overline{x_0}$	$M_0 = x_2 + x_1 + x_0 = \overline{m_0}$
1	001		$m_1 = \overline{x_2} \cdot \overline{x_1} \cdot x_0$	$M_1 = x_2 + x_1 + \overline{x_0} = \overline{m_1}$
2	010		$m_2 = \overline{x_2} \cdot x_1 \cdot \overline{x_0}$	$M_2 = x_2 + \overline{x_1} + x_0 = \overline{m_2}$
3	011		$m_3 = \overline{x_2} \cdot x_1 \cdot x_0$	$M_3 = x_2 + \overline{x_1} + \overline{x_0} = \overline{m_3}$
4	100		$m_4 = x_2 \cdot \overline{x_1} \cdot \overline{x_0}$	$M_4 = \overline{x_2} + x_1 + x_0 = \overline{m_4}$
5	101		$m_5 = x_2 \cdot \overline{x_1} \cdot x_0$	$M_5 = \overline{x_2} + x_1 + \overline{x_0} = \overline{m_5}$
6	110		$m_6 = x_2 \cdot x_1 \cdot \overline{x_0}$	$M_6 = \overline{x_2} + \overline{x_1} + x_0 = \overline{m_6}$
7	111		$m_7 = x_2 \cdot x_1 \cdot x_0$	$M_7 = \overline{x_2} + \overline{x_1} + \overline{x_0} = \overline{m_7}$

Terminology

- **Literal**

Any occurrence of a variable, either in its direct form (e.g. a) or in its complemented form (e.g. \bar{a})

- **Product Term**

A product (AND operation) of two or more literals
(e.g. $ab, a\bar{a}, \bar{a}b, \bar{a}bc, \dots$)

- **Sum Term**

A sum (OR operation) of two or more literals
(e.g. $\bar{a} + b, \bar{a} + b, a + b + c, c + c, \dots$)

- **Minterm**

Given a function of N-input variables, a minterm is a product term of N literals with one literal for each input variable.

(Example: given a function of three input variables $\bar{a}bc$ is a min term, but $\bar{a}b$ or $\bar{a}ab$ are not)

- **Maxterm**

Given a function of N-input variables, a maxterm is a sum term of N literals with one literal for each input variable.

Minterms and maxterms: example

Row #	$x_2 x_1 x_0$	f	Minterm	Maxterm
0	000	1	$m_0 = \overline{x_2} \cdot \overline{x_1} \cdot \overline{x_0}$	$M_0 = x_2 + x_1 + x_0 = \overline{m_0}$
1	001	1	$m_1 = \overline{x_2} \cdot \overline{x_1} \cdot x_0$	$M_1 = x_2 + x_1 + \overline{x_0} = \overline{m_1}$
2	010	0	$m_2 = \overline{x_2} \cdot x_1 \cdot \overline{x_0}$	$M_2 = x_2 + \overline{x_1} + x_0 = \overline{m_2}$
3	011	0	$m_3 = \overline{x_2} \cdot x_1 \cdot x_0$	$M_3 = x_2 + \overline{x_1} + \overline{x_0} = \overline{m_3}$
4	100	0	$m_4 = x_2 \cdot \overline{x_1} \cdot \overline{x_0}$	$M_4 = \overline{x_2} + x_1 + x_0 = \overline{m_4}$
5	101	0	$m_5 = x_2 \cdot \overline{x_1} \cdot x_0$	$M_5 = \overline{x_2} + x_1 + \overline{x_0} = \overline{m_5}$
6	110	0	$m_6 = x_2 \cdot x_1 \cdot \overline{x_0}$	$M_6 = \overline{x_2} + \overline{x_1} + x_0 = \overline{m_6}$
7	111	0	$m_7 = x_2 \cdot x_1 \cdot x_0$	$M_7 = \overline{x_2} + \overline{x_1} + \overline{x_0} = \overline{m_7}$

If a function f is specified in the form of a Truth Table, then an expression that realizes f can be obtained either by considering the rows in the table for which $f=1$ or by considering the rows for which $f=0$

$$\begin{aligned}
 f &= m_0 + m_1 = (m_2 + m_3 + m_4 + m_5 + m_6 + m_7)' = (\overline{m_2} \cdot \overline{m_3} \cdot \overline{m_4} \cdot \overline{m_5} \cdot \overline{m_6} \cdot \overline{m_7})'' \\
 &= M_2 \cdot M_3 \cdot M_4 \cdot M_5 \cdot M_6 \cdot M_7
 \end{aligned}$$

Minterms and maxterms: example

Row #	$x_2 x_1 x_0$	f	Minterm	Maxterm
0	000	1	$m_0 = \overline{x_2} \cdot \overline{x_1} \cdot \overline{x_0}$	$M_0 = x_2 + x_1 + x_0 = \overline{m_0}$
1	001	1	$m_1 = \overline{x_2} \cdot \overline{x_1} \cdot x_0$	$M_1 = x_2 + x_1 + \overline{x_0} = \overline{m_1}$
2	010	0	$m_2 = \overline{x_2} \cdot x_1 \cdot \overline{x_0}$	$M_2 = x_2 + \overline{x_1} + x_0 = \overline{m_2}$
3	011	0	$m_3 = \overline{x_2} \cdot x_1 \cdot x_0$	$M_3 = x_2 + \overline{x_1} + \overline{x_0} = \overline{m_3}$
4	100	0	$m_4 = x_2 \cdot \overline{x_1} \cdot \overline{x_0}$	$M_4 = \overline{x_2} + x_1 + x_0 = \overline{m_4}$
5	101	0	$m_5 = x_2 \cdot \overline{x_1} \cdot x_0$	$M_5 = \overline{x_2} + x_1 + \overline{x_0} = \overline{m_5}$
6	110	0	$m_6 = x_2 \cdot x_1 \cdot \overline{x_0}$	$M_6 = \overline{x_2} + \overline{x_1} + x_0 = \overline{m_6}$
7	111	0	$m_7 = x_2 \cdot x_1 \cdot x_0$	$M_7 = \overline{x_2} + \overline{x_1} + \overline{x_0} = \overline{m_7}$

$$f = \sum m(0,1) = \prod M(2,3,4,5,6,7)$$

Sum-of-Products (SOPs) and Product-of-Sums (POSs)

Any Boolean function f can be expressed either as a sum of product terms (SOPs) or as a product of sum terms (POSs)

- If all the product terms in the SOP are minterms then the expression is called a normal (or canonical or standard) form SOP
- If all the sum terms in the POS are maxterms then the expression is called a normal (or canonical or standard) form POS

Example


$$f(x_2, x_1, x_0) = \sum m(0,1) = x_2' x_1' x_0' + x_2' x_1' x_0 = (x_2' x_1') \overbrace{(x_0' + x_0)}^{=1} = x_2' x_1'$$

canonical SOP form combining theorem

non-canonical SOP form

Minterms and maxterms

Row #	$x_2 x_1 x_0$	f	Minterm	Maxterm
0	000	0	$m_0 = \overline{x_2} \cdot \overline{x_1} \cdot \overline{x_0}$	$M_0 = x_2 + x_1 + x_0 = \overline{m_0}$
1	001	0	$m_1 = \overline{x_2} \cdot \overline{x_1} \cdot x_0$	$M_1 = x_2 + x_1 + \overline{x_0} = \overline{m_1}$
2	010	0	$m_2 = \overline{x_2} \cdot x_1 \cdot \overline{x_0}$	$M_2 = x_2 + \overline{x_1} + x_0 = \overline{m_2}$
3	011	0	$m_3 = \overline{x_2} \cdot x_1 \cdot x_0$	$M_3 = x_2 + \overline{x_1} + \overline{x_0} = \overline{m_3}$
4	100	1	$m_4 = x_2 \cdot \overline{x_1} \cdot \overline{x_0}$	$M_4 = \overline{x_2} + x_1 + x_0 = \overline{m_4}$
5	101	0	$m_5 = x_2 \cdot \overline{x_1} \cdot x_0$	$M_5 = \overline{x_2} + x_1 + \overline{x_0} = \overline{m_5}$
6	110	0	$m_6 = x_2 \cdot x_1 \cdot \overline{x_0}$	$M_6 = \overline{x_2} + \overline{x_1} + x_0 = \overline{m_6}$
7	111	0	$m_7 = x_2 \cdot x_1 \cdot x_0$	$M_7 = \overline{x_2} + \overline{x_1} + \overline{x_0} = \overline{m_7}$

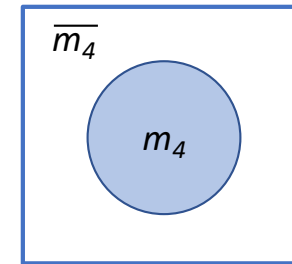

Each minterm “touches” only one row of the truth table (e.g. m_4)

Each maxterm “touches” all but one row of the table (e.g. $M_4 = \overline{m_4}$ so it touches: $m_0; m_1; m_2; m_3; m_5; m_6$ and m_7)

Simplyfing an Equation

Reducing an equation to the **fewest number of implicants**, where each implicant has the **fewest literals**

Recall:

- Implicant: product of literals


ABC, AC, BC

- Literal: variable or its complement


A, A', B, B', C, C'

*Also called **minimizing** the equation*

Design Example: Multiplexer

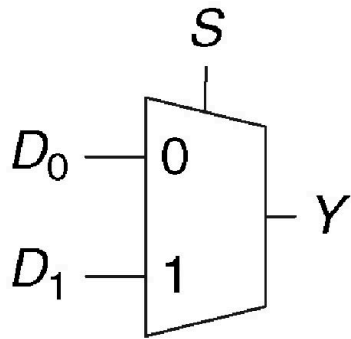
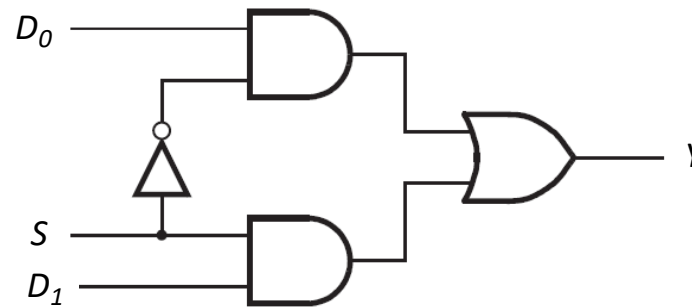
```
if (S == 0)
    Y <= D0;
else
    Y <= D1;
```




S	D ₁	D ₀	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$$\begin{aligned}
 Y &= \sum m(1,3,6,7) = \\
 &= \bar{S} \cdot \bar{D}_1 \cdot D_0 + \bar{S} \cdot D_1 \cdot D_0 + S \cdot D_1 \cdot \bar{D}_0 + S \cdot D_1 \cdot D_0 = \\
 &= \bar{S} \cdot D_0 \cdot \underbrace{(\bar{D}_1 + D_1)}_{=1} + S \cdot D_1 \cdot \underbrace{(\bar{D}_0 + D_0)}_{=1} = \bar{S} \cdot D_0 + S \cdot D_1
 \end{aligned}$$

Design Example: Three way light control

x_1	x_2	x_3	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

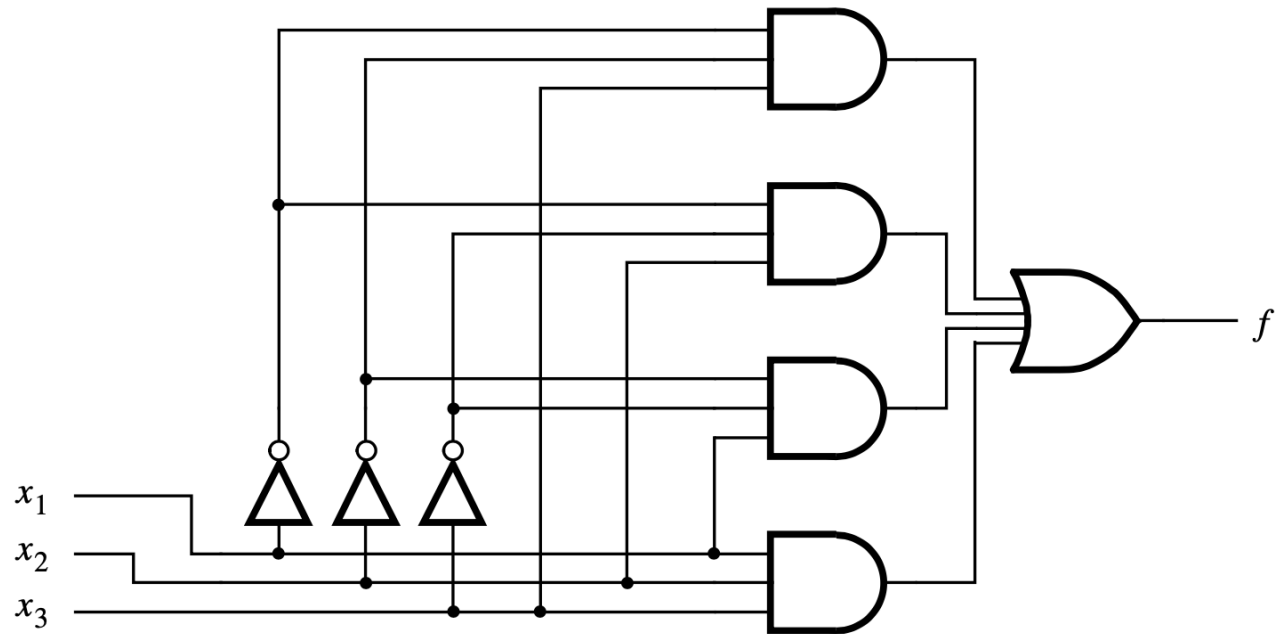


SOP realization

$$f(x_1, x_2, x_3) = m_1 + m_2 + m_4 + m_7 = \overline{x_1} \cdot \overline{x_2} \cdot x_3 + \overline{x_1} \cdot x_2 \cdot \overline{x_3} + x_1 \cdot \overline{x_2} \cdot \overline{x_3} + x_1 \cdot x_2 \cdot x_3$$

Design Example: Three way light control


x_1	x_2	x_3	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

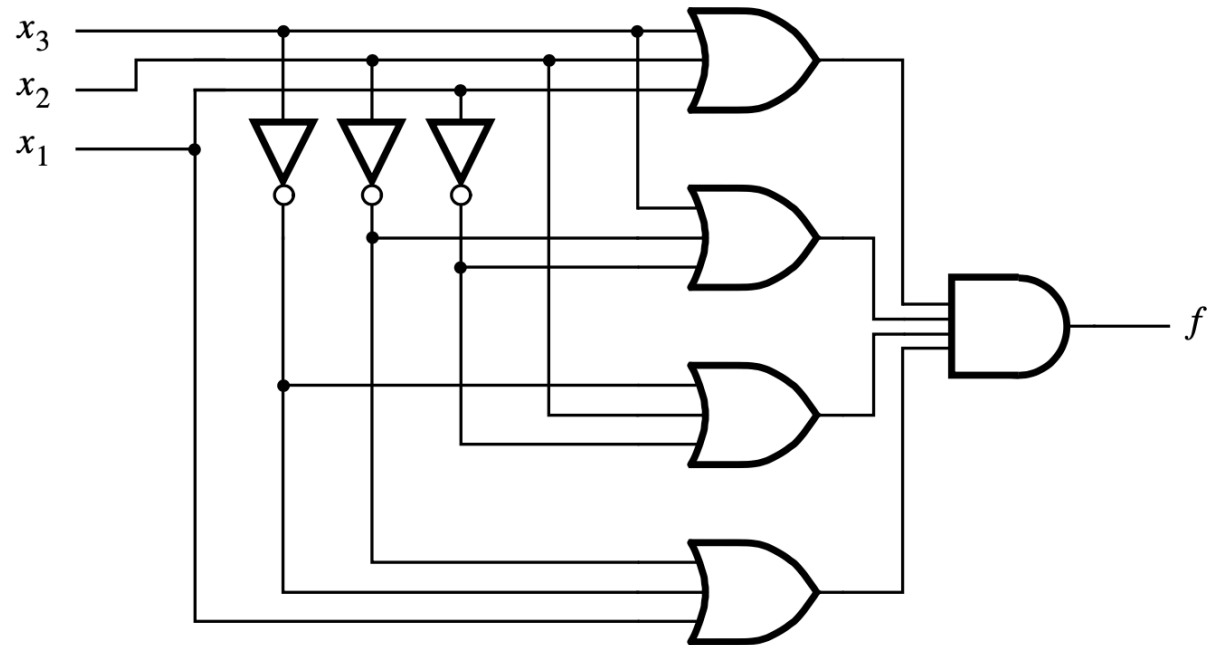


POS realization

$$f(x_1, x_2, x_3) = M_0 \cdot M_3 \cdot M_5 \cdot M_6 = (x_1 + x_2 + x_3) \cdot (x_1 + \overline{x_2} + \overline{x_3}) \cdot (\overline{x_1} + x_2 + \overline{x_3}) \cdot (\overline{x_1} + \overline{x_2} + x_3)$$

NAND-NAND circuits (pushing bubbles)

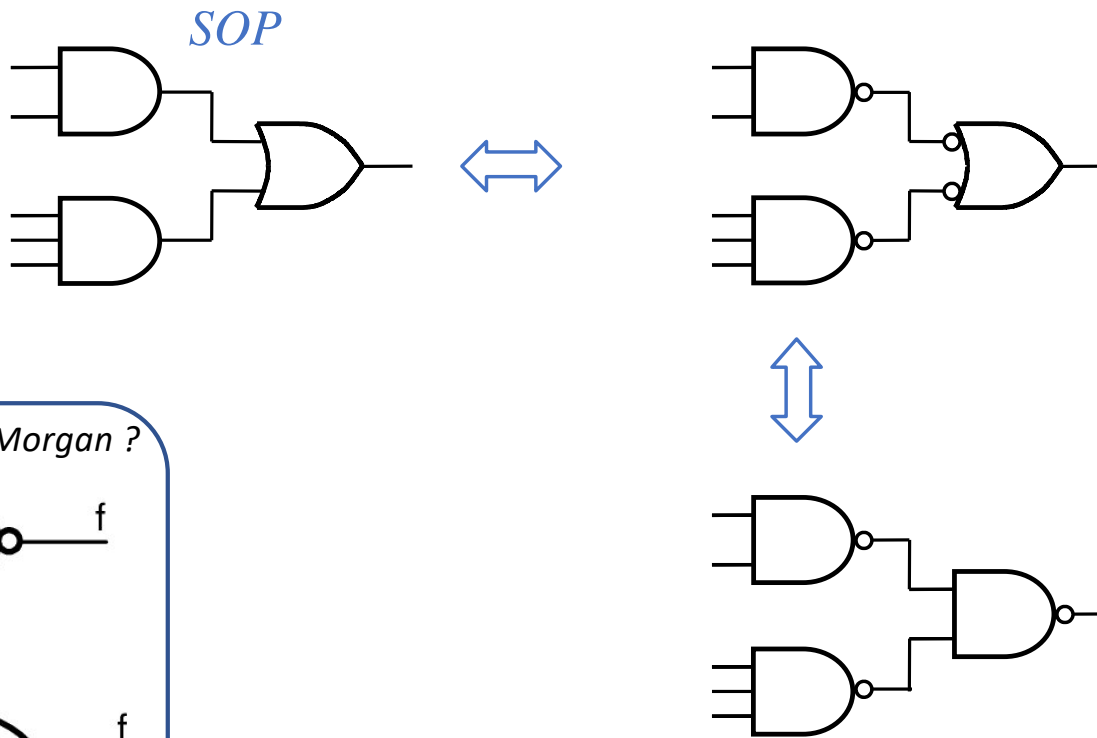


Remember De Morgan ?

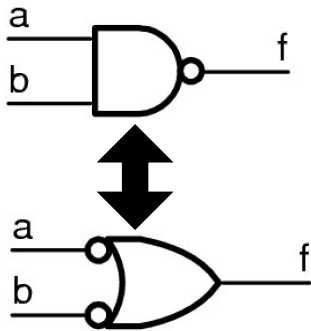


Using NAND gates to implement a sum-of-products.

NOR-NOR circuits (pushing bubbles)

 

Remember De Morgan ?


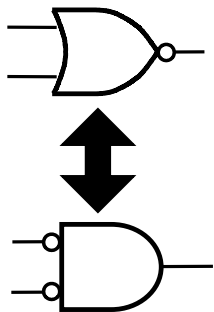


Using NOR gates to implement a product-of sums.

Bubble Pushing



- **Backward:**

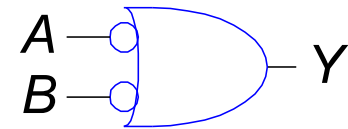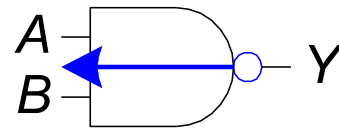- Body gets “squished” (changes shape)
- Adds bubbles to inputs




- **Forward:**

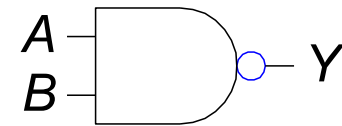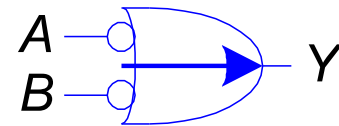- Body gets “squished” (changes shape)
- Adds bubble to output





NAND-NAND vs. NOR-NOR

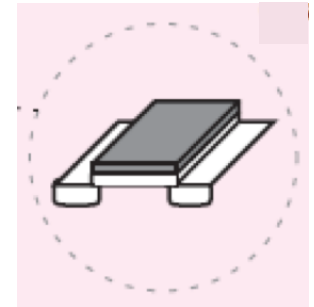
- The propagation delay through a logic gate is proportional to the RC of the switches involved in delivering the desired logic level (either V_{DD} or GND) to the output. The switches (MOS transistors) are not ideal: they have R and C associated to them (the PMOS transistors have more R than the NMOS transistors)




2-input CMOS NAND gate

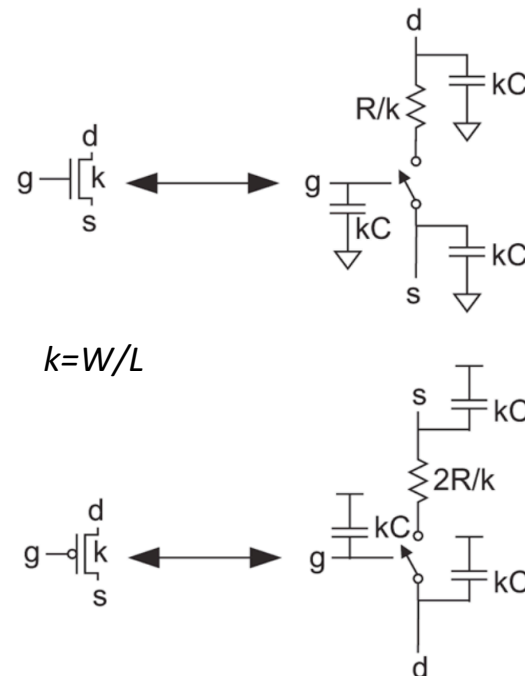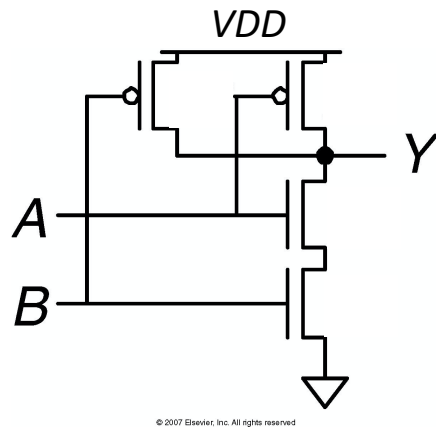


2-input CMOS NOR gate

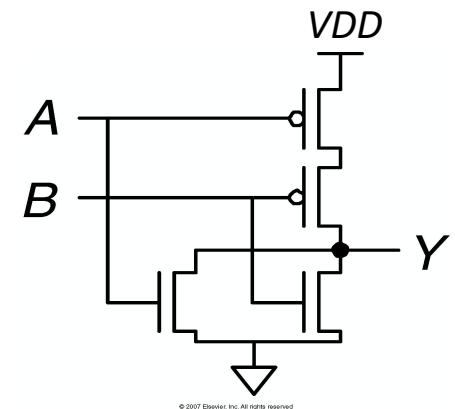

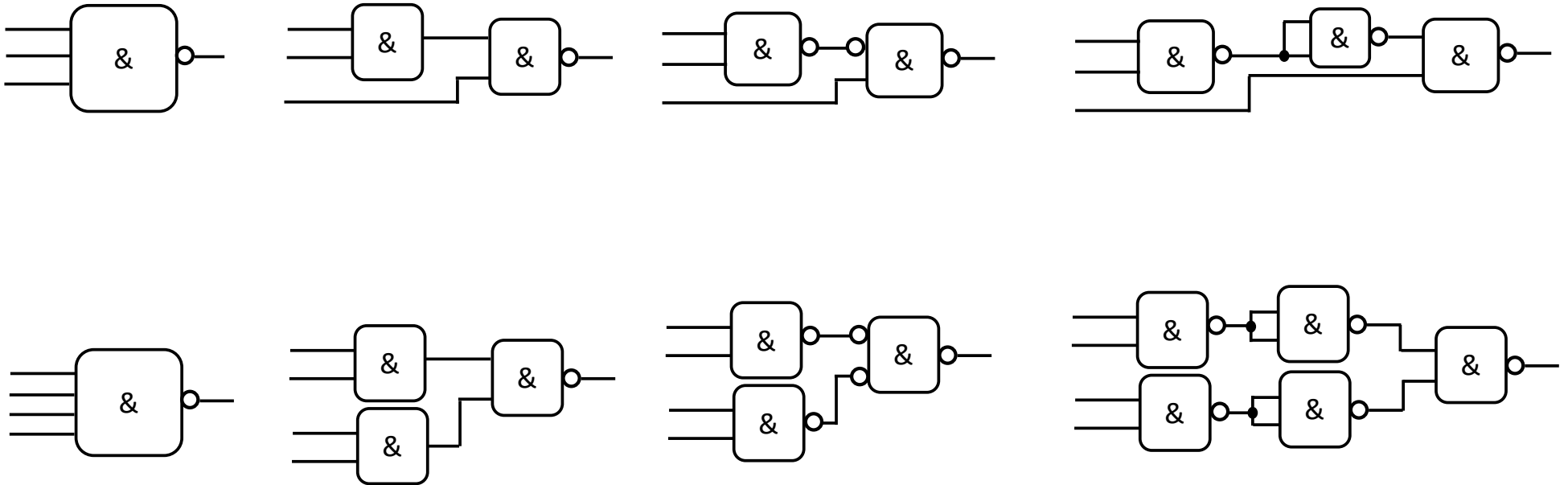Building multiple-input NAND gates using 2-input NAND gates (pushing bubbles)



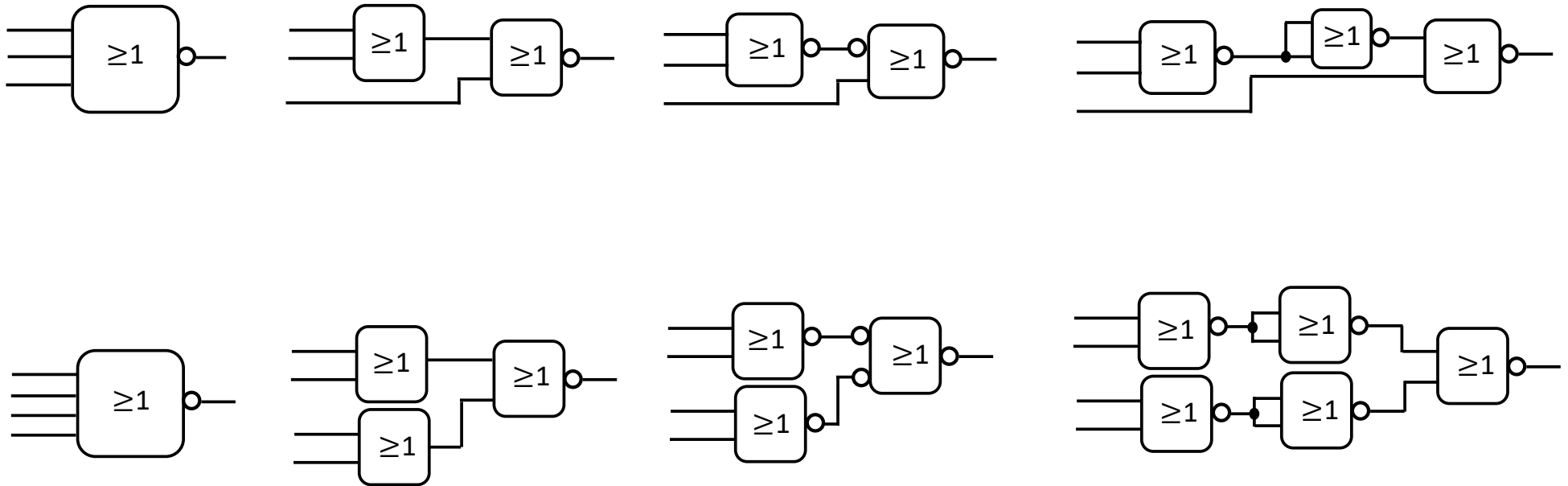Building multiple-input NOR gates using 2-input NOR gates (pushing bubbles)



Next Time

- A first look at Verilog
- K-maps
- Minimization of Boolean Equations using K-maps
- Multiple Drivers (contention Value: X)
- Tri-state Buffer (high impedance state: Z)


K-maps and minimization

CPEN 230 – Introduction to Digital Logic


Review: minterms, maxterms, SOP form and POS form

Row #	$x_2 x_1 x_0$	f	Minterm	Maxterm
0	000	1	$m_0 = \overline{x_2} \cdot \overline{x_1} \cdot \overline{x_0}$	$M_0 = x_2 + x_1 + x_0 = \overline{m_0}$
1	001	1	$m_1 = \overline{x_2} \cdot \overline{x_1} \cdot x_0$	$M_1 = x_2 + x_1 + \overline{x_0} = \overline{m_1}$
2	010	0	$m_2 = \overline{x_2} \cdot x_1 \cdot \overline{x_0}$	$M_2 = x_2 + \overline{x_1} + x_0 = \overline{m_2}$
3	011	0	$m_3 = \overline{x_2} \cdot x_1 \cdot x_0$	$M_3 = x_2 + \overline{x_1} + \overline{x_0} = \overline{m_3}$
4	100	0	$m_4 = x_2 \cdot \overline{x_1} \cdot \overline{x_0}$	$M_4 = \overline{x_2} + x_1 + x_0 = \overline{m_4}$
5	101	0	$m_5 = x_2 \cdot \overline{x_1} \cdot x_0$	$M_5 = \overline{x_2} + x_1 + \overline{x_0} = \overline{m_5}$
6	110	0	$m_6 = x_2 \cdot x_1 \cdot \overline{x_0}$	$M_6 = \overline{x_2} + \overline{x_1} + x_0 = \overline{m_6}$
7	111	0	$m_7 = x_2 \cdot x_1 \cdot x_0$	$M_7 = \overline{x_2} + \overline{x_1} + \overline{x_0} = \overline{m_7}$
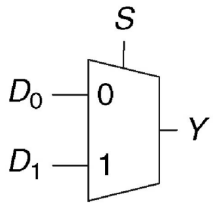
$$f = \sum m(0,1) = \prod M(2,3,4,5,6,7)$$



A first look at Verilog

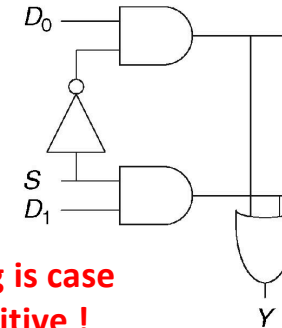

Register Transfer Level (RTL) Verilog Code for synthesizing a 2:1 mux

Verilog is case sensitive !

```
// filename: mux21.v
// two possible coding styles for implementing a 2:1 multiplexer
```

```
module mux21(s,d1,d0,f,y);
  input s, d0, d1;
  output f, y;
```

```
  reg y;
```


```
  assign f = (~s & d0) | (s & d1);
```

```
  always@ (s or d0 or d1)
    if (s == 0)
      y = d0;
    else
      y = d1;
```

```
endmodule
```

concurrent coding style

 always-based (procedural)
coding style
(higher level of abstraction)



```

// filename: mux21_tb.v
// verify the functionality of mux21.v

// set time tick units and precision to ns
`timescale 1ns / 1ns

module mux21_tb;

    // UUT inputs
    reg s;
    reg d0;
    reg d1;
    // UUT outputs
    wire f, y;

    // variables
    integer i;

    // instantiate the unit under test (UUT)
    mux21 uut(
        .s(s),
        .d1(d1),
        .d0(d0),
        .f(f),
        .y(y)
    );

    // initialize inputs
    initial begin
        s = 0;
        d1 = 0;
        d0 = 0;
    end

```

```

// set time format to be ns
initial $timeformat(-9, 1, "ns", 10);
/*
 * $timeformat(unit, precision, "unit", minwidth);
 * unit is the base that time is to be displayed, from 0 to -15 (s to fs)
 * precision is the number of decimal points to display
 * "unit" is a string appended to the time, such as " ns".
 * minwidth is the minimum number of characters that will be displayed.
 */

// output the simulation in graphical format
initial begin
    $dumpfile("mux21.vcd");
    $dumpvars(0, mux21_tb);
end

// generate test patterns
initial begin
    i = 0;
    repeat (8) begin
        {s, d1, d0} = i;
        #1;
        i = i+1;
    end
    $finish;
end

// output the simulation in textual format
initial begin
    $display("time s d0 d1 f y"); // output table: header
    $display("-----"); // output table: header
    $monitor("%4d %1d %1d %1d %1d %1d", // output table: signal formatting
        $time, s, d0, d1, f, y); // output table: signals
end

endmodule

```


A first look at Verilog (iverilog and GTKwave)

```
$ iverilog -o design mux21.v mux21_tb.v
```

```
$ vvp design
```

```
$ gtkwave mux21.vcd
```

time	s	d0	d1	f	y
0	0	0	0	0	0
1	0	1	0	1	1
2	0	0	1	0	0
3	0	1	1	1	1
4	1	0	0	0	0
5	1	1	0	0	0
6	1	0	1	1	1
7	1	1	1	1	1

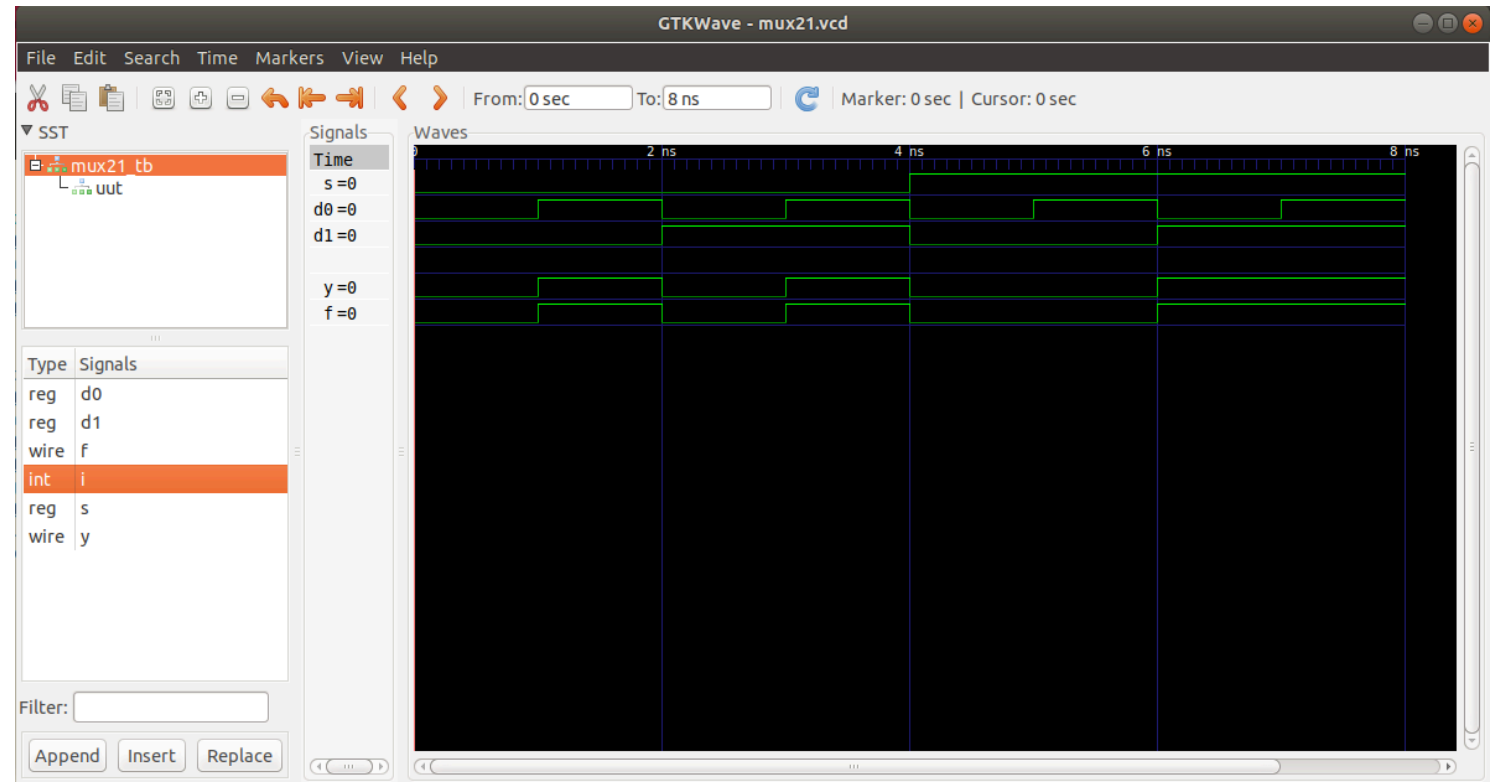

A first look at Verilog (Modelsim)


runmux.scr

```
#!/bin/bash
vlib work
vlog -work work "./mux21.v"
vlog -work work "./mux21_tb.v"
vsim work.mux21_tb -do simmux.do
```

simmux.do

```
restart -f
add wave sim:/mux21_tb/*
run -all
# quit
```


```
$ ./runmux.scr
```

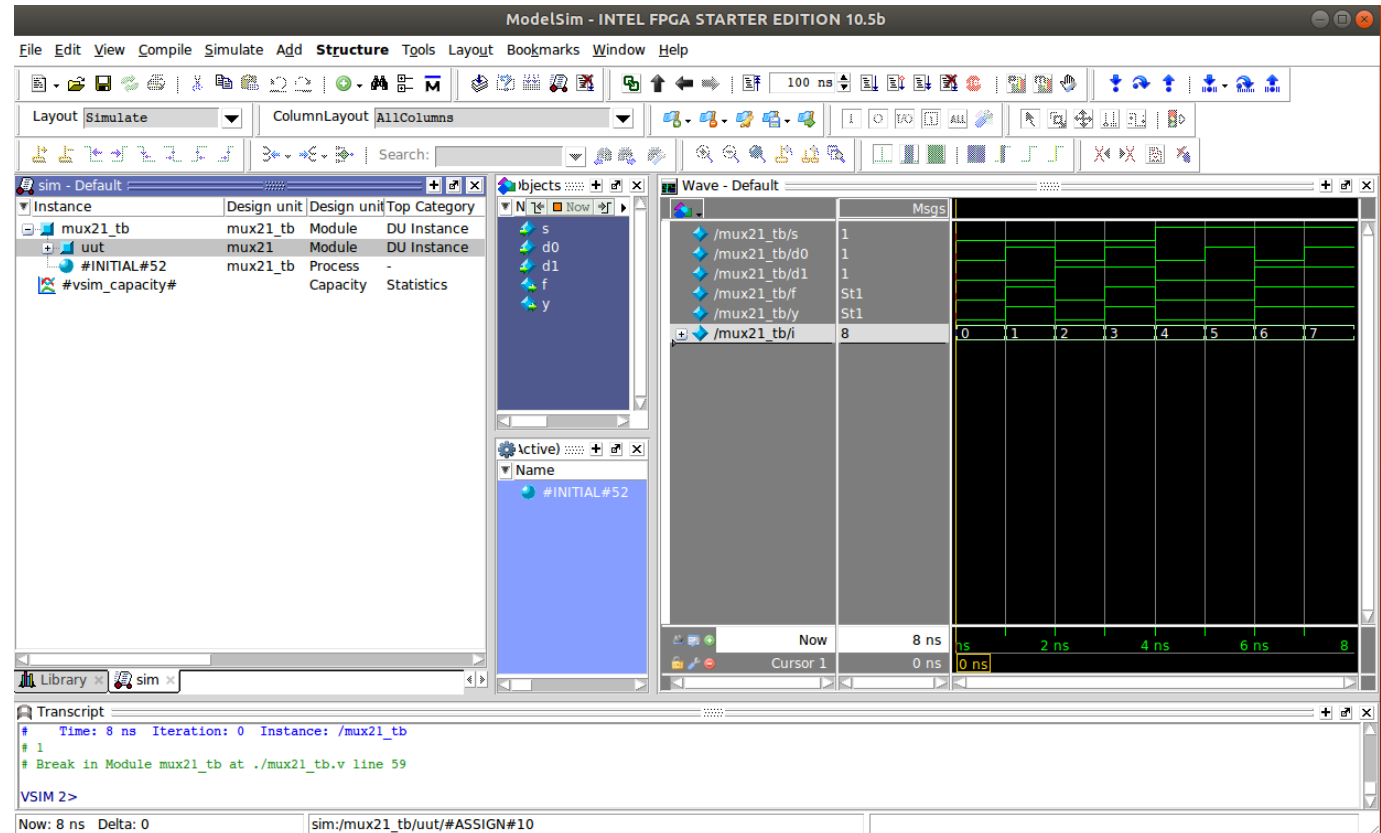

A first look at Verilog (Quartus)




```
$ quartus mux21.qpf
```

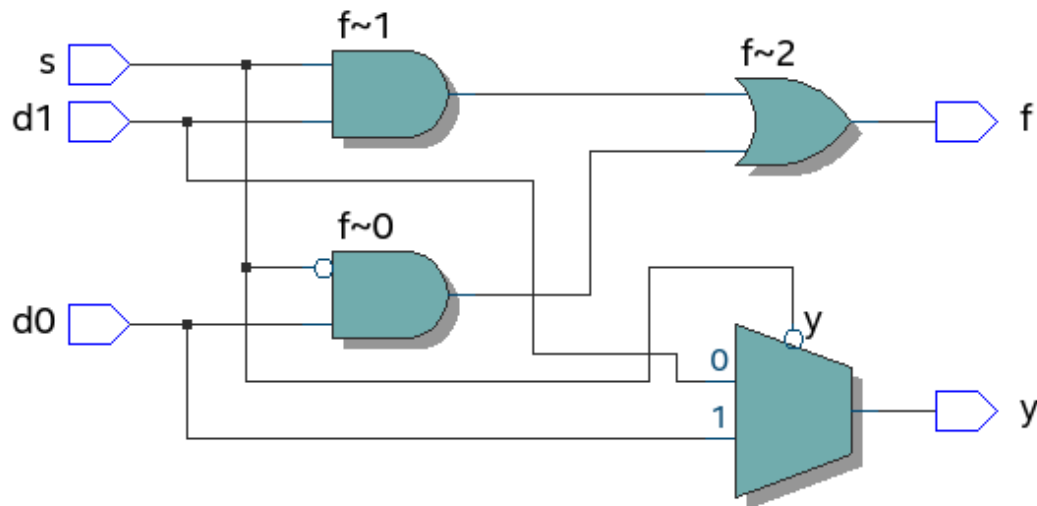From Verilog code (Boolean equations) to gates




Use RTL Viewer to check the circuit synthesized

Two-variable Karnaugh Map

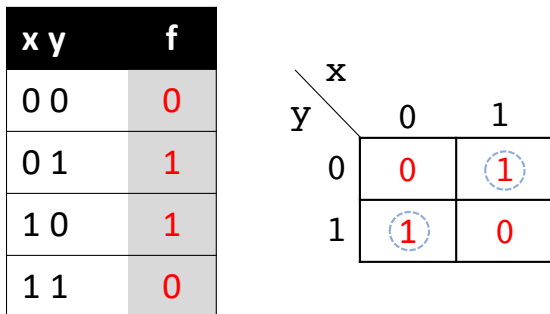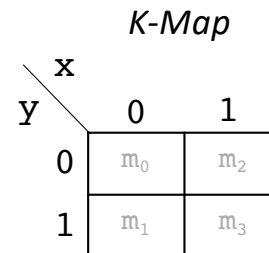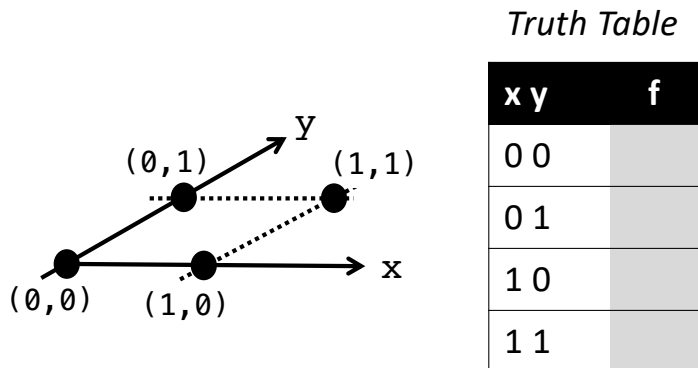
 
$$f = \bar{x} \cdot y + x \cdot \bar{y} = x \oplus y$$



$$g = \bar{x} \cdot y + x \cdot y = y \cdot (\bar{x} + x) = y$$


combining theorem

The K-map makes much easier to “visualize” that there is an opportunity to simplify the logic equation (eliminate a variable using the combining theorem)


Digression: XOR (^) and XNOR (~^) gates

		x	
		0	1
y {	0	0	1
	1	1	0

x	y	f
0	0	0
0	1	1
1	0	1
1	1	0

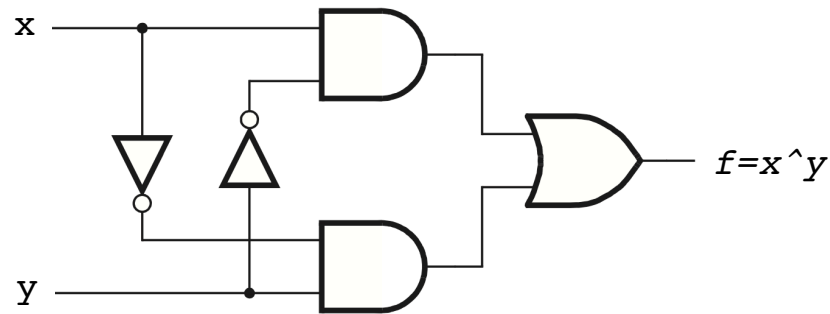

SOP implementation of XOR

 

mux-based implementation of XOR

De Morgan

$$f = x \oplus y = \bar{x} \cdot y + x \cdot \bar{y} = [(x + \bar{y}) \cdot (\bar{x} + y)]'$$

$$f' = \overline{x \oplus y} = \bar{\bar{x} \cdot y + x \cdot \bar{y}} = \overline{\bar{x} \cdot y} + \overline{x \cdot \bar{y}} = (x + \bar{y}) \cdot (\bar{x} + y)$$

Read the K-Map minterms that are at 0 *"Flip" the expressions of f*

Digression: XOR and XNOR gates

x	y	f
0	0	0
0	1	1
1	0	1
1	1	0

XOR

x	y	f'
0	0	1
0	1	0
1	0	0
1	1	1

XNOR

$$f = x \oplus y = \bar{x} \cdot y + x \cdot \bar{y}$$


$$f' = \overline{x \oplus y} = \bar{x} \cdot \bar{y} + x \cdot y \triangleq x \odot y$$

The XNOR is also called the ***coincidence*** operator \odot

XOR and XNOR properties

$$f = x \oplus y = \bar{x} \cdot y + x \cdot \bar{y} = [(x + \bar{y}) \cdot (\bar{x} + y)]'$$
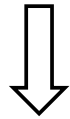
$$f' = \overline{x \oplus y} = \bar{\bar{x} \cdot y + x \cdot \bar{y}} = \overline{\bar{x} \cdot y} + \overline{x \cdot \bar{y}} = (x + \bar{y}) \cdot (\bar{x} + y)$$



$$x \oplus 0 = x \quad (= x \cdot 1 + x' \cdot 0)$$

$$x \oplus 1 = x' \quad (= x \cdot 0 + x' \cdot 1)$$

$$x \oplus x = 0$$

$$x \oplus x' = 1$$


$$x \oplus y = y \oplus x$$

$$x \oplus y \oplus z = (x \oplus y) \oplus z = x \oplus (y \oplus z)$$

$$x(y \oplus z) = xy \oplus xz$$

$$x \oplus y' = (x' \cdot y' + x \cdot y'') = \overline{x \oplus y} = x' \oplus y \quad (= x' \cdot y' + x'' \cdot y)$$

Three-variable Karnaugh Map

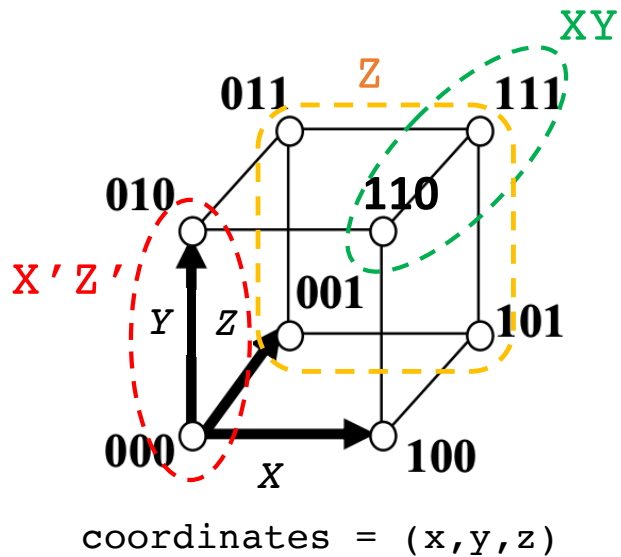







K-Map

		yx			
z		00	01	11	10
0		m_0	m_1	m_3	m_2
1		m_4	m_5	m_7	m_6

		x			
		00	01	11	10
yx	z				
	0	m_0	m_1	m_3	m_2
	1	m_4	m_5	m_7	m_6
		y			

- Clusters of 1 square are minterms
- Clusters of 2 squares eliminate one variable
- Clusters of 4 squares eliminate two variables
- Clusters of 8 squares eliminate three variables
- ...

Logic minimization with K-maps

      

K-map minimization rules

- Each cluster must span a power of 2 (i.e. 1, 2, 4) squares in each direction
- Each cluster must be as large as possible
- A cluster may wrap around the edges of the K-map
- A one in a K-map may be clustered multiple times
- A “don't care” (*d* or *–*) is clustered only if it helps minimize the equation

K-Map definitions (1)

- The basic principle for simplifying SOPs equations is to combine terms using the relationship $P \cdot A + P \cdot A' = P$ (where P may be any product of literals)
- **Implicant** = product of literals
- An equation in SOP form is **minimized** if it uses the least expensive set of implicants
- An implicant is called a **prime implicant** if it cannot be combined with any other implicants to form a new implicant with fewer literals (prime implicants correspond to the largest K-map clusters).
- The implicants in a minimized equation must all be prime implicants, otherwise, they could be combined to reduce the number of literals. However, not all existing prime implicants are needed in forming a minimized equation.

K-Map definitions (2)

- An essential prime implicant is a prime implicant that cover an output of the function that no combination of other prime implicants is able to cover

Example


		yx			
z		00	01	11	10
	0	0	0	1	1
	1	0	1	1	0

$$y \cdot z' + x \cdot z$$

$x \cdot y$ is a prime implicant,
however is not necessary





- Certain functions may have more than one minimized SOP form

Four-variable K-Map

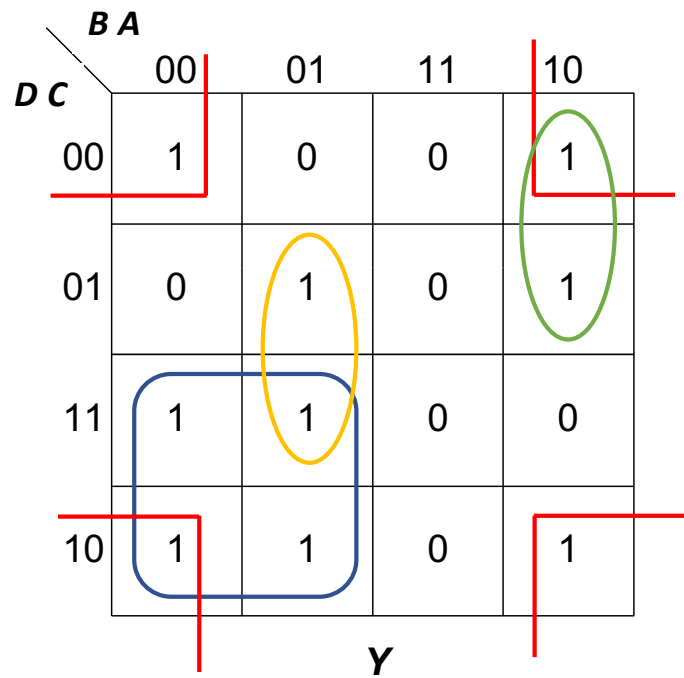


$$Y = C'A' + DB' + CB'A + D'BA'$$

Four-variable K-Map (few more examples)

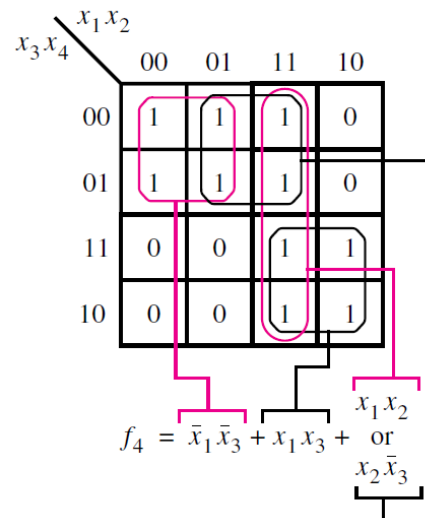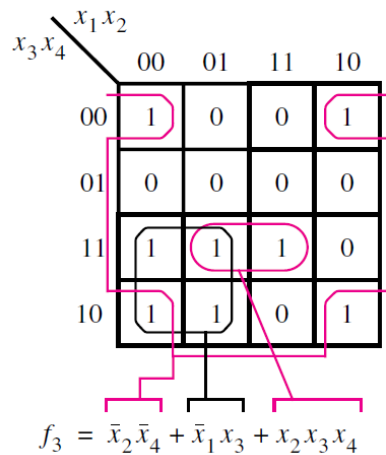  

The function f_4 has two possible SOP minimal forms

Five-variable K-Map

 

This is nothing else than a “graphical representation” of Shannon Expansion’s Theorem


Incompletely specified functions (don't cares)

Sometimes the specification of the digital system we want to design guarantees that certain set of input patterns (i.e. minterms) will never be used.

$$Y = \sum m(0,2,6,8,9,12,13) + \sum d(3,5,7,11,15)$$

$$Y = D + B + \bar{C} \bar{A}$$

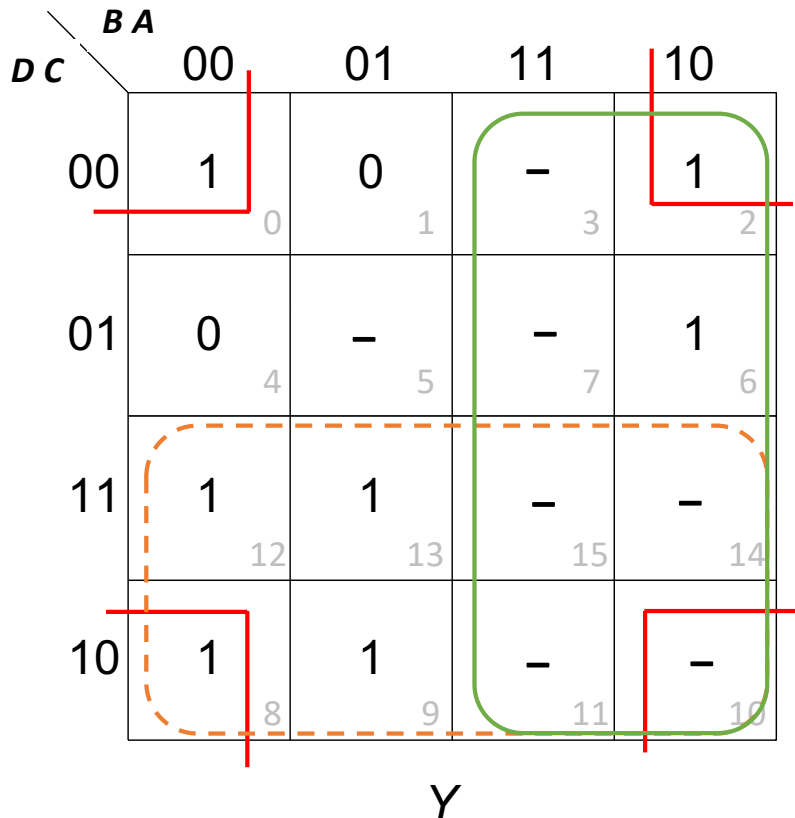NOTE:
besides d and $-$ sometimes people have also the *unfortunate* habit to mark don't cares with X



Map Entered Variables

- With more than 5 variables the K-map rapidly becomes unmanageable. Entering variables in the map reduces the required map size, thereby extending K-maps practical usefulness.
- *In general if a variable P_i is placed in square m_k of a map, this means that $F = 1$ when $P_i = 1$ and the variables of the map are chosen so that $m_k = 1$. Given a map with variables P_1, P_2, \dots , entered into some of the squares, the minimum sum-of-products (MS) expression for F is:*

$$F = MS_0 + P_1 \cdot MS_1 + P_2 \cdot MS_2 + \dots$$

where:

MS_0 is the minimum sum obtained by setting $P_1 = P_2 = \dots = 0$.

MS_1 is the minimum sum obtained by setting $P_1 = 1, P_j = 0 (j \neq 1)$, and replacing all 1's on the map with don't-cares.

MS_2 is the minimum sum obtained by setting $P_2 = 1, P_j = 0 (j \neq 2)$ and replacing all 1's on the map with don't-cares.

		yx			
		00	01	11	10
z	0	w	0	1	1
	1	1	w'	w'	1

Map Entered Variables

		yx			
		00	01	11	10
z	0	w	0	1	1
	1	1	w'	w'	1

		yx			
		00	01	11	10
z	0	0	0	1	1
	1	1	0	0	1

$MS_0 = z'y + zx'$

		yx			
		00	01	11	10
z	0	1	0	-	-
	1	-	0	0	-

$MS_1 = wx'$


		yx			
		00	01	11	10
z	0	0	0	-	-
	1	-	1	1	-

$MS_2 = w'z$

$$f = MS_0 + MS_1 + MS_2 = z'y + \boxed{zx'} + wx' + w'z = z'y + wx' + w'z$$

zx' is a consensus term w.r.t.
 wx' and $w'z$

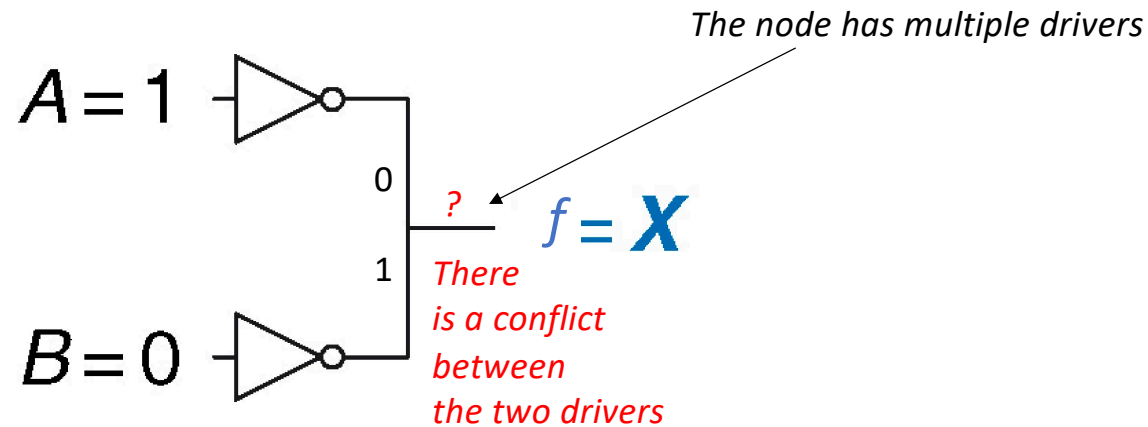
Contention (illegal or indeterminate value X)



*NOTE: When you see a "X" careful with the meaning: the notation X is over-abused !
Sometime X is also used for meaning don't care and sometime for meaning undefined
(undefined U is different than indeterminate !)*

Floating Value (Z = High Impedance)

Tri-State Buffer

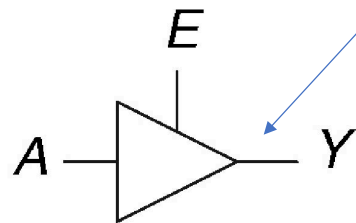


For $E=0$ the node Y is left floating

E	A	Y
0	0	Z
0	1	Z
1	0	0
1	1	1

There are three possible output states:
HIGH (1), LOW(0), and floating (Z)


© 2007 Elsevier, Inc. All rights reserved

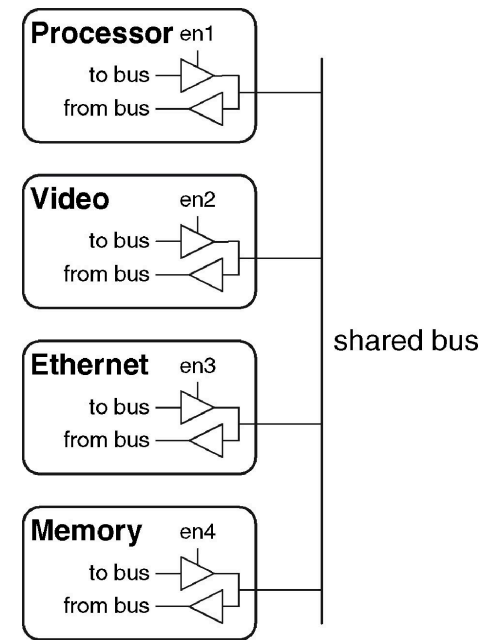In the rather common case that multiple devices need to share a communication bus (shared interconnection) a solution to avoid contention is to use tri-state buffers.



© 2007 Elsevier, Inc. All rights reserved


Tri-state buffer

 


EN	A	Y
0	0	Z
0	1	Z
1	0	1
1	1	0

↑
This is **NOT** a tri-state buffer!
It is a tri-state inverter

Tri-state buffer

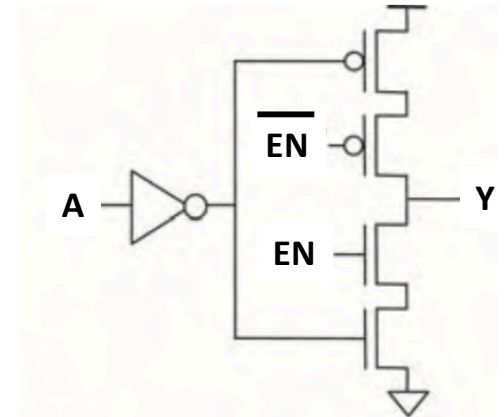


Open Drain Buffer

 

Next Time

- Multiple-output circuits
- Binary Representations and Binary Arithmetic

Problem

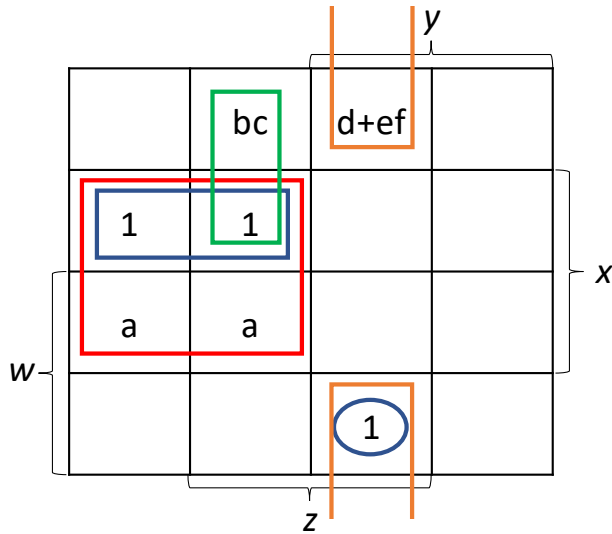

$$MS_0 = w'xy' + wx'yz$$

$$(a=1) \quad MS_1 = axy'$$

$$(bc=1) \quad MS_2 = bcw'y'z$$

$$(d+ef=1) \quad MS_3 = (d + ef)x'yz$$



$$F = w'xy' + wx'yz + axy' + bcw'y'z + (d + ef)x'yz$$

Binary Representations and Arithmetic

CPEN 230 – Introduction to Digital Logic

Review: first steps in Verilog

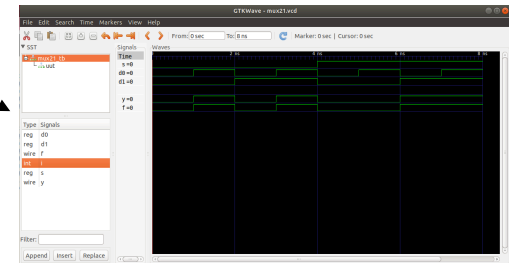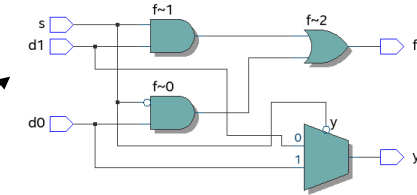- RTL code for the entry of the circuit (Hardware Implementation)
- Behavioral code the testbench (Verification of Functionality)



```
// filename: mux21.v
// two possible coding styles for implementing a 2:1 multiplexer
```

```
module mux21(s,d1,d0,f,y);
  input s, d0, d1;
  output f, y;
```

```
  reg y;
```

```
  assign f = (~s & d0) | (s & d1);
```

```
  always@*
```

```
    if (~s)
```

```
      y = d0;
```

```
    else
```

```
      y = d1;
```

```
endmodule
```

blocking assignment


blocking assignment

concurrent coding style


*procedural coding style
(higher level of abstraction)*

Review: from equations to gates

 - Equations in SOP and POS form result in 2-level logic circuits




 cost = total number of inputs to the logic gates plus number of gates (don't count inversions)



- Minimal SOP and POS are not necessarily the only option nor the “best” option

cost = 8 inputs + 3 gates = 11

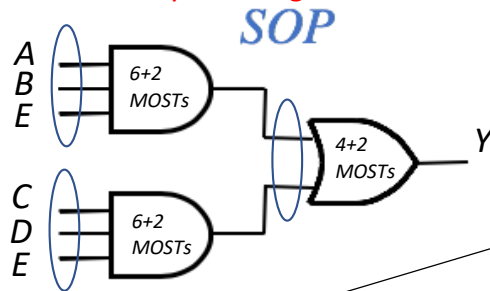


Total MOSTs: 22

Minimal Cost ?
Facts Checking

4-level NAND-NAND circuit

cost = 8 inputs + 4 gates = 12

 

Total MOSTs: $4 \times 4 + 2 = 18$

... And, at least for now, let's sweep the issue of speed under the rug!

Verilog is your friend !


// filename: level3.v
// example showing 4-level logic function vs. SOP

```
module level3(a,b,c,d,e,y,z);
  input a, b, c, d, e;
  output y, z;

  wire n1, n2, n3;

  assign n1 = ~(a & b);
  assign n2 = ~(c & d);
  assign n3 = ~(n1 & n2);

  assign y = (n3 & e); // 4-level nand-nand
  assign z = (a & b & e) | (c & d & e); // sop
endmodule
```

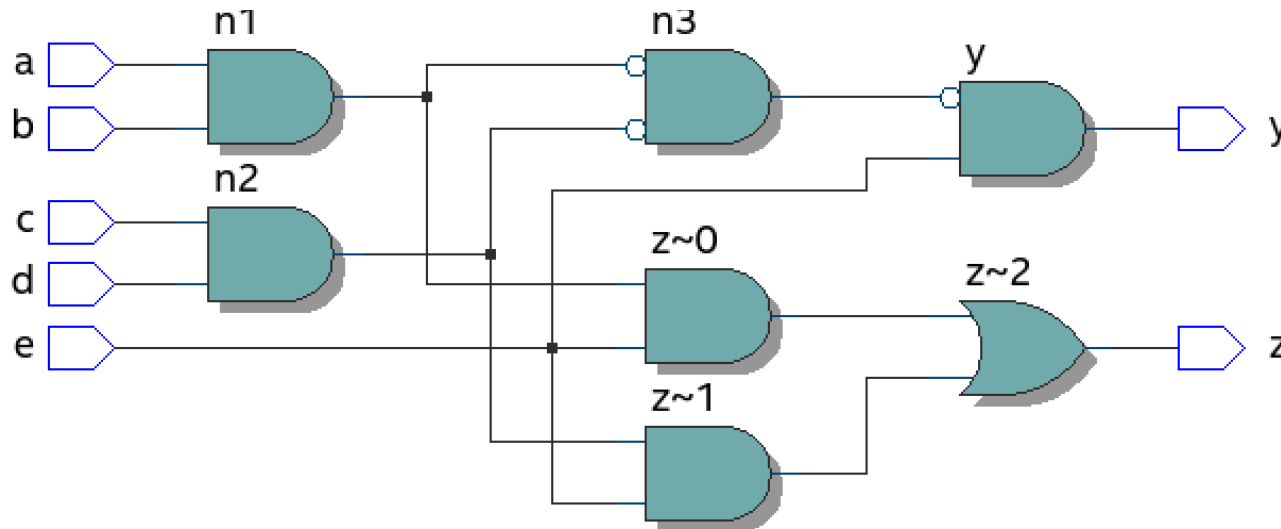


... both for enhancing understanding
and sparing tedious work

row	abcde	y	z
0	00000	0	0
1	00001	0	0
2	00010	0	0
3	00011	0	0
4	00100	0	0
5	00101	0	0
6	00110	0	0
7	00111	1	1
8	01000	0	0
9	01001	0	0
10	01010	0	0
11	01011	0	0
12	01100	0	0
13	01101	0	0
14	01110	0	0
15	01111	1	1
16	10000	0	0
17	10001	0	0
18	10010	0	0
19	10011	0	0
20	10100	0	0
21	10101	0	0
22	10110	0	0
23	10111	1	1
24	11000	0	0
25	11001	1	1
26	11010	0	0
27	11011	1	1
28	11100	0	0
29	11101	1	1
30	11110	0	0
31	11111	1	1

CDAB	Y
0000	1
0001	1
0010	1
0011	0
0100	1
0101	0
0110	0
0111	0
1000	1
1001	0
1010	0
1011	0
1100	1
1101	0
1110	0
1111	0

Review: from equations to gates

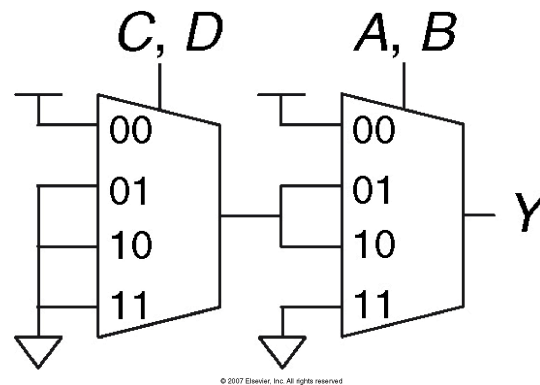
- “Just another brick in the wall”: building logic circuits using muxes



Expressing Boolean functions in terms of if-else statements and case statements is usually more “natural” than any other approach.

$$Y = A' \cdot B' + A' \cdot C' \cdot D' + B' \cdot C' \cdot D'$$

Building logic circuits using muxes.

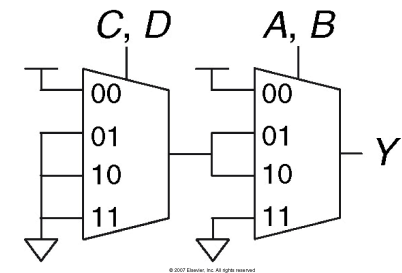

```
// filename: lec5.v
// example showing how to build logic functions using "muxes"
```

```
module lec5(a,b,c,d,f,y);
  input a, b, c, d;
  output f, y;


  reg y;

  assign f = (~a & ~b) | (~a & ~c & ~d) | (~b & ~c & ~d);

  always @*
  begin
    if (a == 0 && b == 0)
      y = 1;
    else if (a == 1 && b == 1)
      y = 0;
    else if (c == 0 && d == 0)
      y = 1;
    else
      y = 0;
  end
endmodule
```

SOP canonical form

logical and

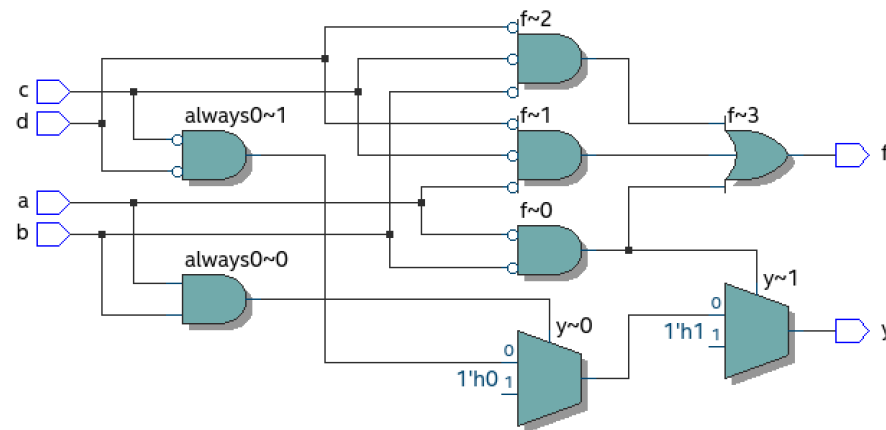

row	cdab	y	f
0	0000	1	1
1	0100	1	1
2	1000	1	1
3	1100	0	0
4	0001	1	1
5	0101	0	0
6	1001	0	0
7	1101	0	0
8	0010	1	1
9	0110	0	0
10	1010	0	0
11	1110	0	0
12	0011	1	1
13	0111	0	0
14	1011	0	0
15	1111	0	0

Review: K-maps and minimization

		yx			
		00	01	11	10
z	0	w	0	1	1
	1	1	w'	w'	1

		yx			
		00	01	11	10
z	0	0	0	1	1
	1	1	0	0	1

$$MS_0 = z'y + zx'$$

		yx			
		00	01	11	10
z	0	1	0	-	-
	1	-	0	0	-

$$MS_1 = wx'$$


		yx			
		00	01	11	10
z	0	0	0	-	-
	1	-	1	1	-

$$MS_2 = w'z$$

$$f = MS_0 + MS_1 + MS_2 = z'y + \boxed{zx'} + wx' + w'z = z'y + wx' + w'z$$

zx' is a consensus term w.r.t.
 wx' and $w'z$

Multiple-output Circuits

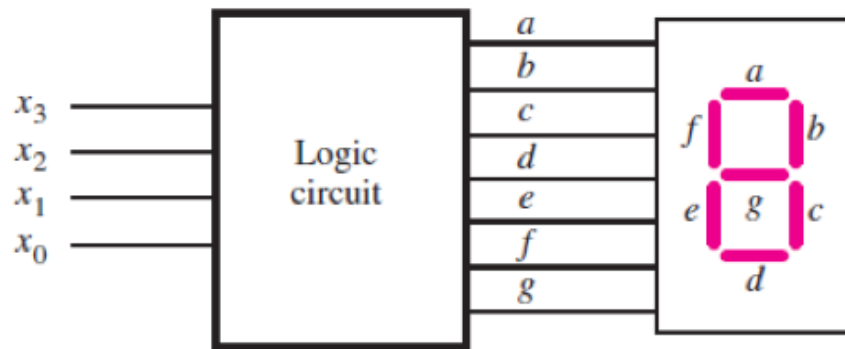

To design the logic circuit interfacing the 7-segment display we need to write a logic function for each output (a, b, c, d, e, f, g)

e.g. write a K-map for each output (a, b, c, d, e, f, g)

	x_3	x_2	x_1	x_0	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	1	0	1	1
	1	0	1	0	0	0	0	0	0	0	0
	1	0	1	1	0	0	0	0	0	0	0
	1	1	0	0	0	0	0	0	0	0	0
	1	1	0	1	0	0	0	0	0	0	0
	1	1	1	0	0	0	0	0	0	0	0
	1	1	1	1	0	0	0	0	0	0	0

K-map for output a

		$x_1 x_0$			
		00	01	11	10
$x_3 x_2$	00	1	0	1	1
	01	0	1	1	1
	11	0	0	0	0
	10	1	1	0	0

x_3	x_2	x_1	x_0	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	0	0	0	0	0	0	0	0
1	0	1	1	0	0	0	0	0	0	0
1	1	0	0	0	0	0	0	0	0	0
1	1	0	1	0	0	0	0	0	0	0
1	1	1	0	0	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

$$a = \overline{x_3} \cdot x_1 + \overline{x_3} \cdot x_2 \cdot x_0 + x_3 \cdot \overline{x_2} \cdot \overline{x_1} + \overline{x_2} \cdot \overline{x_1} \cdot \overline{x_0}$$

Binary “patterns” (Codes and Numbers)

- *Beauty lies in the eye of the Beholder:*
the same “string” of binary digits (bits) may mean very different things !
Example: “1111” = $+15_{10}$ or “1111” = -1_{10}

Decimal number	Binary code	Octal code	Hexadecimal code	Gray code	BCD code
0	0000	00	0	0000	0000
1	0001	01	1	0001	0001
2	0010	02	2	0011	0010
3	0011	03	3	0010	0011
4	0100	04	4	0110	0100
5	0101	05	5	0111	0101
6	0110	06	6	0101	0110
7	0111	07	7	0100	0111
8	1000	10	8	1100	1000
9	1001	11	9	1101	1001
10	1010	12	A	1111	0001 0000
11	1011	13	B	1110	0001 0001
12	1100	14	C	1010	0001 0010
13	1101	15	D	1011	0001 0011
14	1110	16	E	1001	0001 0100
15	1111	17	F	1000	0001 0101

Codes representing decimal numbers from 0 to 15

Codes and Numbers

b ₃ b ₂ b ₁ b ₀	b ₆ b ₅ b ₄							
	000	001	010	011	100	101	110	111
0000	NULL	DLE	SP	0	@	P	`	p
0001	SOH	DC1	!	1	A	Q	a	q
0010	STX	DC2	"	2	B	R	b	r
0011	ETX	DC3	#	3	C	S	c	s
0100	EOT	DC4	\$	4	D	T	d	t
0101	ENQ	NAK	%	5	E	U	e	u
0110	ACK	SYN	&	6	F	V	f	v
0111	BEL	ETB	'	7	G	W	g	w
1000	BS	CAN	(8	H	X	h	x
1001	HT	EM)	9	I	Y	i	y
1010	LF	SUB	*	:	J	Z	j	z
1011	VT	ESC	+	;	K	[k	{
1100	FF	FS	,	<	L	\	l	
1101	CR	GS	-	=	M]	m	}
1110	SO	RS	.	>	N	^	n	~
1111	SI	US	/	?	O	_	o	DEL

ASCII code.

Unsigned Integer Numbers

Range of N -bit numbers: $[0, 2^N - 1]$

- The most straightforward approach to represent an unsigned number in binary notation is to use the same *positional notation* we have been using with decimal (base 10) numbers since grade school.

The unsigned integer number X has $N=3$ digits (a_2, a_1, a_0) and is represented in base (Radix) $R=10$.

$$X = 256_{10} = 2 \times 10^2 + 5 \times 10^1 + 6 \times 10^0$$

In radix 10 using $N=3$ digits we can represent the numbers in the range $[0, 999] = [0, 10^N - 1]$

- In summary (even if we probably never gave too much thought to it) we use a power series expansion.

$$X = (a_{N-1} a_{N-2} \cdots a_1 a_0)_R = \sum_{i=0}^{N-1} a_i R^i$$

Where a_i is the coefficient associated to R^i and can take the values in the range $0 \leq a_i \leq R - 1$


- So in the case of binary notation the interpretation is as follows:

$$X = 111101_2 = 1 \times 2^5 + 1 \times 2^4 + 1 \times 2^3 + 1 \times 2^2 + 0 \times 2^1 + 1 \times 2^0 = 61_{10}$$

must be an odd number

With $N=6$ binary digits we can represent the numbers in the range $[0, 111111_2] = [0, 63_{10}]$

Unsigned Numbers Wheel

 

Powers of 2

To convert between binaries and decimal numbers is useful to memorize the powers of 2 (up to 2^{10})

- $2^0 = 1$
- $2^1 = 2$
- $2^2 = 4$
- $2^3 = 8$
- $2^4 = 16$
- $2^5 = 32$
- $2^6 = 64$
- $2^7 = 128$

- $2^8 = 256$
- $2^9 = 512$
- $2^{10} = 1024$
- $2^{11} = 2048$
- $2^{12} = 4096$
- $2^{13} = 8192$
- $2^{14} = 16384$
- $2^{15} = 32768$

Large powers of 2


- $2^{10} = 1024$ = 1 kilo $\approx 1 \text{ thousand} = 10^3$
- $2^{20} = 1,048,576$ = 1 mega $\approx 1 \text{ million} = 10^6$
- $2^{30} = 1,073,741,824$ = 1 giga $\approx 1 \text{ billion} = 10^9$

Example:

Memorizing the powers of 2 helps finding the “meaning” of a binary quickly

2^5 2^1 2^0

$X = 111101_2$

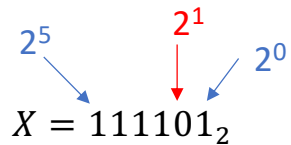

$$111111_2 = 2^6 - 1 = 63$$

$$X = 111101_2 = 63 - 2^1 = 61$$

Unsigned Integers: Decimal to Binary Conversion

- Two methods:
 - **Method 1:** Find the largest power of 2 that fits, subtract and repeat
 - **Method 2:** Repeatedly divide by 2, remainder goes in next most significant bit

Unsigned Integers. Decimal to Binary Conversion Example

Method 1: Find the largest power of 2 that fits, subtract and repeat

53_{10}	32×1	$(32 = 2^5)$
$53 - 32 = 21$	16×1	$(16 = 2^4)$
$21 - 16 = 5$	4×1	$(4 = 2^2)$
$5 - 4 = 1$	1×1	$(1 = 2^0)$

$$= 110101_2$$

Method 2: Repeatedly divide by 2, remainder goes in next most significant bit

$53_{10} =$	$53/2 = 26$	R	1 (MSB)
	$26/2 = 13$	R	0
	$13/2 = 6$	R	1
	$6/2 = 3$	R	0
	$3/2 = 1$	R	1
	$1/2 = 0$	R	1 (LSB)


$$= 110101_2$$

Unsigned Fractional Numbers

- For unsigned fractional binary numbers we continue to use the same notation we have been using for the decimals

$$X = 953.78_{10} = 9 \times 10^2 + 5 \times 10^1 + 3 \times 10^0 + 7 \times 10^{-1} + 8 \times 10^{-2}$$

- i.e. an unsigned fractional number X in base R is given by the following power series expansion:


$$X = (a_{N-1} a_{N-2} \cdots a_1 a_0 . a_{-1} \cdots a_{-M})_R = \sum_{i=-M}^{N-1} a_i R^i$$

- So in the case of binary notation the interpretation is:

$$X = 1011.01_2 = 1 \times 2^4 + 1 \times 2^3 + 0 \times 2^2 + 1 \times 2^1 + 1 \times 2^0 + 0 \times 2^{-1} + 1 \times 2^{-2} = 27.25_{10}$$

Conversion of a fraction from decimal to a binary

- The conversion of a decimal fraction can be done using successive multiplications by the radix R (rather than by successive division by R , as done for the non-fractional part)

$$F = (. a_{-1} \cdots a_{-M})_R = \sum_{i=-M}^{-1} a_i R^i = a_{-1} \times R^{-1} + a_{-2} \times R^{-2} + \cdots + a_{-M} \times R^{-M}$$



$$F \cdot R = a_{-1} + a_{-2} \times R^{-1} + \cdots + a_{-M} \times R^{-M+1} = a_{-1} + F_1$$

$$F_1 \cdot R = a_{-2} + a_{-3} \times R^{-1} \cdots + a_{-M} \times R^{-M+2} = a_{-2} + F_2$$

etc.

- This process is continued until we have obtained a “sufficient” number of digits.

Converting fractions from decimal to binary

Example

Repeatedly multiply by 2. The integer part obtained at each step gives the desired digits (starting from the MSB a_{-1} to the LSB)

0.625_{10}	$0.625 \times 2 = 1.250$	1	$(a_{-1} = 1)$
	$0.250 \times 2 = 0.5$	0	$(a_{-2} = 0)$
	$0.5 \times 2 = 1$	1	$(a_{-3} = 0)$

The process terminates when the product equals 1. However, the process does not always terminate, but if it doesn't, the result is a repeating fraction.

Converting fractions from decimal to binary

Example

0.7_{10}	$0.7 \times 2 = 1.4$	1	$(a_{-1} = 1)$	
	$0.4 \times 2 = 0.8$	0	$(a_{-2} = 0)$	
	$0.8 \times 2 = 1.6$	1	$(a_{-3} = 1)$	
	$0.6 \times 2 = 1.2$	1	$(a_{-4} = 1)$	
	$0.2 \times 2 = 0.4$	0	$(a_{-5} = 0)$	← Process start repeating here because 0.4 was previously obtained

$$0.7_{10} = 0.1 \underbrace{0110} \underbrace{0110} \underbrace{0110} \dots_2$$

Addition of unsigned binaries

- Decimal

$$\begin{array}{r} 11 \leftarrow \text{carries} \\ 3734 \\ + 5168 \\ \hline 8902 \end{array}$$

- Binary

$$\begin{array}{r} 11 \leftarrow \text{carries} \\ 1011 \\ + 0011 \\ \hline 1110 \end{array}$$

bit-wise addition rules

a	b	sum	carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	2 → 0	1

Unsigned Binary Addition Example

- Add the following 4-bit binary numbers

$$\begin{array}{r} 1 \\ 1001 \\ + 0101 \\ \hline 1110 \end{array}$$

- Add the following 4-bit binary numbers

$$\begin{array}{r} 111 \\ 1011 \\ + 0110 \\ \hline 10001 \end{array}$$

Overflow!



- Digital systems operate on a **fixed number of bits**
- Overflow: the result is too big to fit in the available number of bits (with 4 bits we can represent the range [0, 15])

$$\begin{array}{r} 9 \\ + 5 \\ \hline 14 \end{array}$$

$$\begin{array}{r} 11 \\ + 6 \\ \hline 17 \end{array}$$

Signed Integer Numbers

  - Sign-Magnitude Notation
- Two's Complement Notation



We $2^N - 1$ binary patterns and we want to use "some" for representing positive quantities and some for negative quantities

Sign/Magnitude Notation

- Let's use the most significant digit for the sign and the remaining $N-1$ digits for the magnitude.
 - and let's denote positive sign with 0 and negative sign with 1

$$X = (a_{N-1} a_{N-2} \cdots a_1 a_0)_R = (-1)^{a_{N-1}} \sum_{i=0}^{N-2} a_i R^i$$

- This is pretty much the same approach we have been using with decimal numbers. But ... since with decimal numbers we have no limits on the amount of symbols available rather than representing the sign recycling the digits we use the symbol + (to denote positive) and – (to denote negative).
- The range of an N -bit sign/magnitude binary number X is:
$$X \in [-(2^{N-1}-1), (2^{N-1}-1)]$$

Problems with Sign and Magnitude Notation

- There are two representations for the number 0:

1000
0000

- Addition doesn't work!

+6 = 0110
-6 = 1110

6
+ (-6) =

0

0110
+ 1110 =

10100

WRONG !

In decimal this would be $-2^2 = -4$

Any other idea ?

- What makes the subtraction challenging is borrowing.
Can we do a subtraction without ever having to borrow ?

YES WE CAN !



$$\begin{array}{r} 100 \\ - 17 = \\ \hline 83 \end{array}$$

$$\begin{array}{r} 99 \\ - 17 \\ \hline 82 \end{array} + 1 = 83$$

9 is the greatest digit:
so subtracting from 99
does not require borrows

Complement-Radix and Complement-Radix-diminished

$$\begin{array}{r} 99 \\ - 17 \\ \hline \end{array}$$

$$82 + 1 = 83$$

$X^* = 82$ is called the complement-radix-diminished of $X=17$ -->
 Since in our example $R=10$ --> **$X^*=82$ is the complement-9 of $X=17$**

$$X^* + X = 99 = R^N - 1$$

$$\mathbf{X^*+X+1 = 100 = R^N}$$

If our system can only handle up to $N=2$ digits, then $17+83 = 00$ and therefore $83 = 00 - 17 = -17$.
 In other words in our system what 83 really represents is the value -17 .

$83 = X^* + 1 \triangleq X^\#$ is called the complement radix of $X=17$

Since in our example $R=10$ -->

$X^*+1 = X^\# = 83$ is the complement-10 of $X=17$

$$X^*+1+X = X^\#+X = 100 = R^N$$

Further rumination ...

Not all the times the number from which we want to subtract is 100. Can this idea be generalized ?

$Y - X$

$74 - 33 = 41$ Easy: no borrow is needed

$74 - 36 = 38$ Not so easy, because a borrow is needed

$$74 - 36 = 74 + 100 - 100 - 36 = 74 + (100 - 36) - 100 = 74 + \underbrace{(99 + 1 - 36)}_{K_{10} \text{ of } X=36} - 100 = 74 + \underbrace{(99 - 36)}_{K_9 \text{ of } X=36} + 1 - 100$$

easy = 63

$K_{10} = K_9 + 1$

For an N digit number X in base R its R-complement is defined as $K_R = R^N - X$,
while its R-diminished-complement is defined as $K_{R-1} = (R^N - 1) - X$

Thus the required decimal subtraction ($74 - 36$) can be performed by addition of the 10-complement of 36 and deletion of the leading digit:

$$74 - 36 = 74 + 64 - 100 = 138 - 100 = 38$$

The subtraction $138 - 100$ is trivial because it implies ignoring the leading digit (i.e. the carry-out R^N) in 138

Further Rumination ...

Does this really work all the time even when $X < Y$ (in our previous example we used $X \geq Y$) ?

Example 1: $N = 3$

$X = 045, Y = 027$

$$\begin{aligned}X - Y &= 045 - 027 \\&= 045 + 1000 - 1000 - 027 \\&= 045 + (999 - 027) + 1 - 1000 \\&= 045 + 972 + 1 - 1000 \\&= 1018 - 1000 \\&= 018\end{aligned}$$

Example 2: $N = 3$

$X = 027, Y = 045$

$$\begin{aligned}X - Y &= 027 - 045 \\&= 027 + 1000 - 1000 - 045 \\&= 027 + (999 - 045) + 1 - 1000 \\&= 027 + 954 + 1 - 1000 \\&= 982 - 1000\end{aligned}$$

The carry-out ($= 10^3$) can be discarded

$$\begin{aligned}X - Y &= 982 - 1000 \\982 &= X - Y + 1000 \\982 &= 1000 - (Y - X)\end{aligned}$$

982 is the negative number that results when forming the 10's complement of $Y - X = 018$. Thus the number 982 is the 10's complement representation of -18 .

The Two's Complement notation

- In the 2's complement notation a positive number X is represented by a 0 followed by the magnitude as in the sign and magnitude notation, however, a negative number $-X$, is represented by its 2-complement $X^\#$. If a positive number X is represented with N bits, its 2-complement is defined as the word $X^\#$ of length N -bits given by:

$$X^\# = 2^N - X = 2^N - X - 1 + 1 = (2^N - 1 - X) + 1 = X^* + 1$$

$X^\# = \text{complement-2 of } X = \text{complement-1 of } X + 1$

$X^\# = \text{complement-2 of } X = 2^N - X$

$$256 - 97 = 159$$

$X^* = \text{complement-1 of } X = (2^N - 1 - X)$

Example: (N=8) Find the Complement-2 of $X = 97$

$$2^N - 1 = 11111111$$

$$X = 01100001$$

X "flipped" (= not X)

$$X = 97_{10}$$

$$2^N - 1 - X = 10011110 = X^* = X' \longleftarrow X^* = \text{complement-1 of } X (= 2^N - 1 - X)$$

$$+ \quad \quad \quad 1$$

$$X^\# = 10011111 \quad 2^7 + 2^5 - 1 = 128 + 31 = 159$$

$$X^\# = -2^7 + (2^5 - 1) = -128 + 31 = -97_{10}$$

31

$X^\# = \text{complement-2 of } X (= 2^N - X)$

Two's Complement Numbers

- Don't have same problems as sign/magnitude numbers:
 - **Addition works**
 - **There is a single representation for 0**


Two's complement integer numbers

- MSB has value of -2^{N-1}

$$X = a_{N-1}(-2^{N-1}) + \sum_{i=0}^{N-2} a_i \times 2^i$$

- The most significant bit still indicates the sign (1 = negative, 0 = positive)
- Range of an N -bit two's complement number:

$$[-2^{N-1}, +2^{N-1} - 1]$$

 

Taking the Two's Complement

- **Method:**

1. “Flip” (invert) the bits
2. Add 1

Example: Flip the sign of $3_{10} = 0011_2$

1. **1100** ← invert the bits

2. **+ 1**

1101 = -3₁₀

$$\underbrace{-1 \times 2^3 + 1 \times 2^4 + 1 \times 2^0}_{= -8 + 4 + 1 = -3}$$

Two's Complement Examples

- Take the two's complement of $6_{10} = 0110_2$

1. 1001

2. $+ 1$

$$\hline 1010_2 = -6_{10}$$

- What is the decimal value of the two's complement number 1001_2 ? ($-8+1 = -7$)

1. 0110

2. $+ 1$

$$\hline 0111_2 = 7_{10} \rightarrow \text{so } 1001_2 = -7_{10}$$

Two's Complement Addition

*If the two operands are of opposite sign
the result is always within the range of
numbers that can be represented
4 bits range: [-8, 7]*

- Add $6 + (-6)$ using two's complement numbers

$$\begin{array}{r} 111 \\ 0110 \\ + 1010 \\ \hline 10000 \end{array}$$

discard ↗

- Add $-2 + 3$ using two's complement numbers

$$\begin{array}{r} 111 \\ 1110 \\ + 0011 \\ \hline 10001 \end{array}$$

discard ↗

Two's Complement Addition

If adding two operands of the same sign the sign of the result comes out different there is an error (overflow)

- Add $6 + 6$ using two's complement numbers

$$\begin{array}{r} 11 \\ 0110 \\ + 0110 \\ \hline \end{array}$$

12 is out of the range we can represent with 4 bits
(4-bit range $[-8, 7]$)

11100

If we had an extra bit the result would have been just fine ($00110 + 00110 = 01100$)

ERROR

- Add $-6 - 3$ using two's complement numbers

$$\begin{array}{r} 1 \\ 1010 \\ + 1101 \\ \hline \end{array}$$

-9 is out of the range we can represent with 4 bits
(4-bit range $[-8, 7]$)

10111

*If we could have used an extra bit the result would have been just fine
 $11010 + 11101 = 110111$*

ERROR

discard


Increasing Bit Width

Extend number from N to M bits ($M > N$) :

- Sign-extension
- Zero-extension

Sign Extension

 - Sign bit copied to MSB's
- Number value is same
- **Example 1:**
 - 4-bit representation of 3 = 0011
 - 8-bit sign-extended value: 00000011
- **Example 2:**
 - 4-bit representation of -5 = 1011
 - 8-bit sign-extended value: 11111011



Zero Extension

- Zeros copied to MSB's
- Value changes for negative numbers
- Example 1:
 - 4-bit value = $0011 = 3_{10}$
 - 8-bit zero-extended value: $00000011 = 3_{10}$
- Example 2:
 - 4-bit value = $1011 = -5_{10}$
 - 8-bit zero-extended value: $00001011 = 11_{10}$

Signed Fractional Numbers

Example

– 5.75_{10}

First, find the binary representation of (positive) 5.75_{10}

$$5.75_{10} = 0101.1100_2$$

Then convert it to negative using complement 2 notation (as usual invert all bits and add 1 in the LSB position)

$$\begin{array}{r} 0101.1100_2 \longrightarrow 1010.0011_2 \\ + 0000.0001_2 \\ \hline 1010.0100_2 \end{array} \iff -2^3 + 2^1 + 2^{-2} = -8 + 2 + 0.25 = 5.75_{10}$$

$$X = a_{N-1}(-2^{N-1}) + \sum_{i=-M}^{N-2} a_i \times 2^i$$


Signed Binary Numbers (i.e. K_2 Number System)
(Fixed point Notation)

Comparison of Binary Systems

Range of N -bit numbers

System	Range
Unsigned	$[0, 2^N - 1]$
Sign/Magnitude	$[-2^{N-1} + 1, 2^{N-1} - 1]$
Two's Complement	$[-2^{N-1}, 2^{N-1} - 1]$

Comparison of Binary Numbers

 

Number line and 4-bit binary encodings

Binaries vs. Octals and Hexadecimals

Binary = base 2

Octal = base 8

Hexadecimal = base 16

Decimal	Binary	Octal	Hexadecimal
00	00000	00	00
01	00001	01	01
02	00010	02	02
03	00011	03	03
04	00100	04	04
05	00101	05	05
06	00110	06	06
07	00111	07	07
08	01000	10	08
09	01001	11	09
10	01010	12	0A
11	01011	13	0B
12	01100	14	0C
13	01101	15	0D
14	01110	16	0E
15	01111	17	0F
16	10000	20	10
17	10001	21	11
18	10010	22	12

Octals and Hexadecimals are just a short-hand notation of Binaries

Binary/Octal/Hexadecimal conversions

Binary-to-hexadecimal: collect binary digits into groups of four (nibble) and assign each group a hexadecimal digit

0110	1011	0111
6	B	7

Binary-to-octal: Collect binary digits into groups of three and convert each group to the corresponding octal digit

011	010	110	111
3	2	6	7

Hexadecimal-to-binary: Convert each hexadecimal digit to the corresponding binary nibble

A	1	9
1010	0001	1001

Octal-to-binary: Convert each octal digit to the corresponding group of three binary digits

5	0	3	1
101	000	011	001

Next Time

- C.L. Building Blocks
- Gate Delays

C.L. Building Blocks and Gate Delays


CPEN 230 – Introduction to Digital Logic

Review: Binary Numbers Systems

Range of N -bit numbers

System	Range
Unsigned	$[0, 2^N - 1]$
Sign/Magnitude	$[-2^{N-1} + 1, 2^{N-1} - 1]$
Two's Complement	$[-2^{N-1}, 2^{N-1} - 1]$


Review: Binary Numbers Systems

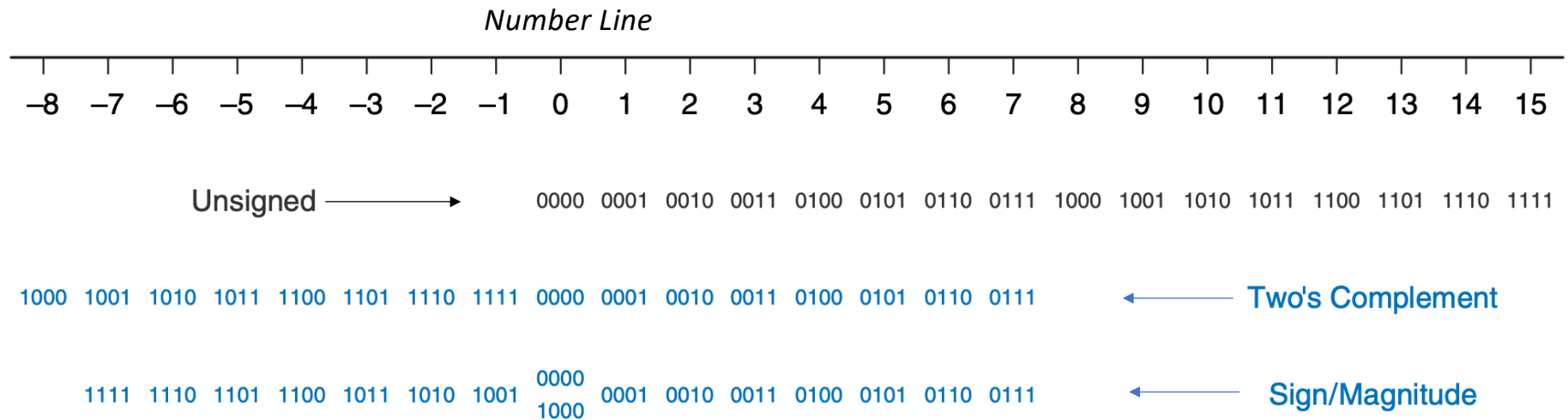

Number line and 4-bit binary encodings


One-bit half adder

a	b	sum	carryout
0	0	0	0
0	1	1	0
1	0	1	0
1	1	2 → 0	1

 

$$S = A \oplus B$$

$$C_{out} = AB$$

 


One-bit Full Adder

$$\begin{array}{r} 1 \\ 0001 \\ +0101 \\ \hline 0110 \end{array}$$

If we need to add multiple bits we must consider whether we have a carry in or not

Figure 5.2 Carry bit

 

S is high when the number of inputs that are high is odd
(*odd-parity function*)

C_{out} is high when two or more inputs are high
(*majority function*)


 
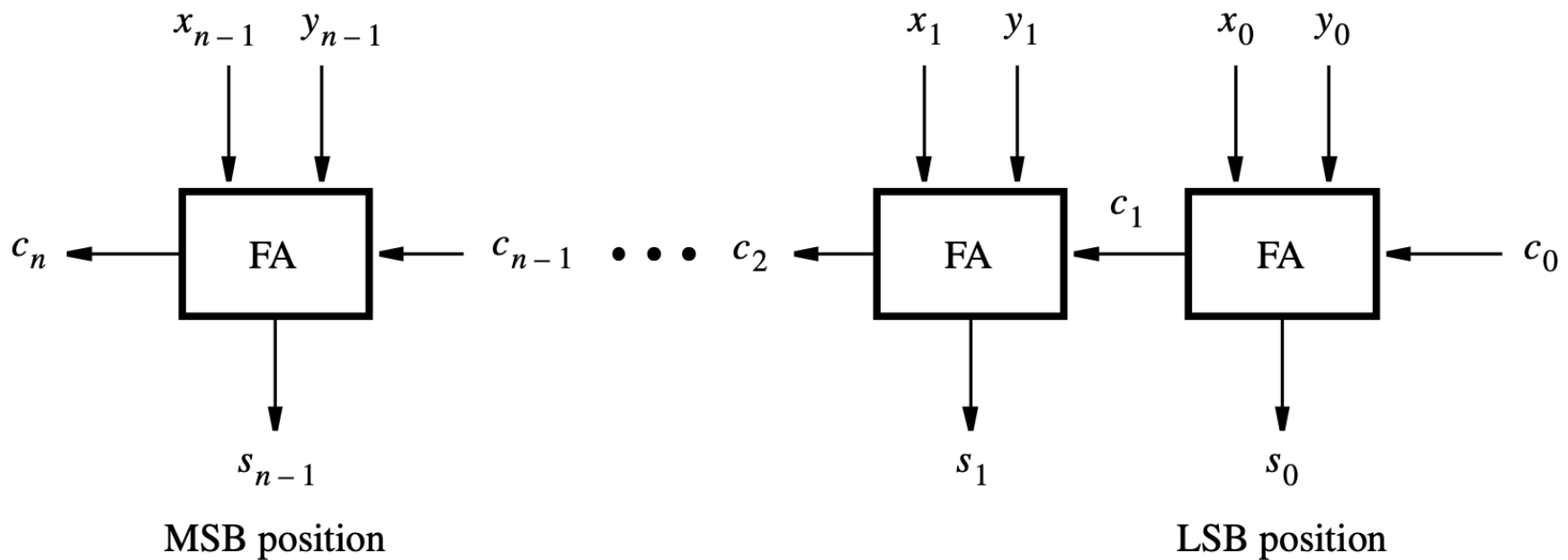


Figure 5.3 1-bit full adder

Multi-bit adder (carry-ripple)

One possible multi-bit adder implementation is given by the carry-ripple architecture

Symbol for multi-bit adder

 

In the LSB position we can use a Half Adder or a Full Adder with c_0 connected to GND

Example: 32-bit ripple-carry adder

 


Figure 5.5 32-bit ripple-carry adder

Example: 4-bit adder in Verilog

```
// filename: adder4.v
// 4-bit adder

module adder4(a, b, ci, co, s);
    input [3:0] a, b;
    input ci;
    output [3:0] s;
    output co;

    assign {co,s} = a + b + ci;
endmodule
```

concatenation



```
// filename: adder4_tb.v
// verify the functionality of adder4.v

// set time tick units and precision to ns
`timescale 1ns / 1ns

module adder4_tb;

    // UUT inputs
    reg [3:0] a;
    reg [3:0] b;
    reg ci;
    // UUT outputs
    wire co;
    wire [3:0] s;

    // instantiate the unit under test (UUT)
    adder4 uut(
        .a(a),
        .b(b),
        .ci(ci),
        .co(co),
        .s(s)
    );

    // initialize inputs
    initial begin
        a = 0;
        b = 0;
        ci = 0;
    end

    // set time format to be ns
    initial $timeformat(-9, 1, "ns", 10);


    // output the simulation in graphical format
    initial begin
        $dumpfile("adder4.vcd");
        $dumpvars(0, adder4_tb);
    end
end
```

```
// generate test patterns
initial begin
    #10;
    a = 4;
    b = 1;
    #10;
    a = 6; ← this test pattern will cause overflow
    b = 2;
    #10;
    a = -1;
    b = -4;
    #10;
    a = -6; ← this test pattern will cause overflow
    b = -3;
    #10;
    $finish;
end

// output the simulation in textual format
initial begin
    $display("time  a    b    ci co  s");
    $display("-----");
    $monitor("%4d  %4b %4b  %1b %1b  %4b",
        $time, a, b, ci, co, s);
end
endmodule
```


time	a	b	ci	co	s	
0	0000	0000	0	0	0000	
10	0100	0001	0	0	0101	
20	0110	0010	0	0	1000	overflow
30	1111	1100	0	1	1011	
40	1010	1101	0	1	0111	overflow

Example: 4-bit adder in Verilog

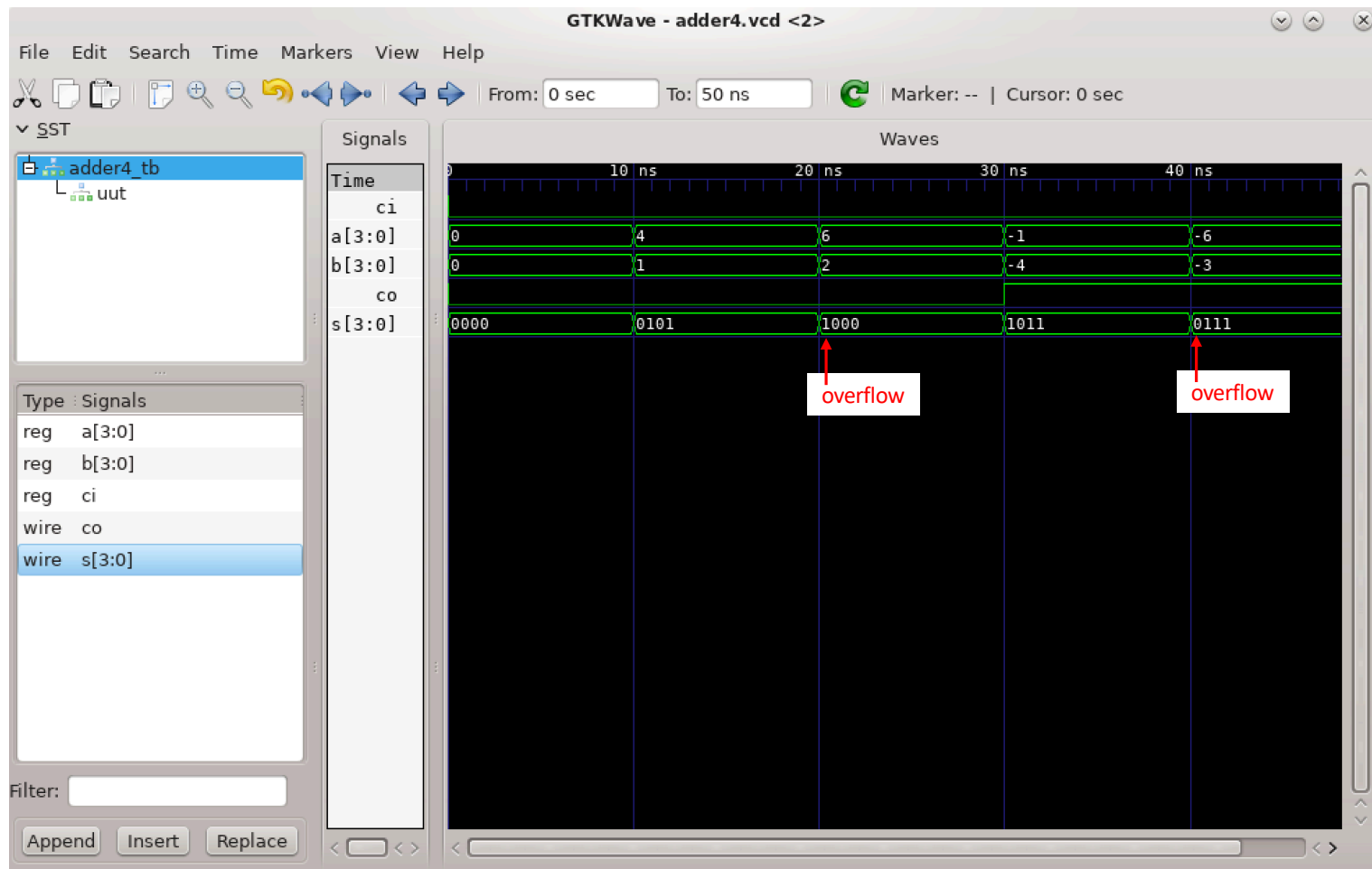

Overflow (N bit adder)

$$V = (a[N - 1] \& b[N - 1] \& \sim s[N - 1]) | (\sim a[N - 1] \& \sim b[N - 1] \& s[N - 1])$$

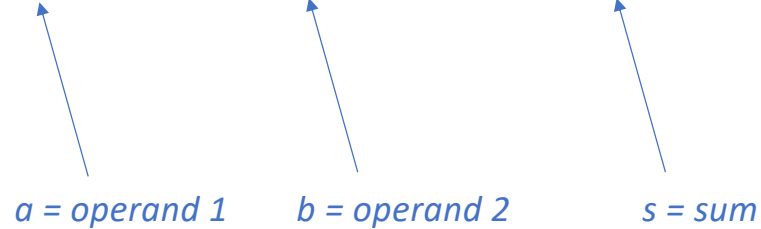
a = operand 1 *b = operand 2* *s = sum*

$$V = s[N - 1] \oplus cout$$

Example: 16 bit adder in Verilog

```
// filename: addern.v
// parameterized n-bit adder
```

```
module addern(ci, a, b, s, co);
  parameter n = 4;
  input [n-1:0] a, b;
  input ci;
  output [n-1:0] s;
  output co;
```

← defining a parameter n with default value 4

```
    assign {co,s} = a + b + ci;
```

```
endmodule
```

```
// file: adder16.v
// 16-bit adder using parameterization
```

```
module adder16(a,b,s,v);
  input [15:0] a,b;
  output [15:0] s;
  output v;
```

← "mapping" the parameter n to 16

```
    addern #(16) u1(1'b0,a,b,s,co);
    assign v = (a[15]&b[15]&~s[15]) | (~a[15]&~b[15]&s[15]);
```


```
endmodule
```

compileadder16.scr


```
#!/bin/bash
vlib work
vlog -work work "./addern.v"
vlog -work work "./adder16.v"
```

Multi-bit subtractor

Symbol

 


Implementation

 



Got a new appreciation for complement-2 notation ?

2:1 Mux

 

S	D_1	D_0	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Figure 2.54 2:1 multiplexer symbol and truth table

  

Circuit with transmission gates



 


Figure 2.56 Multiplexer using tristate buffers


4:1 Mux

 

(a)

 

(b)

 

(c)

Various implementation of 4:1 multiplexer


 



Figure 2.57 4:1 multiplexer

Mux with multi-bit inputs

A multiplexer is a data selector

 

Example

 

Verilog Example (32 bit wide 4-inputs mux)

```
runmux41.scr
```

```
// filename: mux41_32b.v
// 32 bit wide 4:1 mux
```

```
module mux41_32b(s,d3, d2, d1, d0, y);
  input  [1:0] s;
  input  [31:0] d3, d2, d1, d0;
  output [31:0] y;
```

```
  reg [31:0] y;
```

```
  always @*
```

```
  begin
```

```
    case (s)
```

```
      2'b00: y = d0;
```

```
      2'b01: y = d1;
```

```
      2'b10: y = d2;
```

```
      default: y = d3;
```

```
    endcase
```

```
  end
```

```
endmodule
```

*IMPORTANT ASIDE: I "originally" forgot to put [31:0] in front of y
and iverilog did not catch it (fortunately Modelsim caught it!)*

```
# data:
```

```
# -----
```

```
# d0 = 00008888
```

```
# d1 = 1111aaaa
```

```
# d2 = 2222dddd
```

```
# d3 = 3333ffff
```

```
#
```

```
# time  s  y
```

```
# -----
```

```
#    0   0 00008888
```

```
#   10   1 1111aaaa
```

```
#   20   2 2222dddd
```

```
#   30   3 3333ffff
```

```
#!/bin/bash
```

```
vlib work
```

```
vlog -work work "./mux41_32b.v"
```

```
vlog -work work "./mux41_32b_tb.v"
```

```
vsim work.mux41_32b_tb -do simmux41.do
```

```
simmux41.do
```

```
restart -f
```

```
add wave -radix hex sim:/mux41_32b_tb/*
```

```
run -all
```

```
# quit
```

```

// filename: mux41_32b_tb.v
// verify the functionality of mux41_32b.v

// set time tick units and precision to ns
`timescale 1ns / 1ns

module mux41_32b_tb;

    // UUT inputs
    reg [1:0] s;
    reg [31:0] d0;
    reg [31:0] d1;
    reg [31:0] d2;
    reg [31:0] d3;
    // UUT outputs
    wire [31:0] y;

    // instantiate the unit under test (UUT)
    mux41_32b uut(
        .s(s),
        .d3(d3),
        .d2(d2),
        .d1(d1),
        .d0(d0),
        .y(y)
    );

    // initialize inputs
    initial begin
        s = 2'b00;
        d3 = 32'h3333ffff;
        d2 = 32'h2222dddd;
        d1 = 32'h1111aaaa;
        d0 = 32'h00008888;
    end
end

```

<number of bits>'<radix><digits>

```

// set time format to be ns
initial $timeformat(-9, 1, "ns", 10);

// output the simulation in graphical format
initial begin
    $dumpfile("mux41_32b.vcd");
    $dumpvars(0, mux41_32b_tb);
end

// generate test patterns
initial begin
    #10;
    s = 1;
    #10;
    s = 2;
    #10;
    s = 3;
    #10;
    $finish;
end



// output the simulation in textual format
initial begin
    $display("data:");
    $display("-----");
    $display("d0 = %h", d0);
    $display("d1 = %h", d1);
    $display("d2 = %h", d2);
    $display("d3 = %h", d3);
    $display("\ntime s y");
    $display("-----");
    $monitor("%4d %1d %h", $time, s, y);
end

endmodule

```

Decoder

  - Converts an N -bit input into a 2^N -bit output with the output having only one “hot-bit”



x	y
000	00000001
001	00000010
010	00000100
011	00001000
100	00010000
101	00100000
110	01000000
111	10000000

*Truth Table for $N=3$
(3-bit decoder)*

Decoder symbols

Example. 2:4 Decoder

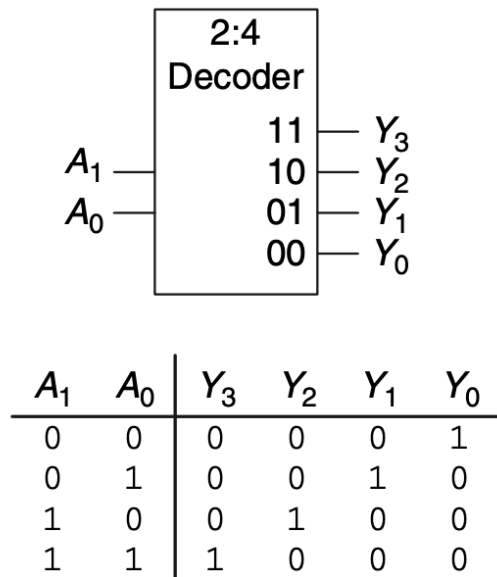


Figure 2.63 2:4 decoder

 


Figure 2.64 2:4 decoder implementation

Decoders can be combined with OR gates to build logic functions.


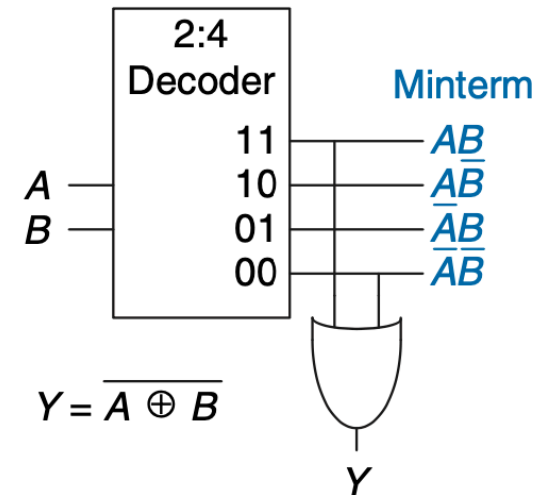



Figure 2.65 Logic function using decoder

Decoder with Enable

 


An n -to- 2^n decoder


Example. 2 to 4 decoder with enable

 

ena	x_1x_0	$y_3y_2y_1y_0$
0	--	0000
1	00	0001
	01	0010
	10	0100
	11	1000

 

Logic circuit

 

Logic circuit
(more compact notation)

Verilog example: 2 to 4 decoder with enable

```
// file: dec2to4.v
// 2 to 4 decoder using for loop

module dec2to4 (w, y, en);
    input [1:0] w;
    input en;
    output reg [3:0] y;

    integer k;


    always @(w, en)
    begin
        for (k=0; k< 4; k=k+1)
            if ( (w == k) && (en == 1) )
                y[k] = 1;
            else
                y[k] = 0;
        end
    endmodule
```

time	en	w	y


0	0	00	0000
10	0	01	0000
20	0	10	0000
30	0	11	0000
40	1	00	0001
50	1	01	0010
60	1	10	0100
70	1	11	1000

Large Decoder

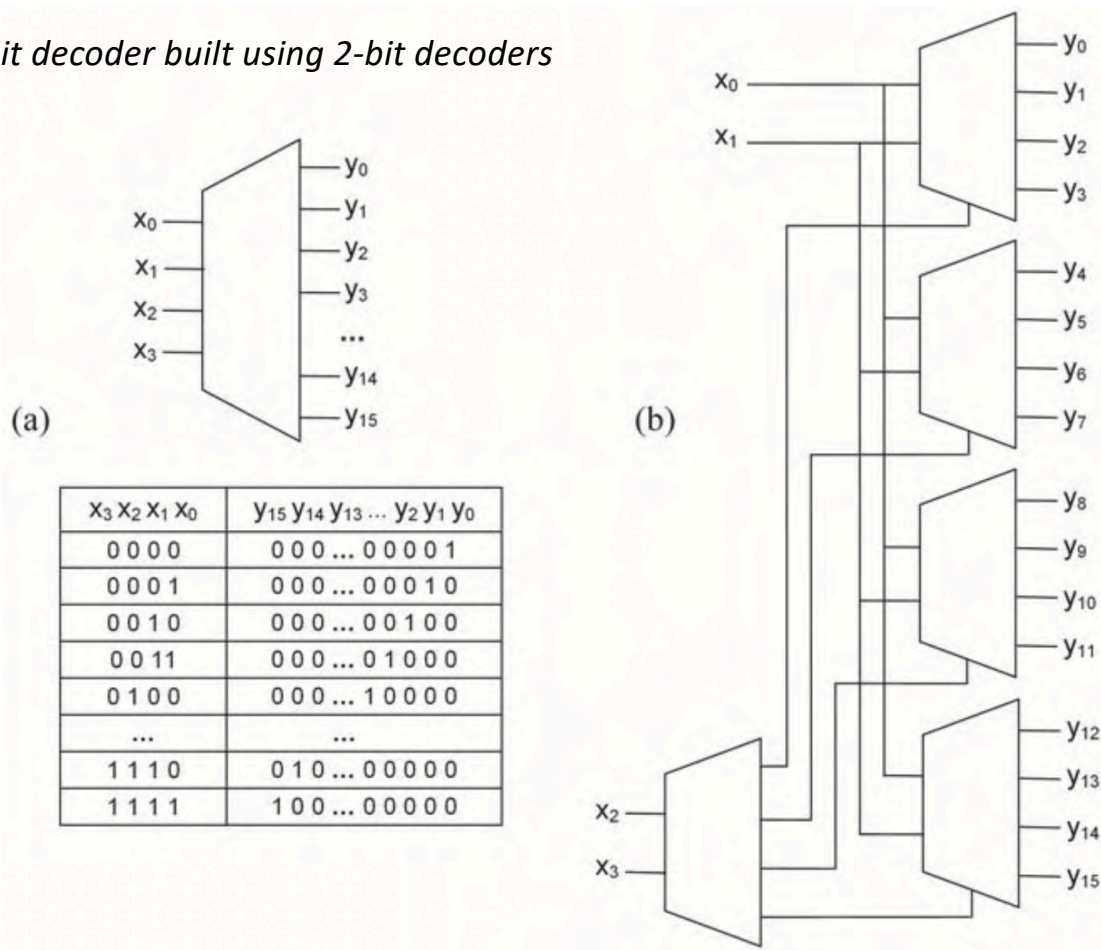Example. 4-bit decoder built using 2-bit decoders




Example

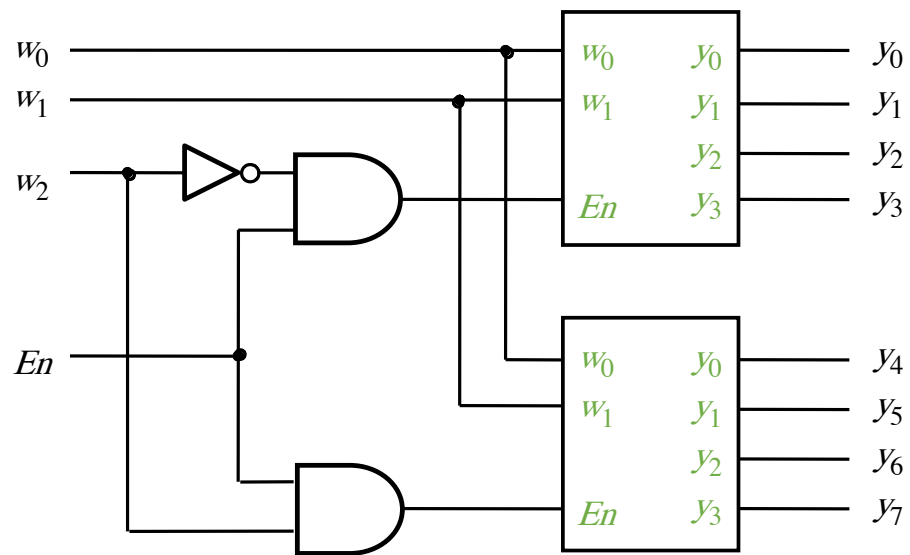

3-to-8 decoder with enable using two 2-to-4 decoders.

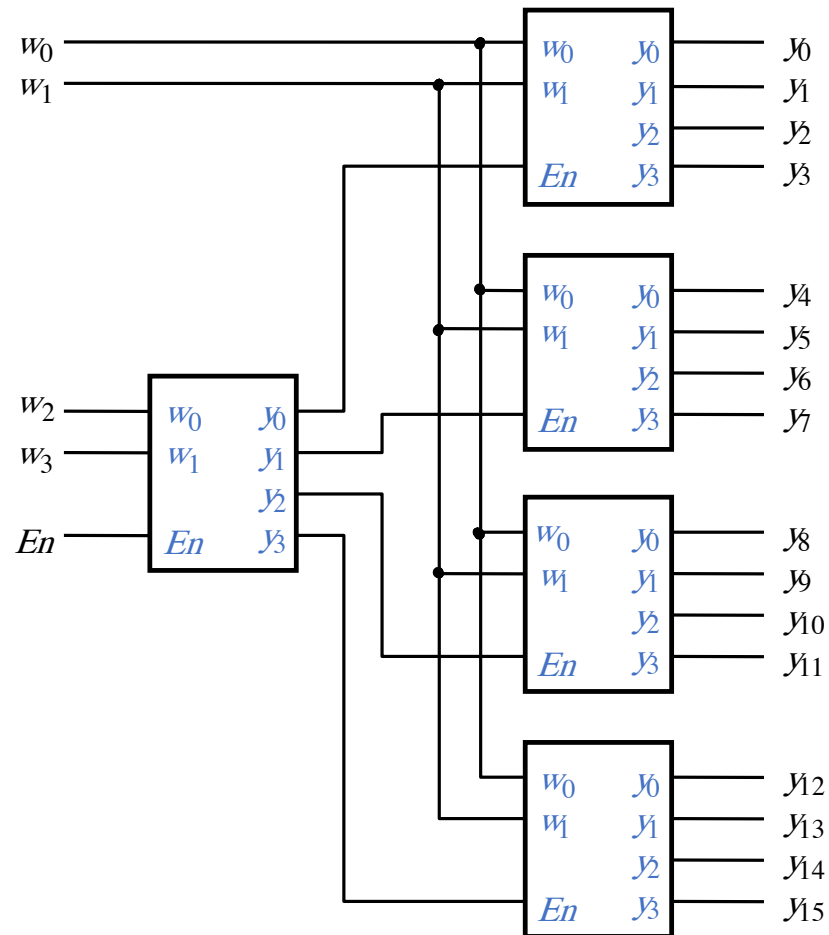
Example

4-to-16 decoder with enable
built using a decoder tree.



Decoder Application

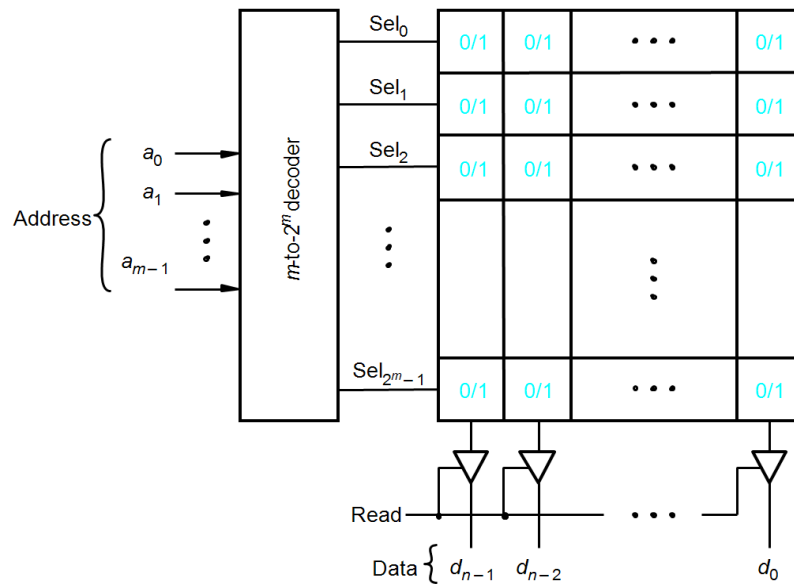
- A common decoder application is decoding the address lines of memory chips



$2^m \times n$ -bit read-only memory (ROM) block.



Another Decoder application: Demultiplexers

 - A demultiplexer places a single data input onto one of the multiple outputs
- A 1-to- 2^n demultiplexer can be implemented using an n -to- 2^n decoder



Encoder

  - An encoder converts its 2^N inputs (of which only one is hot) into N outputs.




Symbols

Example. 4 to 2 Encoder

a3	a2	a1	a0	b1	b0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1


$$b0 = a3 + a1$$

$$b1 = a3 + a2$$

 


Large Encoders

 - Large encoders can be built from a tree of smaller encoders




Example. 16 to 4 encoder

Priority Encoder

 

A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	0
0	1	0	0	0	1	0	0
0	1	0	1	0	1	0	0
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	0
1	0	0	0	1	0	0	0
1	0	0	1	1	0	0	0
1	0	1	0	1	0	0	0
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	0
1	1	1	0	1	0	0	0
1	1	1	1	1	0	0	0

 


A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	X	0	0	1	0
0	1	X	X	0	1	0	0
1	X	X	X	1	0	0	0

A more concise truth table (with don't cares as X)



Priority Encoders

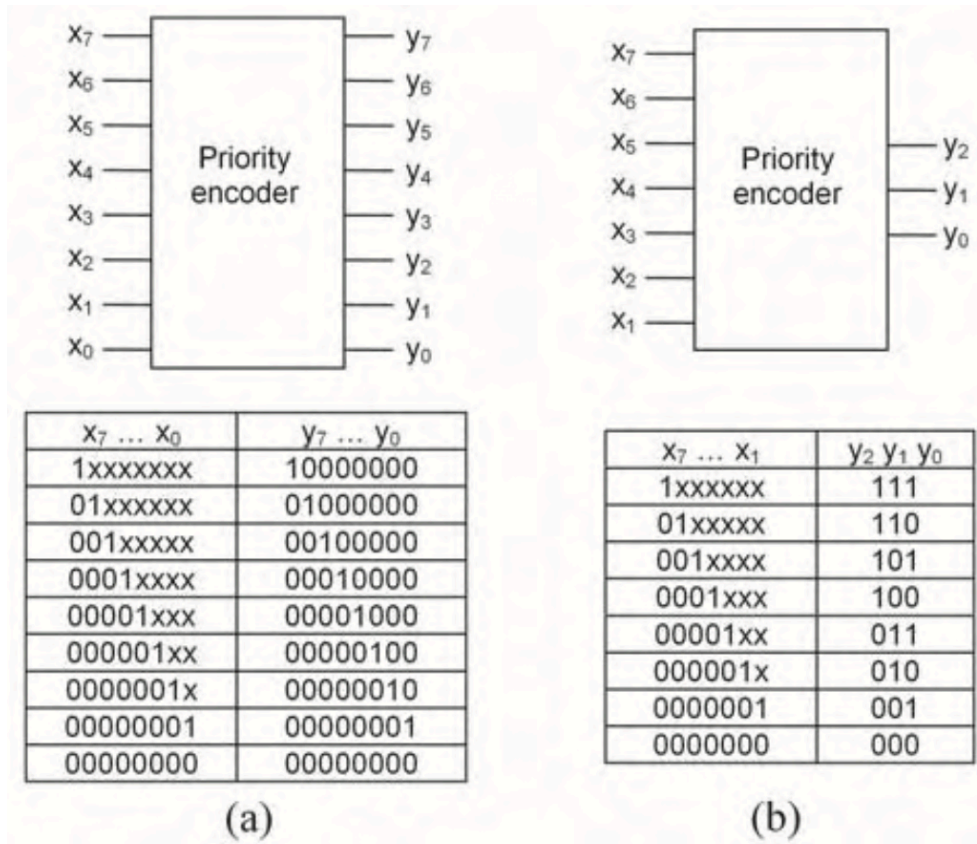- Priority encoders can come in two flavors



(b) the output displays the address of the input bit with highest priority


Comparator

  


Example: A four-bit comparator circuit.

Code Converters


- Example: HEX to 7-seg. Display

 

(a) Code converter

 



(b) 7-segment display

 



w_3	w_2	w_1	w_0	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	0	1	1	1	0	1	1	1
1	0	1	1	0	0	1	1	1	1	1
1	1	0	0	1	0	0	1	1	1	0
1	1	0	1	0	1	1	1	1	0	1
1	1	1	0	1	0	0	1	1	1	1
1	1	1	1	1	0	0	0	1	1	1

(c) Truth table


Delays

  

  
- Delay is caused by capacitance and resistance




Delays

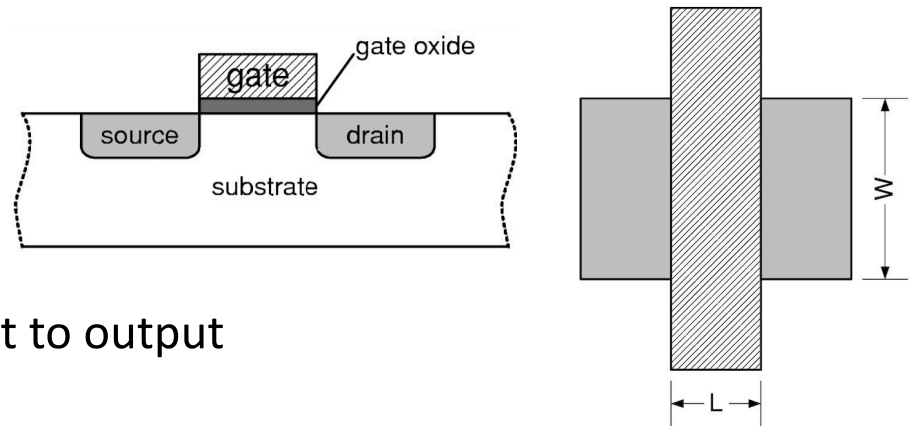

 - Propagation delay: t_{pd} = max delay from input to output
- Propagation delay varies with
 - rise and fall time of the input signals
 - outputs switching
(what outputs switch depends on what inputs switch)
 - temperature, supply voltage, geometry
 - capacitance C_L driven



Critical (long) and Short Paths


 


Critical (Long) Path: $t_{pd} = 2t_{pd_AND} + t_{pd_OR}$

Short Path: $t_{cd} = t_{cd_AND}$

Glitches

  - A single input change causes an output to change multiple times



		AB			
		00	01	11	10
C	0	1	0	0	0
	1	1	1	1	0

$$Y = \bar{A}\bar{B} + BC$$


For A=0 and C=1 $\rightarrow Y \propto \bar{B} + B$
so if B changes it causes a glitch

Fixing the glitch

Y C	AB			
	00	01	11	10
0	1	0	0	0
1	1	1	1	0

$\bar{A}\bar{C}$


$$Y = \bar{A}\bar{B} + BC + \bar{A}C$$

 

Next Time

- Basic sequential logic elements (latches and flip-flops)


Example

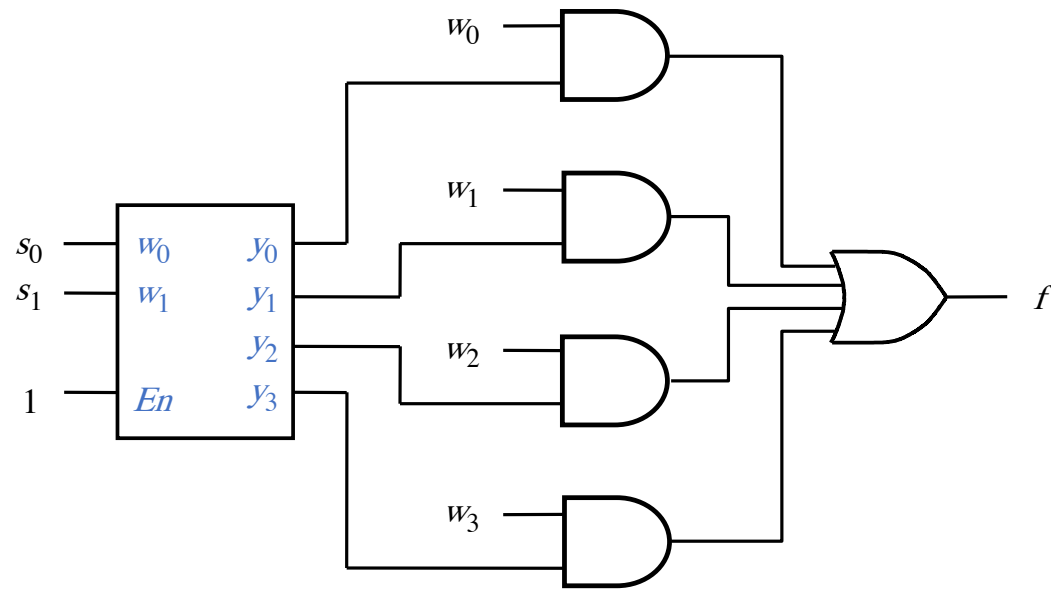

4-to-1 multiplexer built using a decoder.

Examples of logic functions using muxes: 2-input XOR


w_1	w_2	f
0	0	0
0	1	1
1	0	1
1	1	0

 

Implementation using a 4-to-1 multiplexer

w_1	w_2	f
0	0	0
0	1	1
1	0	1
1	1	0

w_1	f
0	w_2
1	$\overline{w_2}$

 

Modified truth table


Implementation using a 2-to-1 multiplexer and a NOT

Using muxes to build logic functions

- The key is to use Shannon's expansion

 Example:

$$f(w_1, w_2, w_3, w_4) = \underbrace{\overline{w_1} \cdot f(0, w_2, w_3, w_4)}_{= f_{\overline{w_1}}} + \underbrace{w_1 \cdot f(1, w_2, w_3, w_4)}_{= f_{w_1}}$$




This strategy is used extensively inside FPGAs

Three input majority function using a 4:1 mux

w_1	w_2	w_3	f		w_1	w_2	f
0	0	0	0	}	0	0	0
0	0	1	0		0	1	w_3
0	1	0	0		1	0	w_3
0	1	1	1		1	1	1
1	0	0	0	}			
1	0	1	1				
1	1	0	1				
1	1	1	1				

(a) Modified truth table

 


(b) Circuit

Three-input majority function using a 2:1 mux

w_1	w_2	w_3	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

w_1	f
0	$w_2 w_3$
1	$w_2 + w_3$

(b) Truth table

 


(b) Circuit

Three-input XOR using 2:1 muxes

w_1	w_2	w_3	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

(a) Truth table

 


(b) Circuit

Three-input XOR using a 4:1 mux

w_1	w_2	w_3	f	
0	0	0	0	} w_3
0	0	1	1	
0	1	0	1	} \bar{w}_3
0	1	1	0	
1	0	0	1	} \bar{w}_3
1	0	1	0	
1	1	0	0	} w_3
1	1	1	1	

(a) Truth table

 

(b) Circuit

S.L. Basic Elements (Latches & Flip-Flops)

CPEN 230 – Introduction to Digital Logic

Review: CL Building Blocks and Delays

- Adders
 - Multiplexers
 - Decoders
 - Demultiplexer
 - Encoders
 - Priority Encoder
 - Comparator
-
- Propagation Delay
 - Critical and Short Path
 - Glitches

One more C.L. design example: Binary-Coded-Decimal (BCD) Representation

- BCD is an intermediate representation between Binary and Decimal
- It represents decimal numbers by encoding each decimal digit in binary form.
- Because there are 10 digits to represent we need four bits.
- Example: $58_{10} = 0101\ 1000_{\text{BCD}}$

Binary-Coded-Decimal Representation

- BCD provides a format that is convenient when numerical information is to be displayed on a simple digit-oriented display
- BCD representation was used in some early computers and many handheld calculators

Decimal digit	BCD code
0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111
8	1000
9	1001

BCD Addition

- The addition of two BCD digits is complicated by the fact that the sum may exceed 9, in which case a correction will have to be made
 - if $X + Y \leq 9$, the addition is the same as the addition of 2 four bit unsigned binary numbers
 - if $X + Y > 9$, then the result requires two BCD digits
- There are two cases where a **correction** has to be made
 - 1) The sum is greater than 9 but no carry-out is generated out of the four bits
 - 2) The sum is greater than 15 so a carry-out is generated out of the four bits

BCD Addition – example

$9 < Z \leq 15 \rightarrow$ *no carry*


X	0111	7
+ Y	+ 0101	+ 5
<hr/>		
Z	1100	12
	+ 0110	
<hr/>		
carry →	10010	
	<u> </u>	
	S = 2	

$Z > 15 \rightarrow$ *carry*

X	1000	8
+ Y	+ 1001	+ 9
<hr/>		
Z	0001	17
	+ 0110	
<hr/>		
carry →	10111	
	<u> </u>	
	S = 7	

Whenever the result of the 4-bit addition (Z) exceeds 9, the correct decimal digit can be generated by adding 6 to the result.


One-Digit BCD Adder

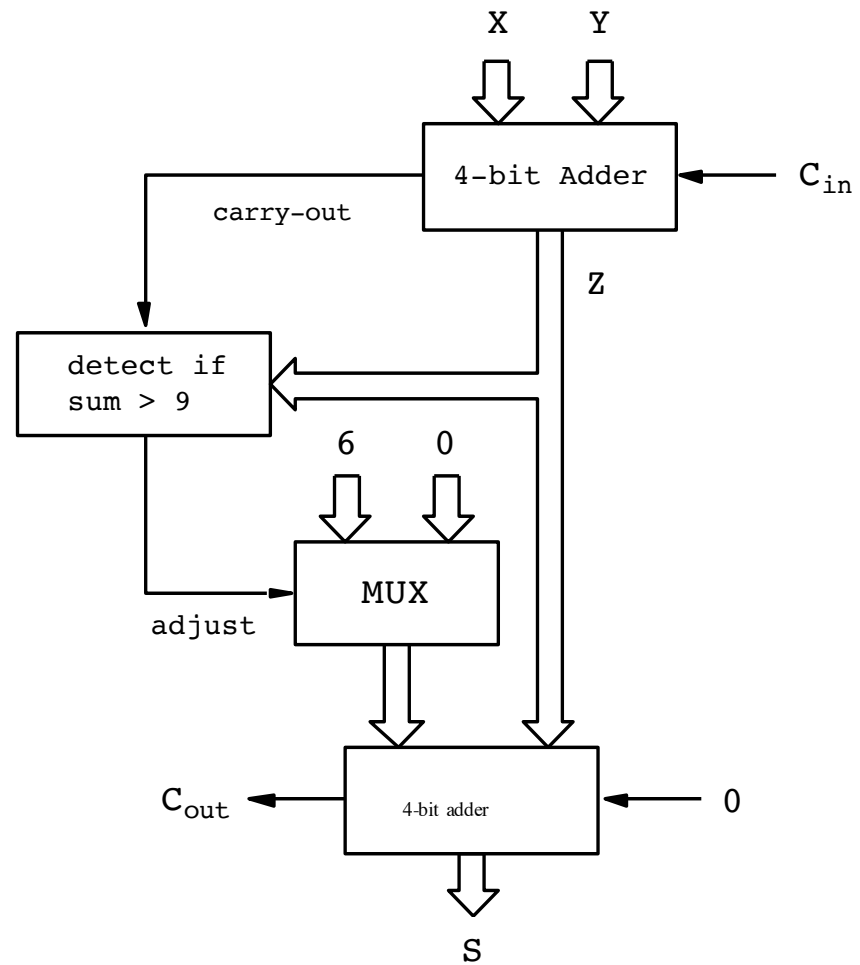

Verilog Code for a One-Digit BCD Adder

```
module bcdadd (Cin, X, Y, S, Cout);  
    input Cin;  
    input [3:0] X, Y;  
    output reg [3:0] S;  
    output reg Cout;  
    reg [4:0] Z;  
  
    always @(X, Y, Cin)  
    begin  
        Z = X + Y + Cin;  
        if (Z < 10)  
            {Cout, S} = Z;  
        else  
            {Cout, S} = Z + 6;  
    end  
  
endmodule
```


Present and Past

 

$$i(t) = C \frac{dv(t)}{dt} \overset{\lim_{\Delta t \rightarrow 0}}{\cong} C \frac{\Delta v}{\Delta t} \cong C \frac{\overset{\text{present}}{v(t)} - \overset{\text{past}}{v(t_0)}}{t - t_0}$$

$$q(t) = C \cdot v(t)$$

$$dq(t) = C \cdot dv(t)$$



Capacitors stores charge (i.e. voltage level $v=q/C$).
Ideally the charge should be stored forever,
but, ... unfortunately in practical capacitors
the charge is not hold forever, eventually it leaks.

Sequential Circuits


- Recall that a combinational circuit produces an output that depends only on the current state of its input --> combinational circuits must be acyclic (no loops).
- If we add a feedback to a combinational circuit, the circuit becomes sequential.
- The output of a sequential circuit depends not only on its current input, but also on the history of its previous inputs. The cycle created by the feedback allows the circuit to store information (i.e. remember) about its previous input.
- We call the information “stored” on the feedback signal as the state of the circuit.

Adding Feedback

  - Easiest option we can think of is to wrap feedback around an inverter




 
- The inverter output will continue to oscillate back and forth between 1 and 0, and it will never reach a stable condition. The rate at which the circuit oscillates is determined by the propagation delay Δt of the inverter.



  
(b) Oscillation at inverter output

Adding Feedback

- Wrapping feedback around an inverter causes the state to keep flipping. Not quite what we are looking for. What we are looking for is holding (remembering) the state in a stable manner.
- ... adding one more inverter does the trick




Feedback is Remembering

 

Analyzing this circuit is different from analyzing a combinational circuit, because it is cyclic: Q depends on \bar{Q} and \bar{Q} depends on Q

 Just as Y is commonly used for the output of combinational logic, Q is commonly used for the output of sequential logic.




To emphasize that the two inverters are cross-coupled the circuit is commonly redrawn as shown above.


case I. $Q = 0 \mapsto$ the cell holds the value “forever” (its “state” is stable)

case II. $Q = 1 \mapsto$ the cell holds the value “forever” (its “state” is stable)

 Because the circuit has two stable states $Q=0$ and $Q=1$, the circuit is said to be **bistable**.




Cross-coupled inverters


 


- Although the cross-coupled inverters can store a bit of information they are not practical because the user has no inputs to control the state.


Cross-coupled inverters behavior

 


metastable

  

Circuit model of cross-coupled bistable.

 


(a)

 

(b)

 There is delay as the signal propagates through the loop



(c)

$$i(t) = \frac{v_{out}(t) - v_{in}(t)}{R}$$

$$v_{out}(t) = G \cdot v_{in}(t)$$

$$i(t) = C \frac{dv_{in}(t)}{dt}$$

$$v_{out}(0) = \Delta V$$




$$\frac{G - 1}{RC} dt = \frac{dv_{out}}{v_{out}} \Leftrightarrow v_{out}(t) = \Delta V \cdot \exp \left[\frac{(G - 1)t}{RC} \right]$$

Sequential circuits

- When power is first applied to a sequential circuit, the initial state is unknown and usually unpredictable. It may differ each time the circuit is turned on.

Latches vs. Flip-Flops

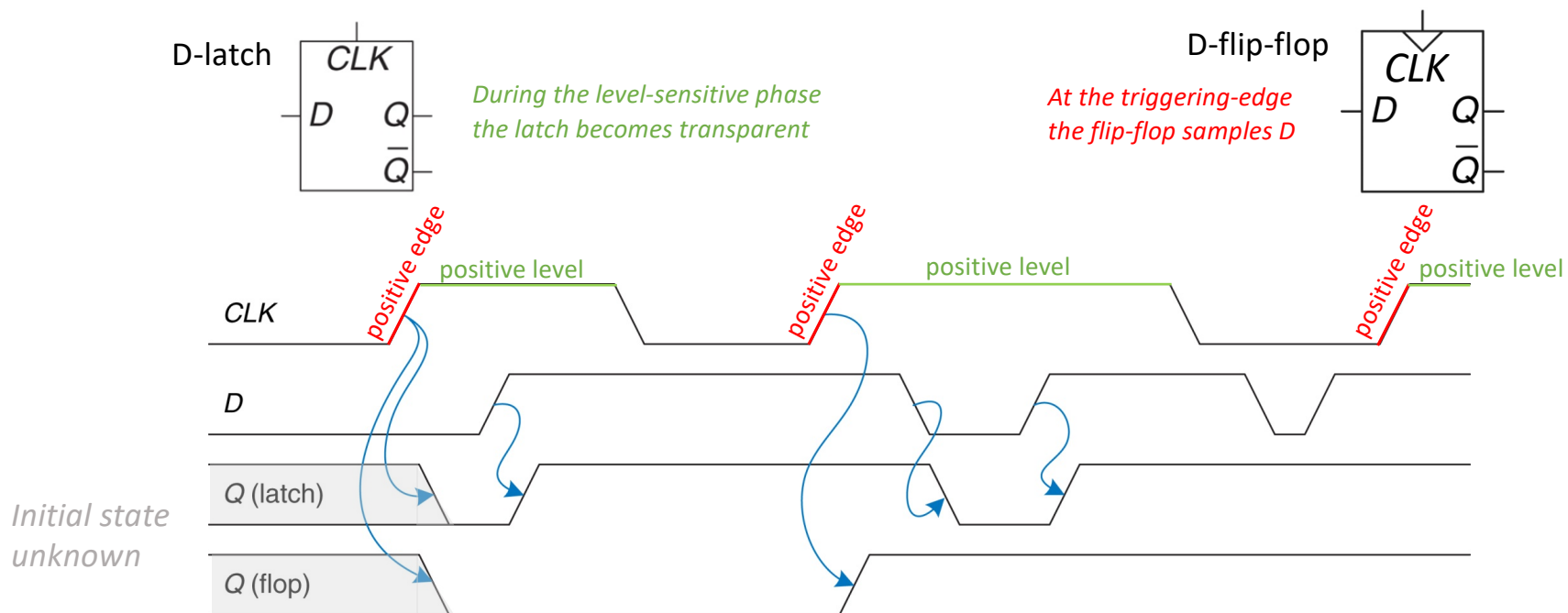- There are two types of storage elements: latches and flip-flops
 - A latch is a 1-bit level-sensitive storage element
 - A flip-flop is a 1-bit edge-triggered storage element




What's inside a D-latch ? What about a D flip-flop?


- Typical “introduction to Digital Logic’s textbook” approach.

*If you like the
NAND better
apply DeMorgan*

 - Let's wrap feedback around our favorite logic gate (e.g. NOR) and find a way to provide the capability of controlling the value (1/0) we want to store.



S-R latch

 

case I. **$R = 1$ and $S = 0$**

since $R=1 \rightarrow$ N2 gives $Q=0$ **reset the output**

since $S=0$ and $Q=0 \rightarrow$ N1 gives $Q'=1$

case II. **$R = 0$ and $S = 1$**

since $S=1 \rightarrow$ N1 gives $Q'=0$

since $Q'=0 \rightarrow$ N2 gives $Q=1$ **set the output**

case III. **$R = 1$ and $S = 1$**

since $S=1 \rightarrow$ N1 gives $Q'=0$

since $R=1 \rightarrow$ N2 gives $Q=0$ **invalid $Q \neq Q'$**

case IV. **$R = 0$ and $S = 0$**

since $S=0 \rightarrow$ we cannot tell what N1 gives unless we know Q

since $R=0 \rightarrow$ we cannot tell what N2 gives unless we know Q'

case IVa. **$R = 0$ and $S = 0$ and $Q=0$**

since $S=0$ and $Q=0 \rightarrow$ N1 gives $Q'=1$

since $R=0$ (and $Q'=1$) \rightarrow N2 gives $Q=0$

case IVb. **$R = 0$ and $S = 0$ and $Q=1$**


since $S=0$ and $Q=1 \rightarrow$ N1 gives $Q'=0$

since $R=0$ (and $Q'=0$) \rightarrow N2 gives $Q=1$

$Q = Q_{\text{prev}}$

Memory !

Summary of SR latch results

 


Case	S	R	Q	\bar{Q}
IV	0	0	Q_{prev}	\bar{Q}_{prev}
I	0	1	0	1
II	1	0	1	0
III	1	1	0	0

Figure 3.5 SR latch truth table

Observation:

in case III ($R=S=1$) the node Q' is equal to 0 just like Q (in all other cases the node Q' was the complement of Q). This issue could be swept under the rug. The output of N1 doesn't have to be necessarily the complement of Q, we can call the node P and do not use it as an output of the cell (so nobody has to know). However there is a worst issue that cannot be ignored, and doesn't not become evident unless we analyze the circuit dynamically. Suppose after $R=S=1$ the inputs both goes simultaneously to $R=S=0$ and assume the delays of the two gates are identical: the circuit start to oscillate.

FIGURE
Improper S-R Latch
Operation

 

SR latch operation

 


Figure 3.6 SR latch symbol

Case	S	R	Q	\bar{Q}
IV	0	0	Q_{prev}	\bar{Q}_{prev}
I	0	1	0	1
II	1	0	1	0
III	1	1	0	0

Figure 3.5 SR latch truth table


← Invalid operation we must avoid case III

Sometime people prefer to call the truth tables for S.L. with the name characteristic tables (to emphasize they are not talking about C.L.)

The Big Picture:

At the end of the day what we want is either set the state to a new value (either 0 or 1) or hold the existing state (and this can all be achieved through cases I, II, and IV).
 
```
if enable == 1  Q <= D ;    // specify the value of the new state
else Q <= Q_prev;          // hold the new state to its old value
```



Toward the D-latch

enable D	S R
00	00
01	00
10	01
11	10

$$S = enable \cdot D$$

$$R = enable \cdot \bar{D}$$

D latch


 



Figure 3.7 D latch: (a) schematic, (b) truth table, (c) symbol

 

(d) Timing diagram

Common conventions to write the characteristic tables

Example: D-latch

 

CLK	D	Q
0	0	Q_{prev}
0	1	Q_{prev}
1	0	0
1	1	1

CLK	D	Q_{new}
0	0	Q_{old}
0	1	Q_{old}
1	0	0
1	1	1

CLK	D	$Q(t+1)$
0	0	$Q(t)$
0	1	$Q(t)$
1	0	0
1	1	1

CLK	D	Q_{n+1}
0	0	Q_n
0	1	Q_n
1	0	0
1	1	1


CLK	D	Q_{next}
0	0	Q
0	1	Q
1	0	0
1	1	1

CLK	D	Q^+
0	0	Q
0	1	Q
1	0	0
1	1	1

CLK	D	Q	Q_{next}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

D flip-flop internal circuit

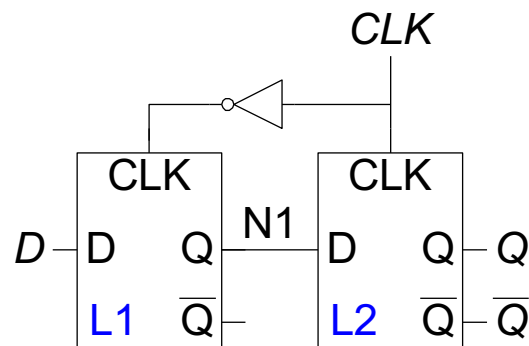
- A D flip-flop can be built from 2 back to back D latches controlled by complementary clocks. The first latch L1 is called the master. The second latch L2 is called the slave.




- When $CLK = 0$
 - L1 is transparent
 - L2 is opaque
 - D passes through to $N1$
- When $CLK = 1$
 - L2 is transparent
 - L1 is opaque
 - $N1$ passes through to Q
- Thus, on the edge of the clock (when CLK rises from 0 to 1)
 - D passes through to Q

D Flip-Flop internal circuit

D Flip-Flop (Rising-Edge Trigger)

 


 (a) Construction from two gated D latches



(b) Timing analysis

D flip-flop

 

DFF Symbol

- Inputs: CLK , D
- Function
 - Samples D on rising edge of CLK
 - When CLK rises from 0 to 1, D passes through to Q
 - Otherwise, Q holds its previous value
 - Q changes only on rising edge of CLK
- Called *edge-triggered*
(i.e. activated on the clock edge)


CLK	D	Q	Q^+
↑	0	0	0
↑	0	1	0
↑	1	0	1
↑	1	1	1

(c) Truth table

$$Q^+ = D$$


Enabled Flip-Flops

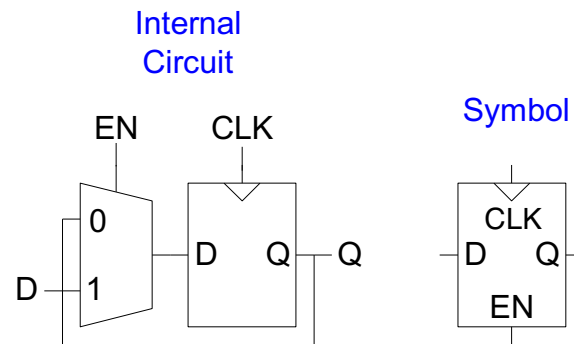- Inputs: CLK , D , EN
 - The enable input (EN) controls when new data (D) is stored
- Function
 - $EN = 1$: D passes through to Q on the clock edge
 - $EN = 0$: the flip-flop retains its previous state




Resettable Flip-Flops

 - Inputs: *CLK*, *D*, *Reset*
- Function:
 - *Reset* = 1: *Q* is forced to 0
 - *Reset* = 0: flip-flop behaves as ordinary D flip-flop





Settable Flip-Flops

 - Inputs: CLK , D , Set
- Function:
 - $Set = 1$: Q is forced to 1
 - $Set = 0$: flip-flop behaves as ordinary D flip-flop




Resettable/Settable Flip-Flops

  - Two types:
 - **Synchronous**: resets/sets at the clock edge only
 - **Asynchronous**: resets/sets immediately when *Reset/Set* = 1
- Asynchronously resettable/settable flip-flop requires changing the internal circuitry of the flip-flop
- Synchronously resettable/settable flip-flop doesn't.



D latch
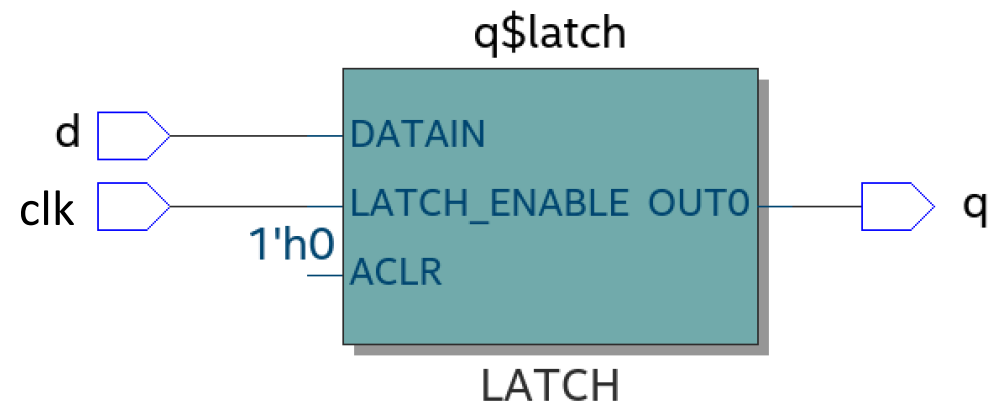
```
module d_latch(d, clk, q);  
    input d, clk;  
    output reg q;  
  
    always @(d, clk)  
    begin  
        if (clk) q <= d;  
    end  
  
endmodule
```




nonblocking assignment
When coding S.L. use only nonblocking assignment

D flip-flop


```
module d_ff(d, clk, q);  
  input d, clk;  
  output reg q;  
  
  always @(posedge clk)  
  begin  
    if (clk) q <= d;  
  end  
  
endmodule
```

nonblocking assignment

 


D flip-flop with asynchronous reset (active low)
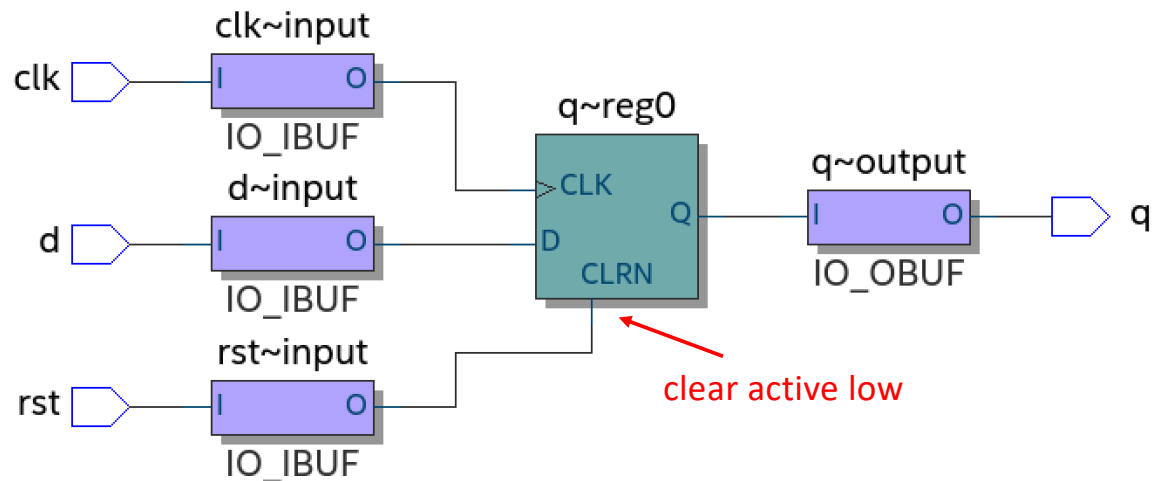
```
module dff_asy (d, rst, clk, q);  
  input d, rst, clk;  
  output reg q;  
  
  always @(negedge rst, posedge clk)  
  begin  
    if (~rst)  
      q <= 0;  
    else  
      q <= d;  
  end  
endmodule
```






D flip-flop with synchronous reset (active low)

 
```
module dff_syn (d, rst, clk, q);  
  input d, rst, clk;  
  output reg q;  
  
  always @(posedge clk)  
    if (~rst) q <= 0;  
    else q <= d;  
  
endmodule
```



Transistor level D-latch

   

Transistor level D flip-flop

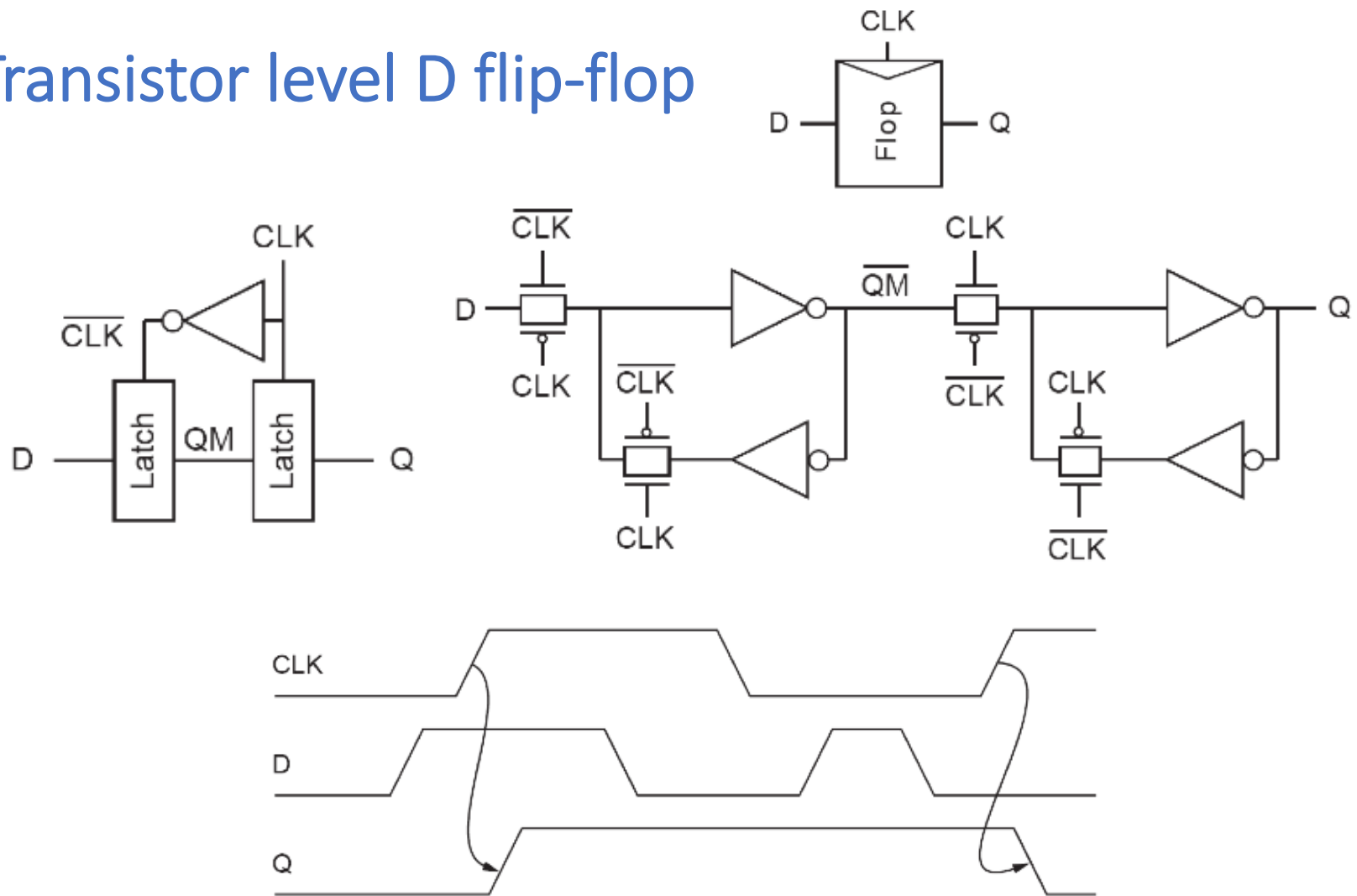


Next Time

- Sequential logic building blocks
 - JK Flip-Flop and T Flip-Flop
 - Registers
 - Shift Registers
 - Counters

S.L. Building Blocks


CPEN 230 – Introduction to Digital Logic

Review: Latches and Flip-Flops

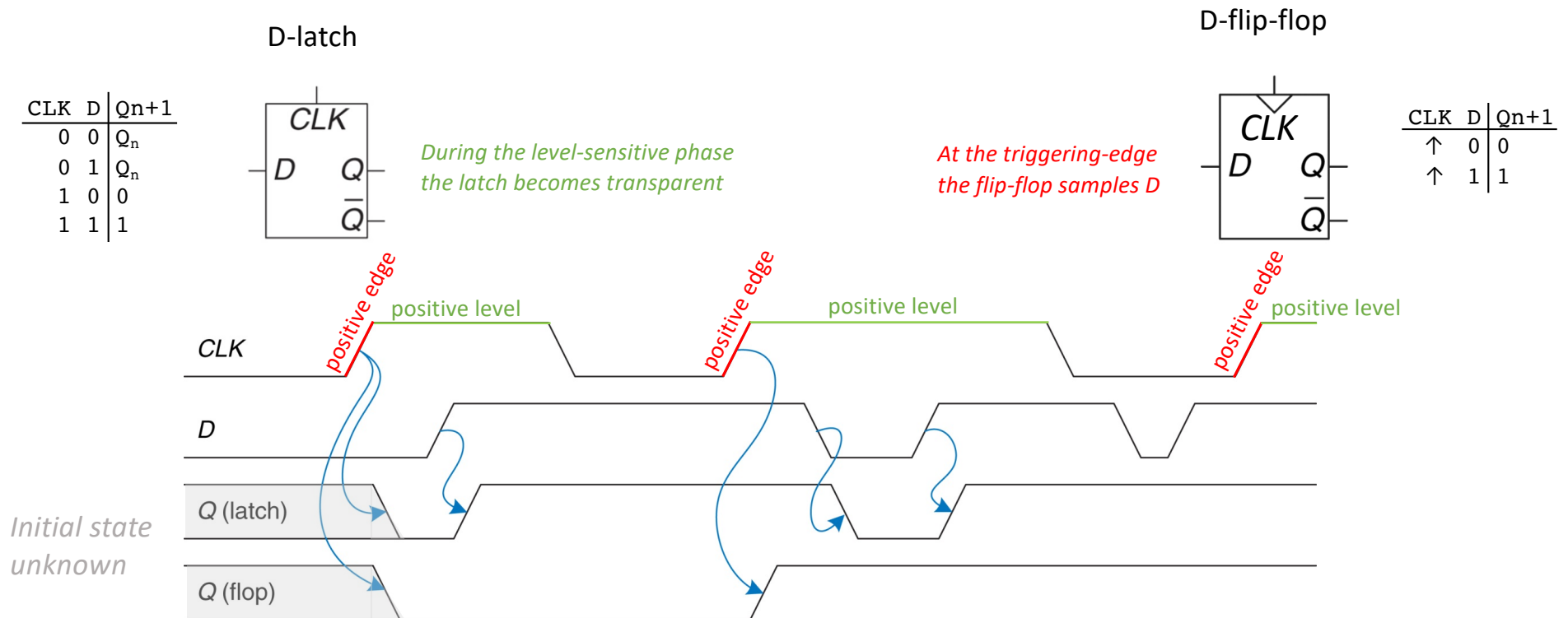


Review: D latch in Verilog
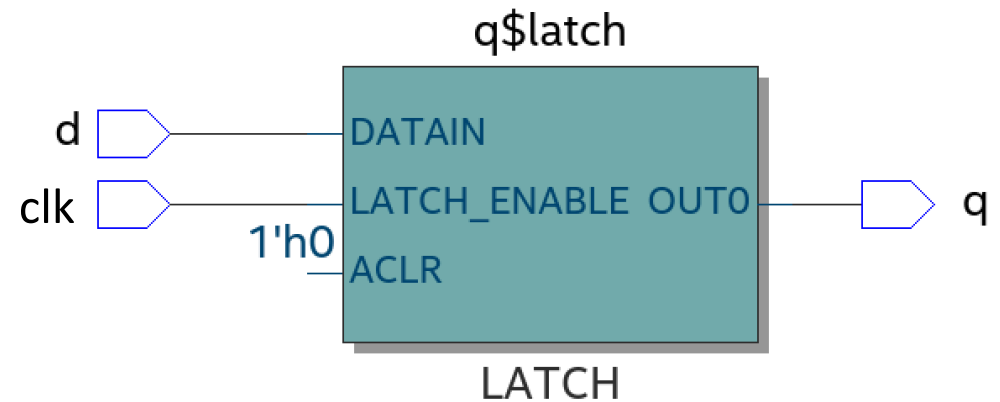
```
module d_latch(d, clk, q);  
    input d, clk;  
    output reg q;  
  
    always @(d, clk)  
    begin  
        if (clk) q <= d;  
    end  
  
endmodule
```




Review: D flip-flop in Verilog
 
```
module d_ff(d, clk, q);  
  input d, clk;  
  output reg q;  
  
  always @(posedge clk)  
  begin  
    if (clk) q <= d;  
  end  
  
endmodule
```




Review: D flip-flop with async. reset in Verilog
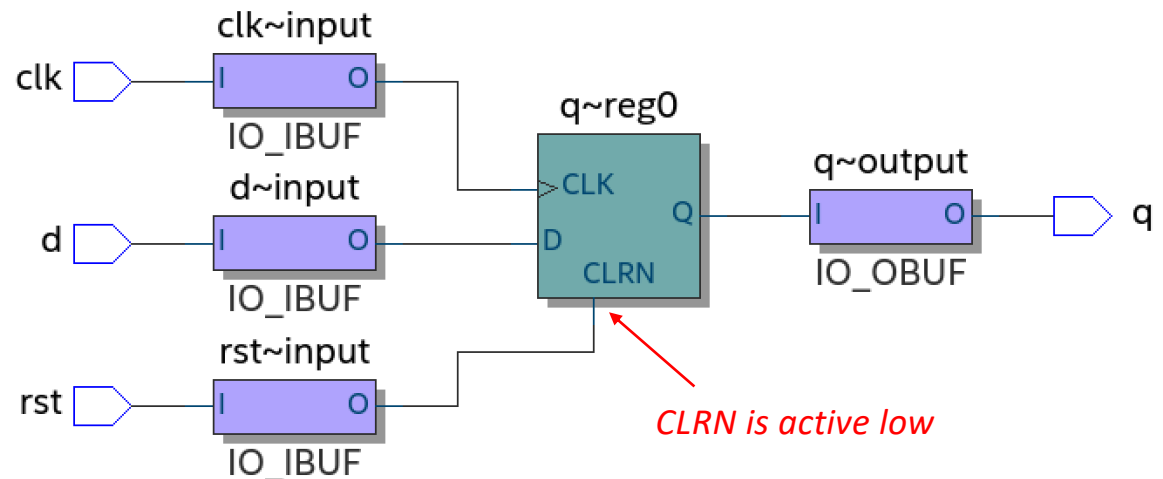
```
module dff_asy (d, rst, clk, q);  
  input d, rst, clk;  
  output reg q;  
  
  always @(negedge rst, posedge clk)  
  begin  
    if (~rst)  
      q <= 0;  
    else  
      q <= d;  
  end  
endmodule
```




Review: D flip-flop with sync. reset in Verilog
 
```
module dff_syn (d, rst, clk, q);  
  input d, rst, clk;  
  output reg q;  
  
  always @(posedge clk)  
    if (~rst) q <= 0;  
    else q <= d;  
  
endmodule
```



J-K Flip-Flop

 

J	K	$Q(t+1) = Q_{next} = Q_{new} = Q_{n+1} = Q^+$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	$\bar{Q}(t)$

		J	
		0	1
K	0	Q	1
	1	0	Q'



		J	
		0	1
K	0	0	1
	1	0	0

		J	
		0	1
K	0	1	-
	1	0	0


		J	
		0	1
K	0	0	-
	1	0	1

$$Q_{next} = \underbrace{J \cdot \bar{K}}_{\text{consensus term}} + Q \cdot \bar{K} + \bar{Q} \cdot J = Q \cdot \bar{K} + \bar{Q} \cdot J$$


J-K Flip-Flop schematic

$$Q_{next} = Q \cdot \bar{K} + \bar{Q} \cdot J$$

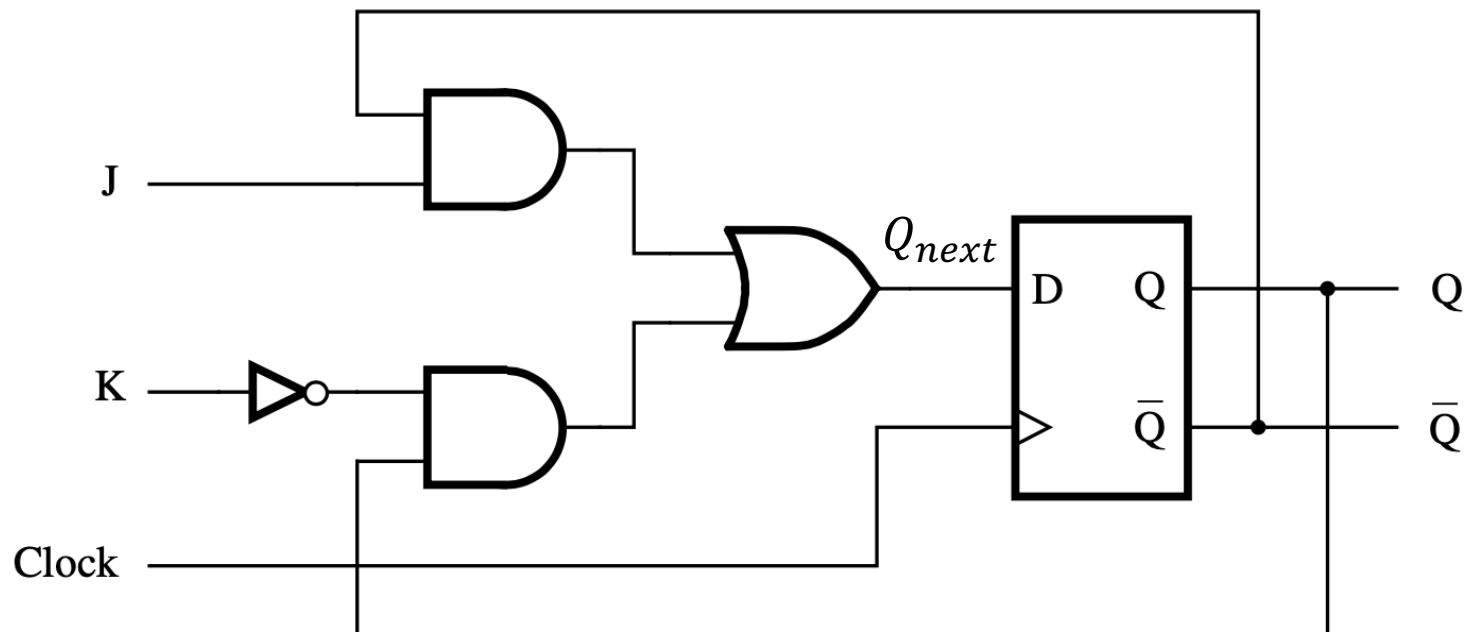*mux with Q as selection
and K' and J as data*




T Flip-Flop

 


T	$Q(t+1) = Q_{next} = Q_{new} = Q_{n+1} = Q^+$
0	$Q(t)$
1	$\bar{Q}(t)$
 
$$Q_{next} = \bar{T} \cdot Q + T \cdot \bar{Q} = T \oplus Q$$




Timing diagram

T Flip-Flop schematic

 

$$Q_{next} = \underbrace{\bar{T} \cdot Q + T \cdot \bar{Q}} = T \oplus Q$$

 *mux with T as selection
and Q' and Q as data
or Q as selection and
T' and T as data*




- It is possible to use any flip-flop for building any other flip-flop

Converting a J-K Flip-Flop into a D Flip-Flop

J	K	Q	Q _{next}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

D	Q	Q _{next}
0	0	0
0	1	0
1	0	1
1	1	1

 


Converting a J-K Flip-Flop into a T Flip-Flop

J	K	Q_{next}

0	0	Q
0	1	0
1	0	1
1	1	Q'


T	Q_{next}

0	Q
1	Q'

 

Register

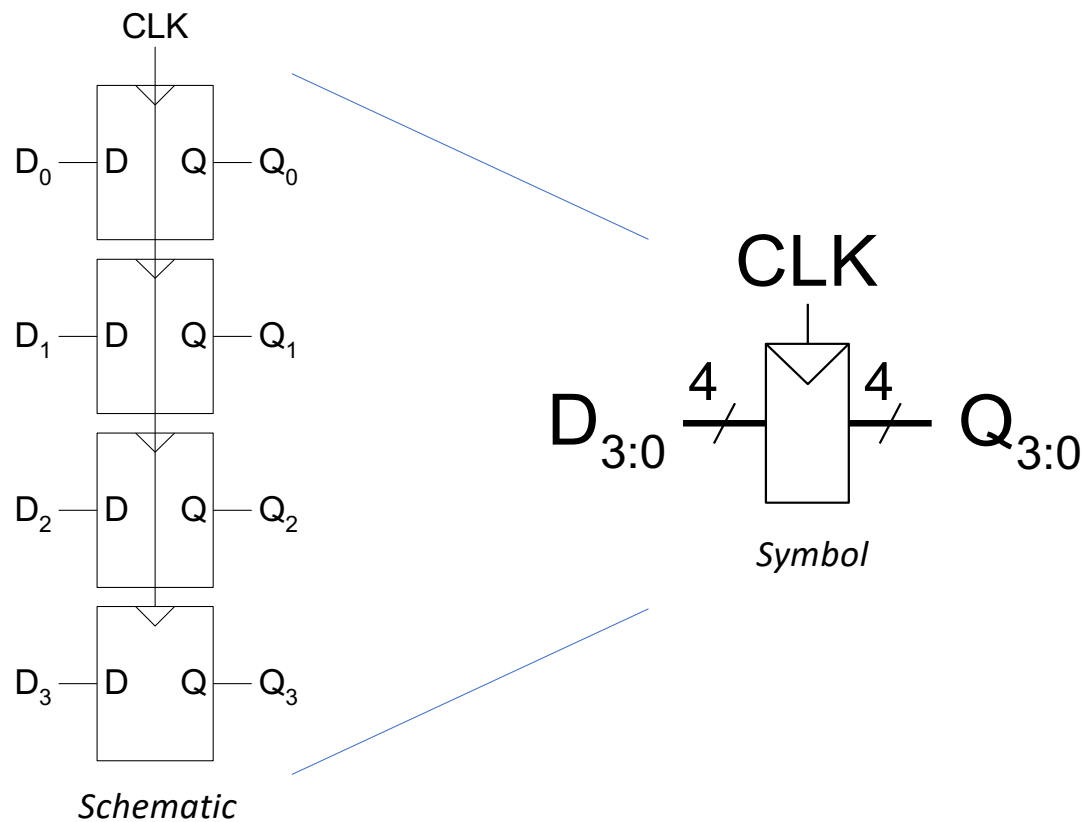
- An N-bit register is simply a bank of N flip-flops



4-bit register with async. reset: Verilog

```
// file: reg_n.v  
// n-bit register with async. clear
```
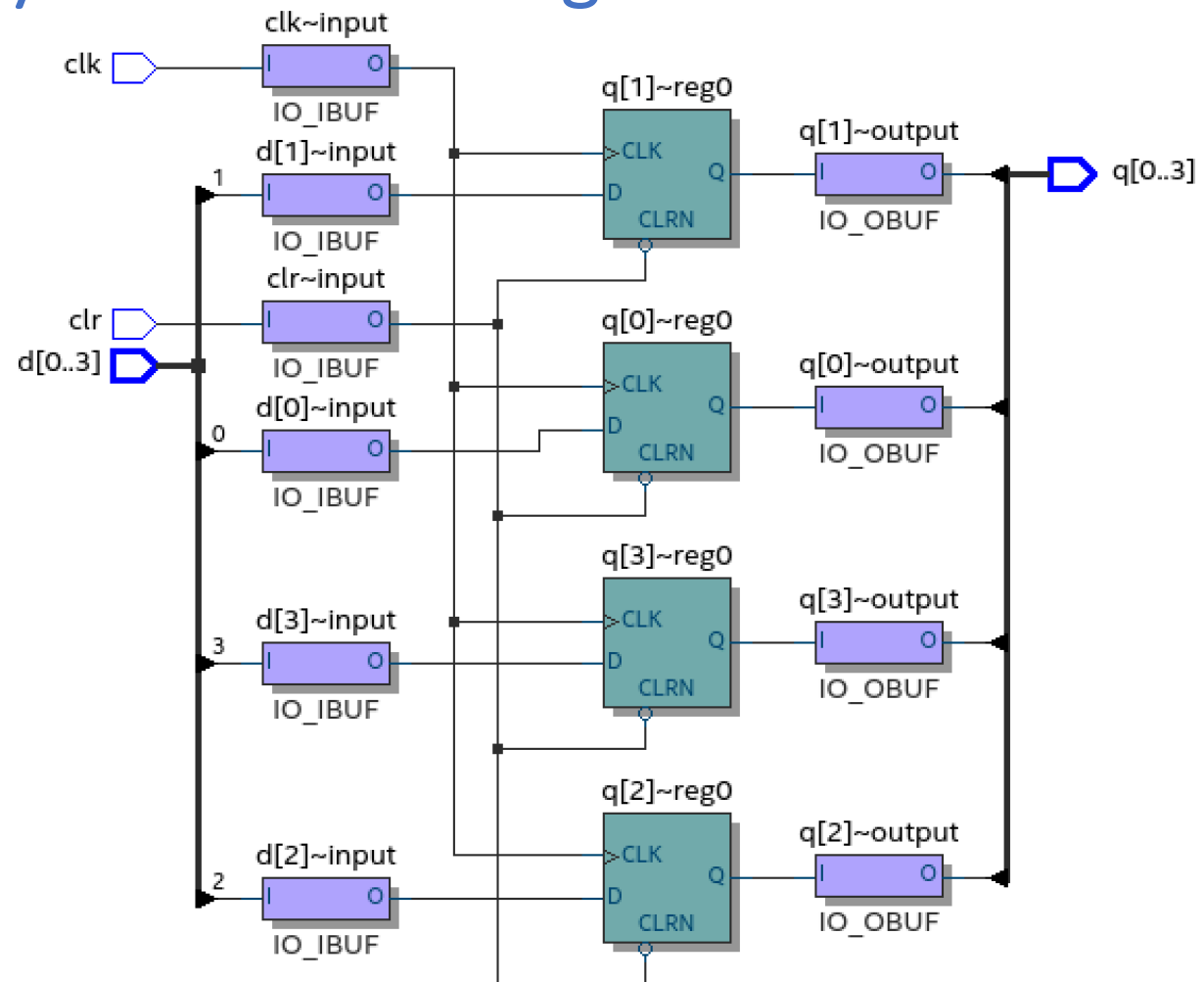
```
module reg_n(d, clk, clr, q);  
    parameter n = 4;  
    input [n-1:0] d;  
    input clr, clk;  
    output reg [n-1:0] q;  
  
    always @(posedge clr, posedge clk)  
    begin  
        if (clr == 1) q <= 0;  
        else q <= d;  
    end  
  
endmodule
```



```

// filename: reg_n_tb.v
// verify the functionality of reg_n.v

// set time tick units and precision to ns
`timescale 1ns / 1ns

module reg_n_tb;

    // UUT inputs
    reg [3:0] d;
    reg clk;
    reg clr;
    // UUT outputs
    wire [3:0] q;

    // parameters
    parameter T = 50; // clock period

    // instantiate the unit under test (UUT)
    reg_n uut(
        .d(d),
        .clk(clk),
        .clr(clr),
        .q(q)
    );

    // generate clock
    // 50 ns clock running forever
    always
    begin
        clk = 1'b0;
        #(T/2);
        clk = 1'b1;
        #(T/2);
    end

    // initialize inputs
    initial
    begin
        d = 4'hf;
        clr = 0;
    end

```

4-bit register testbench

```

// set time format to be ns
initial $timeformat(-9, 1, "ns", 10);

// output the simulation in graphical format
initial begin
    $dumpfile("reg_n.vcd");
    $dumpvars(0, reg_n_tb);
end


// generate test patterns
initial begin
    // test async. clear
    #113;
    clr = 1;
    #4;
    clr = 0;
    // test the register sample a new data value
    #25;
    d = 4'ha;
    #200;
    $finish;
end

// output the simulation in textual format
initial begin
    $display("\ntime clr d q");
    $display("-----");
    $monitor("%4d %1b %h %h", $time, clr, d, q);
end

endmodule


```

4-bit register simulation

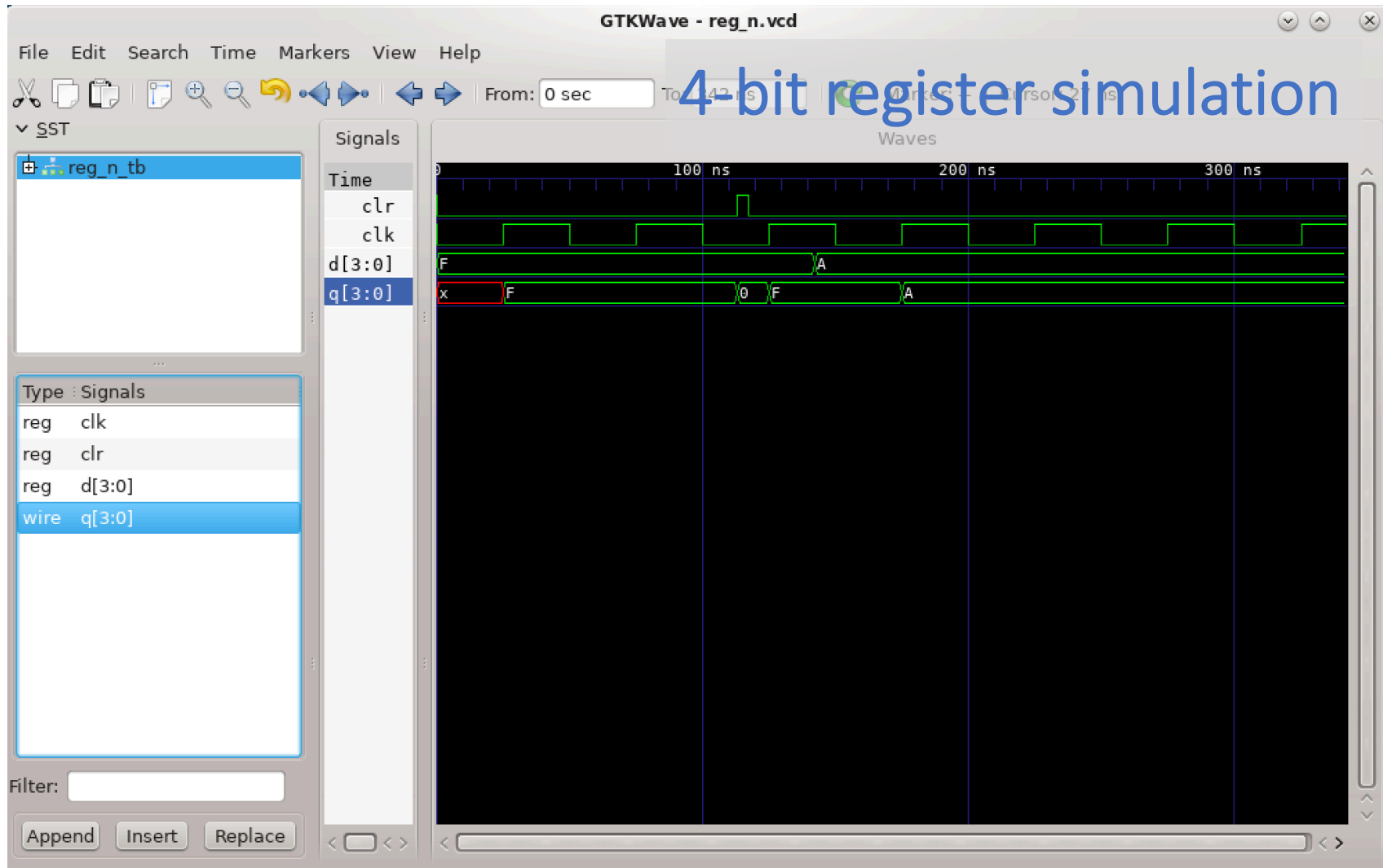

Shift-register


Example: 4-bit shift register

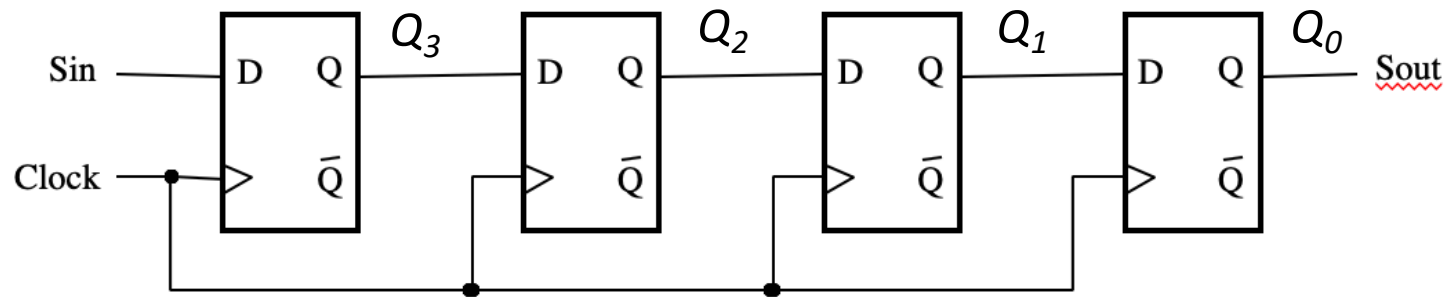


Shift Register in Verilog

```
// file: sreg_n.v  
// n-bit shift register
```
 
```
module sreg_n(si, clk, so);  
    parameter n = 4;  
    input si, clk;  
    output so;  
  
    reg [n-1:0] q;  
    integer k;  
  
    always @(posedge clk)  
    begin  
        for (k=0; k<n-1; k=k+1) q[k] <= q[k+1];  
        q[n-1] <= si;  
    end  
  
    assign so = q[0];  
  
endmodule
```




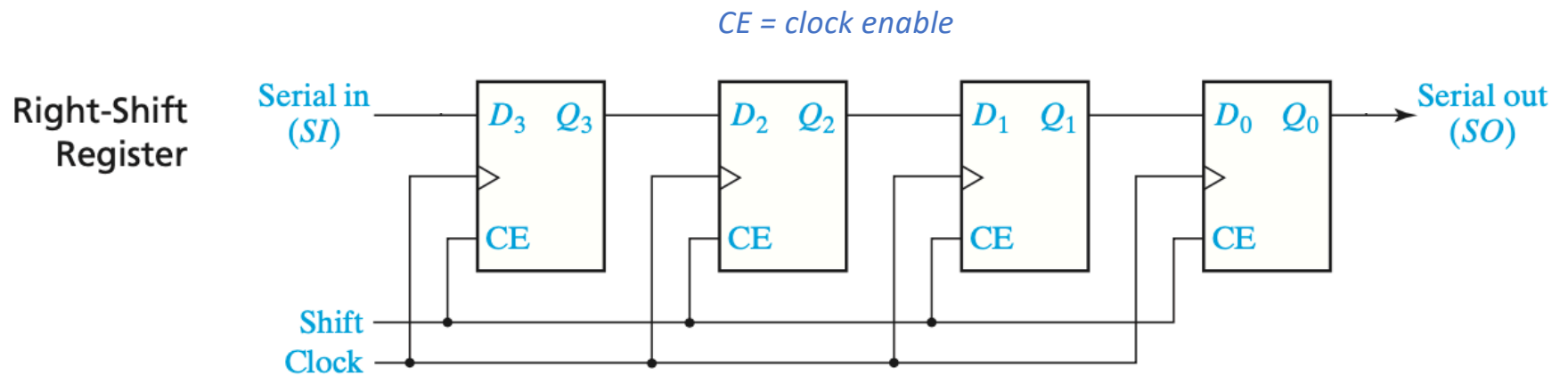Shift Register (with shift enable) (Example: 4-bit)



Parallel Access Shift Register

(Example: 4-bit)

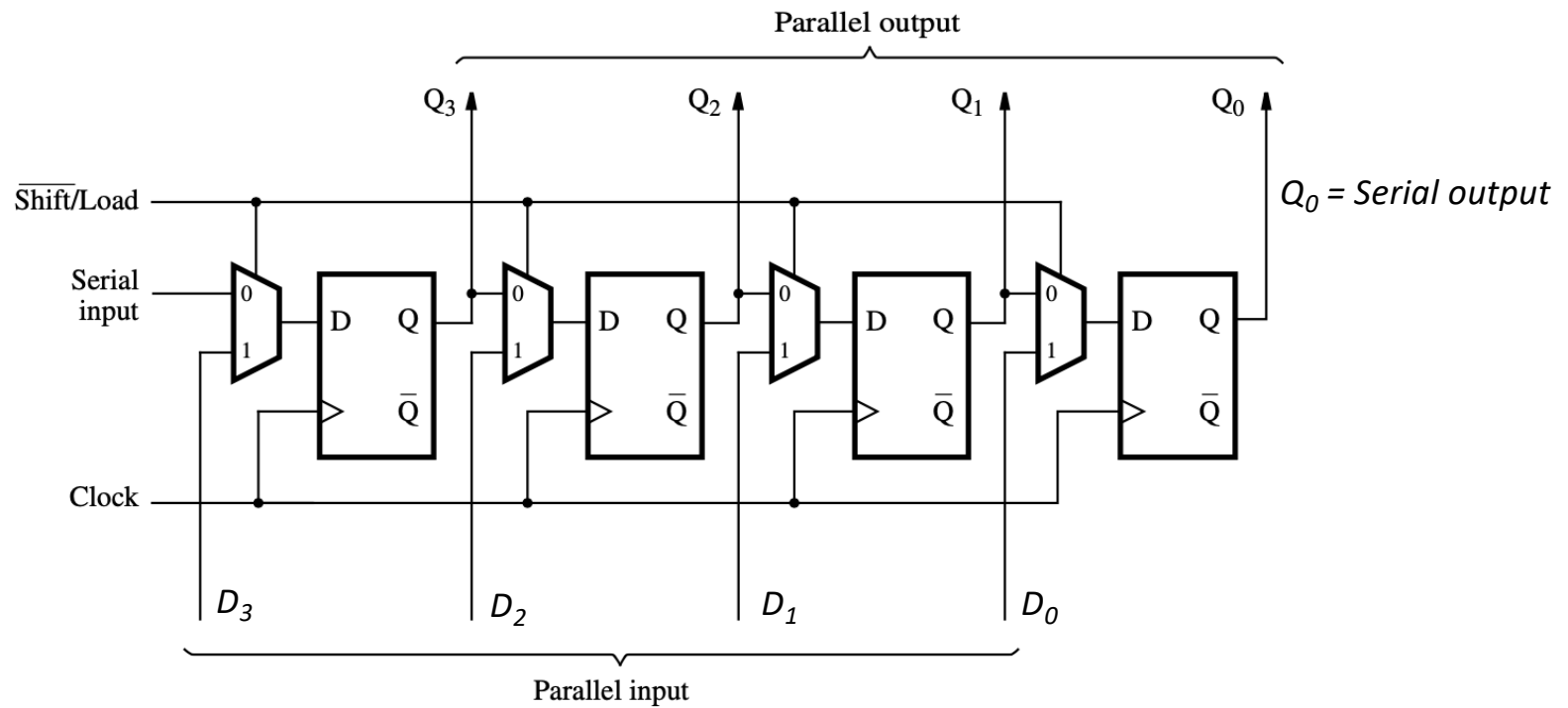

Parallel Access Shift Register in Verilog

```
// file: pa_sreg_n.v
// n-bit parallel access shift register

module pa_sreg_n(si, clk, d, q, ld, so);
    parameter n = 4;
    input si, clk, ld;
    input [n-1:0] d;
    output so;
    output reg [n-1:0] q;

    integer k;

    always @(posedge clk)
    begin
        if(ld)
            q <= d;
        else
            begin
                for (k=0; k<n-1; k=k+1) q[k] <= q[k+1];
                q[n-1] <= si;
            end
        end
    end


    assign so = q[0];

endmodule
```

Parallel Access Shift Register (with shift enable)

(Example: 4-bit)

Shift Enable has priority on Load Enable

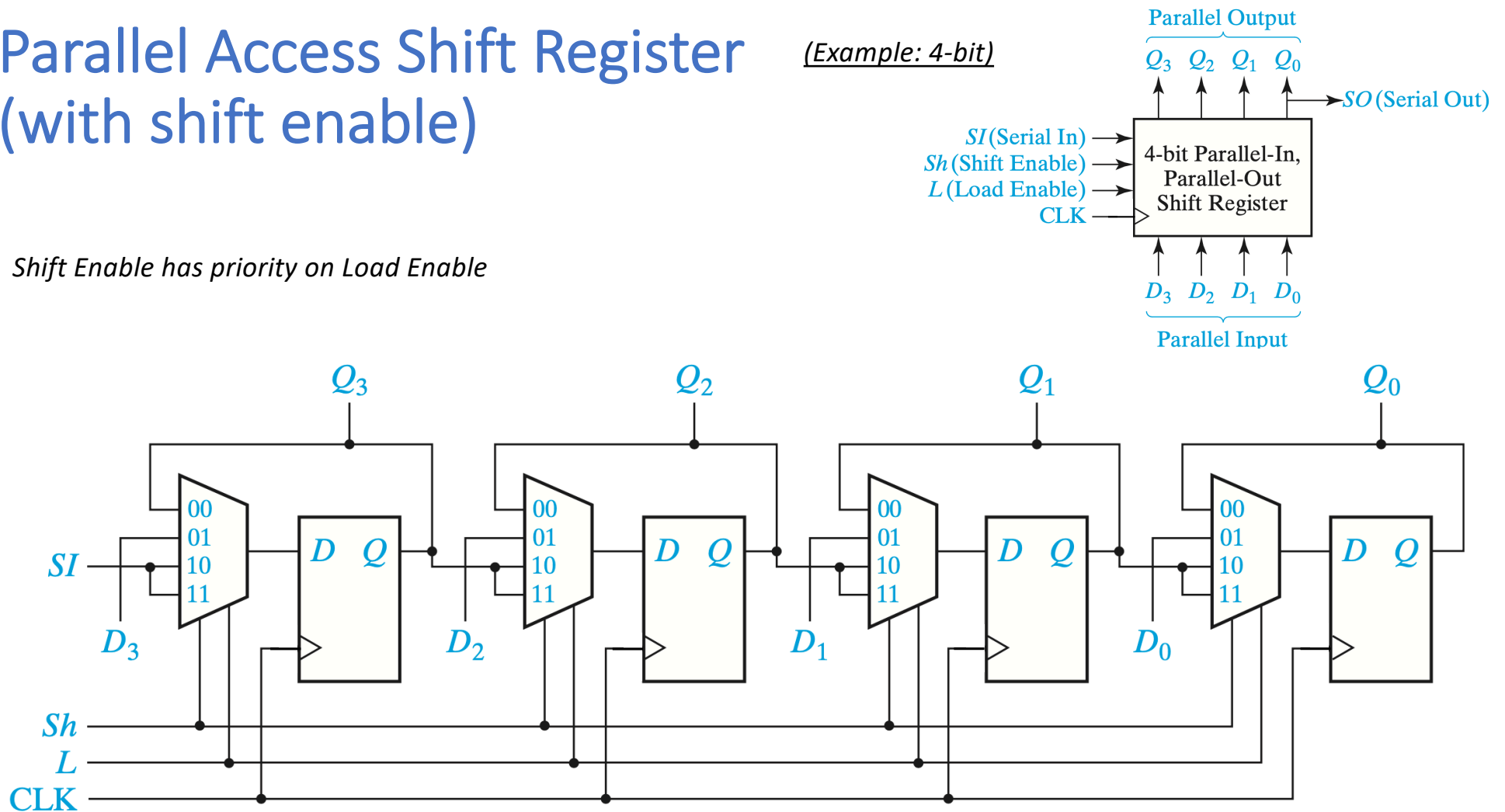


Next Time

- Counters
 - Asynchronous (don't use them!)
 - Synchronous
- Finite State Machines
 - Mealy
 - Moore

When writing Verilog think Hardware !


```
// file: pipe.v
// flip-flops pipelined
module pipe(d, clk, q1, q0);
  input d, clk;
  output reg q1, q0;

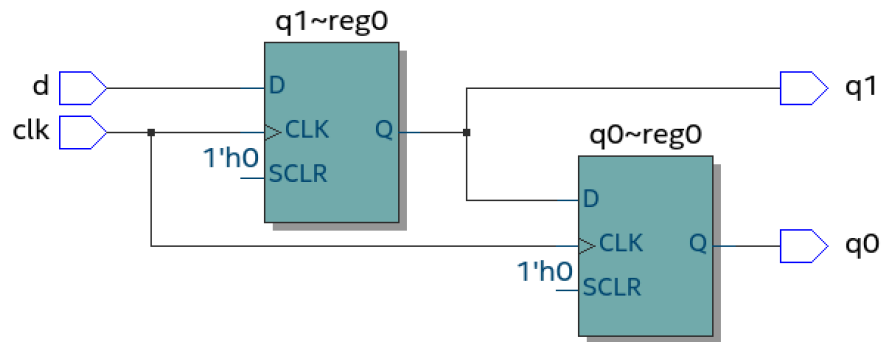  always @(posedge clk)
  begin
    if (clk)
      q1 <= d; //nonblocking
      q0 <= q1; //nonblocking
    end
  end
endmodule
```



```
// file: red.v
// redundant flip flop
module red(d, clk, q1, q0);
  input d, clk;
  output reg q1, q0;

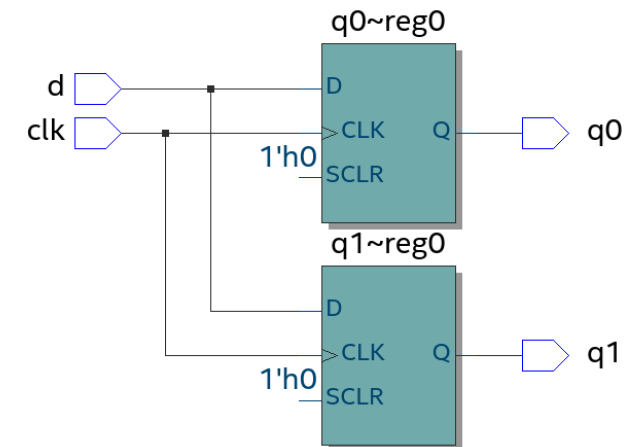  always @(posedge clk)
  begin
    if (clk)
      q1 <= d; //nonblocking
      q0 <= d; //nonblocking
    end
  end
endmodule
```



S.L. Building Blocks (continued)

CPEN 230 – Introduction to Digital Logic

Review

- D latch
- D flip-flop
- J-K flip-flop
- T flip-flop
- Registers
- Shift Registers


Counters

- Two categories of counters
 - Asynchronous (to be avoided at all costs)
 - Synchronous
 - binaries counters (T flip-flop based and D-flip-flop based)
 - shift register counters (ring counter and Johnson Counter) --> Fast Counters


Asynchronous modulo- 2^N upward counter

Example: $N=3$

**AVOID
ASYNCHRONOUS
COUNTERS !**

 

(a) Circuit

 


(b) Timing diagram


Asynchronous modulo- 2^N downward counter

Example: $N=3$

**AVOID
ASYNCHRONOUS
COUNTERS !**

 

(a) Circuit

 

(b) Timing diagram

The delay is not the same. It Increases with each flip-flop we go through.

Synchronous counters


- Synchronous counters are built by clocking all flip-flops with a single clocking source (this makes them more reliable than asynchronous counters)

Binary counter (using T flip-flops)


count	Q_2	Q_1	Q_0
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1

The operation of the counter is based on the observation that the state of the flip-flop in stage i *flips* only if all preceding flip-flops are in the state $Q = 1$.
 
$$\begin{aligned}
 T_0 &= 1 \\
 T_1 &= Q_0 \\
 T_2 &= Q_0 Q_1 \\
 &\dots \\
 T_{n-1} &= Q_0 Q_1 \dots Q_{n-2}
 \end{aligned}$$




(a) Circuit for 4-bit binary counter

 

(b) Timing diagram

Adding Enable and Clear Capability

 

Binary counter (using D flip-flops)

Clock cycle	Q_2	Q_1	Q_0	$(Q_2 Q_1 Q_0)_{\text{next}}$
0	0	0	0	0 0 1
1	0	0	1	0 1 0
2	0	1	0	0 1 1
3	0	1	1	1 0 0
4	1	0	0	1 0 1
5	1	0	1	1 1 0
6	1	1	0	1 1 1
7	1	1	1	0 0 0

$$D_0 = \overline{Q_0} = Q_0 \oplus 1$$


$$D_1 = Q_1 \oplus Q_0$$

$$D_2 = Q_2 \oplus Q_1 Q_0$$

...

$$D_{n-1} = Q_{n-1} \oplus Q_{n-2} \cdots Q_1 Q_0$$

 The operation of the counter is based on the observation that the state of the flip-flop in stage i *flips* only if all preceding flip-flops are in the state $Q = 1$.



Adding Enable and Clear capability

$$D_0 = Q_0 \oplus Enable$$


$$D_1 = Q_1 \oplus Q_0 \cdot Enable$$

$$D_2 = Q_2 \oplus Q_1 \cdot Q_0 \cdot Enable$$

$$D_3 = Q_3 \oplus Q_2 \cdot Q_1 \cdot Q_0 \cdot Enable$$


...

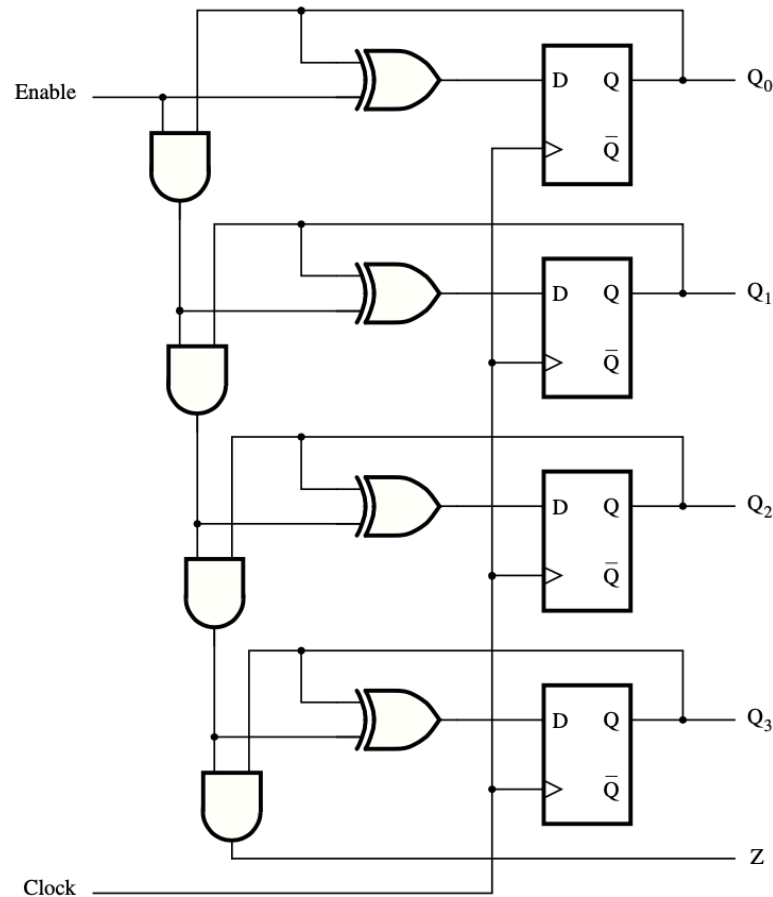If $Enable = 0$ the state of the flip-flop in stage i does not change ($Q_i \oplus 0 = Q_i$)



In case we want to cascade another counter (Z serves as the Enable for the next counter)

Adding parallel-load capability

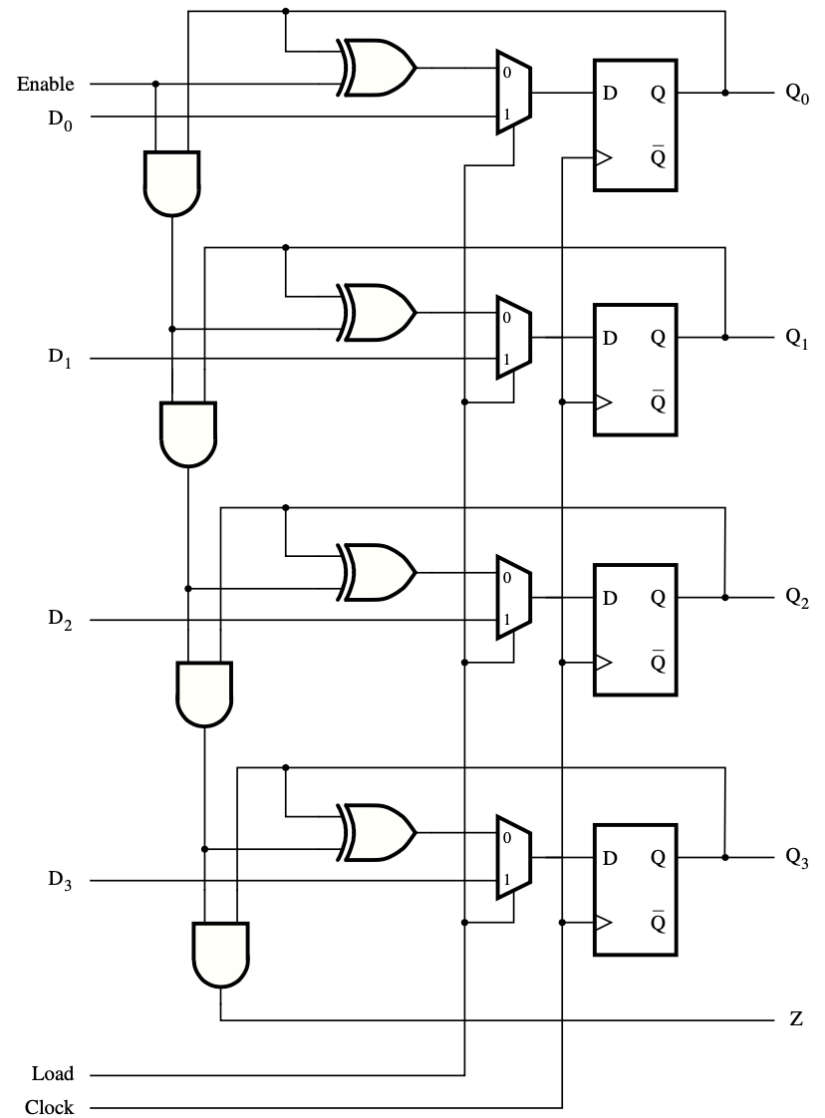


“Counting” in Verilog

```
// file: upcount_4bit.v
// 4-bit binary (up) counter with enable

module upcount_4bit(clk, rst_n, en, q);
    parameter n = 4;
    input clk, rst_n, en;
    output reg [n-1:0] q;

    always @(posedge clk, negedge rst_n)
    begin
        if(~rst_n)
            q <= 0;
        else if (en)
            q <= q + 1;
    end

endmodule
```

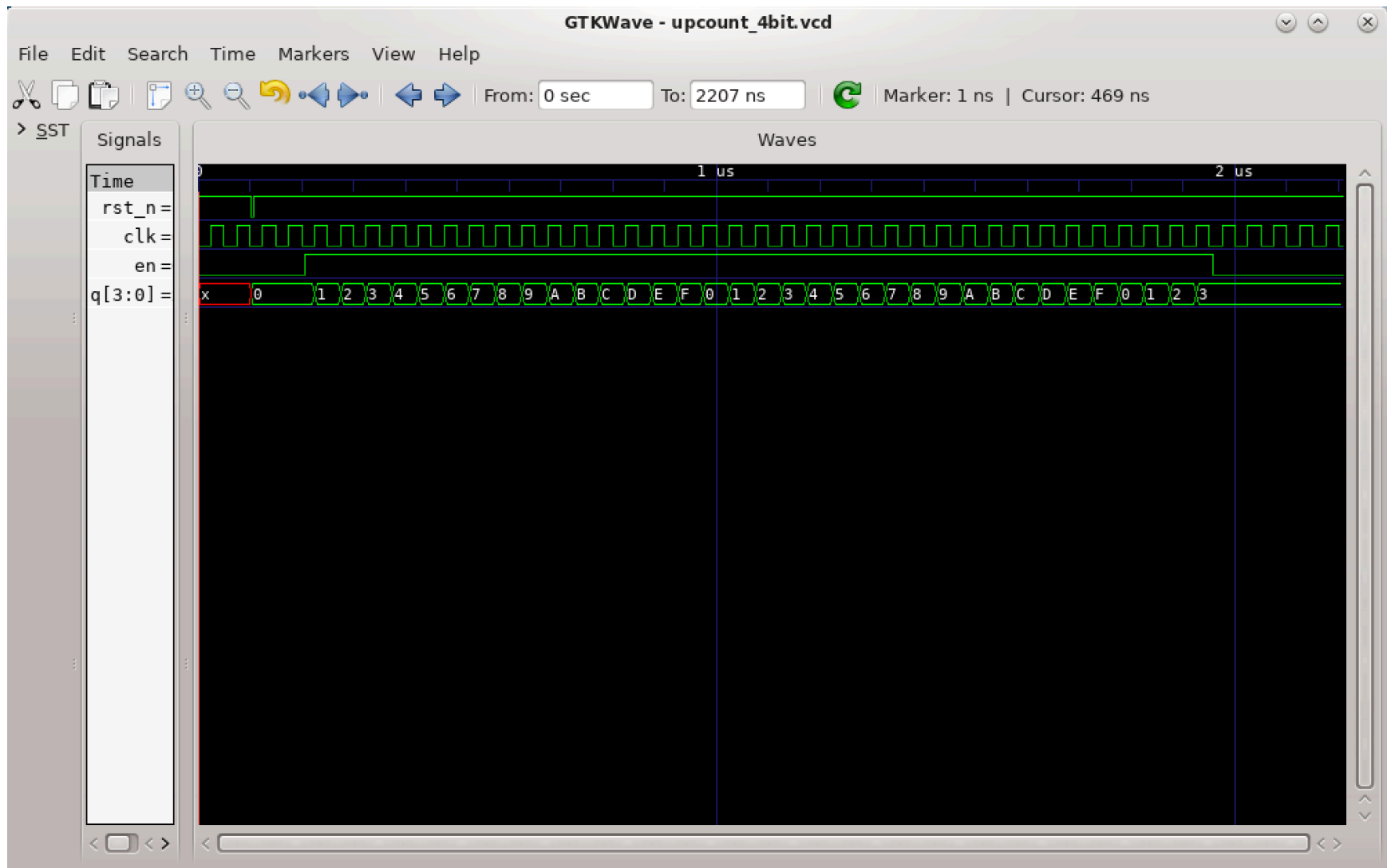

Example: adding parallel- load capability

```
// file: upcountpl_4bit.v
// 4-bit binary (up) counter with enable and parallel load

module upcountpl_4bit(clk, rst_n, en, ld, d, q);
    parameter n = 4;
    input clk, rst_n, en, ld;
    input [n-1:0] d;
    output reg [n-1:0] q;

    always @(posedge clk, negedge rst_n)
    begin
        if(~rst_n)
            q <= 0;
        else if (ld)
            q <= d;
        else if (en)
            q <= q + 1;
    end
endmodule
```

Example: adding down- count capability

```
// file: updowncountpl_4bit.v
// 4-bit binary (up/down) counter with enable and parallel load


module updowncountpl_4bit(clk, rst_n, en, ud, ld, d, q);
    parameter n = 4;
    input clk, rst_n, en, ud, ld;
    input [n-1:0] d;
    output reg [n-1:0] q;

    always @(posedge clk, negedge rst_n)
    begin
        if(~rst_n)
            q <= 0;
        else if (ld)
            q <= d;
        else if (en)
            if (ud)
                q <= q + 1;
            else
                q <= q - 1;
    end
endmodule
```


module-M counter

Not all the time we need to count for 2^N

Example: module-6 counter

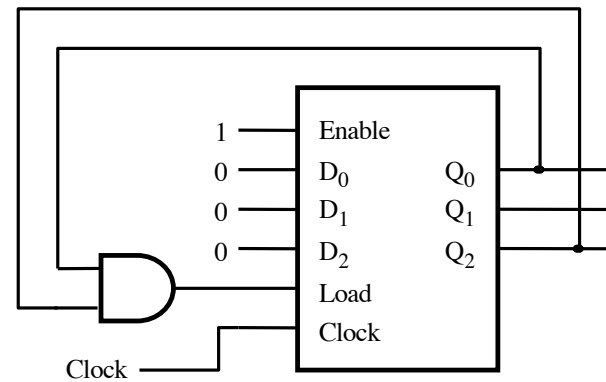

(a) Circuit

 

(b) Timing diagram


Example: modulo-6 counter

```
// file: counter.v
// modulo-6 counter

module counter(clk, rst_n, en, q);
    input clk, rst_n, en;
    output reg [2:0] q;

    always @(posedge clk, negedge rst_n)
    begin
        if(~rst_n)
            q <= 0;
        else if (en)
            if (q < 5)
                q <= q + 1;
            else
                q <= 0;
    end


endmodule
```

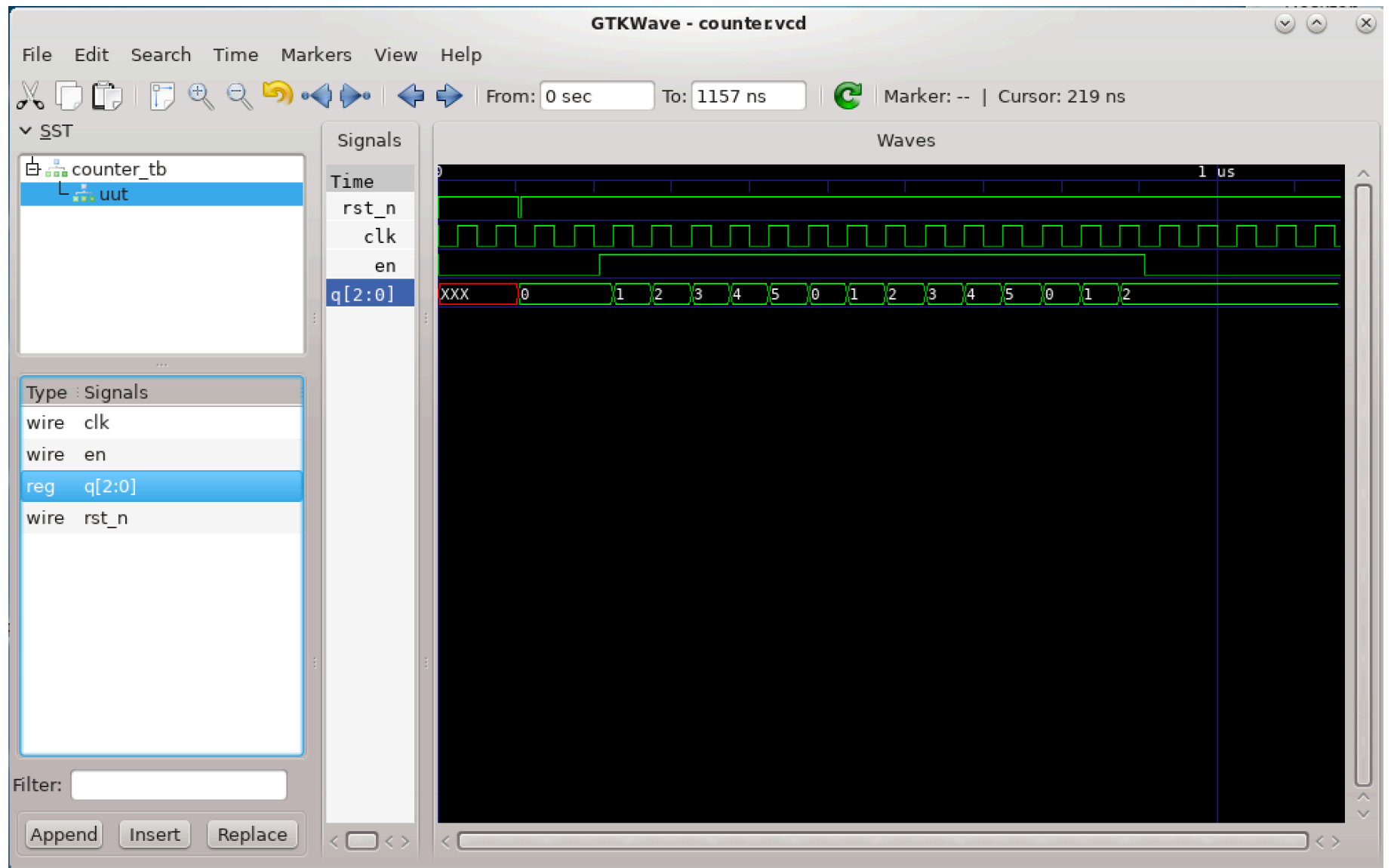

Ring counter

An n -bit counter of this type generates a counting sequence of length n

 
For example a 4-bit counter produces the sequence: 1000, 0100, 0010, 0001, ...



Johnson Counter

An n-bit counter of this type generates a counting sequence of length $2n$

 For example a 4-bit counter produces the sequence: 0000, 1000, 1100, 1110, 1111, 0111, 0011, 0001, 0000, ...




Next Time

- Finite State Machines
 - Mealy
 - Moore

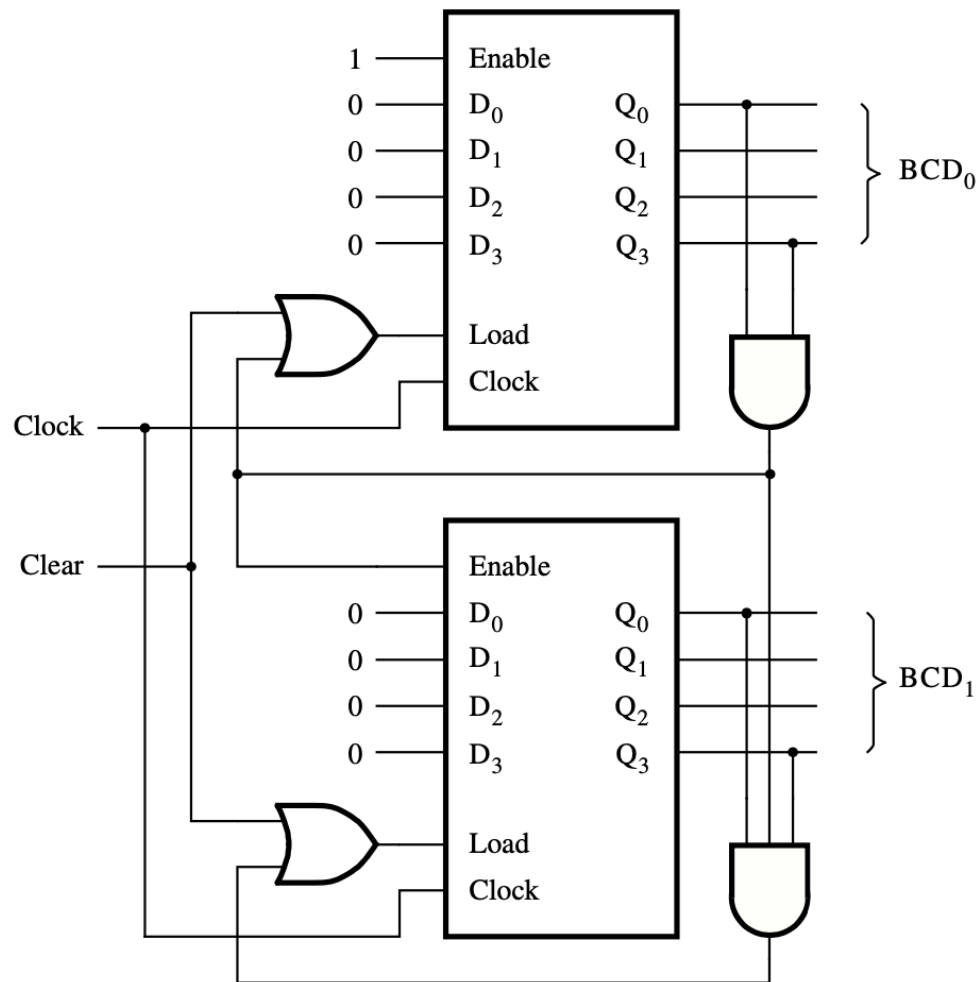Example: Two digit BCD Counter

*It consists of two modulo-10 counters.
One for each BCD digit*



Finite State Machines

CPEN 230 – Introduction to Digital Logic

Review


- Synchronous counters
 - Binary Counters (modulo- 2^N and modulo-M)
 - Fast counters (Ring counter and Johnson counter)

Digital Synchronous Systems


- In general, all circuits that are non combinational are sequential.
- Combinational circuits have no cyclic paths (feedback loops).
- **Cyclic paths can cause undesirable races or unstable behavior.**
- To avoid these problems, designers break the cyclic paths by inserting registers somewhere in the path.
- This way the state of the circuit can change only at the clock edge (is synchronized to the clock).
- **Synchronous sequential circuits:** combinational logic followed by a bank of flip-flops (register).
- Virtually all digital sequential systems are synchronous.

A problematic sequential circuit (astable behavior)


Ring Oscillator

 

 Suppose each inverter has a propagation delay of 1 ns (--> each node oscillates with a period of 6 ns)




 
The circuit has no stable states, so it is said unstable or astable.



Another problematic sequential circuit (D-latch with a race condition)

CLK	D	Q_{prev}	Q
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1
  
$$Q = CLK \cdot D + \overline{CLK} \cdot Q_{prev}$$



Suppose the delay through the inverter is rather long compared to the delays of the AND and OR gates. Since N1 and Q may both fall before CLK rises, then N2 will never rise, and Q becomes stuck at 0 (despite the latch should remember its old value of Q=1)


Synchronous Sequential Logic Design

- Breaks cyclic paths by **inserting registers**
- Registers contain **state** of the system
- State changes at clock edge: system **synchronized** to the clock
- **Rules** of synchronous sequential circuit composition:
 - Every circuit element is either a register or a combinational circuit
 - At least one circuit element is a register
 - All registers receive the same clock signal
 - Every cyclic path contains at least one register
- **A common synchronous sequential circuit**
 - Finite State Machines (FSMs)

Finite State Machines (FSMs)

- **Three blocks:**

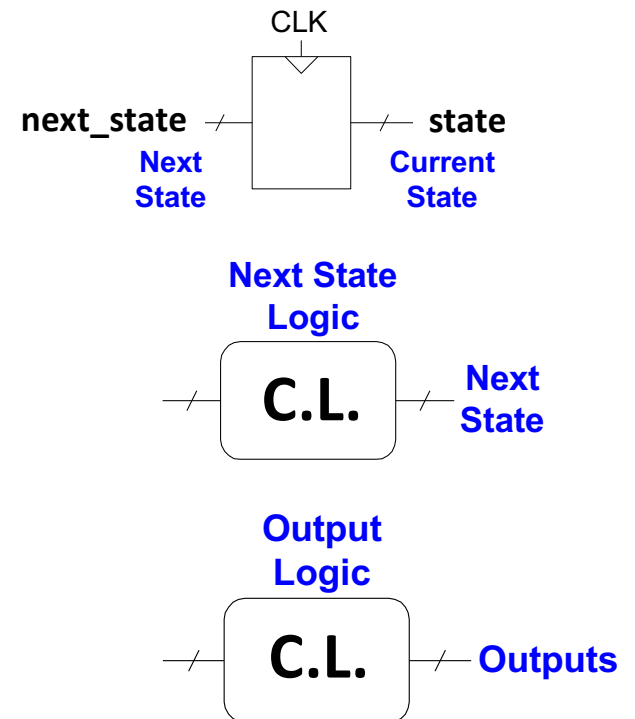- next state logic (C.L.)
 - Computes the next state
- state register (S.L.)
 - Stores current state
 - Loads next state at clock edge
- output logic (C.L.)
 - Computes the outputs




A circuit with k flip-flops can be in one of a finite number (2^k) of unique states


Finite State Machines (FSMs)

- **Next state** determined by current state and inputs
- Two types of finite state machines differ in **output logic**:
 - **Moore FSM**: outputs depend only on current state
 - **Mealy FSM**: outputs depend on current state *and* inputs


Moore FSM

 

Mealy FSM

 


Counters and FSMs are closely related !

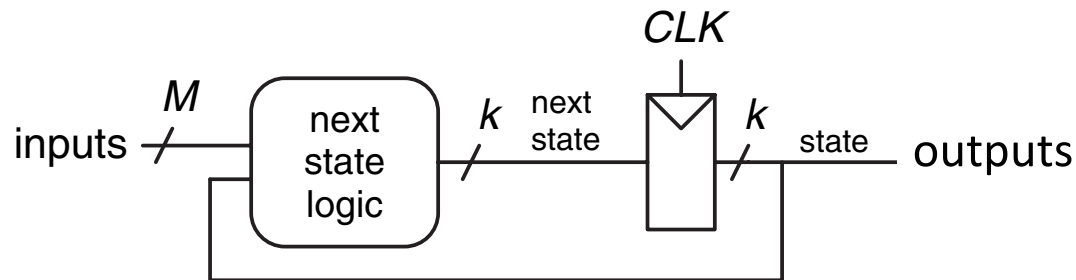


- **Perspective #1:** we can think of a counter as an FSM without the output logic block (and often with the next state logic having no inputs).
- **Perspective #2:** counters are the “core” of FSMs. They provide the next logic block and the state register block. All it remains for building an FSM out of a counter is adding the output logic block.

Moore vs. Mealy FSM

 
- Maggie T. Hacker has a snail that crawls down a paper tape with 1's and 0's on it. The snail smiles whenever the last two digits it has crawled over are 01. Design Moore and Mealy FSMs of the snail's brain.



Design Example (Moore FSM)

 

State Transition Diagram

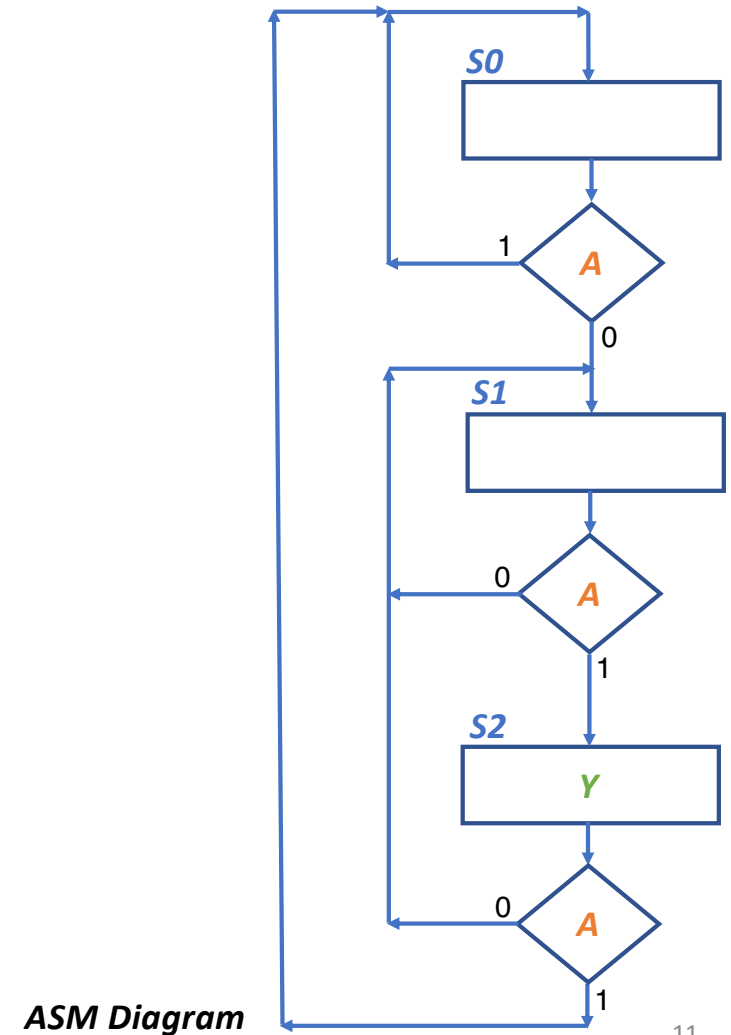


ASM Diagram

Moore FSM Tables

Moore state transition table

Current State S	Input A	Next State S^+
S0	0	S1
S0	1	S0
S1	0	S1
S1	1	S2
S2	0	S1
S2	1	S0

 


Moore output table

Current State S	Output Y
S0	0
S1	0
S2	1

Binary Encoding of the states

State	Encoding
S0	00
S1	01
S2	10

Moore FSM Tables with encodings

 

Moore state transition table with state encodings

Current State		Input A	Next State	
S_1	S_0		S_1^+	S_0^+
0	0	0	0	1
0	0	1	0	0
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	0

Moore output table with state encodings

Current State		Output Y
S_1	S_0	
0	0	0
0	1	0
1	0	1

$$S_1^+ = S_0 \cdot A$$

$$S_0^+ = \bar{A}$$


$$Y = S_1$$

Moore FSM Schematic


$$S_1^+ = S_0 \cdot A$$

$$S_0^+ = \bar{A}$$

$$Y = S_1$$

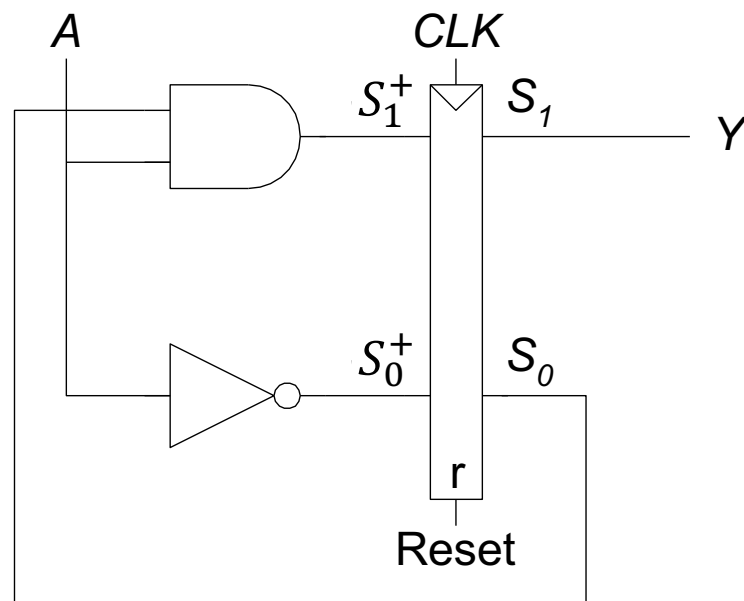


Design Example (Mealy FSM)

 

State Transition Diagram


ASM Diagram

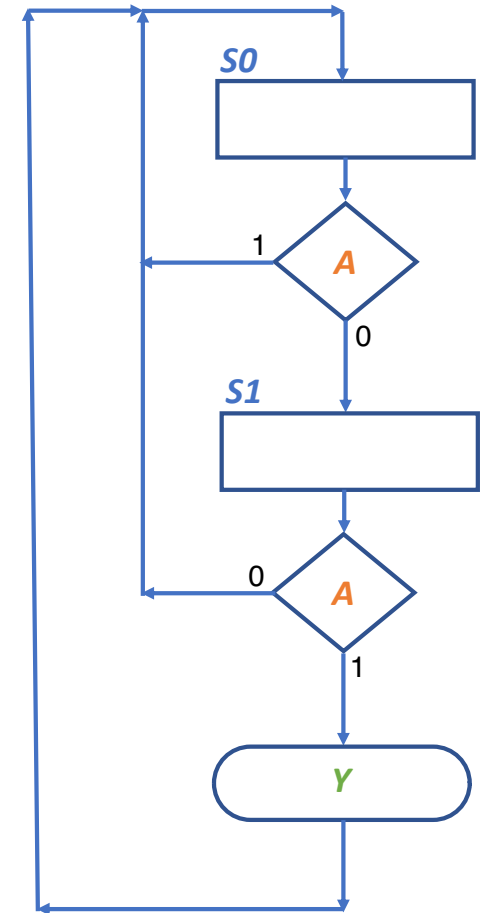

Mealy FSM Tables

Mealy state transition and output table


Current State <i>S</i>	Input <i>A</i>	Next State <i>S⁺</i>	Output <i>Y</i>
S0	0	S1	0
S0	1	S0	0
S1	0	S1	0
S1	1	S0	1

 

Binary encoding of the states

State	Encoding
S0	0
S1	1

Mealy FSM Tables with encodings

 

Mealy state transition and output table with state encodings

Current State S_0	Input A	Next State S_0^+	Output Y
0	0	1	0
0	1	0	0
1	0	1	0
1	1	0	1


$$S_0^+ = \bar{A}$$

$$Y = S_0 \cdot A$$


Mealy FSM Schematic

$$S_0^+ = \bar{A}$$


$$Y = S_0 \cdot A$$

 

 FSM schematics for (a) Moore and (b) Mealy machines




(a)

 


(b)

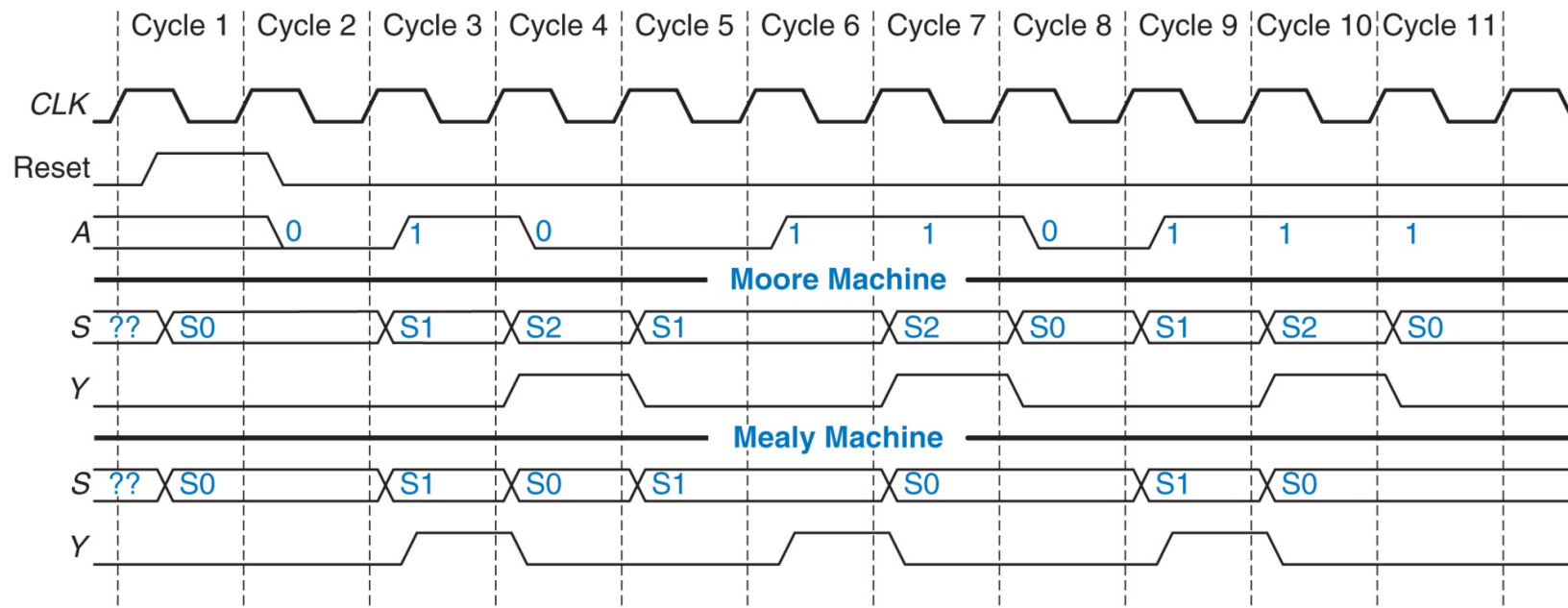Timing diagrams for Moore and Mealy machines



FSMs in Verilog

(Pattern Detector: Moore's FSM)

 

```
// file: patternMoore.v
// Moore FSM to detect pattern

module patternMoore
(
    input clk,
    input reset,
    input a,
    output reg y
);

    reg [1:0] state, nextstate;


    // declare states
    parameter S0 = 2'b00,
               S1 = 2'b01,
               S2 = 2'b10;

    // state register
    always @(posedge clk, posedge reset) begin
        if (reset) state <= S0;
        else state <= nextstate;
    end
```

```
// next state logic
always @(state, a) begin
    case (state)
        S0: if (a) nextstate = S0;
            else nextstate = S1;
        S1: if (a) nextstate = S2;
            else nextstate = S1;
        S2: if (a) nextstate = S0;
            else nextstate = S1;
        default: nextstate = S0;
    endcase
end

// output logic (output depends only on the state)
always @(state) begin
    if (state == S2)
        y = 1'b1;
    else
        y = 1'b0;
    end
endmodule
```

Pattern Detector: Moore's FSM

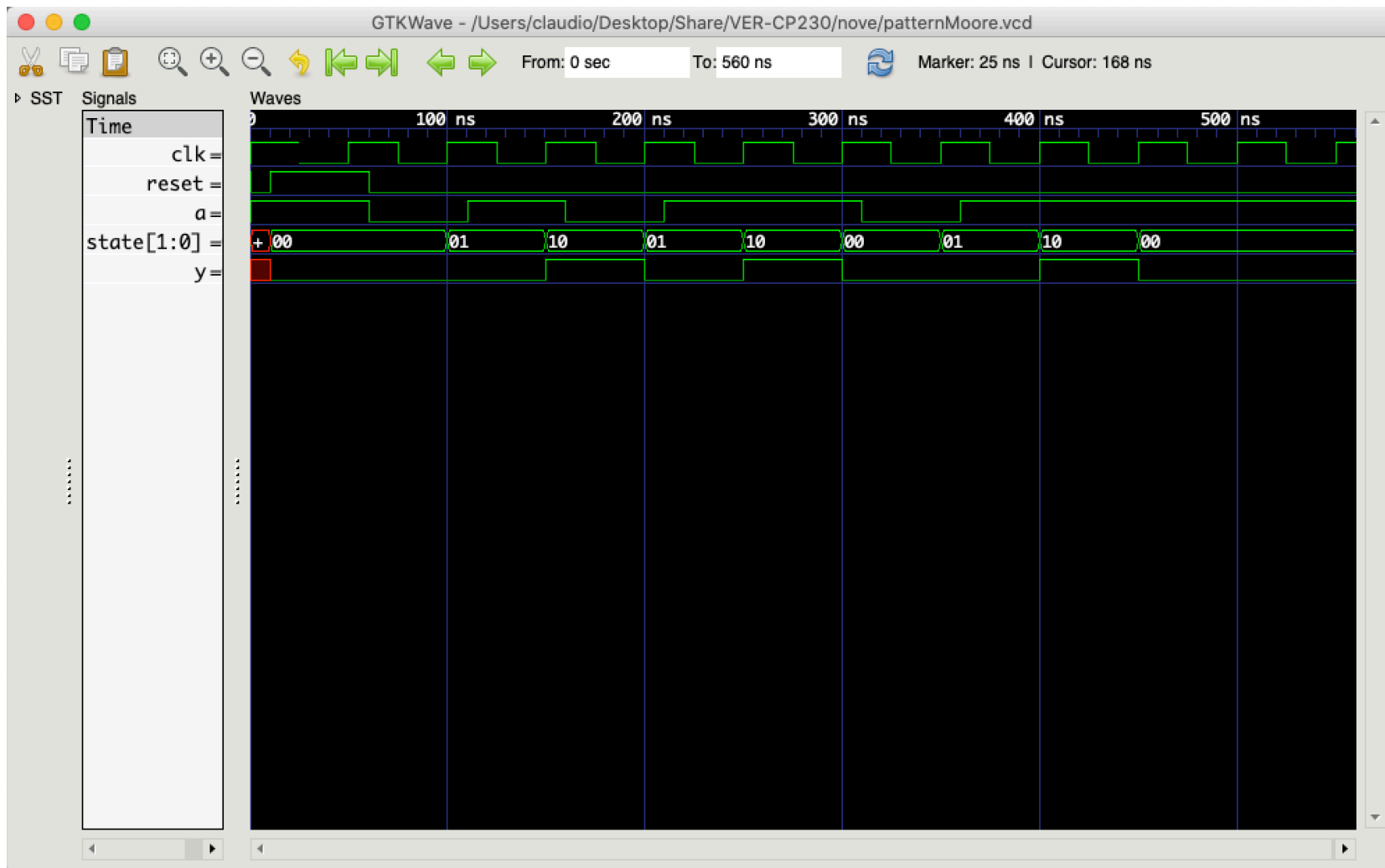

FSMs in Verilog

(Pattern Detector: Mealy's FSM)

```
// file: patternMealy.v
// Mealy FSM to detect pattern

module patternMealy
(
    input clk,
    input reset,
    input a,
    output y
);

    reg state, nextstate;



    // define state
    parameter S0 = 0, S1 = 1;

    // state register
    always @(posedge clk, posedge reset) begin
        if (reset) state <= S0;
        else state <= nextstate;
    end

    // next state logic
    always @(state, a) begin
        case (state)
            S0: if (a) nextstate = S0;
                else nextstate = S1;
            S1: if (a) nextstate = S0;
                else nextstate = S1;
            default: nextstate = S0;
        endcase
    end

    // output logic
    assign y = (a & state == S1);

endmodule
```

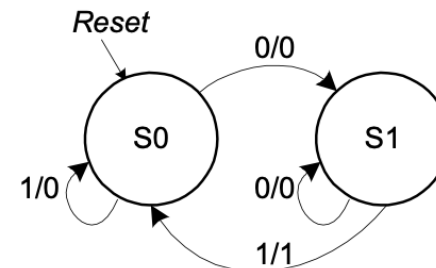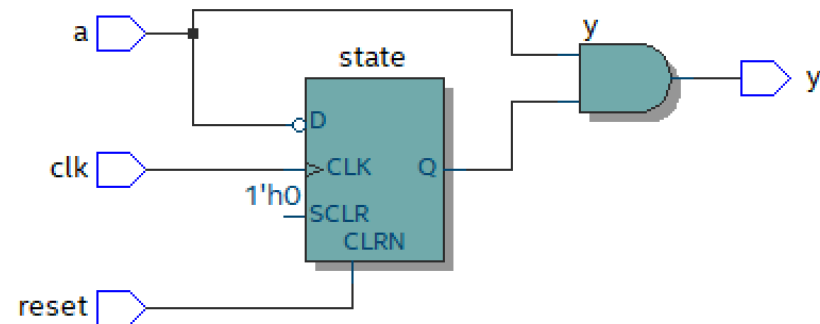


FSM State Encodings

- **Binary** encoding:
 - i.e., for four states, 00, 01, 10, 11
- **One-hot** encoding
 - One state bit per state
 - Only one state bit HIGH at once
 - i.e., for four states, 0001, 0010, 0100, 1000
 - Requires more flip-flops
 - Often next state and output logic is simpler

 Example: Divide-by-N counter


- Design a divide-by-3 counter using binary and one-hot state encoding

The output Y is HIGH for one clock cycle out of every 3



(a)

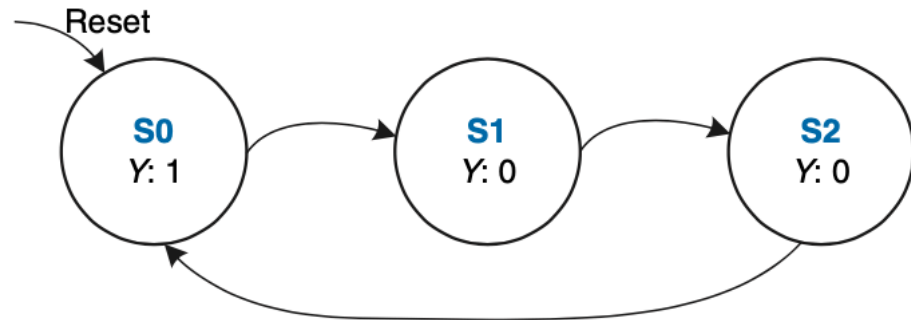Divide-by-3 counter
(a) waveform and (b) state
transition diagram



(b)

Divide-by-3 counter

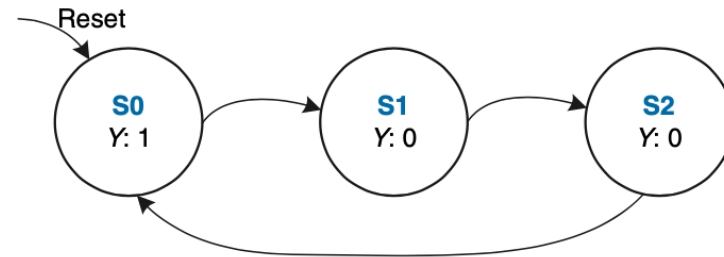


Table 3.6 Divide-by-3 counter state transition table

Current State	Next State
S0	S1
S1	S2
S2	S0

Table 3.7 Divide-by-3 counter output table

Current State	Output
S0	1
S1	0
S2	0



Divide-by-3 counter

Table 3.8 One-hot and binary encodings for divide-by-3 counter

State	One-Hot Encoding			Binary Encoding	
	S_2	S_1	S_0	S_1	S_0
S0	0	0	1	0	0
S1	0	1	0	0	1
S2	1	0	0	1	0

Table 3.9 State transition table with binary encoding



Current State		Next State	
S_1	S_0	S_1^+	S_0^+
0	0	0	1
0	1	1	0
1	0	0	0

 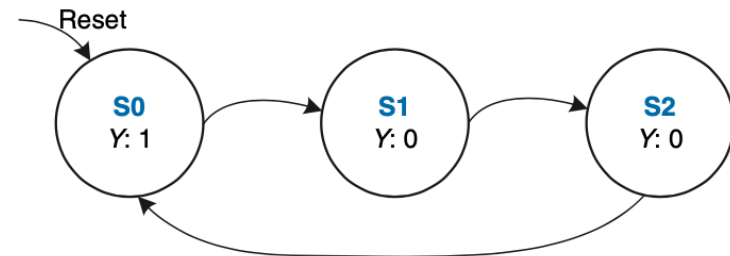

Divide-by-3 counter

Table 3.10 State transition table with one-hot encoding

Current State			Next State		
s_2	s_1	s_0	s_2^+	s_1^+	s_0^+
0	0	1	0	1	0
0	1	0	1	0	0
1	0	0	0	0	1

  

Divide-by-3 counter (one-hot encoding) in Verilog

```
// file: divideby3.v
// divide by 3 counter using one-hot encoding

module divideby3
(
    input clk,
    input reset,
    output y
);

    reg [2:0] state, nextstate;


    // define states
    parameter S0 = 3'b001,
               S1 = 3'b010,
               S2 = 3'b100;

    // state register
    always @(posedge clk, posedge reset) begin
        if (reset) state <= S0;
        else state <= nextstate;
    end

    // next state logic
    always @(state) begin
        case (state)
            S0: nextstate = S1;
            S1: nextstate = S2;
            S2: nextstate = S0;
            default: nextstate = S0;
        endcase
    end

    // output logic
    assign y = (state == S0);

endmodule
```

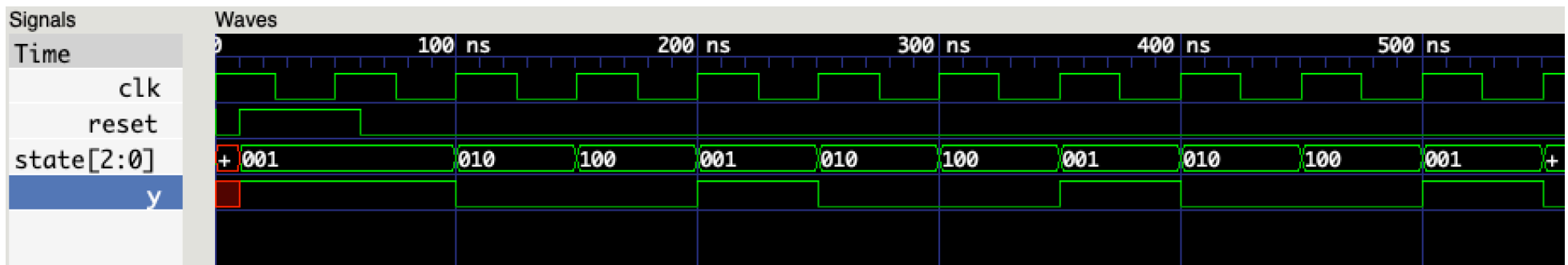

Review of FSM Design Procedure

1. Identify inputs and outputs
2. Sketch state transition diagram or ASM diagram
3. Write state transition table
4. Select state encodings
5. For Moore machine:
 - a. Rewrite state transition table with state encodings
 - b. Write output table
6. For a Mealy machine:
 - a. Rewrite combined state transition and output table with state encodings
7. Write Boolean equations for next state and output logic
8. Sketch the circuit schematic

Next time


- S.L. Timing
 - Setup time
 - Hold Time
 - Clock Skew
 - Metastability

Timing of Synchronous S.L. circuits

CPEN 230 – Introduction to Digital Logic

Review

- Synchronous S.L. circuits
 - Breaks cyclic paths by **inserting registers** (combinational logic followed by register)
- Finite State Machines (FSMs)
 - Three blocks
 - Next state logic (C.L.)
 - State Register (S.L.)
 - Output Logic (C.L.)
- Types of FSMs
 - Moore (outputs depend only on current state)
 - Mealy (outputs depend on current state and current inputs)
- FSM State Encodings
- Coding FSMs in Verilog

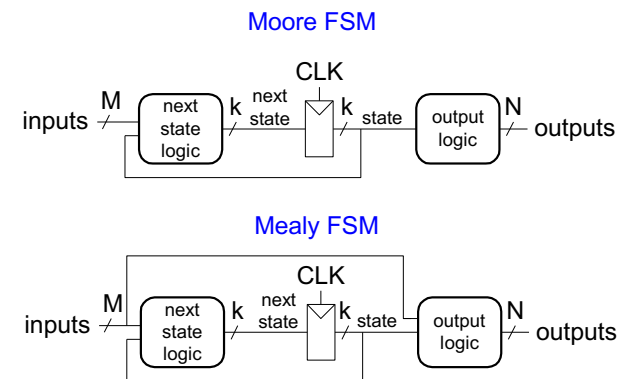

Review: FSM Design


1. Identify inputs and outputs
2. Sketch state transition diagram or ASM diagram
3. Write state transition table
4. Select state encodings
5. For Moore machine:
 - a. Rewrite state transition table with state encodings
 - b. Write output table
6. For a Mealy machine:
 - a. Rewrite combined state transition and output table with state encodings
7. Write Boolean equations for next state and output logic
8. Sketch the circuit schematic

Timing

- Flip-flop samples D at clock edge
- D must be stable when sampled
- Similar to a photograph, D must be stable around clock edge (both ahead and after the edge = aperture time)
- If not, metastability can occur


Input Timing Constrains

 - **Setup time:** t_{setup} = time *before* clock edge data must be stable (i.e. not changing)
- **Hold time:** t_{hold} = time *after* clock edge data must be stable
- Aperture time: t_a = time *around* clock edge data must be stable ($t_a = t_{\text{setup}} + t_{\text{hold}}$)





Output Timing Constrains

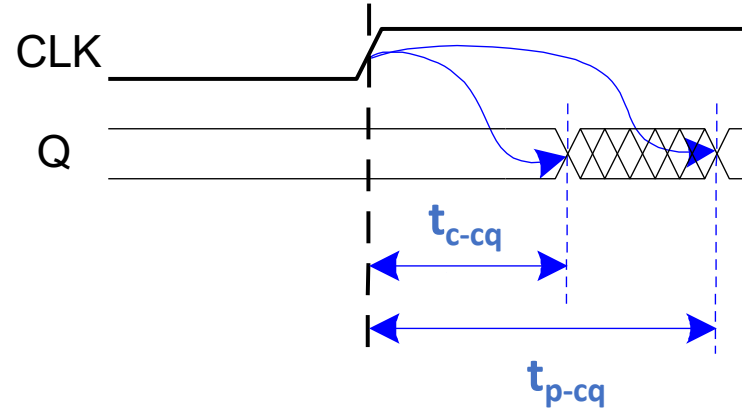- **Propagation delay:** t_{p-cq} = time after clock edge the output Q is guaranteed to be stable (i.e., to stop changing)
- Contamination delay: t_{c-cq} = time after clock edge Q might start being unstable (i.e., start changing)



 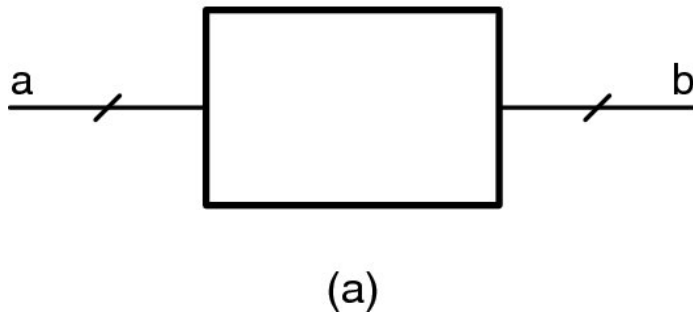
Propagation delay vs. Contamination delay




- Propagation delay t_{d-ab} and contamination delay t_{c-ab} .
- The contamination delay of a logic block is the time from when the first input signal first changes to when the first output signal first changes.
- The propagation delay of a logic block is the time from when the last input signal last changes to when the last output signal last changes

Dynamic Discipline

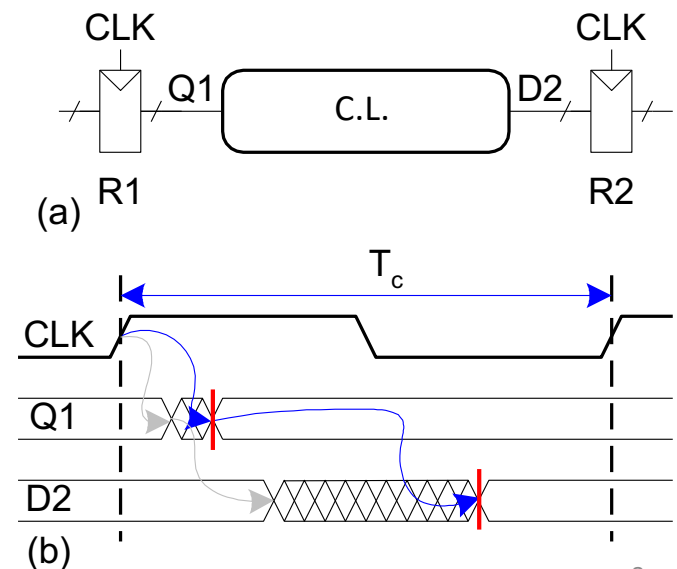- Any generic path in a synchronous sequential circuit, can be mapped in the RTL (register transfer level) structure of figure (a)
- Synchronous sequential circuit inputs must be stable during aperture (setup and hold) time around clock edge. In other words, inputs must be stable
 - at least t_{setup} before the clock edge
 - at least until t_{hold} after the clock edge



Setup Time Constraint

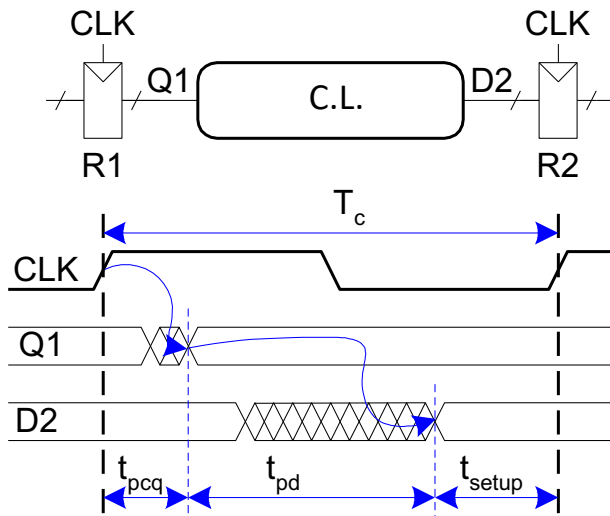

- The input to register R2 must be stable at least t_{setup} before clock edge
- It depends on the **maximum delay** it takes to process the signal sampled by R2 (i.e., the maximum delay it takes to go through R1 and the combinational logic)

$$T_c \geq t_{p-cq} + t_{pd} + t_{setup}$$


clock period

max delay through R1

max delay through C.L.

setup time of R2

Hold Time Constraint

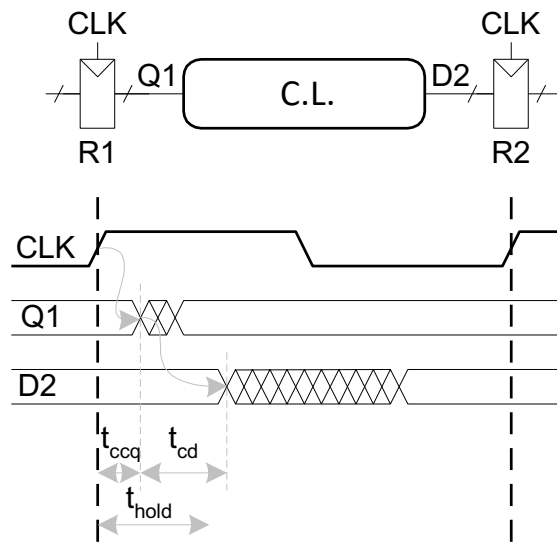

- The input to register R2 must be stable for at least t_{hold} after the clock edge
- It depends on the **minimum** delay it takes to go through register R1 and the combinational logic

$$t_{hold} < t_{c-cq} + t_{c-d}$$


hold time of R2

min delay through R1



min delay through C.L.

The effect of clock skew

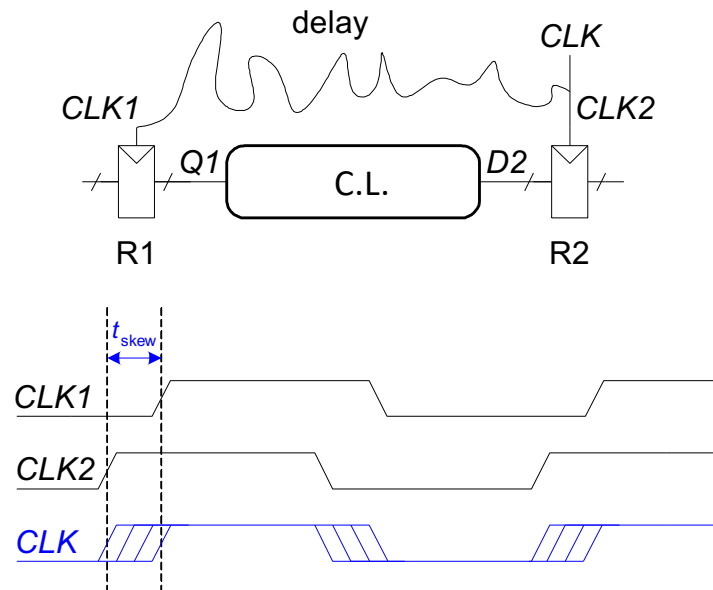- The clock doesn't arrive at all registers at same time
- **Skew**: difference between two clock edges
- Perform **most problematic case analysis** to guarantee dynamic discipline is not violated for any register (many registers in a system!)




Setup Time constraint with skew

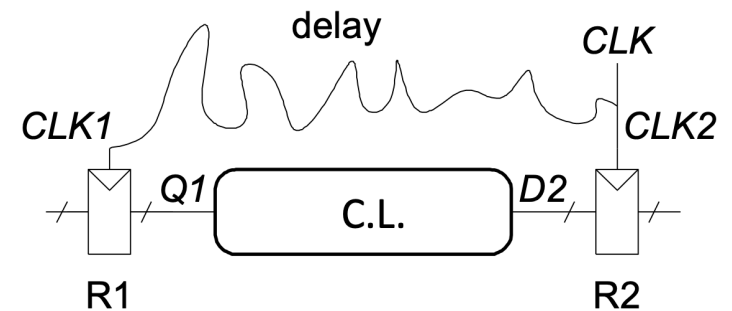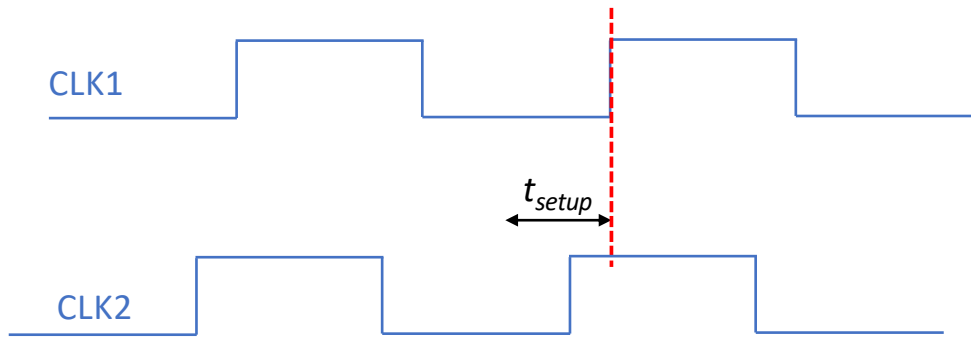

- The most problematic scenario occurs when CLK2 is earlier

$$T_c \geq t_{p-cq} + t_{pd} + t_{setup} + t_{skew}$$

Hold Time constraint with skew


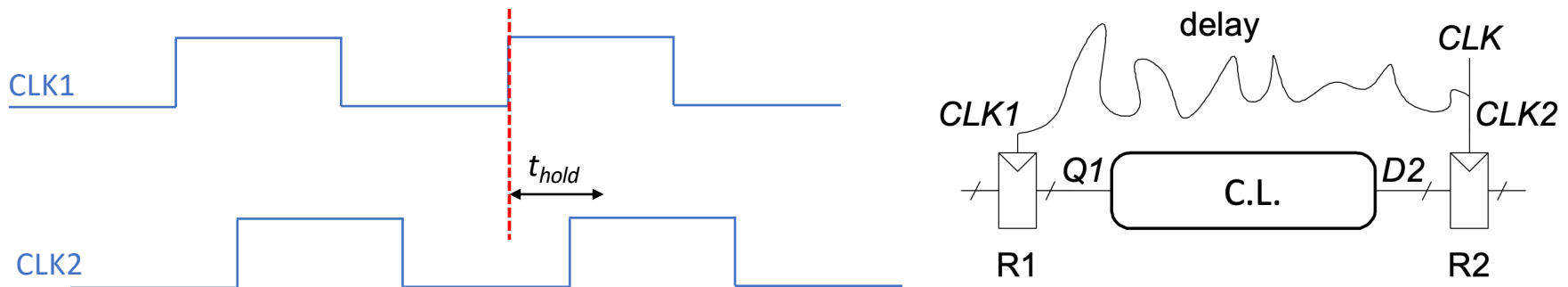


- The most problematic scenario occurs when CLK2 is later


$$t_{hold} \leq t_{c-cq} + t_{c-d} - t_{skew}$$

Violating the Dynamic Discipline

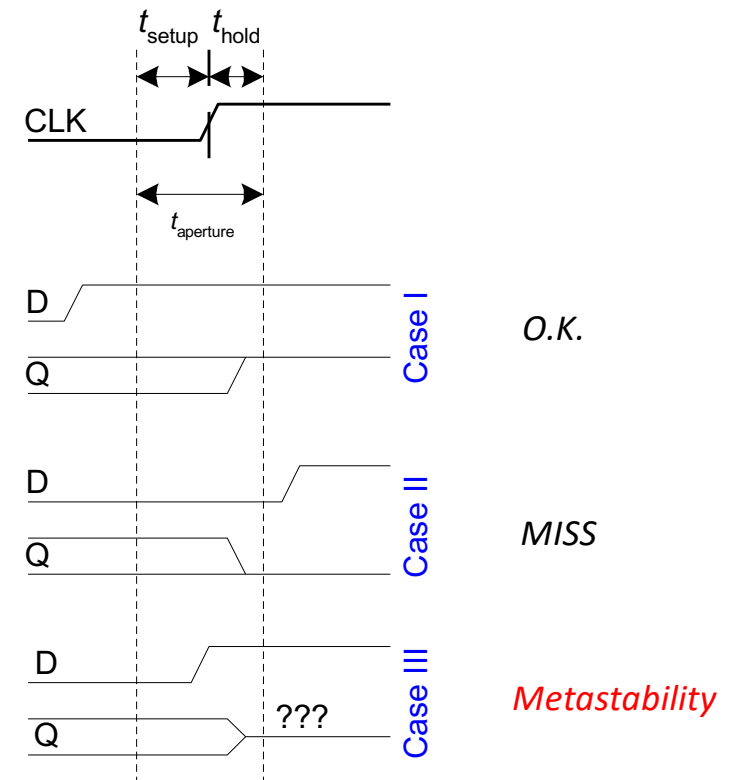 
Asynchronous inputs (for example, user inputs) might violate the dynamic discipline



Metastability: Example

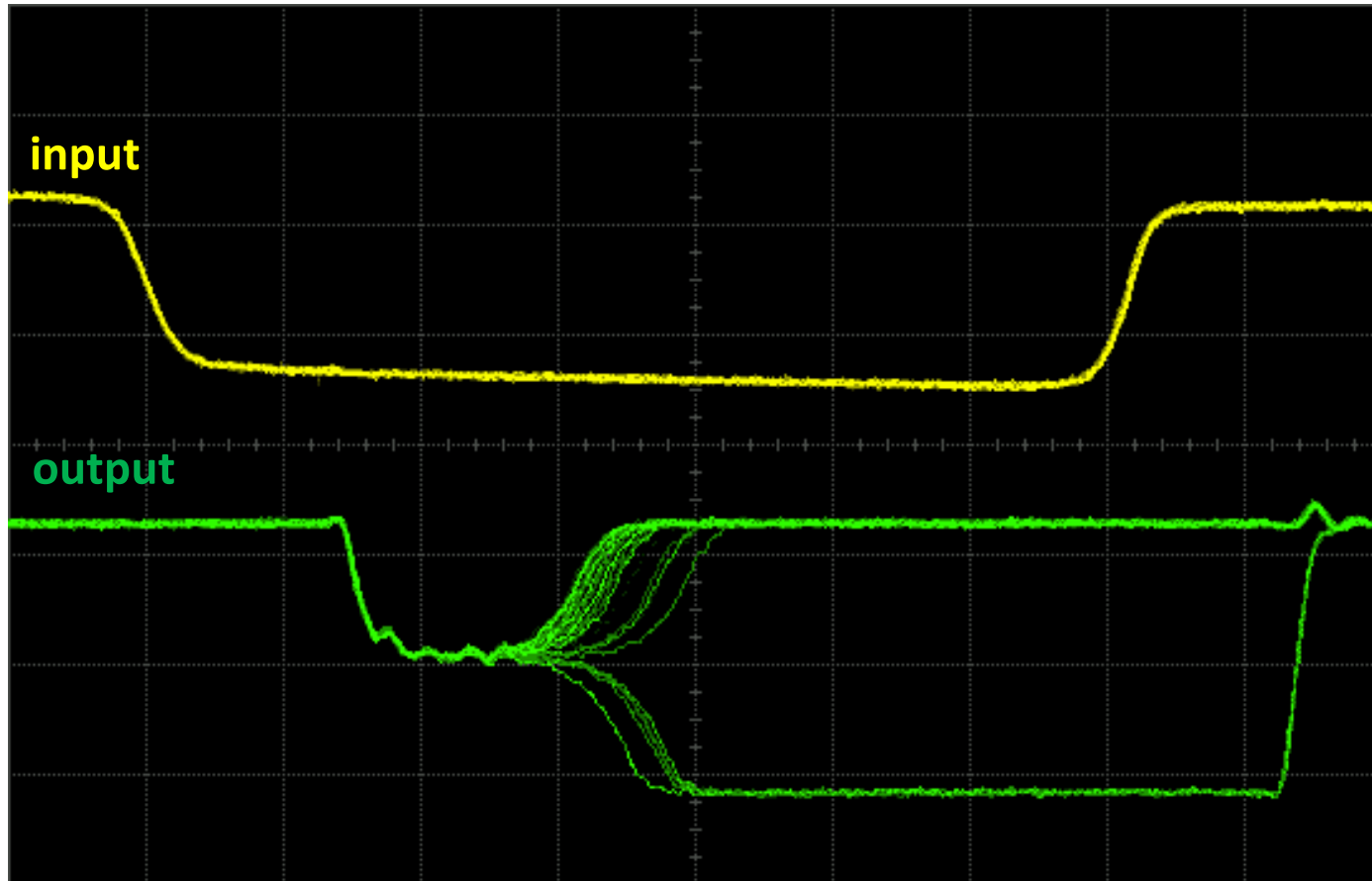

Metastability: Example

 

One Last FSM Design Example

CPEN 230 – Introduction to Digital Logic

FSM Design

1. Identify inputs and outputs
2. Sketch state transition diagram or ASM diagram
3. Write state transition table
4. Select state encodings
5. For Moore machine:
 - a. Rewrite state transition table with state encodings
 - b. Write output table
6. For a Mealy machine:
 - a. Rewrite combined state transition and output table with state encodings
7. Write Boolean equations for next state and output logic
8. Sketch the circuit schematic

Example: Design a Rising-edge Detector

- A rising-edge detector is a circuit that generates a one-clock cycle high level value when the input signal change from 0 to 1.

In class Activity