

## CP230 – Problem Set 1

### Problem 1.71 [H&H]

**Exercise 1.71** Draw the symbol, Boolean equation, and truth table for

- (a) a three-input OR gate
- (b) a three-input exclusive OR (XOR) gate
- (c) a four-input XNOR gate


### Problem 1.72 [H&H]

**Exercise 1.72** Draw the symbol, Boolean equation, and truth table for

- (a) a four-input OR gate
- (b) a three-input XNOR gate
- (c) a five-input NAND gate

### Problem 1.73 [H&H]

**Exercise 1.73** A *majority gate* produces a TRUE output if and only if more than half of its inputs are TRUE. Complete a truth table for the three-input majority gate shown in [Figure 1.41](#).

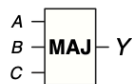

**Figure 1.41** Three-input majority gate

### Problem 1.75 [H&H]


**Exercise 1.75** A three-input *OR-AND-INVERT (OAI) gate* shown in [Figure 1.43](#) produces a FALSE output if C is TRUE and A or B is TRUE. Otherwise it produces a TRUE output. Complete a truth table for the gate.



**Figure 1.43** Three-input OR-AND-INVERT gate

Problem 1.88 [H&H]

**Exercise 1.88** Write a truth table for the function performed by the gate in Figure 1.51. The truth table should have three inputs,  $A$ ,  $B$ , and  $C$ .

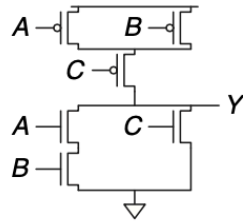

**Figure 1.51** Mystery schematic