

One-bit Full Adder: The Bad and the Ugly way

Attempt at using Boolean algebra to prove that Full Adder Sum = 3-Way Light Control, and that Full Adder Carry Out = Majority Gate.

$$\begin{aligned}
 So &= A \wedge B \wedge C \\
 &= (A \wedge B) \wedge C \\
 &= (AB' + A'B) \wedge C \\
 &= (AB' + A'B)*C' + (AB' + A'B)'*C \\
 &= AB'C' + A'BC' + C*(AB')' * (A'B)' \\
 &= AB'C' + A'BC' + C*(A' + B) * (A + B') \\
 &= AB'C' + A'BC' + C*(A'A + A'B' + BA + BB') \\
 &= AB'C' + A'BC' + C*(0 + A'B' + AB + 0) \\
 &= AB'C' + A'BC' + C*(A'B' + AB) \\
 &= AB'C' + A'BC' + A'B'C + ABC \quad (3\text{-Way Light Control})
 \end{aligned}$$

$$\begin{aligned}
 Co &= (C*(A \wedge B)) \wedge (AB) \\
 &= C*(AB' + A'B) \wedge (AB) \\
 &= (AB'C + A'BC) \wedge (AB) \\
 &= (AB'C + A'BC)(AB)' + (AB)(AB'C + A'BC)' \\
 &= (AB'C + A'BC)(A' + B') + (AB)(AB'C)' * (A'BC)' \\
 &= (AB'CA' + AB'CB' + A'BCA' + A'BCB') + \\
 &\quad + (AB)(A'+B+C') * (A+B+C') \\
 &= (0+AB'C+A'BC+0) + \\
 &\quad + (AB)(0+A'B'+A'C' + AB+0+BC' + AC'+B'C'+C') \\
 &= AB'C + A'BC + (AB)(A'B'+A'C'+AB+BC'+AC'+B'C'+C') \\
 &= AB'C + A'BC + (0 + 0 + AB + ABC' + ABC' + 0 + ABC') \\
 &= AB'C + A'BC + AB + ABC' \\
 &= AB'C + A'BC + AB(C' + C) + ABC' \\
 &= AB'C + A'BC + ABC' + ABC + ABC' \\
 &= AB'C + A'BC + ABC' + ABC \\
 &= AB'C + A'BC + ABC' + ABC + ABC + ABC \\
 &= (AB'C + ABC) + (A'BC + ABC) + (ABC' + ABC) \\
 &= AC + BC + AB \quad (\text{Majority Gate})
 \end{aligned}$$