

---

# Designing Reliable Digital Systems


# Design **only** Synchronous Systems

---

- Asynchronous circuits may cause problems, especially when “glitch” prone combinational logic is used to clock or reset storage elements
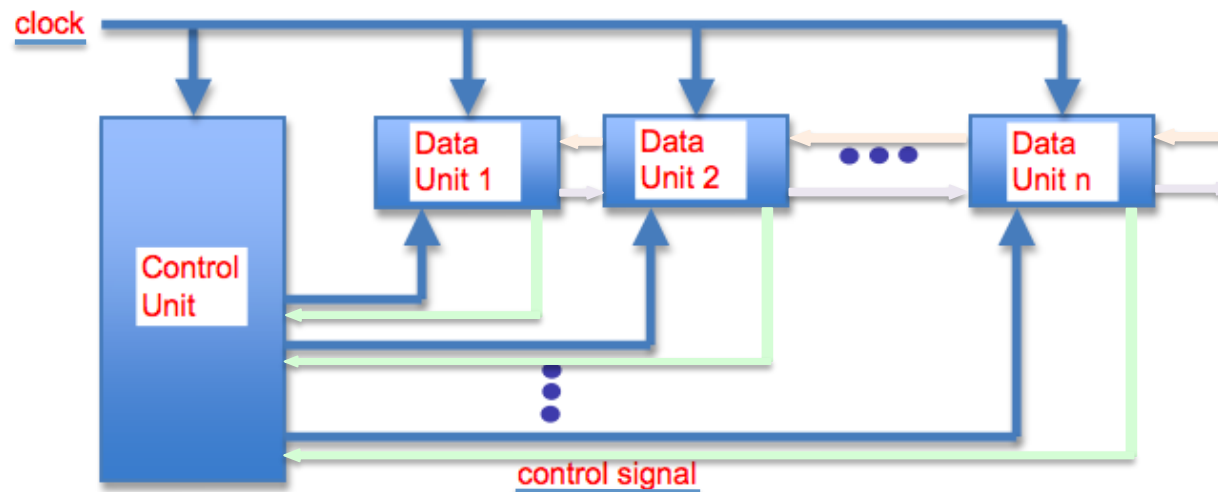
# Synchronous Systems

- All clock inputs to flip flops, registers, counters, and FSMs are driven directly from the system clock
- All state changes occur immediately following the active edge of the clock signal
- All switching transients (glitches), and switching noise occur between clock pulses and have no effect on system functionality



We can think of any digital system as composed of a control section and a data path section.

# No glitches in the control signals

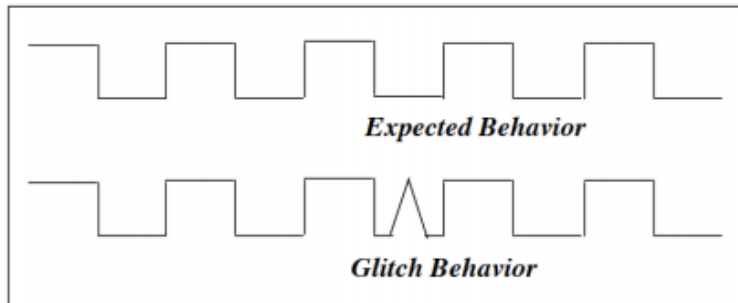


Figure 4.4  
Glitch Behavior

Some circuits, such as the 2-to-1 multiplexer in Figure 4.5, invariably cause glitches.

 


Figure 4.5  
Glitch Generating Mux

However:


 


Figure 4.7  
The Glitch Doesn't Matter Here

# Avoid gated clocks

 

*Figure 4.8*  
A Gated Clock

 


Fig. 4.9  
Control the Data instead of gating the clock