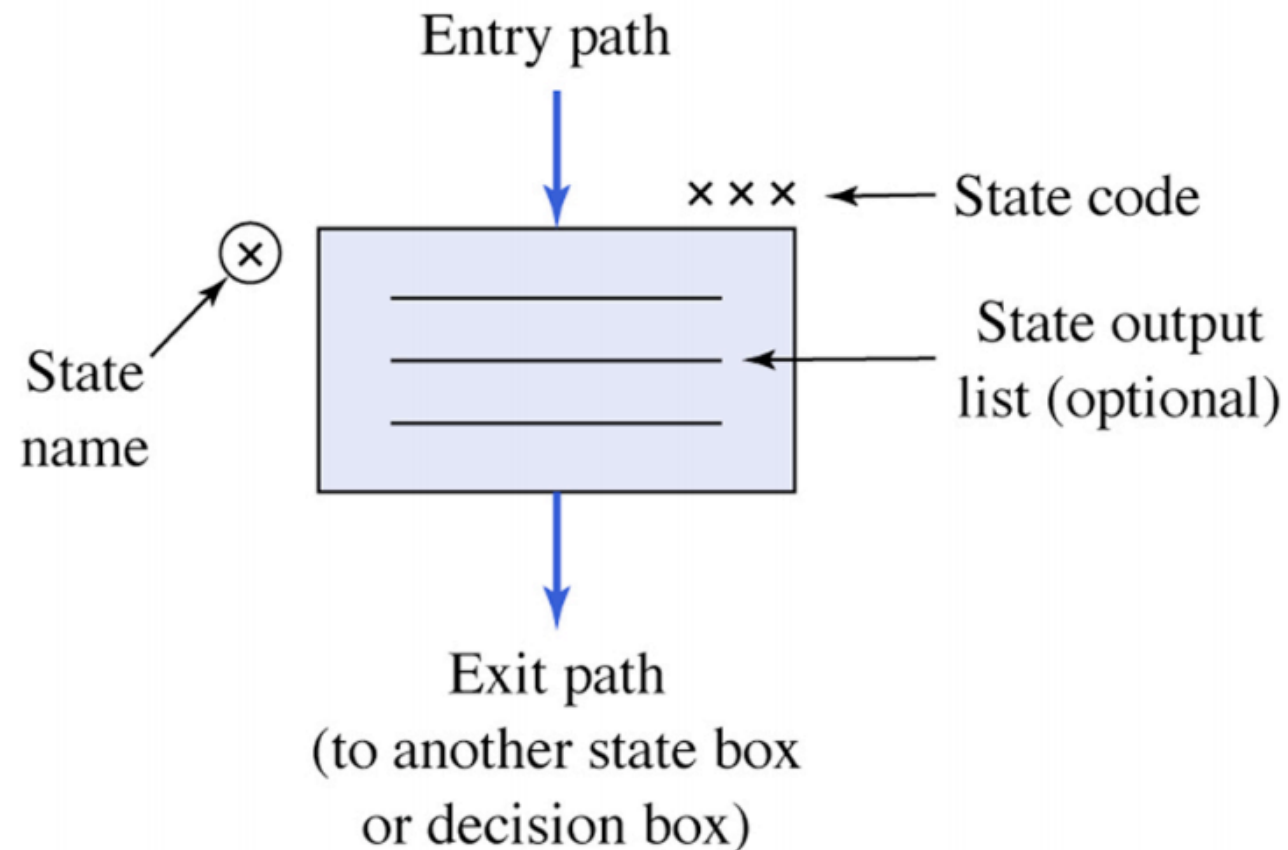


FSM Design using ASM Charts


Algorithmic State Machines

- ASMs have three types of building blocks:
 - State Box
 - Decision Box
 - Conditional Output Box

The State Box




The Decision Box

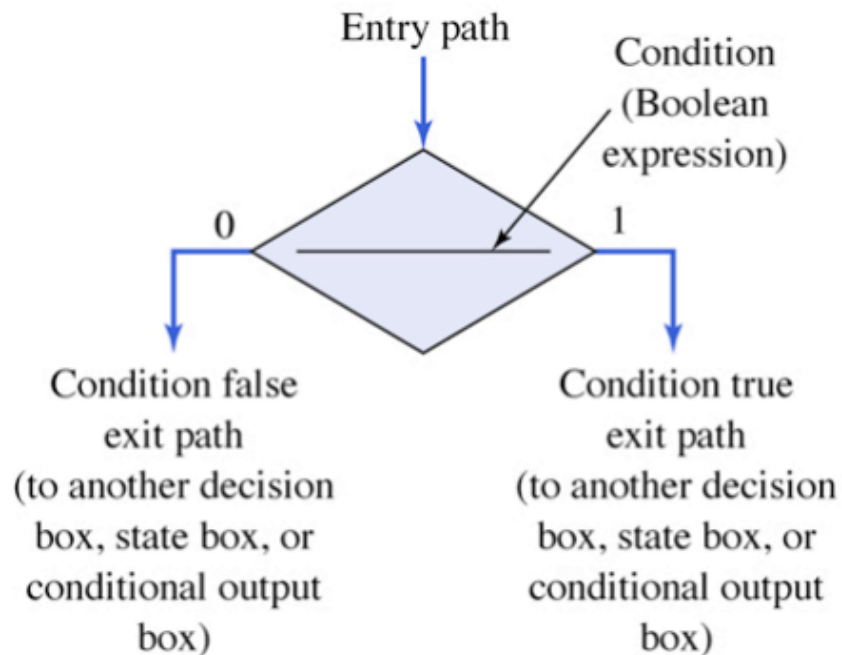

(a)


Symbol

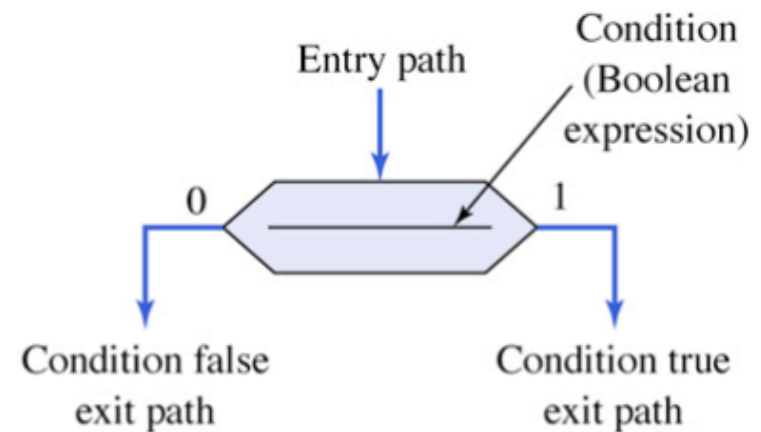


(b)

Alternate Symbol

The Conditional Output Box

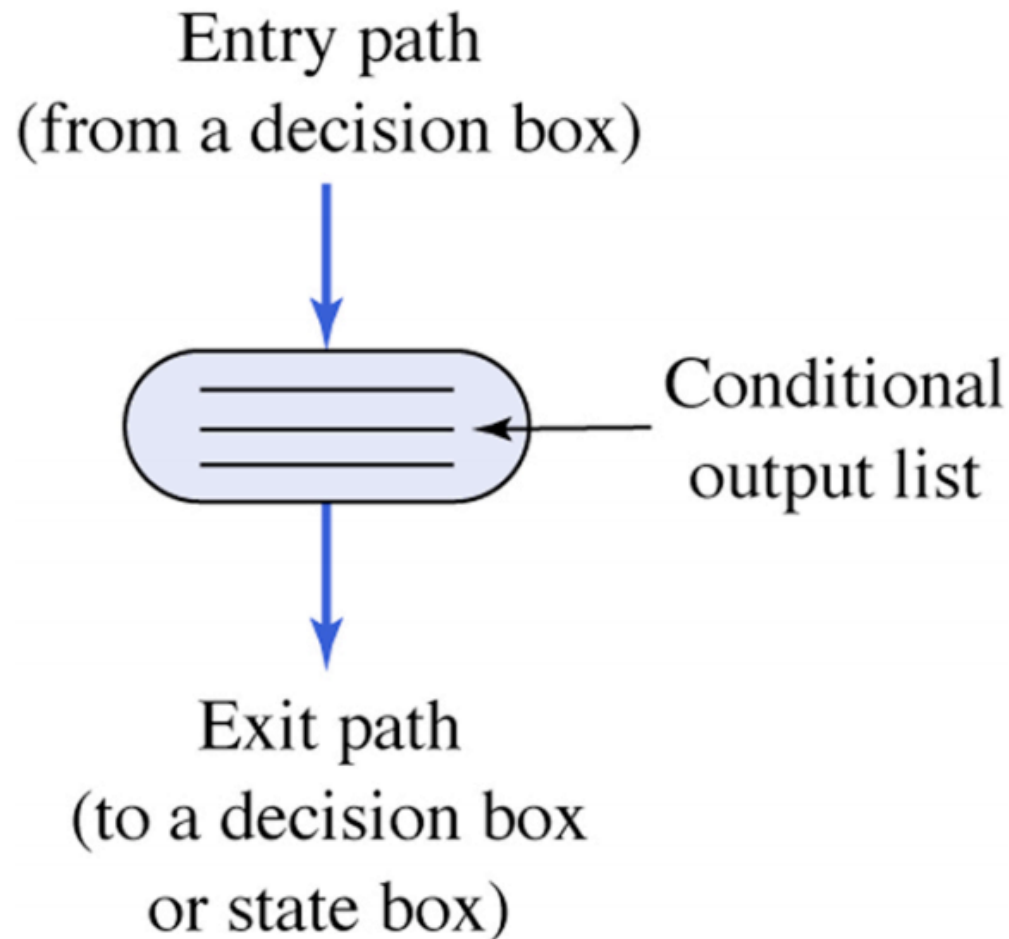


Example: ASM for a 3-bit binary counter

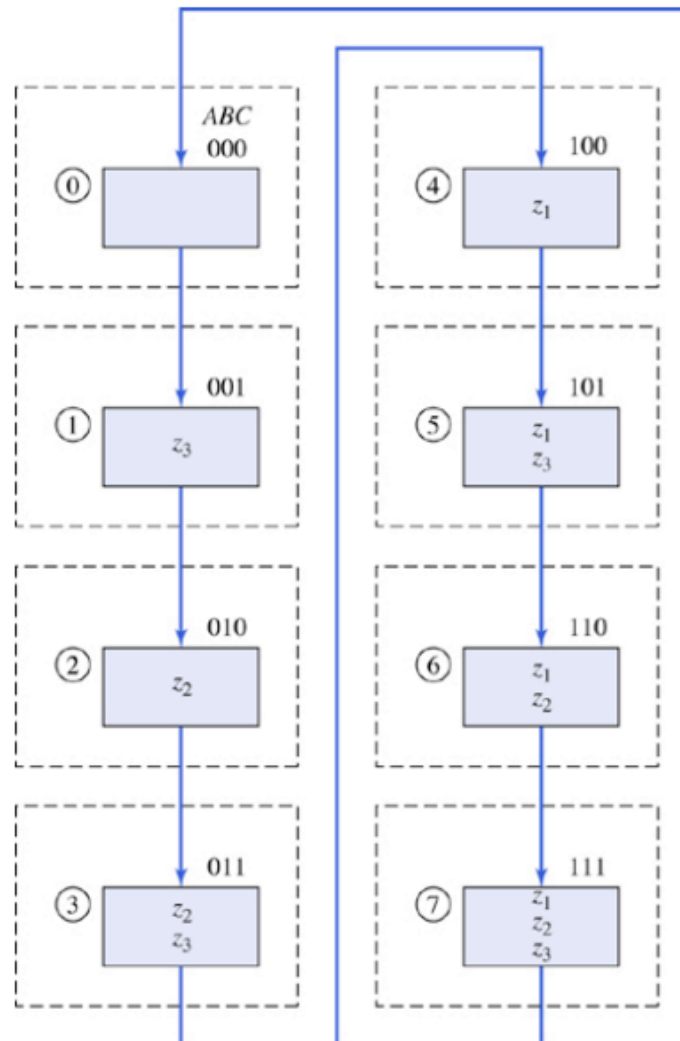

Example: ASM for a 3-bit binary up/down counter

Input I
controls
direction

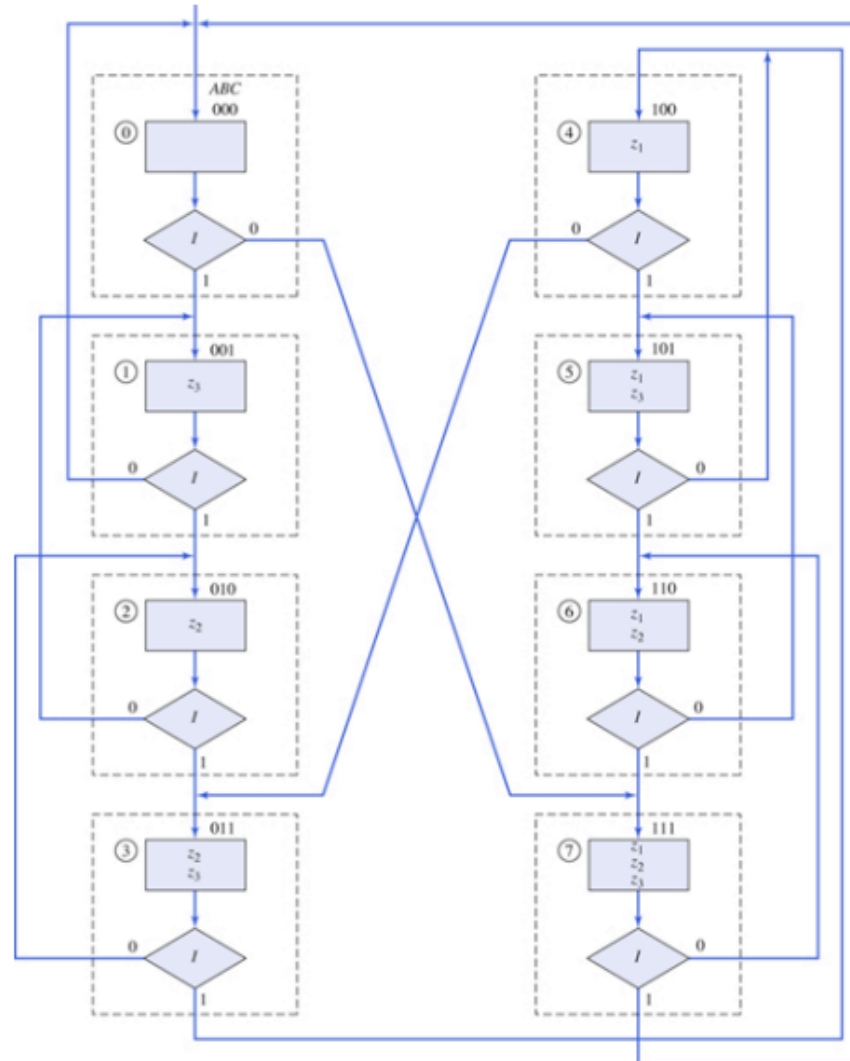

Example: ASM Chart

State/NextState Sequence:

A → A, B

B → A, C, D

C → C, D


D → E

E → A


3 state bits needed

Assign codes to each state

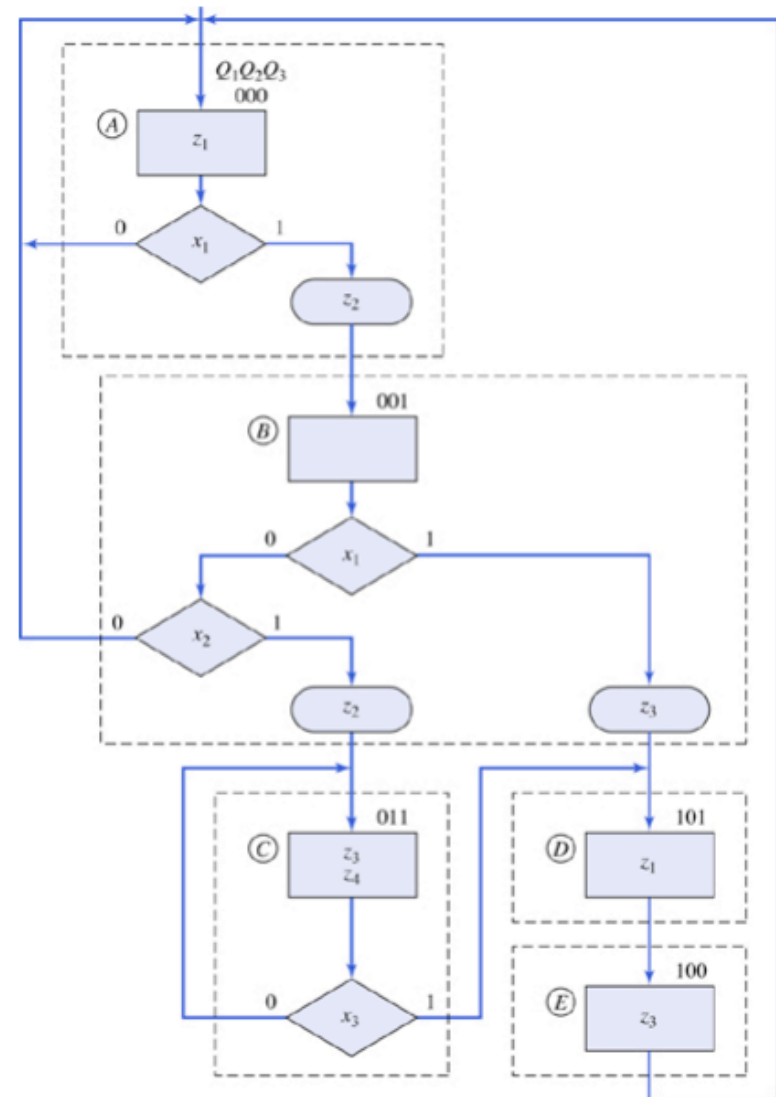(Possibly arrange adjacent states to be at Hamming distance of 1)





State Diagrams vs. ASM Charts

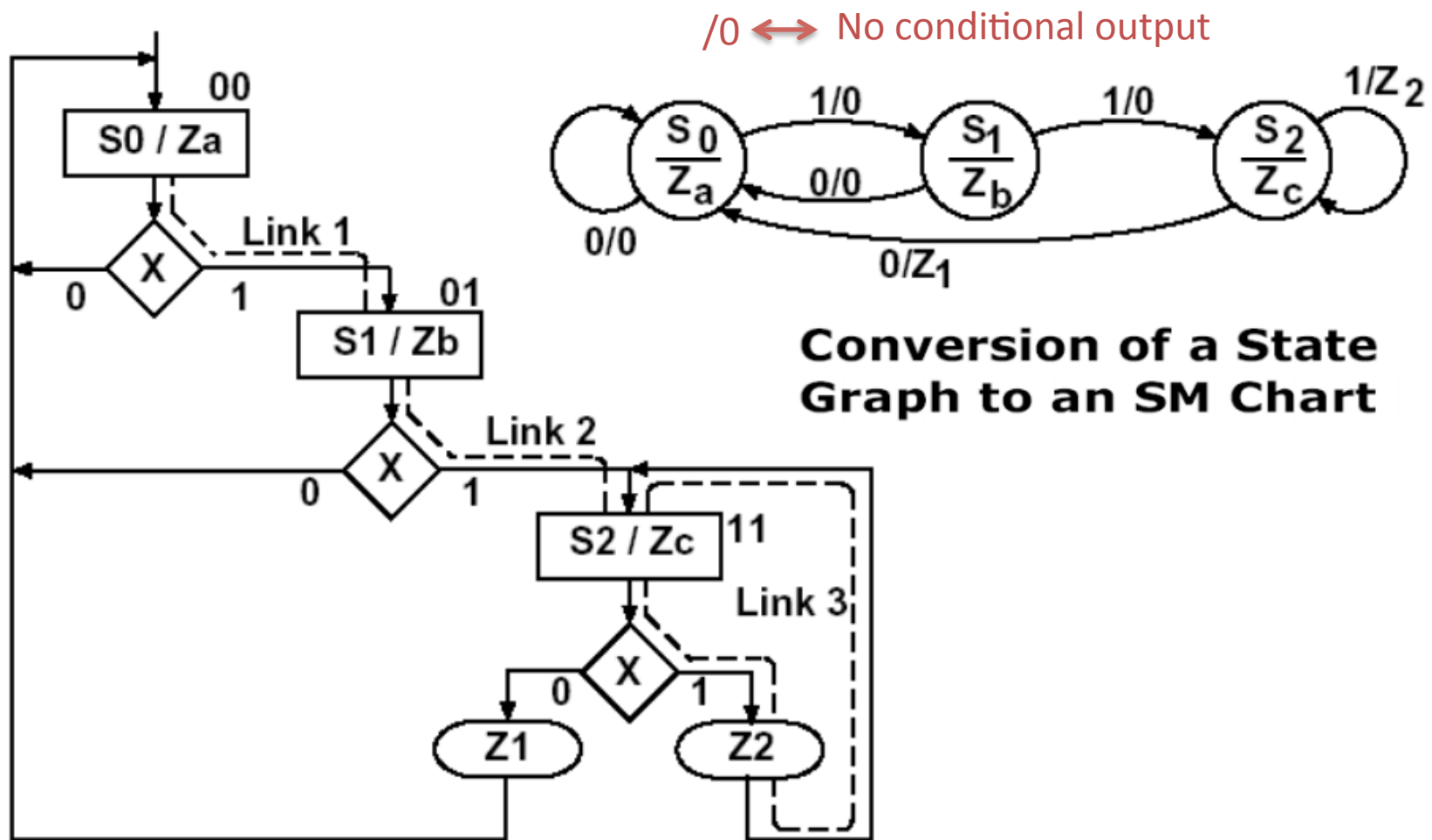

Mapping ASM blocks to Logic Elements

Example:

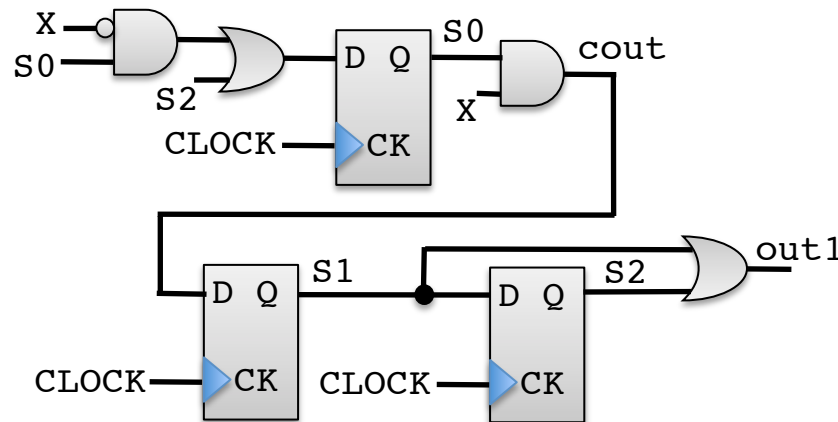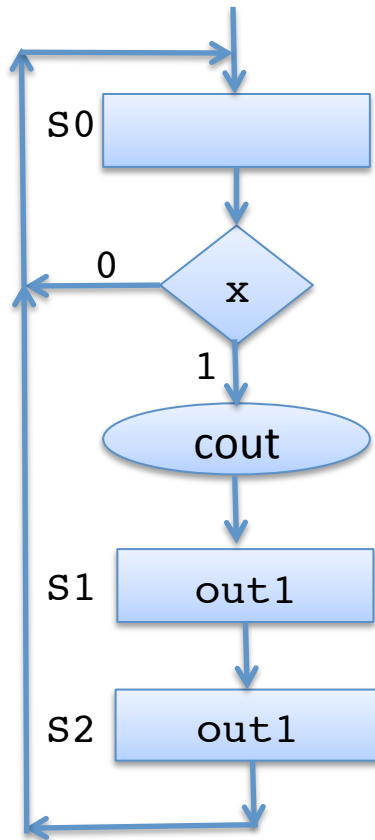


NOTE:
to make the mapping simpler the logic "synthesized" is sub-optimal (min # state FFs = \log_2 state boxes)

State boxes \rightarrow flip-flops
 Decision Boxes \rightarrow combinational logic gates
 Conditional Output Boxes \rightarrow combinational logic of state bits and inputs
 Non Conditional Outputs \rightarrow combinational logic of state bits

Moore

Mealy

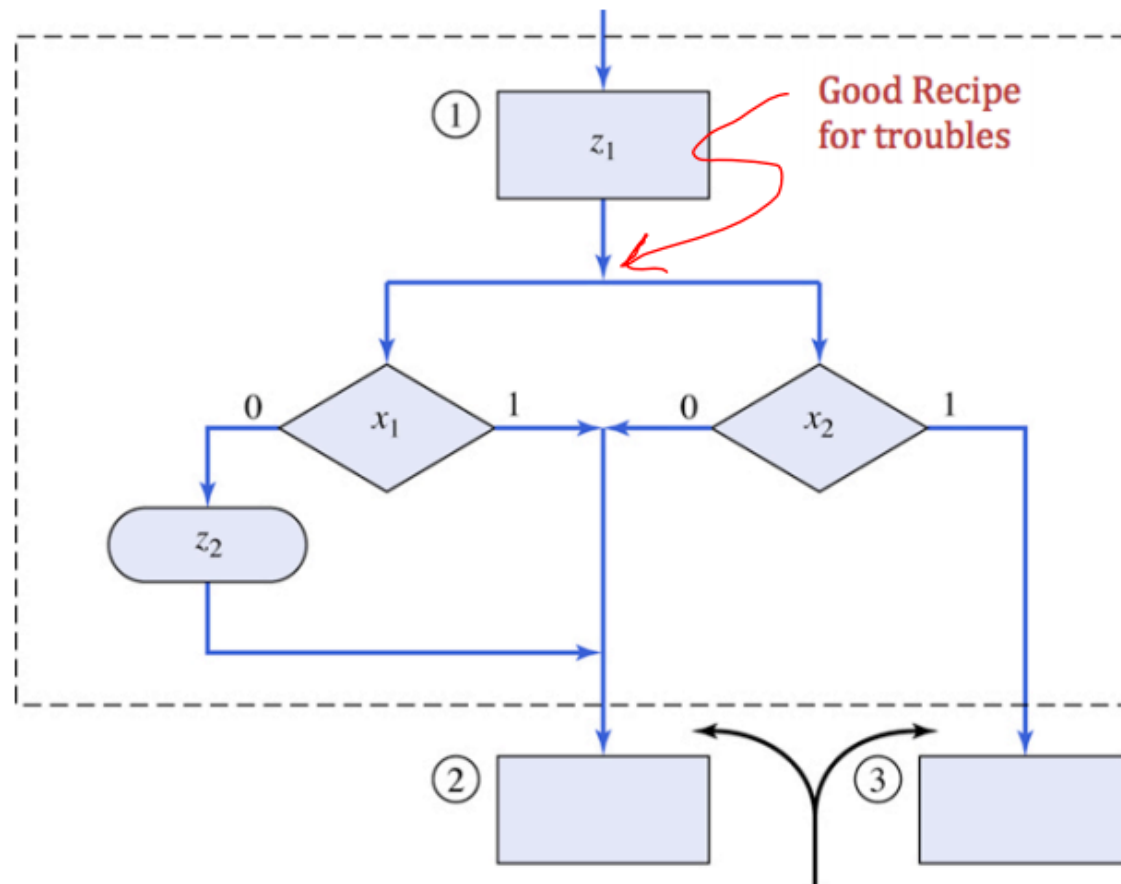Invalid ASM block having nonunique next states.




**Both exits selected when
both inputs are 1**


(i.e. when in state ① if $x_1 * x_2 = 1$ the next state is not unique)

Looping.

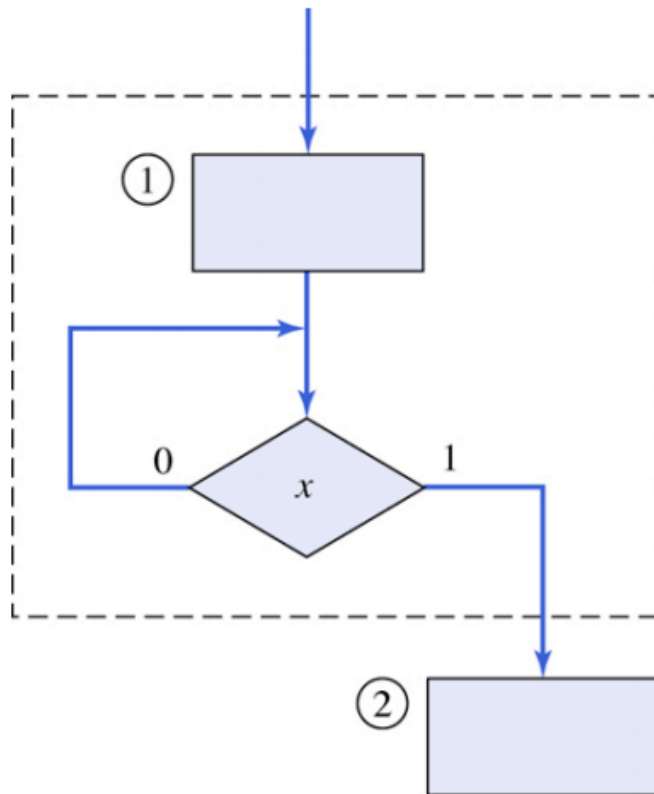Any closed loop must contain at least one state box ← **RULE**



(a) Incorrect.

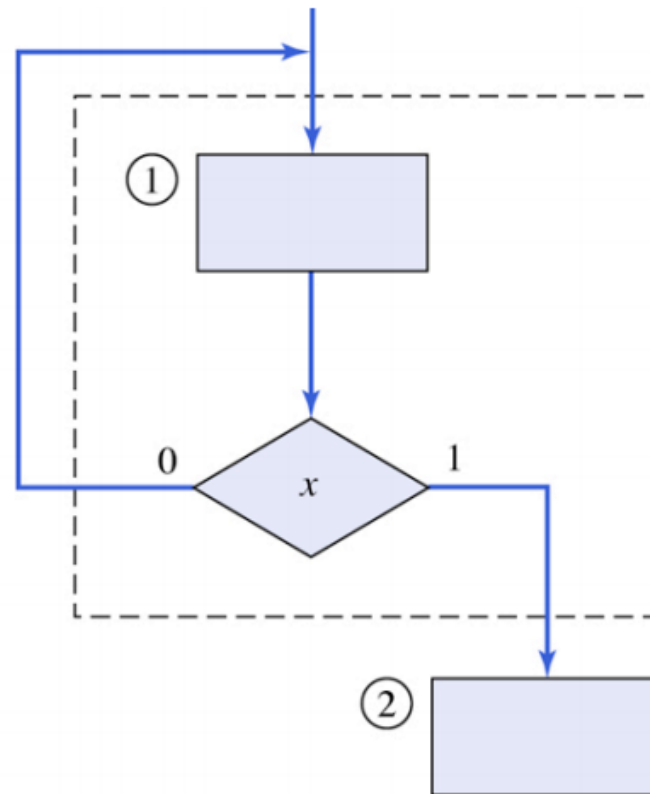


(b) Correct.

It forms a combinational feedback loop


Another Looping example

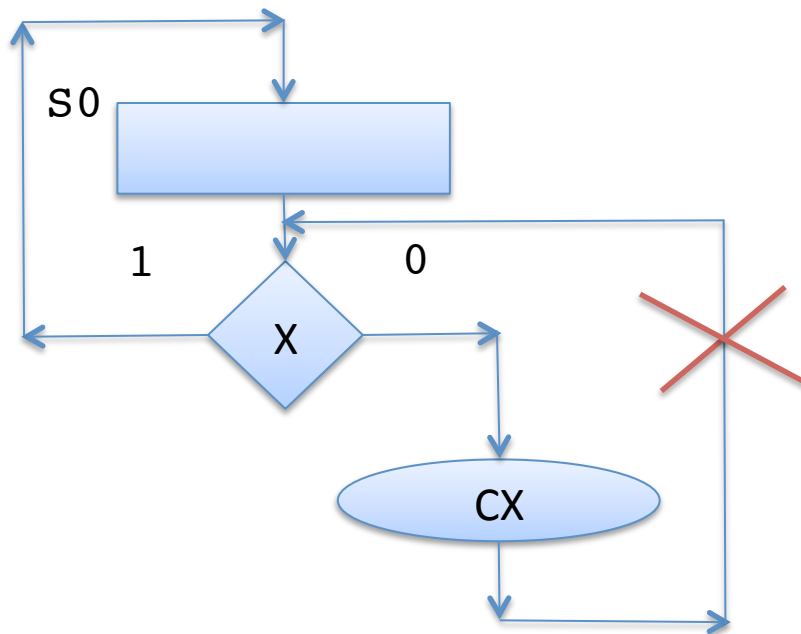Any closed loop must contain at least one state box ← **RULE**



(a) Incorrect.

It forms a combinational feedback loop

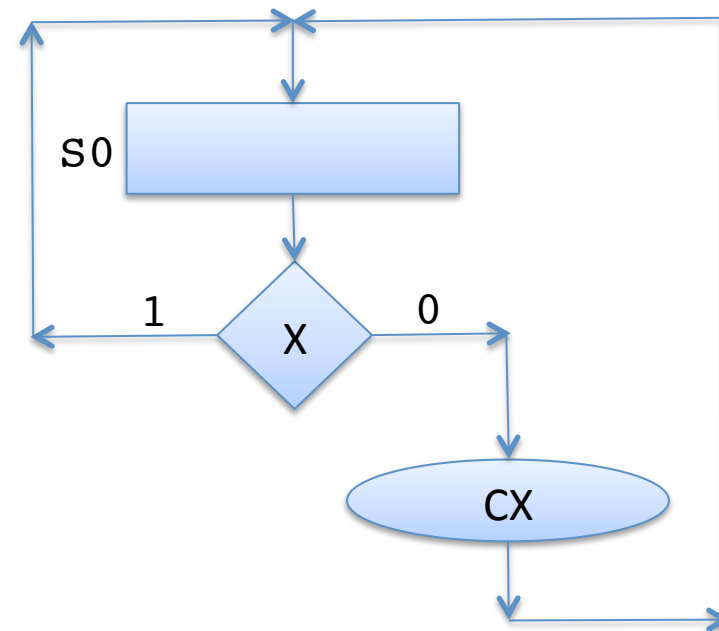

(b) Correct.

Linked State Machines

When a machine becomes large and complex is desirable to divide the machine up into several smaller machines that are linked together

