
VHDL: Packages and Components



Code Reuse

- Frequently used pieces of VHDL code can be written in the form of:
 - COMPONENTs
 - FUNCTIONs
 - PROCEDUREs
 - These “units” can be located in the MAIN code
- ↓
- ... However since the main purpose is to allow common pieces of code to be reused and shared it is more usual to place them in a PACKAGE which is finally compiled in a LIBRARY

Package



A LIBRARY may contains several packages

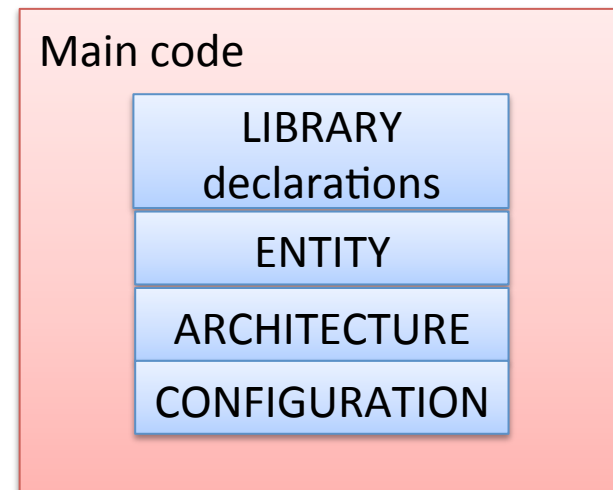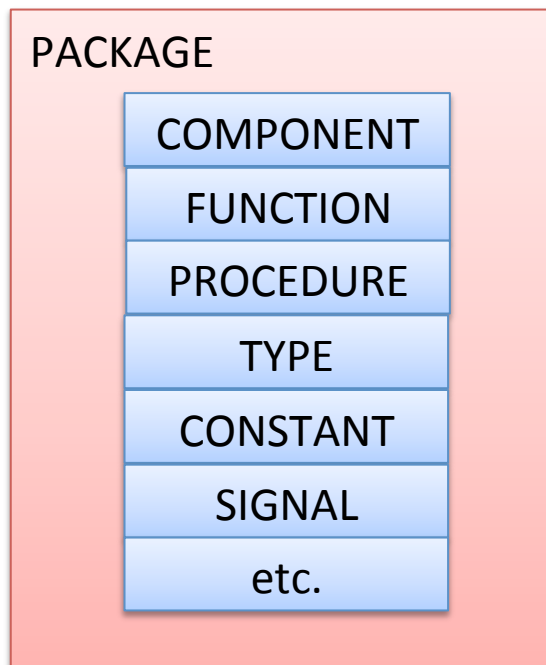

Package syntax

```
PACKAGE package_name IS  
    (declarations)  
END package_name;
```



Package Declaration
List

```
[PACKAGE BODY package_name IS  
    (FUNCTION and PROCEDURE descriptions)  
END package_name;]
```



Package Body =
descriptions

- The PACKAGE declaration list can contain:
 - TYPE
 - CONSTANT
 - SIGNAL
 - FUNCTION
 - PROCEDURE
 - etc.

See sections 4.7-4.9 of
IEEE Std 1076-2008 for
more details

PACKAGE: Example

```
1 -----
2 LIBRARY ieee;
3 USE ieee.std_logic_1164.all;
4 -----
5 PACKAGE my_package IS
6     TYPE state IS (st1, st2, st3, st4);
7     TYPE color IS (red, green, blue);
8     CONSTANT vec: STD_LOGIC_VECTOR(7 DOWNT0 0) := "11111111";
9 END my_package;
10 -----
```

To make use of the package
in the VHDL main code we
need:

1. Compile the VHDL package

the package become part of
the WORK LIBRARY

2. add a new USE clause
to the main code.

```
-----
LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE work.my_package.all;
-----
```

```
ENTITY...
...
ARCHITECTURE...
...
-----
```

PACKAGE: Example

```
1  -----
2  LIBRARY ieee;
3  USE ieee.std_logic_1164.all;
4  -----
5  PACKAGE my_package IS
6      TYPE state IS (st1, st2, st3, st4);
7      TYPE color IS (red, green, blue);
8      CONSTANT vec: STD_LOGIC_VECTOR(7 DOWNT0 0) := "11111111";
9      FUNCTION positive_edge(SIGNAL s: STD_LOGIC) RETURN BOOLEAN;
10 END my_package;
11 -----
12 PACKAGE BODY my_package IS
13     FUNCTION positive_edge(SIGNAL s: STD_LOGIC) RETURN BOOLEAN IS
14     BEGIN
15         RETURN (s'EVENT AND s='1');
16     END positive_edge;
17 END my_package;
18 -----
```

COMPONENT

- A COMPONENT is simply a piece of **conventional code** (= LIBRARY declarations + ENTITY + ARCHITECTURE)
- However, by declaring the code as a COMPONENT, it can be used within another circuit



Allowing the construction of **hierarchical** designs.

COMPONENT

- To use a component it must be:
 - Declared
 - Instantiated

COMPONENT declaration:

```
COMPONENT component_name IS
  PORT (
    port_name : signal_mode signal_type;
    port_name : signal_mode signal_type;
    ...);
END COMPONENT;
```



COMPONENT instantiation:

```
label: component_name PORT MAP (port_list);
```


Basic ways of declaring COMPONENTS

- Declaring COMPONENTS
 - in the **main code**
 - in a **package**

Main code

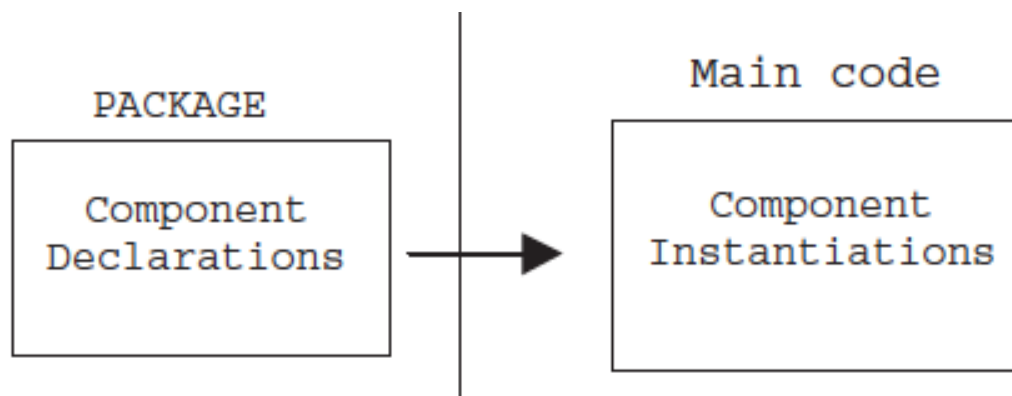 

Example:

Components declared in the main (1)

```
1 ----- -- File inverter.vhd: -----
2 LIBRARY ieee;
3 USE ieee.std_logic_1164.all;
4 -----
5 ENTITY inverter IS
6     PORT (a: IN STD_LOGIC; b: OUT STD_LOGIC);
7 END inverter;
8 -----
9 ARCHITECTURE inverter OF inverter IS
10 BEGIN
11     b <= NOT a;
12 END inverter;
13 -----
1 ----- -- File nand_2.vhd: -----
2 LIBRARY ieee;
3 USE ieee.std_logic_1164.all;
4 -----
5 ENTITY nand_2 IS
6     PORT (a, b: IN STD_LOGIC; c: OUT STD_LOGIC);
7 END nand_2;
8 -----
9 ARCHITECTURE nand_2 OF nand_2 IS
```


```
10 BEGIN
11     c <= NOT (a AND b);
12 END nand_2;
13 -----
1 ----- -- File nand_3.vhd: -----
2 LIBRARY ieee;
3 USE ieee.std_logic_1164.all;
4 -----
5 ENTITY nand_3 IS
6     PORT (a, b, c: IN STD_LOGIC; d: OUT STD_LOGIC);
7 END nand_3;
8 -----
9 ARCHITECTURE nand_3 OF nand_3 IS
10 BEGIN
11     d <= NOT (a AND b AND c);
12 END nand_3;
13 -----
```

Disclaimer:

The purpose of this example is to show VHDL syntax. It is NOT an endorsement to work at such a low level of abstraction !!!

Example:

Components declared in the main (2)

 

```

1  --- File project.vhd: -----
2  LIBRARY ieee;
3  USE ieee.std_logic_1164.all;
4  -----
5  ENTITY project IS
6      PORT (a, b, c, d: IN STD_LOGIC;
7            x, y: OUT STD_LOGIC);
8  END project;
9  -----
10 ARCHITECTURE structural OF project IS
11     -----
12     COMPONENT inverter IS
13         PORT (a: IN STD_LOGIC; b: OUT STD_LOGIC);
14     END COMPONENT;
15     -----
16     COMPONENT nand_2 IS
17         PORT (a, b: IN STD_LOGIC; c: OUT STD_LOGIC);
18     END COMPONENT;
19     -----
20     COMPONENT nand_3 IS
21         PORT (a, b, c: IN STD_LOGIC; d: OUT STD_LOGIC);
22     END COMPONENT;
23     -----
24     SIGNAL w: STD_LOGIC;
25 BEGIN
26     U1: inverter PORT MAP (b, w);
27     U2: nand_2 PORT MAP (a, b, x);
28     U3: nand_3 PORT MAP (w, c, d, y);
29 END structural;
30 -----

```

Example:

Components declared in a package (1)

```

1  ----- -- File inverter.vhd: -----
2  LIBRARY ieee;
3  USE ieee.std_logic_1164.all;
4  -----
5  ENTITY inverter IS
6      PORT (a: IN STD_LOGIC; b: OUT STD_LOGIC);
7  END inverter;
8  -----
9  ARCHITECTURE inverter OF inverter IS
10 BEGIN
11     b <= NOT a;
12 END inverter;
13 -----

1  ----- -- File nand_2.vhd: -----
2  LIBRARY ieee;
3  USE ieee.std_logic_1164.all;
4  -----
5  ENTITY nand_2 IS
6      PORT (a, b: IN STD_LOGIC; c: OUT STD_LOGIC);
7  END nand_2;
8  -----
9  ARCHITECTURE nand_2 OF nand_2 IS

```

```

10 BEGIN
11     c <= NOT (a AND b);
12 END nand_2;
13 -----

1  ----- -- File nand_3.vhd: -----
2  LIBRARY ieee;
3  USE ieee.std_logic_1164.all;
4  -----
5  ENTITY nand_3 IS
6      PORT (a, b, c: IN STD_LOGIC; d: OUT STD_LOGIC);
7  END nand_3;
8  -----
9  ARCHITECTURE nand_3 OF nand_3 IS
10 BEGIN
11     d <= NOT (a AND b AND c);
12 END nand_3;
13 -----

```

Disclaimer:

The purpose of this example is to show VHDL syntax. It is NOT an endorsement to work at such a low level of abstraction !!!

Example:

Components declared in a package (2)

```


1  ----- File my_components.vhd: -----
2  LIBRARY ieee;
3  USE ieee.std_logic_1164.all;
4  -----
5  PACKAGE my_components IS
6      ----- inverter: -----
7      COMPONENT inverter IS
8          PORT (a: IN STD_LOGIC; b: OUT STD_LOGIC);
9      END COMPONENT;
10     ----- 2-input nand: ---
11     COMPONENT nand_2 IS
12         PORT (a, b: IN STD_LOGIC; c: OUT STD_LOGIC);
13     END COMPONENT;
14     ----- 3-input nand: ---
15     COMPONENT nand_3 IS
16         PORT (a, b, c: IN STD_LOGIC; d: OUT STD_LOGIC);
17     END COMPONENT;
18     -----
19 END my_components;
20 -----

```

```

1  ----- File project.vhd: -----
2  LIBRARY ieee;
3  USE ieee.std_logic_1164.all;
4  USE work.my_components.all;
5  -----
6  ENTITY project IS
7      PORT ( a, b, c, d: IN STD_LOGIC;
8            x, y: OUT STD_LOGIC);
9  END project;
10 -----
11 ARCHITECTURE structural OF project IS
12     SIGNAL w: STD_LOGIC;
13 BEGIN
14     U1: inverter PORT MAP (b, w);
15     U2: nand_2 PORT MAP (a, b, x);
16     U3: nand_3 PORT MAP (w, c, d, y);
17 END structural;
18 -----

```

 

PORT MAPPING

- There are two ways to map the PORTS of a COMPONENT during its instantiation:
 - positional mapping
 - nominal (by name) mapping

```
COMPONENT inverter IS
  PORT (a: IN STD_LOGIC; b: OUT STD_LOGIC);
END COMPONENT;
...
U1: inverter PORT MAP (x, y); -- positional mapping
...
U2: inverter PORT MAP (x => a, y =>b); -- nominal mapping
```

- Ports can also be left unconnected (using the keyword OPEN)