

CPEN430 - Problem Set

Problem #1

- (a) What do the acronyms VHDL and VHSIC stand for?
- (b) How does a hardware description language like VHDL differ from an ordinary programming language?
- (c) What are the advantages of using a hardware description language as compared with schematic capture in the design process?

Problem #2

Given the concurrent VHDL statements:


```
B <= A and C after 3ns;  
C <= not B after 2ns;
```

- (a) Draw the circuit the statements represent.
- (b) Draw a timing diagram if initially $A = B = '0'$ and $C = '1'$, and A changes to $'1'$ at time 5 ns.

Problem #3

Write VHDL code for the following circuit. Assume that the gate delays are negligible.

 - (a) Use concurrent statements.
- (b) Use a process with sequential statements.



Problem #4

- (a) What device does the following VHDL code represent?

```
process(CLK, Clr, Set)  
begin  
  if Clr = '1' then Q <= '0';  
  elsif Set = '1' then Q <= '1';  
  elsif CLK'event and CLK = '0' then  
    Q <= D;  
  end if;  
end process;
```

- (b) What happens if $Clr = Set = '1'$ in the device in part (a)?
- (c) Write the complete code and synthesize it with Altera's Quartus. Attach a snapshot of the synthesized code (hint: use RTL view)
- (d) Write a testbench for the circuit and simulate it using Modelsim. Attach a snapshot of your simulation's waveforms. NOTE: The background must be white !!!