

- A voltage-dependent current source can form an amplifier along with a load resistor. Bipolar transistors are electronic devices that can operate as voltage-dependent current sources.
  - The bipolar transistor consists of two  $pn$  junctions and three terminals: base, emitter, and collector. The carriers flow from the emitter to the collector and are controlled by the base.
  - For proper operation, the base-emitter junction is forward-biased and the base-collector junction reverse-biased (forward active region). Carriers injected by the emitter into the base approach the edge of collector depletion region and are swept away by the high electric field.
- 
- The base terminal must provide a small flow of carriers, some of which go to the emitter and some others recombine in the base region. The ratio of collector current and base current is denoted by  $\beta$ .
  - In the forward active region, the bipolar transistor exhibits an exponential relationship between its collector current and base-emitter voltage.
  - In the forward active region, a bipolar transistor behaves as a constant current source.
  - The large-signal model of the bipolar transistor consists of an exponential voltage-dependent current source tied between the collector and emitter, and a diode (accounting for the base current) tied between the base and emitter.
  - The transconductance of a bipolar transistor is given by  $g_m = I_C/V_T$  and remains independent of the device dimensions.
  - The small-signal model of bipolar transistors consists of a linear voltage-dependent current source, a resistance tied between the base and emitter, and an output resistance.
  - If the base-collector junction is forward-biased, the bipolar transistor enters saturation and its performance degrades.
  - The small-signal models of  $nnp$  and  $pnp$  transistors are identical.