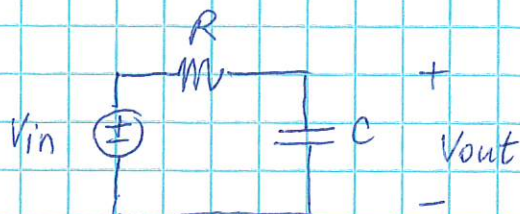


A Few simple circuits: examples

EE303 Handout

Example 1




$$V_{out} = 0 \text{ for } s \rightarrow \infty$$

$$\frac{V_{out}}{V_{in}} = \frac{1}{1 + sRC}$$

$$\omega_p = \frac{1}{RC}$$

1 POLE SYSTEM

Example 2

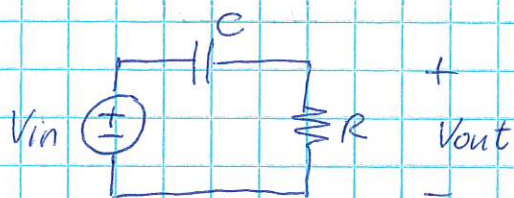


$$\omega_z = 0$$

$$\omega_p = \frac{1}{RC}$$

1 POLE
1 ZERO SYSTEM


$$\frac{V_{out}}{V_{in}} = \frac{R}{1/sC + R} = \frac{sRC}{1 + sRC}$$

For $s \rightarrow \infty$

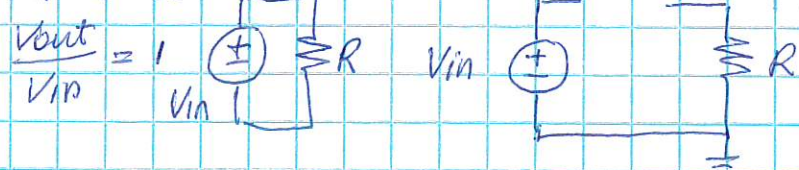

at $s \rightarrow 0$
 $V_{out} = 0$

Example 3


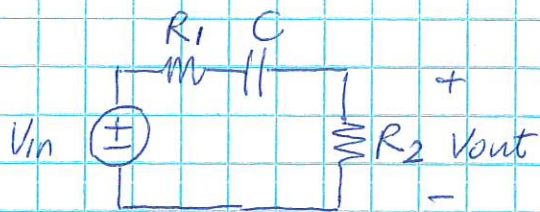


$$\omega_z = 0$$


$$\omega_p = \frac{1}{(R_1 + R_2)C}$$

$$\frac{V_{out}}{V_{in}} = \frac{R_2}{\frac{1}{sC} + R_1 + R_2} = \frac{sRC_2}{1 + sC(R_1 + R_2)}$$

1 POLE
1 ZERO SYSTEM

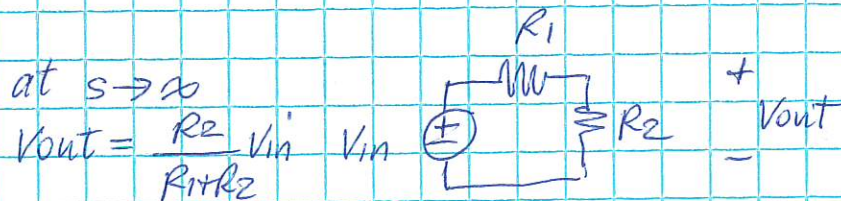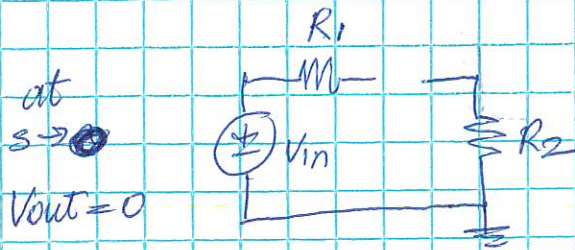


Example 4

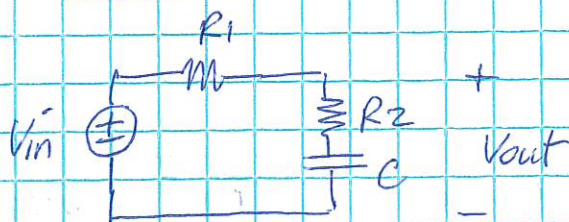


$$\omega_z = \frac{1}{R_2 C}$$

$$\omega_p = \frac{1}{(R_1 + R_2) C}$$
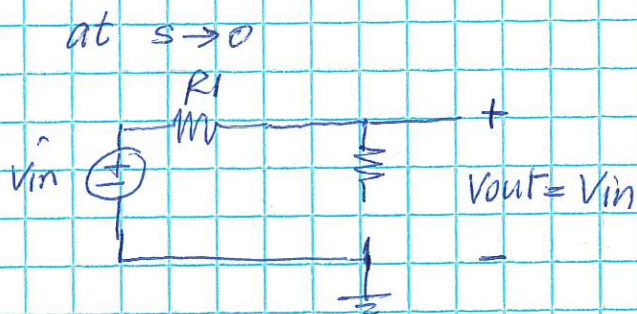
$$\frac{V_{out}}{V_{in}} = \frac{R_2 + \frac{1}{sC}}{R_1 + R_2 + \frac{1}{sC}} = \frac{1 + R_2 C \cdot s}{1 + s(R_1 + R_2) \cdot C}$$



1 POLE	SYSTEM
1 ZERO	

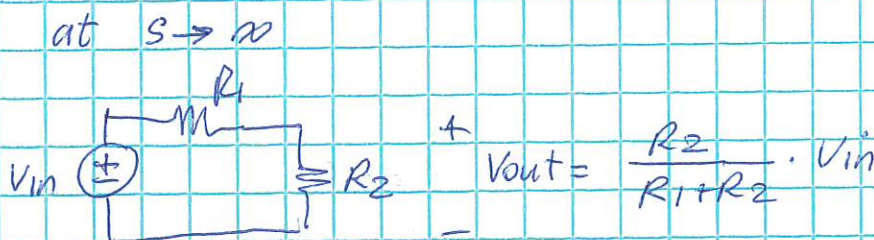


at $s = s_z \Rightarrow V_{out} = 0$

$$V_{out} = R_2 \cdot I + I \cdot \frac{1}{sC} = I \left(R_2 + \frac{1}{sC} \right) = 0 \Rightarrow$$

$$\Rightarrow R_2 + \frac{1}{s_z C} = 0 \Rightarrow s_z = - \frac{1}{R_2 C}$$


Example 5

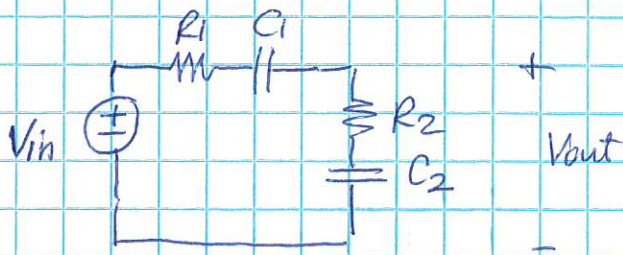

$$\omega_z = \frac{1}{R_2 C_2}$$

$$\omega_p = \frac{1}{\frac{C_1 C_2}{C_1 + C_2} (R_1 + R_2)}$$


at $s \rightarrow 0$

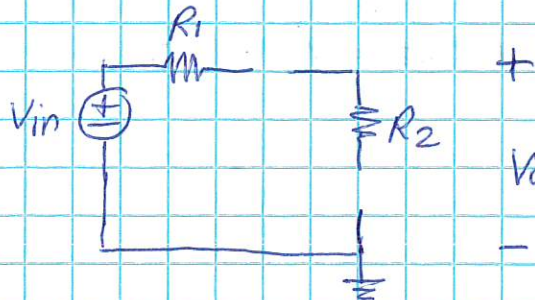

"C₁ does not contribute any zeros at the origin"


V_{out} ?? ← cannot tell!
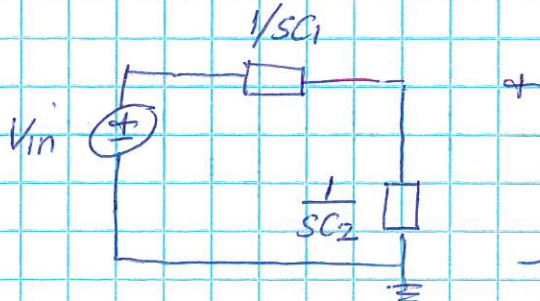
$$\frac{1}{sC_1} \gg R_1 \text{ and } \frac{1}{sC_2} \gg R_2$$



$$\begin{aligned} V_{out} &= \frac{(\frac{1}{sC_2}) V_{in}}{\frac{1}{sC_1} + \frac{1}{sC_2}} = \frac{(\frac{1}{sC_2}) V_{in}}{\frac{(C_1 + C_2)}{s \cdot C_1 \cdot C_2}} \\ &= \frac{C_1}{C_1 + C_2} \cdot V_{in} \end{aligned}$$


at $s \rightarrow \infty$

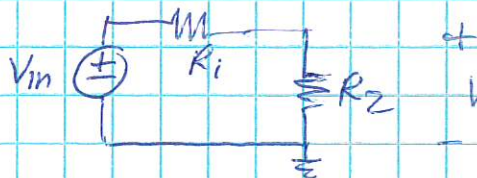

$$V_{out} = V_{in} \cdot \frac{R_2}{R_1 + R_2}$$

1 POLE
1 ZERO SYSTEM
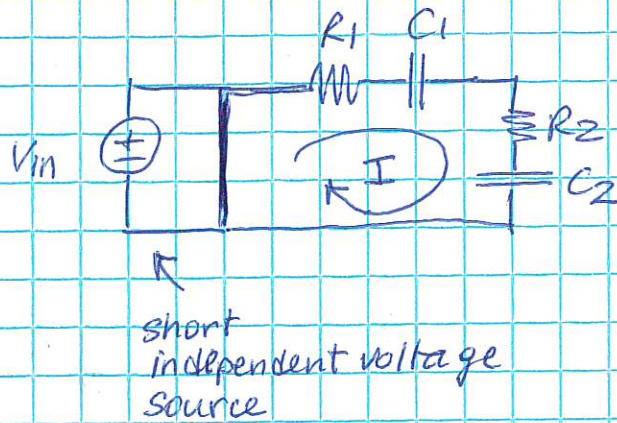
$$\omega_p = \frac{1}{\frac{C_1 + C_2}{C_1 C_2} (R_1 + R_2)}$$




C_1 and C_2
are in series :

$$C_T = \frac{C_1 C_2}{C_1 + C_2}$$

$$V_{R1} + V_{R2} = V_{C1} + V_{C2}$$

at $s = s_z \rightarrow V_{out} = 0$

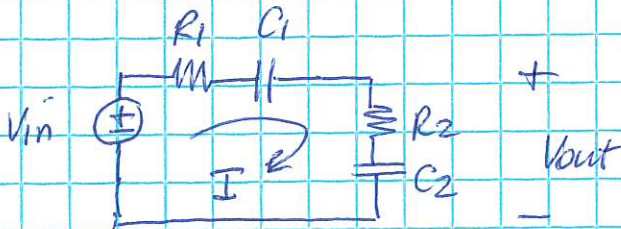

$$V_{out} = I \cdot R_2 + I \frac{1}{s C_2} = 0 \rightarrow I \left(R_2 + \frac{1}{s C_2} \right) = 0 \Rightarrow$$

$$s_z = - \frac{1}{R_2 C_2}$$