

# **Voltage Biasing Considerations (From the CS atom toward the differential pair atom)**

**Claudio Talarico, Gonzaga University**

# Voltage Biasing Considerations

---

- In addition to bias currents, building a complete analog circuit requires the generation of various bias voltages
- The CS stage is very sensitive to variations in its input bias voltage
  - In the majority of practical cases CS circuits are embedded in feedback networks that regulate the input bias voltage to the proper value, therefore absorbing process variations and mismatch effects (CMFB)
  - This complication typically does not exist for CG stages and CD stages


## Assumptions so far ...

---

- So far we have implicitly assumed
  - We have nearly ideal current and voltage sources available to set up the transistors' bias points
  - Transistor parameters and supply voltage do not vary
- As we move toward the practical implementation of transistor stages we must
  - Focus on biasing schemes that are insensitive to variations commonly seen in IC technology

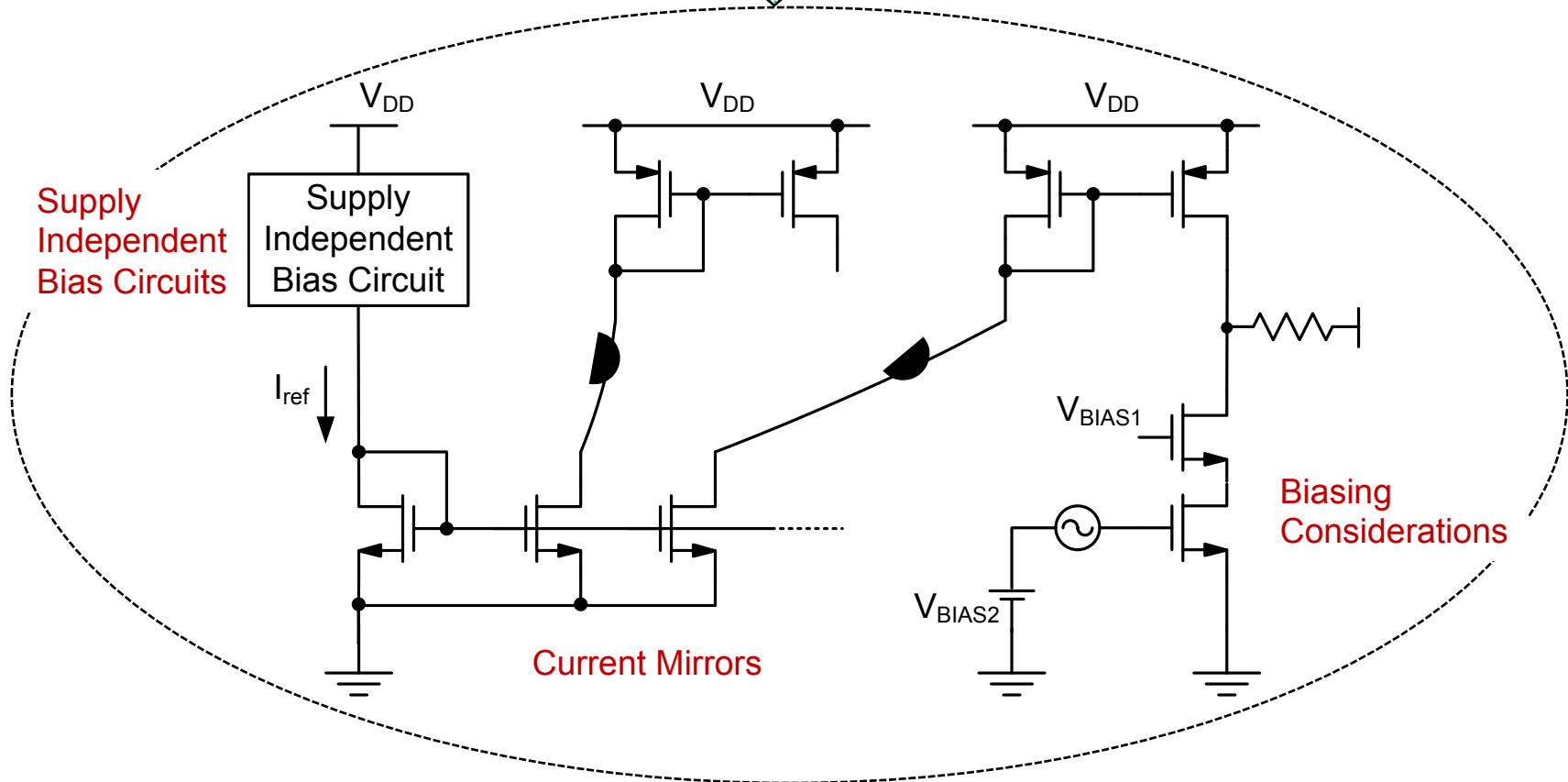
# Overview

Process, Voltage and Temperature Variations, Device mismatch


 
# Variations

- Process-Voltage-Temperature (PVT) variations
  - global variations → they affect the devices on a chip uniformly
- Device mismatches
  - Local variations → Typically follows Gaussian distribution
- Process Corners: slow, nominal fast



nominal =  $P, V, T$   
 slow =  $P_{slow}, V \downarrow, T \uparrow$   
 fast =  $P_{fast}, V \uparrow, T \downarrow$

$$\mu \propto T^{-3/2} \Leftrightarrow T \uparrow \rightarrow \mu \downarrow$$

[ more temperature = more collisions = less mobility ]

$$I \propto V^2 \Leftrightarrow V \uparrow \rightarrow I \uparrow$$


[ more voltage = more current = less time to charge/discharge caps. ]

# PVT Variations


---

- PROCESS
  - Variations between production lots
  - "Slow, Nominal and Fast" corners
- VOLTAGE
  - $V_{DD}$  is usually specified only within  $\pm 10\%$
  - E.g.  $V_{DD} = 4.5 \dots 5.5 \text{ V}$
- TEMPERATURE
  - Ambient temperature variations
  - $0 \dots 70^\circ\text{C}$  (or  $-40 \dots +125^\circ\text{C}$ )

# Process Variations

 

 Wafer made yesterday  
 All NMOS are “slow”  
 All PMOS are “nominal”  
 All R are nominal  
 All C are “fast”



Wafer made today  
 All NMOS are “fast”  
 All PMOS are “fast”  
 All R are nominal  
 All C are “slow”

Parameter	“Slow”	“Nominal”	“Fast”
$V_T$	0.65V	0.5V	0.35V
$\mu C_{ox}$ (NMOS)	40 $\mu A/V^2$	50 $\mu A/V^2$	60 $\mu A/V^2$
$\mu C_{ox}$ (PMOS)	20 $\mu A/V^2$	25 $\mu A/V^2$	30 $\mu A/V^2$
$R_{poly2}$	60 $\Omega/\square$	50 $\Omega/\square$	40 $\Omega/\square$
$R_{nwell}$	1.4 k $\Omega/\square$	1 k $\Omega/\square$	0.6 k $\Omega/\square$
$C_{poly-poly2}$	1.15 fF/ $\mu m^2$	1 fF/ $\mu m^2$	0.85 fF/ $\mu m^2$

# Temperature Coefficients

Mostly due to the dependence on T of the surface potential  $\Phi_s$

Parameter	Approximate TC
$V_T$	-1.2 mV/°C
$\mu C_{ox}$ (NMOS)	-0.33 %/°C
$\mu C_{ox}$ (PMOS)	-0.33 %/°C
$R_{poly2}$	+0.2 %/°C
$R_{nwell}$	+1 %/°C
$C_{poly-poly2}$	-30 ppm/°C

Mostly due to the dependence on T of mobility

← Temperature expands and contracts dielectric thickness

$$T \downarrow \Leftrightarrow t \downarrow \Leftrightarrow C \uparrow$$

\* The default temperature in Spice is 25 degrees Celsius

\* The following command sets the temperature to 100 degrees Celsius

```
.temp 100
```



## Aside: $V_T$ dependence on temperature

$$V_T = V_{T0} + \Delta V_T = V_{T0} + \gamma \left( \sqrt{\Phi_s - V_{BS}} - \sqrt{\Phi_s} \right)$$

- Both  $V_{T0}$  and  $\Delta V_T$  depends on  $\Phi_S$

$$V_{T0} \propto \Phi_S$$

$$\Phi_S = \frac{2KT}{q} \ln \frac{N_{bulk}}{n_i} = \text{Surface Potential} \equiv \text{PHI}$$

$$\gamma = \frac{\sqrt{2q\epsilon_S N_{bulk}}}{\epsilon_{ox}/t_{ox}} = \text{Body Effect Coefficient} \equiv \text{GAMMA}$$

The higher the doping  $N_{bulk}$  the more voltage is required to produce an inversion layer:  $N_{bulk}$  goes up  $\rightarrow V_T$  goes up  
 If  $C_{ox} = \epsilon_{ox}/t_{ox}$  is higher (=  $t_{ox}$  thinner) the less voltage is required to produce an inversion layer ( $Q=CV$ ):  $C_{ox}$  goes up  $\rightarrow V_T$  goes down

- The dependence on temperature of  $n_i$  is stronger than the linear dependence in the thermal voltage term ( $KT/q$ )

– As a result:  $for T \uparrow \Leftrightarrow V_T \downarrow$

Source: Muller and Kamins


 


FIGURE 2.10 The intrinsic carrier density  $n_i$  in silicon between 300 and 1200°C [10].

# Voltage Biasing for a CS stage

- CS stage revisited

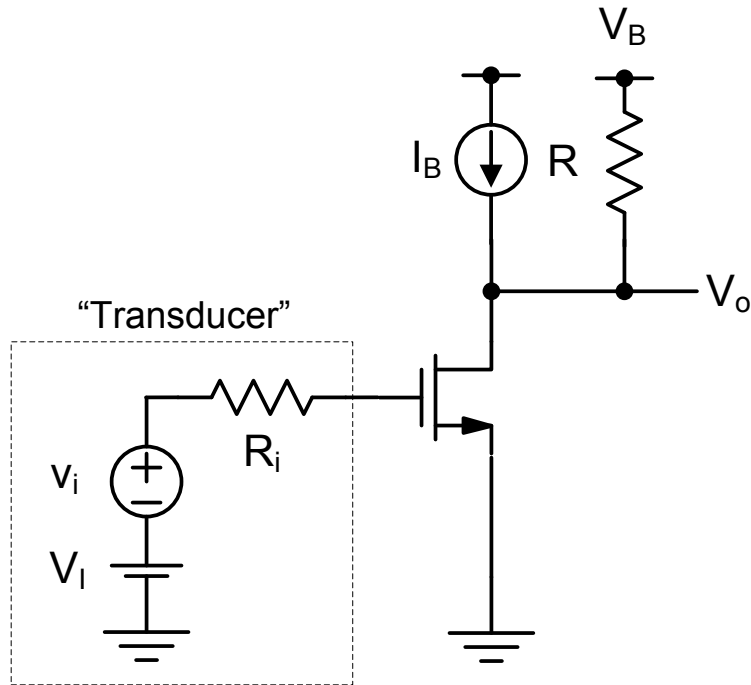

Example:

$$V_B = 2.5V$$

$$V_1 = 1.394V$$

$$I_B = 500\mu A$$

$$W/L = 20\mu m/1\mu m$$

$$R = 5k\Omega$$

$$R_i = 50k\Omega$$

- Nominal conditions:  $KP=50\mu A/V^2$ ,  $V_{T0}= 0.5V$ ,  $TEMP=25^\circ C$
- Fast conditions:  $KP=60\mu A/V^2$ ,  $V_{T0}= 0.35V$ ,  $TEMP=-20^\circ C$

# HSPICE .OP output

---

```
*** .op output (nominal)
element 0:mn1
region    Saturati
  id      499.6020u
  vgs     1.3940
  vds     2.5020
  vth     500.0000m
  vod     894.0000m
  beta    1.2502m
  gm      1.1177m
  gds     39.9618u
...
```

```
*** .op output (fast, -20degC)
element 0:mn1
region    Linear
  id      817.8268u
  vgs     1.3940
  vds     910.8661m
  vth     402.0530m
  vod     991.9470m
  beta    1.6735m
  gm      1.5243m
  gds     210.6442u
...
```

Ouch !!

# The Problem with This Circuit

---

- Process and temperature variations cause large changes in  $V_T$  and mobility ( $\mu$ )
  - But  $V_I$  is kept constant, causing large changes in  $I_D$ , forcing the device into the triode region
- First cut idea
  - Use another MOSFET to “compute”  $V_I$  such that  $I_D$  stays roughly constant and tracks process and temperature
  - Note that the same “trick” is used in a current mirror



# HSPICE .OP Output

---


```
*** .op output (nominal)
element    0:m1      0:m2
region     Saturati  Saturati
id         538.2075u 500.0000u
vgs        1.4351   1.4351
vds        2.3090   1.4351
vth        500.0000m 500.0000m
beta       1.2309m   1.1435m
gm         1.1511m   1.0694m
gds        43.7248u   43.7248u
...
```

```
*** .op output (fast, -20degC)
element    0:m1      0:m2
region     Saturati  Saturati
id         548.8001u 500.0000u
vgs        1.1662   1.1662
vds        2.2560   1.1662
vth        402.0530m 402.0530m
beta       1.8798m   1.7127m
gm         1.4364m   1.3087m
gds        44.7781u   44.7781u
...
```


Great!
 
# Remaining Issue with first cut solution

- What if we do not have access to the “-” node of the input transducer?
  - Consider e.g. a sensor or another amplifier that produces a ground referenced signal with “arbitrary” quiescent voltage


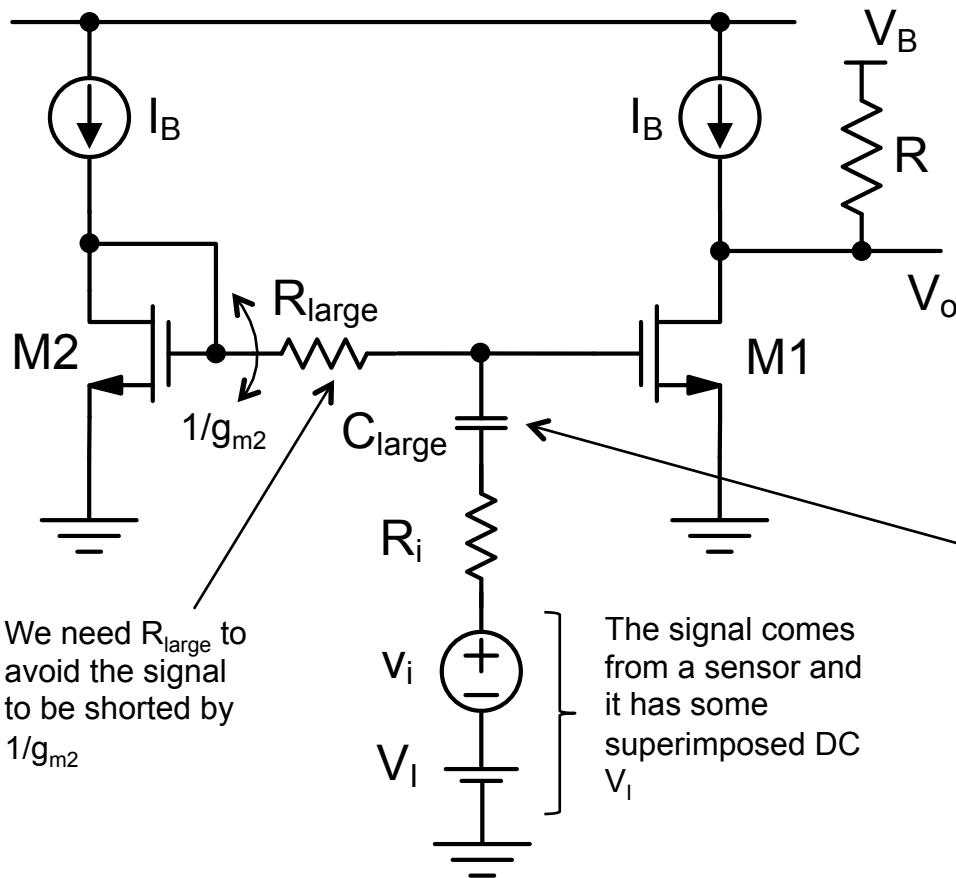
# Second Attempt: Replica Biasing with AC Coupling



We need  $R_{large}$  to avoid the signal to be shorted by  $1/g_{m2}$

The signal comes from a sensor and it has some superimposed DC  $V_1$

## Issues


- Don't like  $R_{large}$ ,  $C_{large}$  in integrated circuits
- $R_i$  and  $R_{large}(+1/g_{m2})$  form a resistive divider
  - Problematic if  $R_i$  is large
- $C_{large}$  keeps the DC  $V_1$  from reaching the gate of M1
- it also makes possible to do not waste DC power on  $R_i$




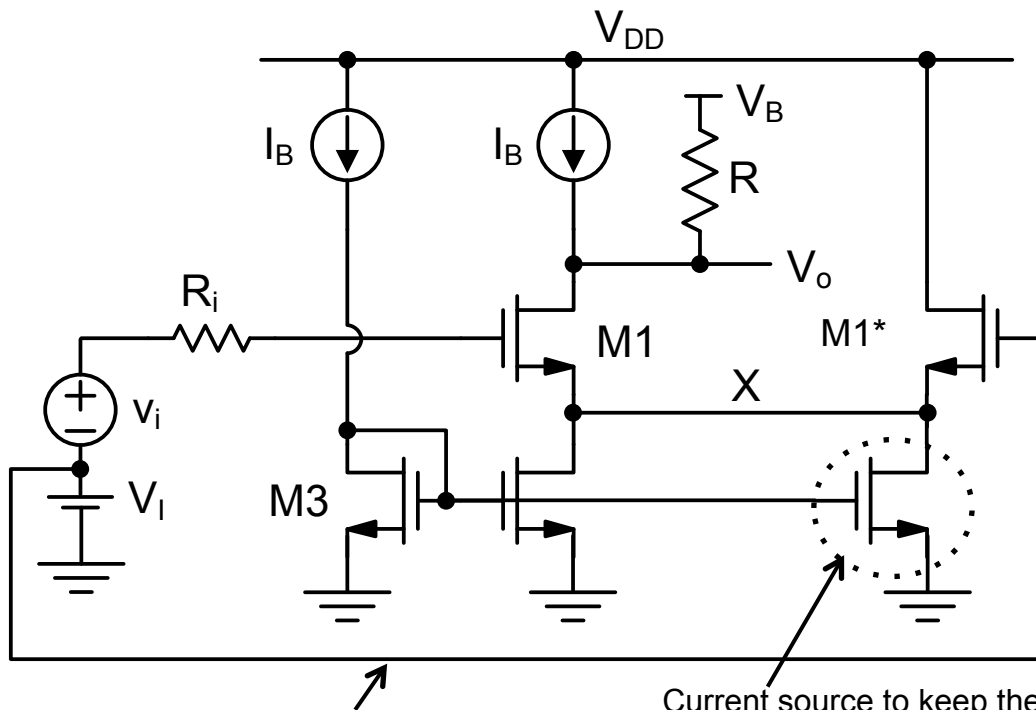
# Yet Another Idea (A really good one): Forth Attempt

- Instead of AC shorting node X with a cap. why not use another MOSFET (M1\*) to provide low impedance at node X.
- As before, circuit is insensitive to changes in  $V_i$  and transistor  $V_T$ 
  - No large caps or resistors needed to accomplish this!





“recycle”  $V_i$  to bias the gate of M1\*

Current source to keep the DC current through M1\* roughly constant

The price is we lost  $0.5g_m$   
(Not too bad given the alternative: a circuit that doesn't work !)

$$A_v \cong -\frac{g_{m1}}{2} R$$

ac equivalent

  

$$M_1 = M_1^*$$

$$g_{m1'} = g_{m1} + g_{mb1}$$


# Comments on the “Improved CS” Solution

---


- The structure we arrived to “improve” the CS is so good that it has its own name: ***Differential Pair***
- The Differential Pair main feature is to evaluate the difference between two voltages
  - In our “improved CS” the two voltages are  $V_1$  and  $V_1+v_i$
  - To first order changes in  $V_1$  and process and temperature do not affect the output voltage

# Differential Pair vs. “Improved CS” stage

Differential Pair

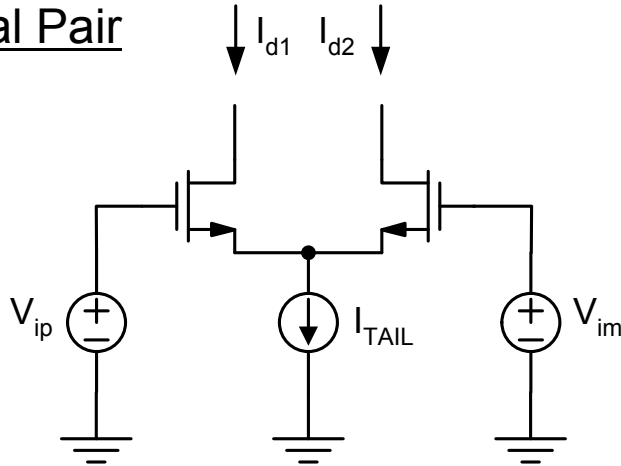

“Improved CS”

 

■ Differences:


- We do not necessarily need the second bottom transistor
- $$I_{M1} = I_{M1^*} = I_{TAIL} / 2$$
- We usually put signal both at the gate of M1 and at the gate of M1\*

# Voltage Biasing for a CG stage (1)

- Compared to a CS stage, setting up the bias voltage for the gate of a CG stage is usually less intricate

## Example 1 – Cascode Stage

Source: B. Murmann Textbook p. 137

 


$$m = 5 \rightarrow V_{DS1} = 1.45 V_{OV}$$

## Voltage Biasing for a CG stage (2)

### Example 2 – CG stage interfacing a Photodiode

Source: B. Murmann Textbook p. 137

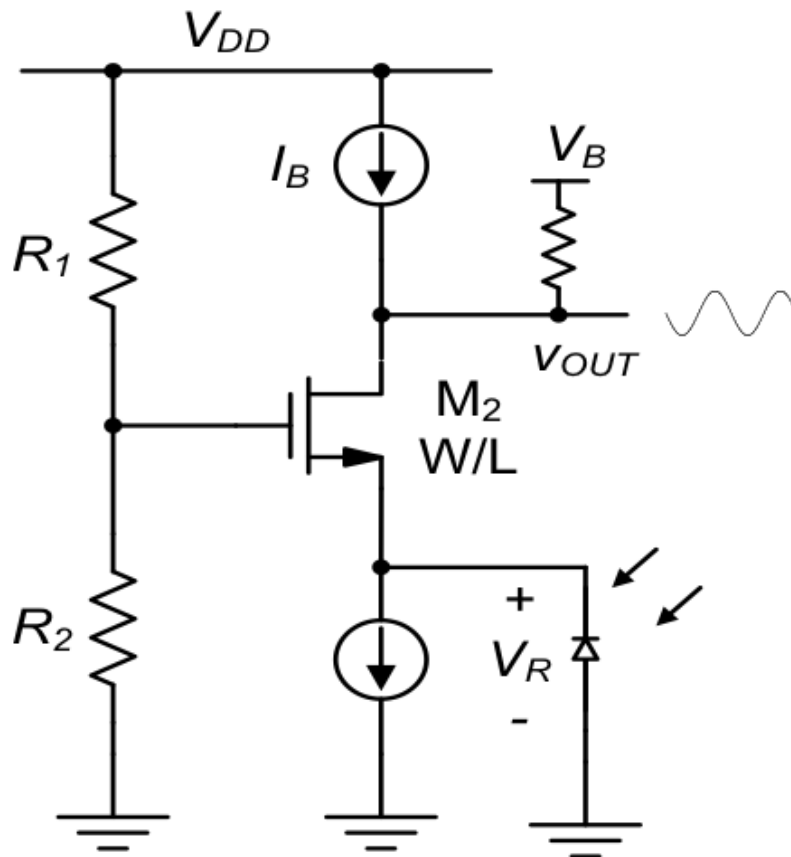


- In this circuit the output swing is usually not very large, and thus the bias voltage  $V_{G2}$  is not tightly constrained by voltage swing requirements.
- Typically,  $V_{G2}$  is set such that the photodiode is biased at a suitable reverse bias. This is accomplished by sizing  $R_1$  and  $R_2$  properly.

$R_1$  and  $R_2$  are AC shorted ( $G_2$  is at AC ground)
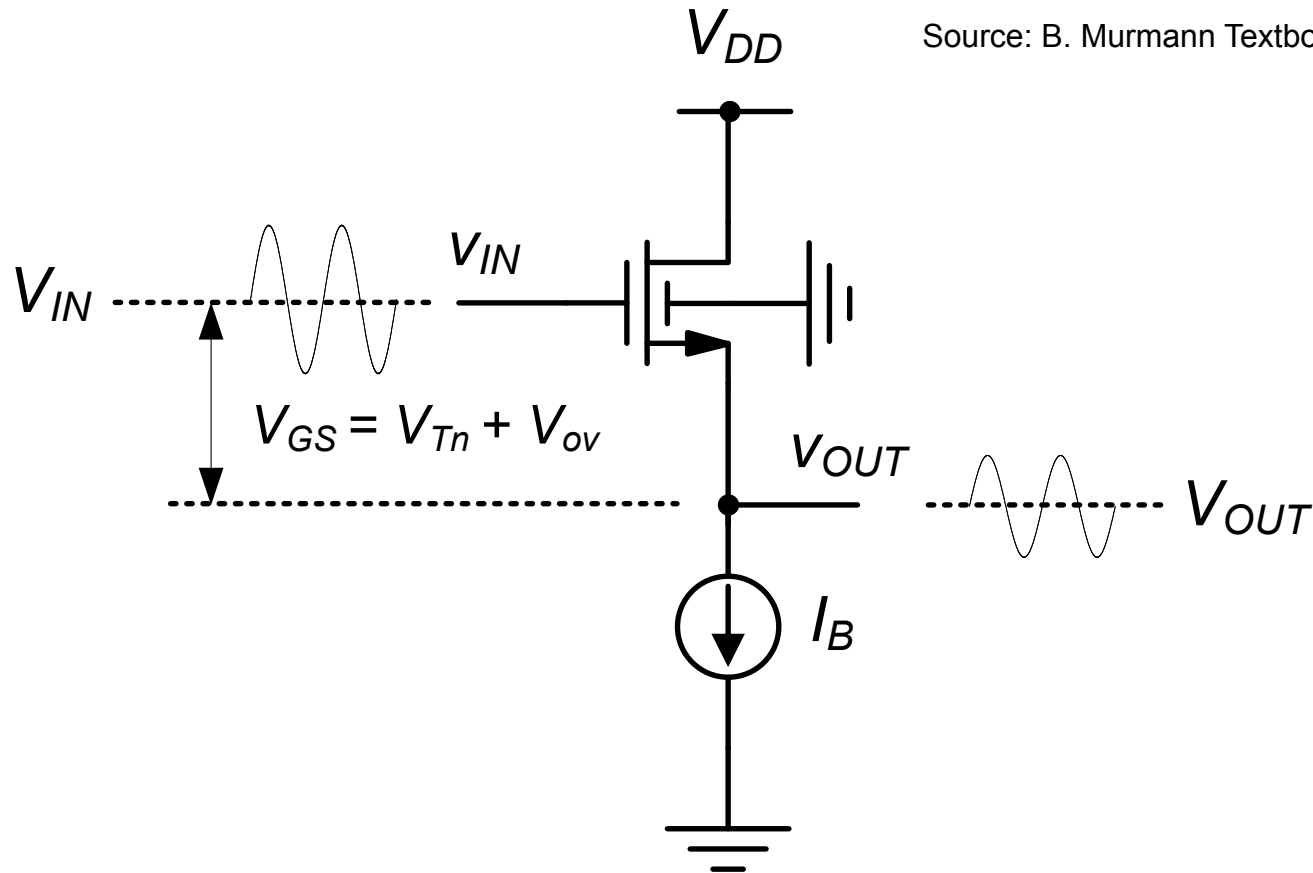
# Voltage Biasing for a CD stage (1)


- In a CD stage the input and output voltage bias are directly coupled
- Proper voltage biasing in a CD stage boils down to making sure that the input and output bias voltages are compatible with the circuits that are connecting to.



## Voltage Biasing for a CD stage (2)

- In some application, the shift between the input and output bias is undesired. In this case a p-MOS CD stage can be used to provide a shift in the opposite direction
- $M_1$  can be sized such that the bias voltages  $V_{IN}$  and  $V_{OUT}$  are approximately the same

Source: B. Murmann Textbook p. 139

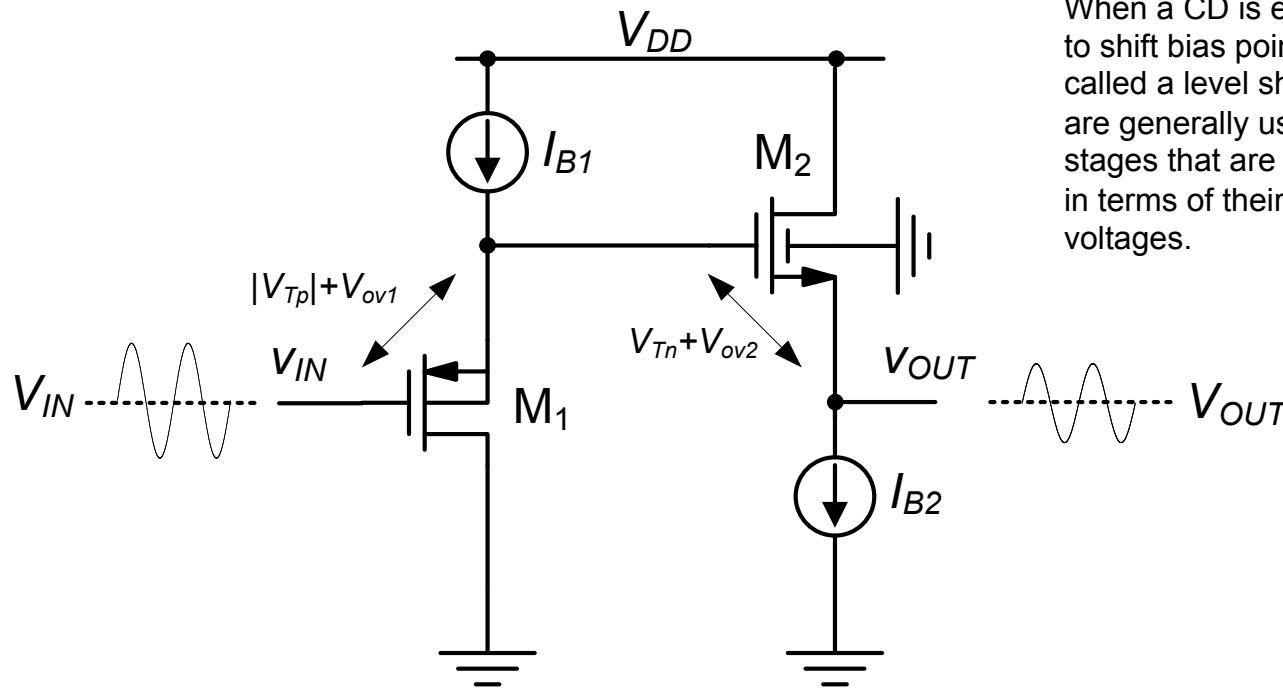


When a CD is employed primarily to shift bias points the circuit is called a level shifter. Level shifters are generally useful to interface two stages that are otherwise incompatible in terms of their bias input/output voltages.


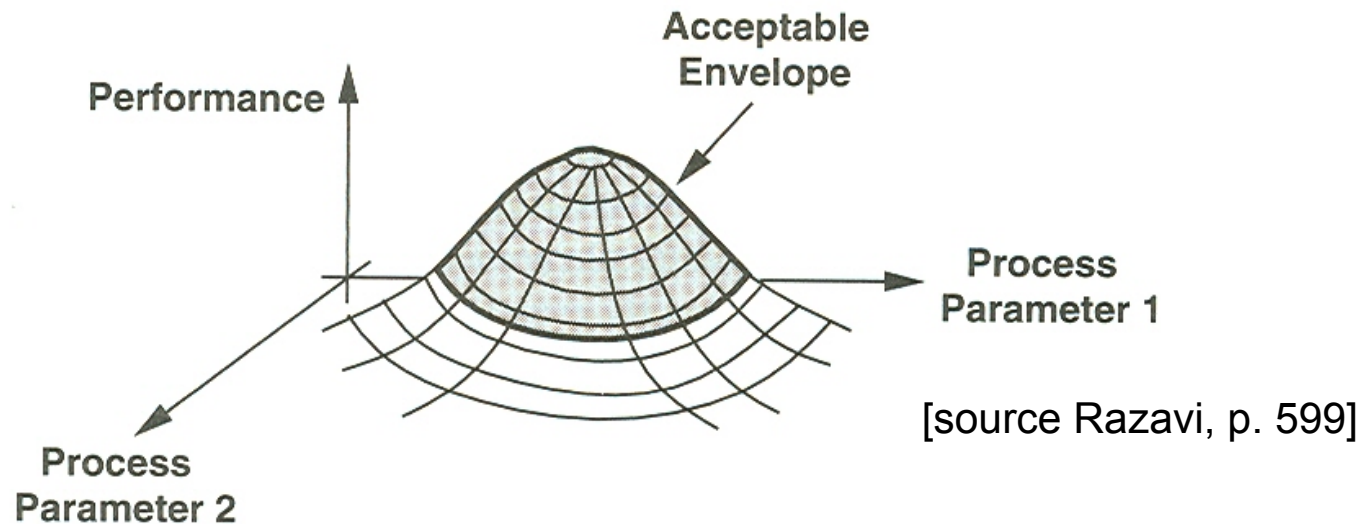
# The Challenge for Circuit Designers


---

- Making sure that the circuit is biased properly across all possible conditions
  - And also maintain a set of performance specs (gain, bandwidth, power dissipation, ...) in presence of parameter variations


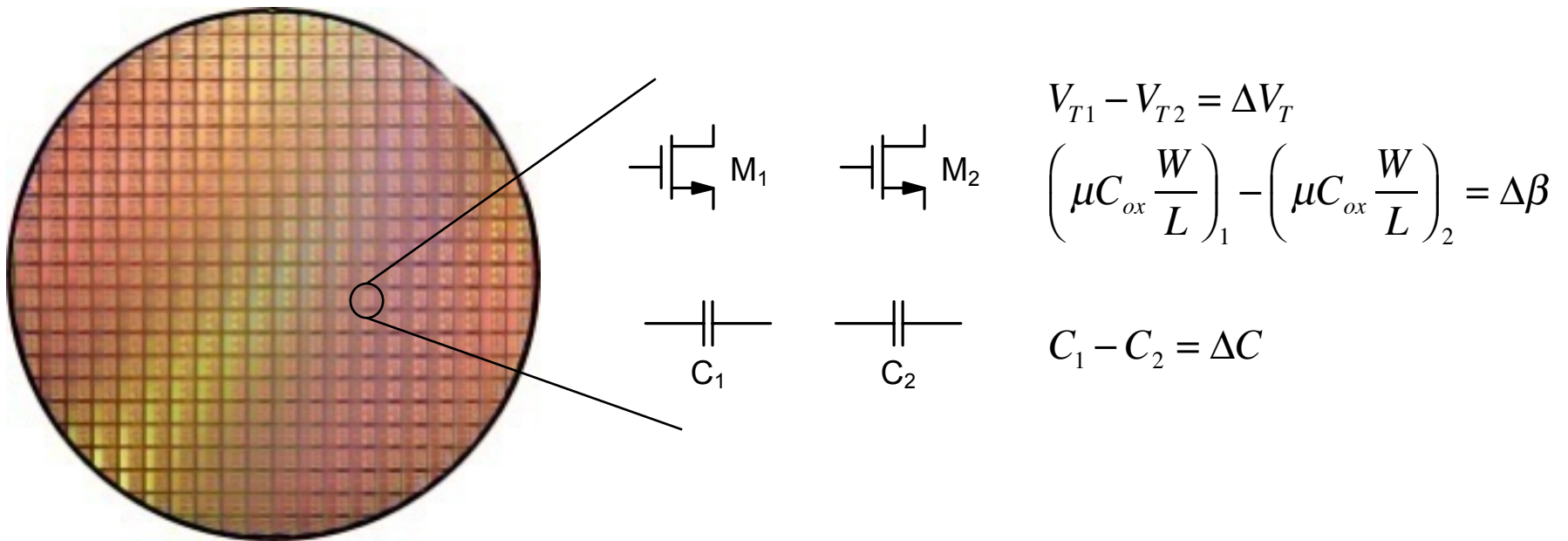
# Mismatch

- Upon closer inspection, device parameters not only vary from lot-to-lot or wafer-to-wafer, but there are also differences between closely spaced, nominally identical devices on the same chip (local variations)
  - These differences are called mismatch



# Statistical Model

---

- Experiments over the past decades have shown that mismatches in device parameters ( $\Delta V_T$ ,  $\Delta C$ , ...) are typically “random” and well-described by a Gaussian distribution
  - With zero mean and a standard deviation that depends on the process and the size of the device
- Empirically, the standard deviation of the mismatch between two closely spaced devices can be modeled using the following expression

$$\sigma_{\Delta X} = \frac{A_X}{\sqrt{WL}}$$

where  $WL$  represents the area of the device, and  $X$  is the device parameter under consideration

# Example of Coefficients for 1 $\mu\text{m}$ Technology

---


Parameter	Value
$A_{V_t}$	20 mV- $\mu\text{m}$
$A_{\Delta\beta/\beta}$	2 %- $\mu\text{m}$
$A_{\Delta C/C}$ (Poly-Poly2 capacitor)	2.5 %- $\mu\text{m}$
$A_{\Delta R/R}$ (Poly2 resistor)	10 %- $\mu\text{m}$

# Example

 - Example: MOSFET with  $W=20\mu\text{m}$ ,  $L=1\mu\text{m}$

$$\sigma_{\Delta V_t} = \frac{20\text{mV}}{\sqrt{20}} = 4.5\text{mV} \quad \sigma_{\frac{\Delta\beta}{\beta}} = \frac{2\%}{\sqrt{20}} = 0.45\%$$

[http://en.wikipedia.org/wiki/Image:Standard\\_deviation\\_diagram.svg](http://en.wikipedia.org/wiki/Image:Standard_deviation_diagram.svg)



$$3\sigma_{\Delta V_t} = 13.5\text{mV}$$

$$3\sigma_{\frac{\Delta\beta}{\beta}} = 1.35\%$$