


Common Gate Stage

Cascode Stage

Claudio Talarico, Gonzaga University

Common Gate Stage

 The overdrive due to V_B must be “consistent” with the current pulled by the DC source I_B




Driving Circuit
(e.g. photodiode)



R_i models finite resistance in the driving circuit
 C_i models parasitic capacitance in the driving circuit

careful with signs:

$$V_{gs} = V_{bs} = -v_i$$

 

Define: $C_S = C_{gs} + C_{sb} + C_i$

$$C_D = C_{gd} + C_{db}$$

$$\underline{g'_m = g_m + g_{mb}}$$

“enhanced” g'_m
 due to both “gates”

Common Stage Bias Point Analysis

- Assume R_i is large: (very reasonable for a reverse biased photodiode)

↓
 $I_D \cong I_B$

$$I_B \cong I_D = \frac{1}{2} \mu C_{OX} \frac{W}{L} (V_{GS} - V_t)^2 \quad V_t = V_{t0} + \gamma \left(\sqrt{PHI + V_{SB}} - \sqrt{PHI} \right)$$


$V_{SB} = V_S$

$$V_{OUT} = V_{DD} - R_D I_B$$

$$V_{GS} = V_t + \sqrt{\frac{I_B}{0.5 \mu C_{OX} W / L}}$$

$$V_S = V_B - V_{GS} = V_B - V_t - \sqrt{\frac{I_B}{0.5 \mu C_{OX} W / L}}$$

 A precise solution requires numerical iterations. Since the dependency of V_t on V_S is weak a few iterations are satisfactory for hand calculation



Once V_S is computed we can check that M1 operates in saturation:

$$V_{DS} = V_{OUT} - V_S > V_{Dsat} = V_{GS} - V_t$$

CG biasing (1)

- Example:

$$V_{DD} = 5V; V_B = 2.5V; I_B = 400\mu A; R_D = 3K\Omega; W = 100\mu m; L = 1\mu m; V_{t0} = 0.5V$$

```
* CG stage
* filename: cgbias.sp
* C. Talarico, Fall 2014

*** device model
.model simple_nmos nmos kp=50u vto=0.5 lambda=0.1 cox=2.3e-3 capop=2
+ cgdo=0.5n cgso=0.5n cj=0.1m cjsw=0.5n pb=0.95 mj=0.5 mjsw=0.95
+ acm=3 cjgate=0 hdif=1.5u gamma=0.6 PHI=0.8


*** useful options
.option post brief nomod accurate

*** circuit
VDD vdd 0 5
* IB vi 0 dc 400u
VS vi 0 dc 1.3077 *** value for .op analysis
VB vb 0 dc 2.5
*** d g s b
mn1 vo vb vi 0 simple_nmos w=100u l=1u
Rd vdd vo 3k
*** calculate operating point
.op
*** large signal analysis (sweep Vi)
.dc VS 0 5 0.01

.end
```

```
element 0:mn1
model 0:simple_n
region Saturati
id 400.0000u
ibs -13.0770f
ibd -38.0000f
vgs 1.1923
vds 2.4923
vbs -1.3077
vth 834.4189m
vdsat 357.8811m
vod 357.8811m
beta 6.2462m
gam eff 600.0000m
gm 2.2354m
gds 32.0197u
gmb 461.9214u
cdtot 75.6690f
cgtot 256.1831f
cstot 246.0823f
cbtot 69.7376f
cgs 203.3341f
cgd 50.7643f
```

CG biasing (2)

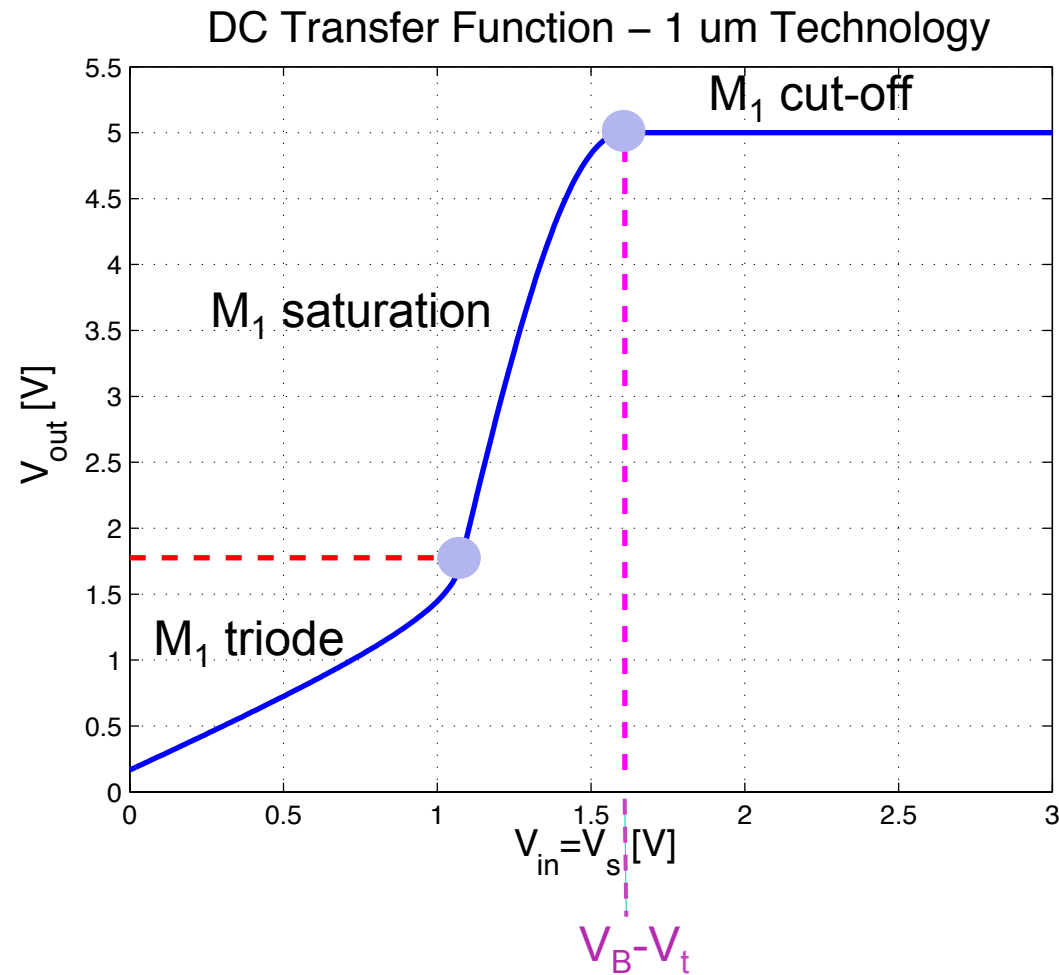


- The I/O characteristic is flipped w.r.t. the CS stage (small signal voltage gain $A_V = dV_{out}/dV_{in}$ is positive !)

CG small signal model

- Depending on how the CG is used the output variable of interest may be:
 - The current that flows into the output (Current Buffer)
 - The voltage at the output (Transresistance Amplifier)

careful with signs:


$$V_{bs} = V_{gs} = -V_s$$

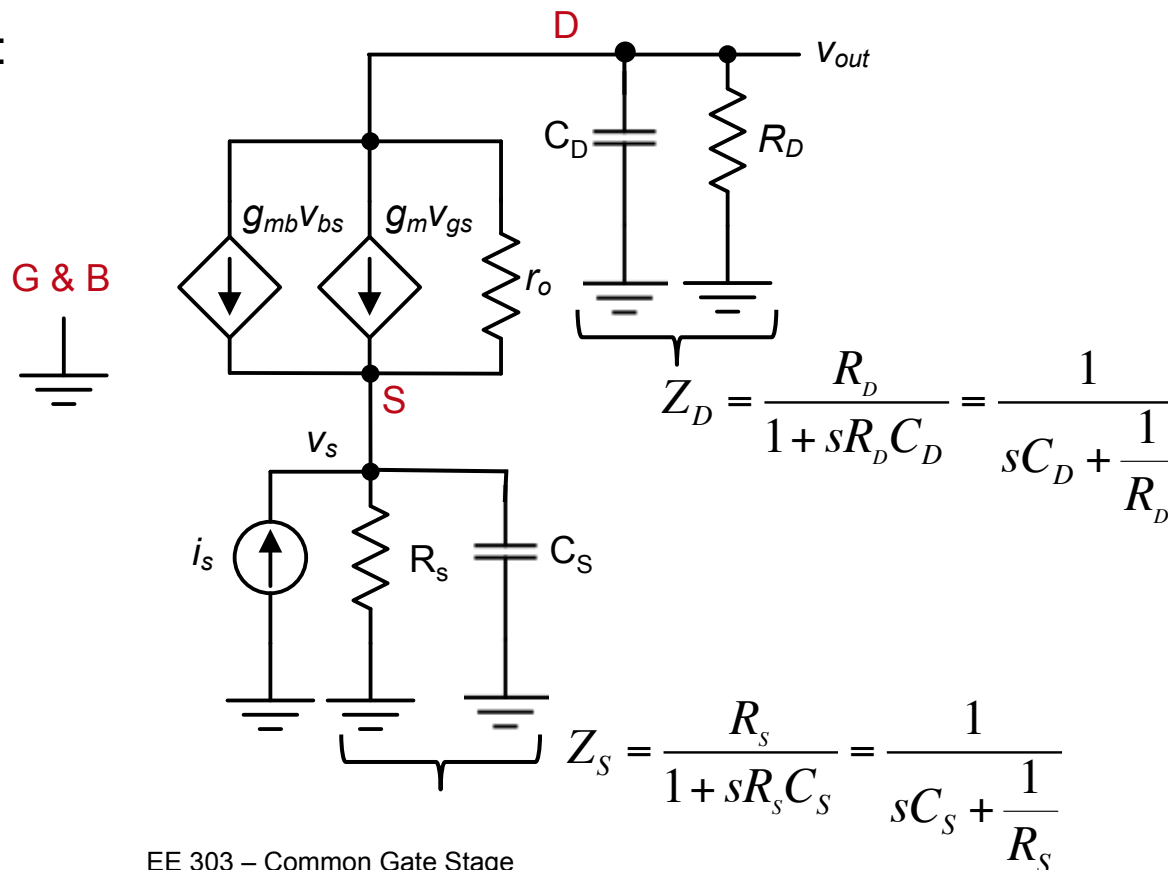

CG input impedance (1)

First pass:

Z_S in || to v_{test} so let's temporarily "remove" it

 

KCL @ v_o :

$$0 = \frac{v_o}{Z_D} + \frac{v_o}{r_o} - \frac{v_{test}}{r_o} - g'_m v_{test} \Rightarrow v_o \cong g'_m (Z_D \parallel r_o) v_{test}$$

w.r.t. ($g'_m r_o \gg 1$)

KCL @ v_{test} : w.r.t. ($g'_m r_o \gg 1$)

$$i_{test} = g'_m v_{test} + \frac{v_{test}}{r_o} - \frac{v_o}{r_o}$$




$$\frac{i_{test}}{v_{test}} \cong g'_m - g'_m \frac{Z_D r_o}{r_o (Z_D + r_o)} = \frac{g'_m r_o}{Z_D + r_o}$$

Aside: if $g'_m r_o$ is not $\gg 1$

$$\frac{v_{test}}{i_{test}} = \frac{1 + \frac{Z_D}{r_o}}{g'_m + \frac{1}{r_o}}$$

CG input impedance (2)

Final Pass: Let's bring back Z_S :

 

$$Y_{in} \cong \frac{g'_m r_o}{Z_D + r_o} + sC_S + \frac{1}{R_S} = \frac{g'_m r_o}{\left(R_D \parallel \frac{1}{sC_D}\right) + r_o} + sC_S + \frac{1}{R_S}$$

$$Z_{in} \cong \frac{r_o + \left(R_D \parallel \frac{1}{sC_D}\right)}{g'_m r_o} \parallel \frac{1}{sC_S} \parallel R_S$$

$g'_m r_o \gg 1$
(always true with our technology !!)

CG input impedance: Summary (1)

$$Z_{in} \cong \frac{r_o + \left(R_D \parallel \frac{1}{sC_D} \right)}{g'_m r_o} \parallel \frac{1}{sC_S} \parallel R_S$$

- At low frequency: $R_{in} \cong \frac{r_o + R_D}{g'_m r_o} \parallel R_S$

- Two interesting cases:

- $R_D \ll r_o$

$$R_{in} \cong \frac{1}{g'_m} \parallel R_S$$

Typically $R_S \gg 1/g'_m$
 If not most of the driving current instead of going to the MOS is lost !!

Well known result !

- R_D is not $\ll r_o$

This happen quite often !!
 (example: R_D is a current source load)

Not so Well known ...

CG input impedance: Summary (2)

$$Z_{in} \cong \frac{r_o + \left(R_D \parallel \frac{1}{sC_D} \right)}{g'_m r_o} \parallel \frac{1}{sC_S} \parallel R_S$$

- At high frequency
 - As long as $R_D \ll r_o$ (regardless of the term C_D)

Typically $R_S \gg 1/g'_m$

$$Z_{in} \cong \frac{1}{g'_m} \parallel \frac{1}{sC_S} \parallel R_S \cong \frac{1}{g'_m} \parallel \frac{1}{sC_S}$$


NOTE:

$R_D \parallel \frac{1}{sC_D}$ is always < than R_D .

If $R_D \ll r_o$ so is $R_D \parallel \frac{1}{sC_D}$

CG output impedance (1)

- At low frequency

 

$$i_{test} = \frac{v_{test}}{r_o} - \frac{v_s}{r_o} - g'_m v_s \quad \text{w.r.t. } (g'_m r_o \gg 1)$$

$$v_s = R_S \cdot i_{test}$$



$$R_{out} = \frac{v_{test}}{i_{test}} \cong r_o (1 + g'_m R_S)$$

(Very high if $g'_m R_S \gg 1$)


$$R_{out} = \frac{v_{test}}{i_{test}} \cong r_o g'_m R_S$$

Aside: if $g'_m r_o$ is not $\gg 1$

$$R_{out} = \frac{v_{test}}{i_{test}} = R_S + r_o (1 + g'_m R_S)$$

CG output impedance (2)

- At high frequency

 


$$Z_{out} \cong r_o \left[1 + g'_m \left(R_S \parallel \frac{1}{sC_S} \right) \right] \parallel \frac{1}{sC_D}$$

Typically $C_S / (g'_m r_o) \ll C_D$

$$\text{If } g'_m R_S \gg 1 \longrightarrow Z_{out} \cong g'_m r_o R_S \parallel \frac{g'_m r_o}{sC_S} \parallel \frac{1}{sC_D} \cong g'_m r_o R_S \parallel \frac{1}{sC_D}$$


CG current transfer (1)

 

w.r.t. ($g'_m r_o \gg 1$)

$$i_{out} = \cancel{\frac{v_s}{r_o}} - \frac{v_{out}}{r_o} + g'_m v_s \cong -\frac{R_D i_{out}}{r_o} + g'_m v_s$$

 
$$i_{out} \left(1 + \frac{R_D}{r_o} \right) \cong g'_m v_s$$



NOTE:

for $r_o \gg R_D \rightarrow i_{out} \cong g'_m v_s$ ➡ The CG stage is approx. unilateral

CG current transfer (2)

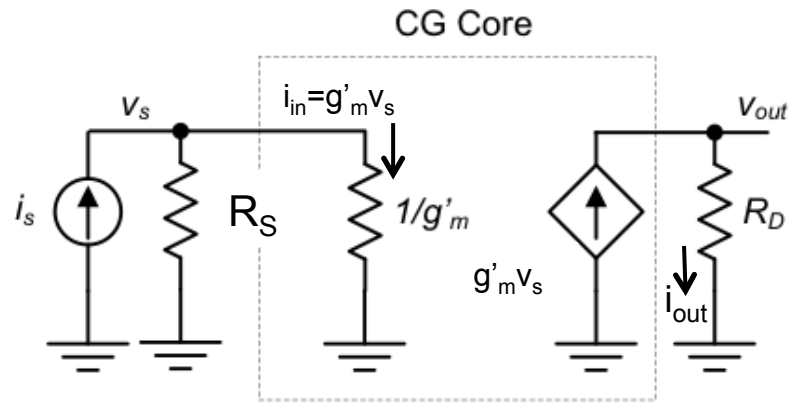

CG stage model valid for:
 $g'_m r_o \gg 1$ and $r_o \gg R_D$


- At low frequency:
 - for $g'_m r_o \gg 1$ and $r_o \gg R_D$)

$$\frac{i_{out}}{i_s} = \frac{i_{out}}{i_{in}} \frac{i_{in}}{i_s} \cong \frac{R_S}{\frac{1}{g'_m} + R_S} \cong 1$$

Typically $g'_m R_S \gg 1$

This is a current buffer !!!
 $A_{I0} \cong 1$, R_{in} small, R_{out} large

CG current transfer (3)

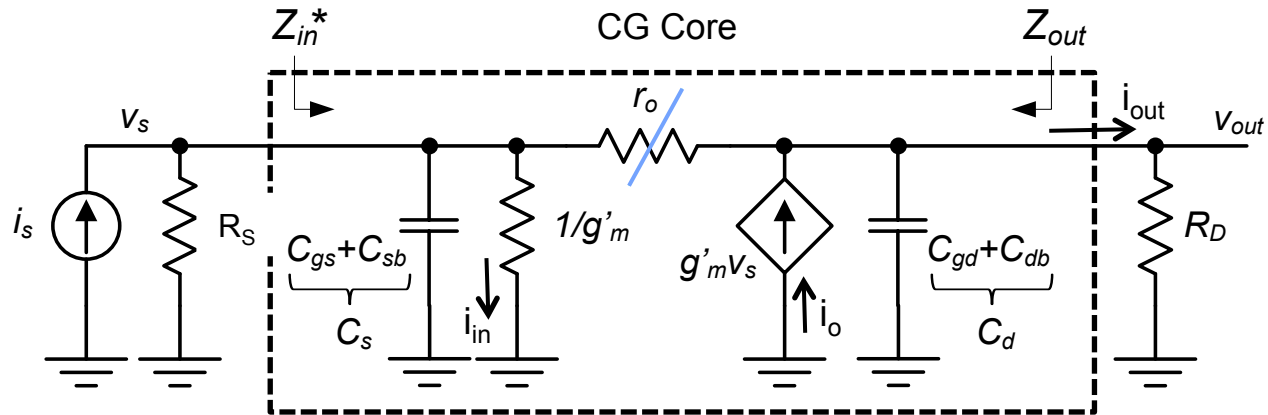


- At high frequency:

- for $g'_m r_o \gg 1$ and $r_o \gg R_D$ (since $R_D > R_D \parallel \frac{1}{sC_D}$, $r_o \gg R_D$ implies $r_o \gg Z_D$)

$$\frac{i_o}{i_s} \cong \frac{g'_m v_s}{\left(\frac{1}{R_S} + sC_S + g'_m\right)v_s} = \frac{g'_m R_S}{1 + sR_S C_S + g'_m R_S} = \frac{A_{I0}}{1 - \frac{s}{p_1}} = \frac{g'_m R_S}{1 + g'_m R_S} \cdot \frac{1}{1 + s \frac{C_S}{g'_m + \frac{1}{R_S}}}$$

CG current transfer (4)

 


$$\frac{i_{out}}{i_s} = \frac{i_{out}}{i_o} \frac{i_o}{i_s} \cong \frac{1}{\frac{1}{sC_D} + R_D} \cdot \frac{g'_m R_S}{1 + g'_m R_S} \cdot \frac{1}{1 + s \frac{C_S}{g'_m + \frac{1}{R_S}}} = \underbrace{\frac{1}{1 + sC_D R_D}}_{\frac{1}{1 - \frac{s}{p_2}}} \cdot \underbrace{\frac{g'_m R_S}{1 + g'_m R_S}}_{A_{I0}} \cdot \underbrace{\frac{1}{1 + s \frac{C_S}{g'_m + \frac{1}{R_S}}}}_{\frac{1}{1 - \frac{s}{p_1}}}$$

$$\frac{i_{out}}{i_s} \cong \frac{1}{(1 + sC_D R_D) \left(1 + s \frac{C_S}{g'_m}\right)}$$


Typically $g'_m R_S \gg 1$

CG Input-Output RC Time Constants

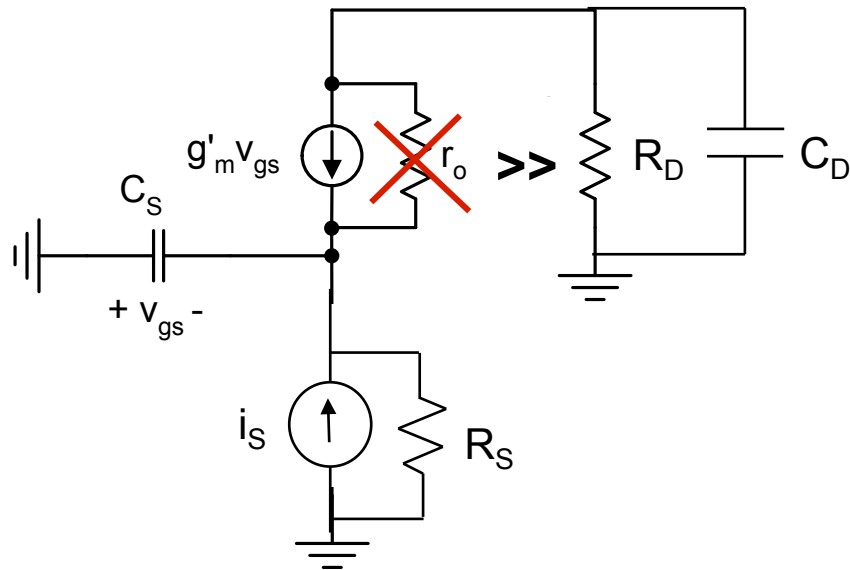

- For this specific configuration and assumptions ($r_o \gg R_D$ and $g'_m r_o \gg 1$) input and output are decoupled \rightarrow “RC time constants” are = 1/poles
 - Input RC: $\sim C_S(1/g'_m)$ ($R_S \gg 1/g'_m$)
 - Output RC: $R_D C_D$

CG Frequency Response

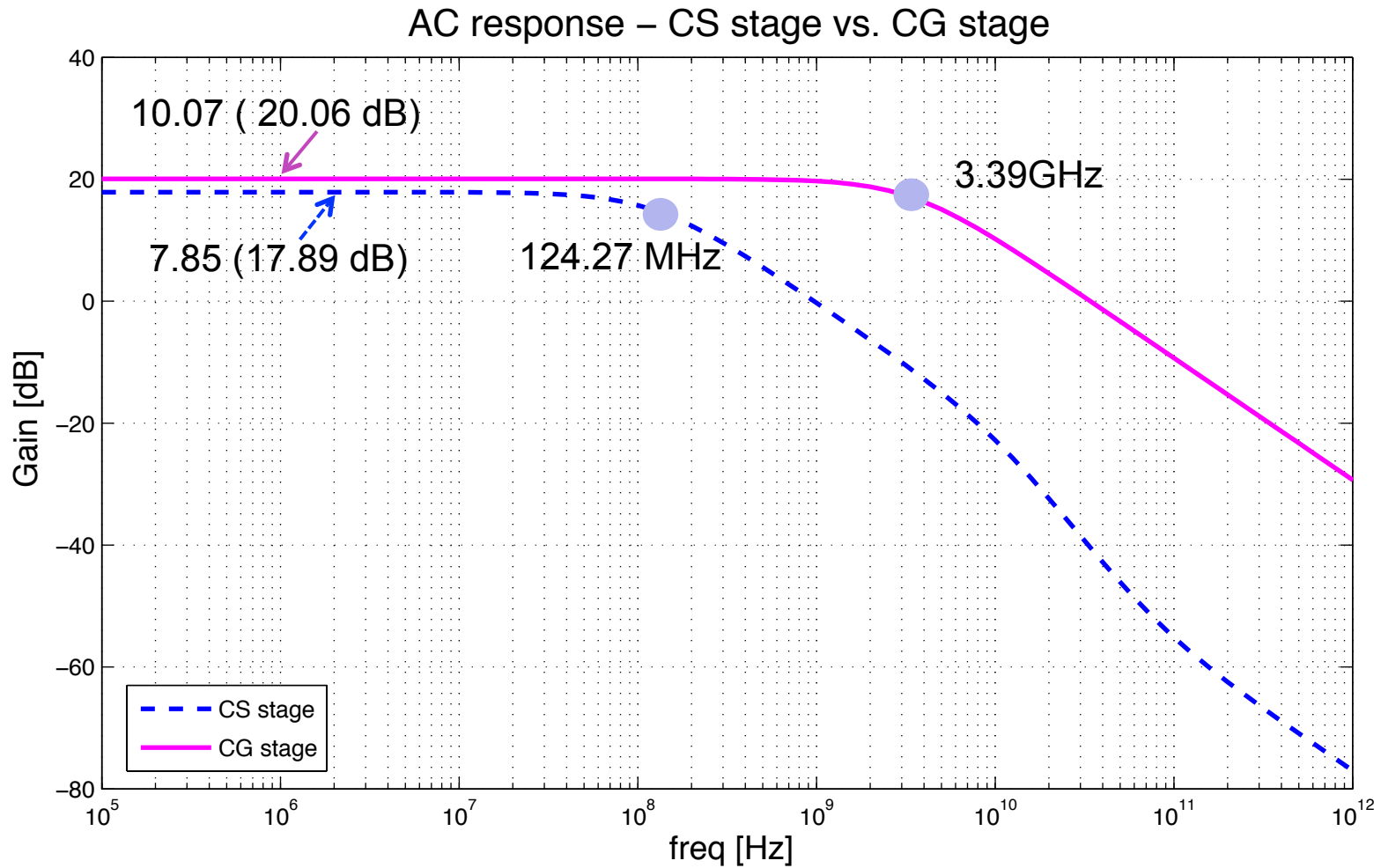

$$A_{v0_CS} \cong -g_m R_D$$


$$A_{v0_CG} \cong g'_m R_D$$

CG Summary

- Current gain is about unity up to very high frequencies
 - The CG stage absorbs most of the current from the input source and it passes the current to the output terminal
- The CG does not contain a FB capacitance between input and output (no Miller effect)
 - The effect of large values of R_D on the frequency response is much less than in CS stage (for a desired BW we can extract more gain out of the CG stage)
- Input impedance is “typically” very low ($R_{in} \cong 1/g'_m$)
 - At least when the output is terminated with some reasonable impedance ($R_D \ll r_o$)
- Can achieve very high output resistance ($R_{out} \approx r_o g'_m R_S$)
- In summary, a common gate stage is ideal for turning a decent current source into a much better one
 - Seems like this is something we can use to improve our common source stage
 - Which is indeed nothing but a decent (voltage controlled) current source

“Aside”

 - If we cannot assume $r_o \gg R_D$, the unilateral model used for the CG stage falls apart. Computing the current transfer gain is a little harder.




$$\frac{i_{out}}{i_s} = \frac{R_S(1 + g'_m r_o)}{R_D + r_o + R_S + g'_m r_o R_S} \quad \leftarrow \text{pp.13-14 Murmann's Textbook}$$

- The poles of the circuit are no longer isolated. However, computing the bandwidth using ZVTC is not too difficult.

$$\tau_1 = C_S \left[\left(\frac{1 + \frac{R_D}{r_o}}{g'_m + \frac{1}{r_o}} \right) \parallel R_S \right] \quad \text{and} \quad \tau_2 = C_D \left[(R_S + r_o(1 + g'_m R_S)) \parallel R_D \right]$$


Cascode Stage (CS + CG)

 - One of the “most important” application of the CG.
- M_1 is a transconductor ($i_1 = g_{m1} v_{in}$) and M_2 buffers the current fed by M_1 ($i_2 \approx i_1$)



“Super transistor”
(Cascode)

 Low-frequency,
small-signal
equivalent circuit




$$G_m = \frac{i_{out}}{v_{in}} = \frac{i_2}{i_1} \cdot \frac{i_1}{v_{in}} = \frac{i_2}{i_1} \cdot g_{m1} \approx g_{m1}$$

$$R_o \approx r_{o1} \cdot g'_{m2} r_{o2}$$


$$G_m R_o \approx g_{m1} r_{o1} \cdot g'_{m2} r_{o2} \propto (g_m r_o)^2$$

Intrinsic gain
of cascode

Low Frequency Benefits

 

 
- Output resistance very high ($\approx g_m r_o^2$)
 - The cascode device “shields” the input device from voltage variations at the output node V_o



$$\Delta V_x = \Delta V \cdot \frac{\left(\frac{1}{g'_{m2}} \parallel r_{o1} \right)}{\left(\frac{1}{g'_{m2}} \parallel r_{o1} \right) + r_{o2}} \ll \Delta V$$

- application: precision current source/mirror
- Intrinsic gain very high $(g_m r_o)^2$
 - application: OTA/OA
- Input resistance of CS stage ($R_{in} \approx \infty$)

High Frequency Benefits

 

$$\frac{v_x}{v_i} = -g_{m1} (Z_x \parallel r_{o1}) \cong -g_{m1} \left[\left(\frac{1}{g'_{m2}} \left(1 + \frac{R}{r_{o2}} \right) \right) \parallel r_{o1} \right]$$


$g'_{m2} r_{o2} \gg 1$

- For moderate value of R: v_x/v_i very close to -1
 - Mitigates Miller effect ($C_{in} \approx C_{gs1} + 2C_{gd1}$)
 - Even if R is large, there is often a load capacitance that provides a low impedance termination to help maintain this feature (R is AC shorted by the load capacitance)
- For not so moderate values of R ($R \approx r_{o2}$): v_x/v_i very close to -2
 - Still mitigate Miller effect quite a bit ($C_{in} \approx C_{gs1} + 3C_{gd1}$)
- Additional benefit
 - Cascode mitigates direct forward coupling from V_i to V_o at high frequencies (RHP zero at $z = +g_{m1}/C_{gd1}$)

$$I_{C_{gd1}} = sC_{gd1} \cdot (V_i - V_x)$$

if we could make $V_i \approx V_x \longrightarrow I_{C_{gd1}} \approx 0$
 which would be the same as cancelling the zero !!

Example Revisited

 


- What we expect to see after adding the cascode device
 - Bandwidth should increase (reduction of Miller effect)
 - Easy to compute using a ZVTC analysis
 - Non-dominant pole around some fraction of f_T of cascode device
 - Drain current of MN1 runs into a current divider between $1/g'_{mc}$ and total capacitance at this node (dominated by C_{gs} of MNC)

$$V_B = 0.9V; V_I = 0.627V; V_{DD} = 1.8V;$$

$$V_{BCAS} = 1.077V; I_B = 400\mu A; R = 2k\Omega;$$

$$R_i = 10k\Omega; W/L = 21.34 \mu m / 0.18 \mu m$$


Simulated Frequency Response

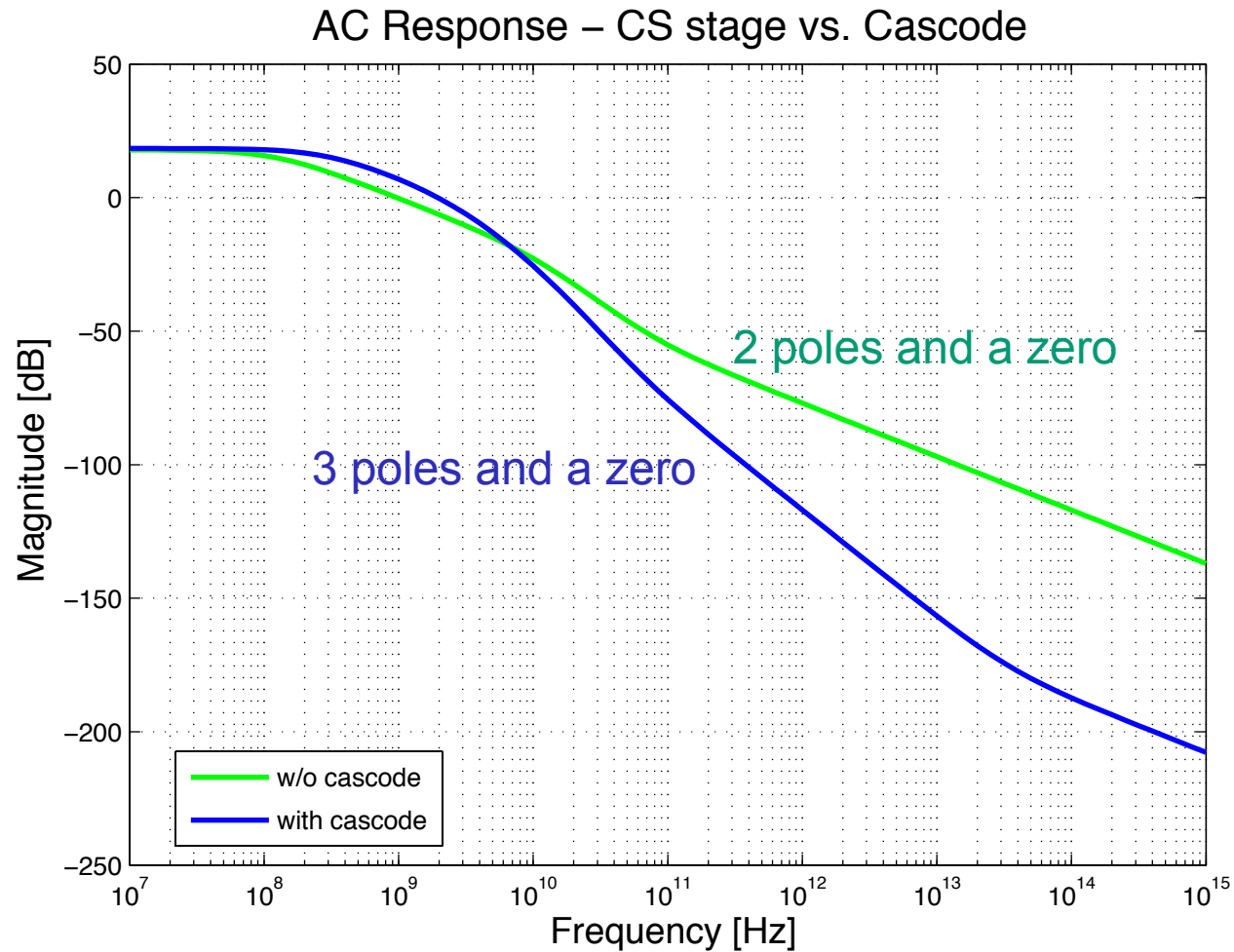

3-dB bandwidth increased from 124.57 MHz to **291.69 MHz** ($\approx 2.34x$)

$|gain_{cs}| = 17.84$ dB; $|gain_{cas}| = 18.40$ dB

Supply Headroom Issue (1)

 

- Even if we adjust V_{BCAS} such that V_{DS1} is small, adding a cascode reduces the available signal swing
- This can be a big issue when designing circuits with $V_{DD} \approx 1V$
 - Typically need each $V_{DS} > \sim 0.2V$



Supply Headroom Issue (2)

- Is the issue really as “bad” as it sounds ?
- For a given bias current, let’s compare the “price” of increasing gain using cascoding vs. the “price” of increasing gain augmenting the transistor’s length in a CS stage

$$I_D = \frac{1}{2} \mu C_{OX} \frac{W}{L} V_{OV}^2 \qquad g_m = \frac{2I_D}{V_{OV}} \qquad r_o \propto \frac{L}{I_D}$$


Source:
Razavi

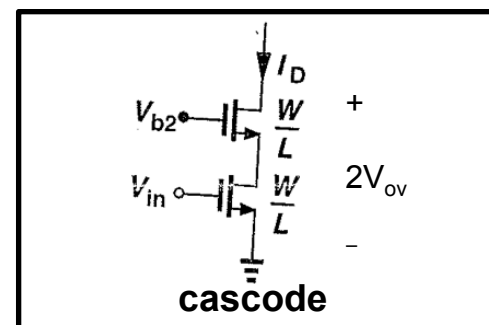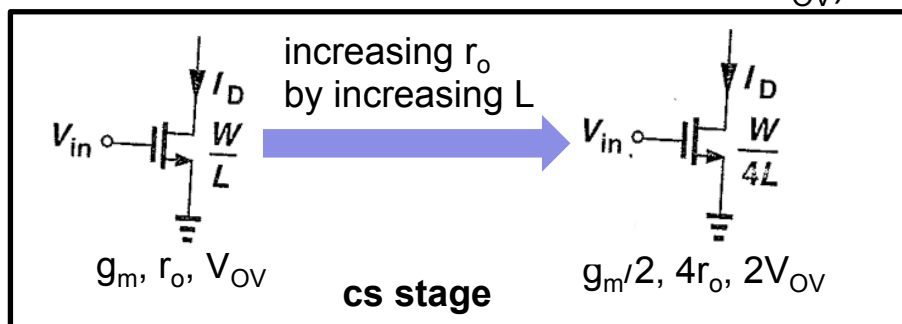Example: let’s quadruple L (if we quadruple L, to maintain the same I_D we need to double V_{OV})



- Very Interesting result:**
 - By quadruplicating L we consume an extra V_{OV} of headroom, (we consume 4x more area), and we get a 2x increase in the intrinsic gain ($\approx 2g_m r_o$)
 - By cascoding we also consume an extra V_{OV} of headroom, (we consume only 2x more area), but we get a significant better intrinsic gain ($\approx g_m r_o$)²

Cascode Bias Analysis

 

Source: Razavi

- M_1 saturation: $V_x > V_{in} - V_{T1}$

$$V_x = V_B - V_{GS2} > V_{in} - V_{T1} \iff \underline{V_B > V_{in} - V_{T1} + V_{GS2}}$$

- M_2 saturation: $V_{out} - V_x > V_{GS2} - V_{T2}$



$$V_{out} > \underbrace{V_B - V_{GS2}}_{= V_x} + V_{GS2} - V_{T2} \longrightarrow V_{out} > \underbrace{V_{in} - V_{T1}}_{= V_{OV1}} + \underbrace{V_{GS2} - V_{T2}}_{= V_{OV2}}$$

- The minimum output DC level for which both transistors operate in saturation is:

$$V_{out}(\min) = V_{OV1} + V_{OV2}$$

I/O DC characteristic of cascode stage

 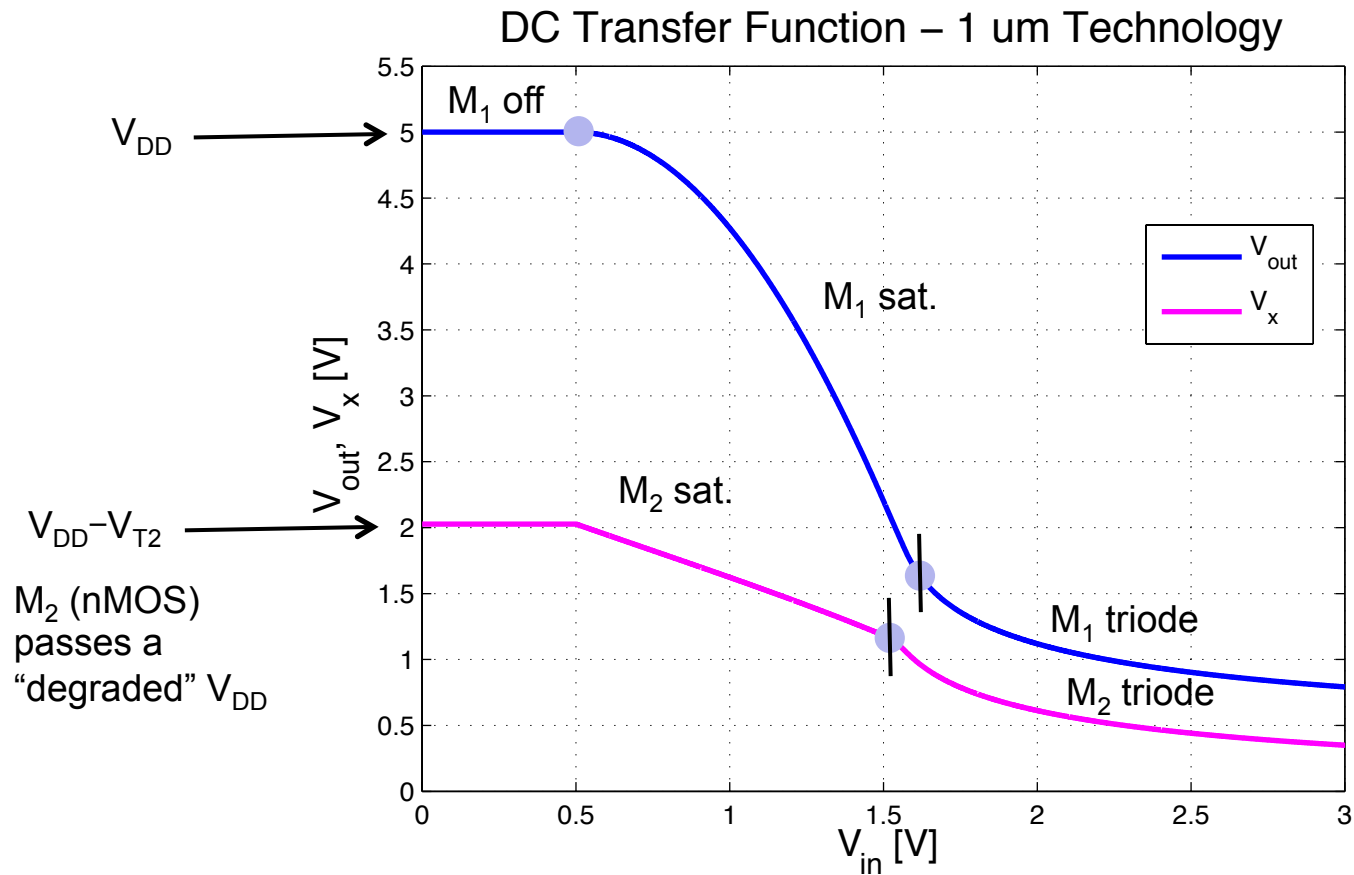- Example: $V_{DD}=5V$, $V_B = 3V$, $W/L = 20\mu\text{m}/1\mu\text{m}$, $R_D=5K\Omega$




$$V_{out}(\text{max}) = V_{DD}$$

$$V_{out}(\text{min}) = V_{OV1} + V_{OV2}$$

- As V_{in} assumes sufficiently large values
 - V_x drops below V_{in} by V_{T1} forcing M_1 into triode
 - V_{out} drops below V_B by V_{T2} forcing M_2 into triode
- Depending of the device dimensions and the values of R_D and V_B one effect may occur before the other

Detailed Transistors operation

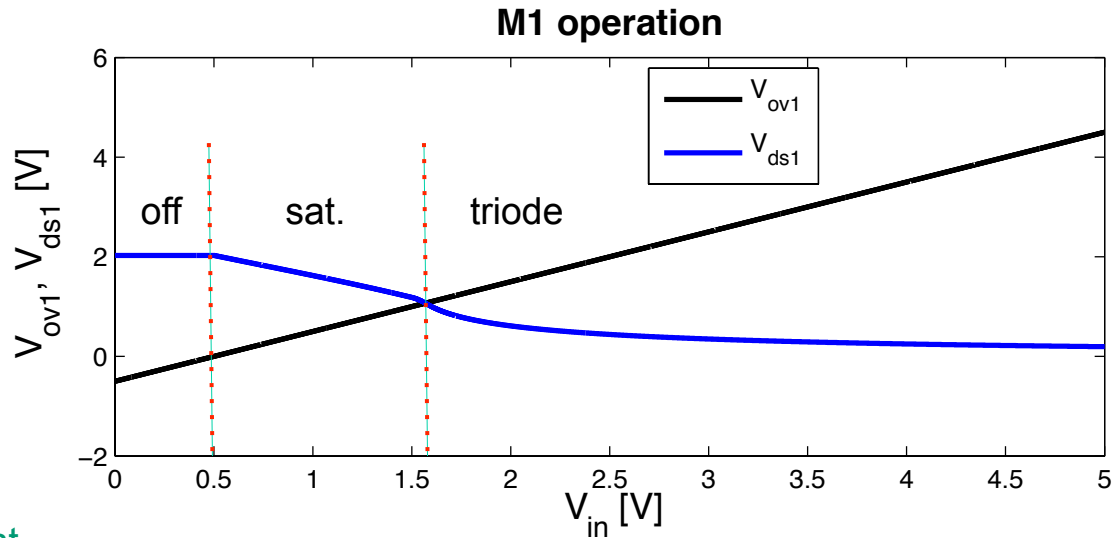

all M_2 current goes into charging cap. at node x

