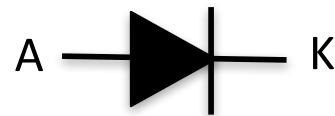


Chapter 4

Electronics I - Diode models



Fall 2017

Effect of Temperature on I/V curves

Source: Hu

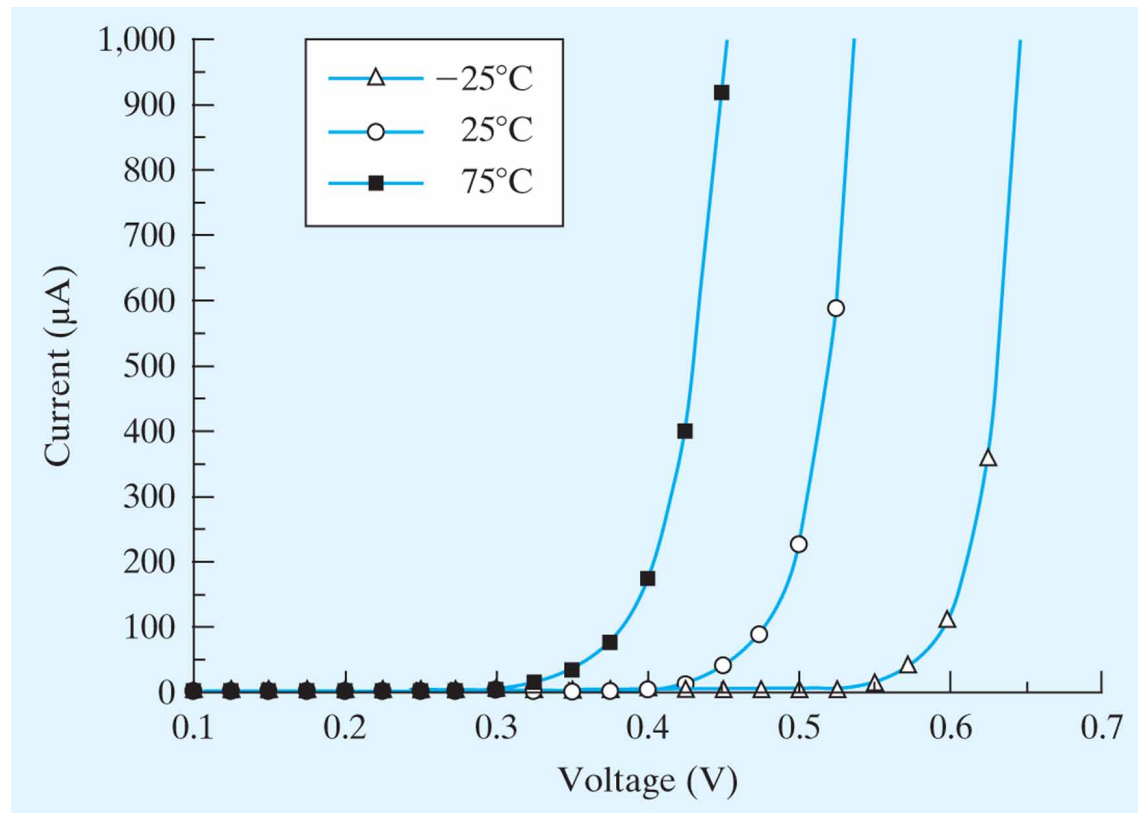


Figure 4.21 The *I/V* curves of the silicon PN diode shift to lower voltages with increasing temperature

Effect of Temperature on I/V curves

- For a given I_D we want to understand how the diode voltage V_D varies with temperature
- The diode's I/V equation contains temperature in two places: $V_T = KT/q$ and I_S

$$I_D = I_S \left(e^{\frac{V_D}{V_T}} - 1 \right) \quad \text{where: } I_S = qAn_i^2 \left(\frac{D_p}{L_p N_d} + \frac{D_n}{L_n N_a} \right) = qAn_i^2 \left(\frac{\mu_p V_T}{L_p N_d} + \frac{\mu_n V_T}{L_n N_a} \right)$$

- Inside the expression of I_S the terms n_i and μ also depends on temperature:

$$\mu \propto T^{-3/2} \quad n_i^2 = N_C N_V e^{\frac{-E_G}{KT}} = A_C A_V T^3 e^{\frac{-E_G}{KT}}$$

- N_V and N_C are respectively the effective density of energy states in valence band and conduction band

$$N_C = A_C T^{3/2} \quad \text{and} \quad N_V = A_V T^{3/2}$$

Effect of Temperature on I/V curves

- If for simplicity we ignore the weak temperature dependence of the effective mass density of the conduction band electrons (m_n^*) and the valence band holes (m_p^*) the values of A_C and A_V are about constant (sources: Pierret p. 51):

$$n_i^2 = A_C A_V T^3 e^{\frac{-E_G}{KT}} \quad \text{with:}$$

$$A_C = 2 \left[\frac{m_n^* k}{2\pi\hbar^2} \right]^{3/2} \approx 6.2 \times 10^{15} \text{ cm}^{-3} \text{ K}^{-3/2}$$

$$A_V = 2 \left[\frac{m_p^* k}{2\pi\hbar^2} \right]^{3/2} \approx 3.52 \times 10^{15} \text{ cm}^{-3} \text{ K}^{-3/2}$$

$$\left. \begin{array}{l} A_C \\ A_V \end{array} \right\} \rightarrow \begin{array}{l} n_i^2 = A_C A_V \times T^3 e^{\frac{-E_G}{KT}} \\ \Downarrow \\ n_i = \sqrt{A_C A_V} \times T^{3/2} e^{\frac{-E_G}{2KT}} = B \times T^{3/2} e^{\frac{-E_G}{2KT}} \end{array}$$

- k = Boltzmann's constant = 8.62×10^{-5} eV/K = 1.38×10^{-23} Joule/K
- \hbar = Reduced Planck's constant = 1.055×10^{-34} Joule-sec
- $m_n^* = 1.18 \times m_0$
- $m_p^* = 0.81 \times m_0$
- m_0 = electron rest mass = 9.11×10^{-31} Kg

Effect of Temperature on I/V curves

- Therefore \approx :
$$n_i = B \times T^{3/2} e^{\frac{-E_G}{2KT}} \quad \text{with } B \cong 5 \times 10^{15} \text{ cm}^{-3} \text{ K}^{-3/2}$$

- If for simplicity we ignore the weak temperature dependence of the band gap energy:

source: Plummer

$$E_G = E_{G0} - \frac{4.73 \times 10^{-4} \times T^2}{T + 636} \approx 1.16 - 3 \times 10^{-3} \times T$$

where E_{G0} is the band gap energy at 0K ($E_{G0} \approx 1.17$ eV) and the temperature T is expressed in K

- We can finally write I_S as follows:

$$I_S = qAB^2 T^3 e^{\frac{-E_G}{kT}} \left(\frac{\kappa_{\mu,p} T^{-1.5} kT / q}{L_p N_d} + \frac{\kappa_{\mu,n} T^{-1.5} kT / q}{L_n N_a} \right) \equiv \zeta \cdot T^{2.5} \cdot e^{\frac{-E_G}{kT}}$$

Effect of Temperature on I/V curves

- First pass:

$$I_S = qAB^2T^3 e^{\frac{-E_G}{kT}} \left(\frac{\kappa_{\mu,p} T^{-1.5} kT / q}{L_p N_d} + \frac{\kappa_{\mu,n} T^{-1.5} kT / q}{L_n N_a} \right) \equiv \zeta \cdot T^{2.5} \cdot e^{\frac{-E_G}{kT}}$$

- the temperature dependence caused by the polynomial term is weak compared to the one caused by the exponential term, so we will ignore it

$$I_S = \underbrace{\zeta \cdot T^{2.5}}_{=\zeta} \cdot e^{\frac{-E_G}{kT}} \equiv \zeta \cdot e^{\frac{-E_G}{kT}}$$

- Let's get back to our objective:

given a fixed value of current I_D we want to find out the voltage variation occurring ΔV_D when there is a temperature variation ΔT occurring

$$TC \equiv \left. \frac{dV_D}{dT} \right|_{@I_D=const}$$

Effect of Temperature on I/V curves

- Let's assume forward bias and flip the I/V eq.:

$$I_D \approx I_S \left(e^{\frac{V_D}{V_T}} \right) \Rightarrow \frac{I_D}{I_S} = e^{\frac{V_D}{V_T}} \Rightarrow V_D \approx V_T \ln \frac{I_D}{I_S} = \frac{kT}{q} \ln \left(\frac{I_D}{I_S} \right)$$



$$\frac{dV_D}{dT} = \frac{d}{dT} \left[\frac{kT}{q} \ln \left(\frac{I_D}{I_S} \right) \right] = \frac{k}{q} \ln \left(\frac{I_D}{I_S} \right) + \frac{kT}{q} \frac{d}{dT} (\ln I_D - \ln I_S) \cong$$

$$\cong \frac{k}{q} \cdot \frac{V_D}{kT} + \frac{kT}{q} \frac{d}{dT} \left(\ln I_D - \ln \xi + \frac{E_G}{kT} \right) \cong \frac{V_D}{T} + \frac{kT}{q} \frac{d}{dT} \left(\frac{E_G}{kT} \right) \cong$$

$$\cong \frac{V_D}{T} - \frac{E_G}{qT}$$

constant

constant

E_G and k are constants
take them out of the
derivative

And let's keep in mind a couple of useful math rules:

$$\frac{d(uv)}{dx} = v \frac{du}{dx} + u \frac{dv}{dx}$$


$$\frac{d}{dx} (\ln u) = \frac{1}{u} \frac{du}{dx}$$

$$\frac{d}{dx} (x^N) = N \cdot x^{N-1}$$

Effect of Temperature on I/V curves

$$TC \equiv \frac{dV_D}{dT} \cong \frac{V_D}{T} - \frac{E_G / q}{T}$$

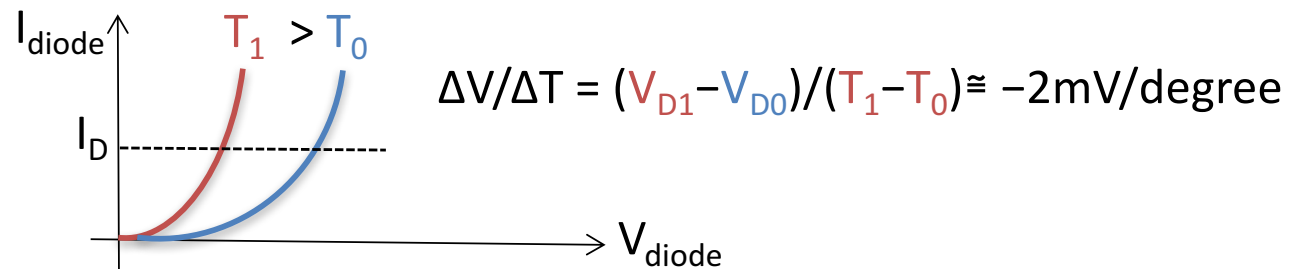- Assuming $V_D=0.5V$ and $T=300K$: $TC = \frac{0.5-1.12}{300} = -2.1 \text{ mV/K} = -2.1 \text{ mV/degree}$
- At room temperature, a diode's forward voltage-drop has a thermal coefficient of about -2mV per degree



- If we know the diode voltage at some reference temperature T_0 we can estimate the diode voltage at any other temperature T as follows:

$$V_D(T) \cong V_D(T_0) - 2 \text{ mV/degree} \times (T - T_0) = V_D(T_0) + TC \times (T - T_0)$$

Aside: second pass

- If we want to consider also the temperature dependence caused by the polynomial term, all we have to do is a little more work taking the derivative:

$$\begin{aligned} \frac{dV_D}{dT} &= \frac{d}{dT} \left[\frac{kT}{q} \ln \left(\frac{I_D}{I_S} \right) \right] = \frac{k}{q} \ln \left(\frac{I_D}{I_S} \right) + \frac{kT}{q} \frac{d}{dT} (\ln I_D - \ln I_S) \cong \\ &\cong \frac{V_D}{T} + \frac{kT}{q} \frac{d}{dT} \left(\ln I_D - \ln \zeta - \ln T^{2.5} + \frac{E_G}{kT} \right) \cong \\ &\cong \frac{V_D}{T} - \frac{2.5V_T}{T} - \frac{E_G/q}{T} \end{aligned}$$

$I_S = \zeta \cdot T^{2.5} \cdot e^{-\frac{E_G}{kT}}$

$\frac{d}{dT} (\ln T^m) = \frac{1}{T^m} \frac{d}{dT} (T^m) = \frac{m}{T^m} T^{m-1} = \frac{m}{T}$

- The term V_D/T results from the temperature dependence on V_T . The negative terms results from the temperature dependence of I_S , and does not depend on the voltage across the diode

- Assuming $V_D=0.5V$ and $T=300K$: $TC = \frac{0.5 - 2.5 \times 26 \times 10^{-3} - 1.12}{300} = -2.3 \text{ mV/degree}$

- So for conservative design it is common to assume: $TC = \frac{dV_D}{dT} \cong -2.5 \text{ mV/degree}$

Effect of Temperature on I/V curves

- In reverse bias we find out that the variation of I_s with T is about 14.6% percent/degree:

Recalling:

$$\frac{d}{dx}(\ln u) = \frac{1}{u} \frac{du}{dx}$$

$$\frac{d}{dT}(\ln I_s) = \frac{1}{I_s} \frac{dI_s}{dT} \Rightarrow \frac{dI_s}{dT} = I_s \cdot \frac{d(\ln I_s)}{dT}$$

$$\frac{d}{dT} \left[\ln \left(\underbrace{\zeta \cdot T^{2.5} \cdot e^{-\frac{E_G}{kT}}}_{=I_s} \right) \right] = \frac{d}{dT} \left(\ln \zeta + \ln T^{2.5} - \frac{E_G}{kT} \right) = \frac{2.5}{T} + \frac{E_G}{kT^2} = \frac{2.5}{T} + \frac{E_G}{kT^2} \frac{q}{q} = \frac{2.5}{T} + \frac{E_G / q}{T \cdot V_T}$$

$$\frac{dI_s}{dT} = I_s \left(\frac{2.5}{T} + \frac{E_G / q}{T \cdot V_T} \right)$$


- At room temperature: $\frac{dI_s}{dT} = I_s \left(\frac{2.5}{300} + \frac{1.12}{300 \cdot 26 \cdot 10^{-3}} \right) = I_s \times \frac{15.2}{100} \text{ [A/degree]}$

- Since $(1.152)^5 \approx 2$ we conclude that the saturation current approximately doubles for every 5 degrees rise in temperature

Effect of Temperature on I/V curves

- In reverse bias:

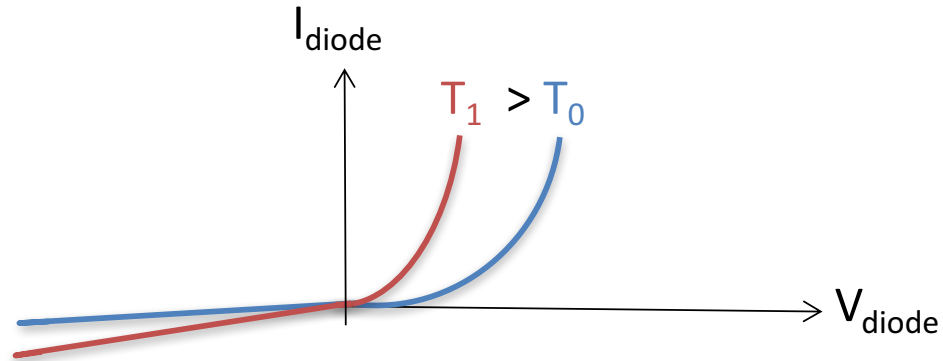
$$I_S(T) = I_S(T_0) \times 2^{(T-T_0)/5}$$



- Although still quite small, real diodes exhibit reverse currents that are much larger than I_S . A large part of the reverse current is due to leakage effects. These leakage effects are proportional to the junction area A just as I_S is.
- As a rule of thumb I_R doubles for every 10 degree rise in temperature

$$I_R(T) = I_R(T_0) \times 2^{(T-T_0)/10}$$

Different Models

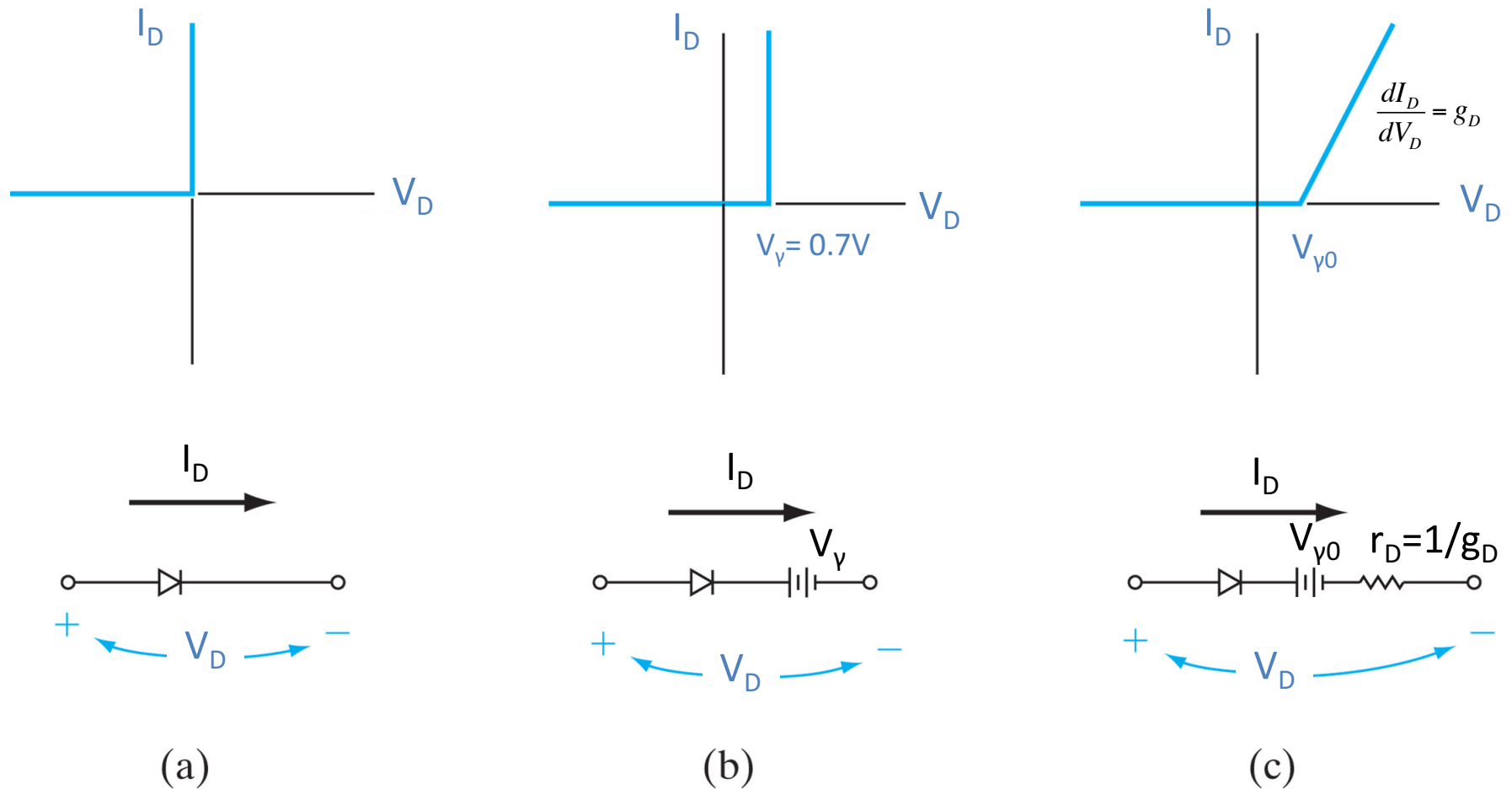

Copyright ©2015 Pearson Education, All Rights Reserved

Figure 5-23 Streetman

approximations of junction diode characteristics: (a) the ideal diode; (b) ideal diode with an offset voltage; (c) ideal diode with an offset voltage and a resistance to account for slope in the forward characteristic.

Ideal diode with voltage offset

source: Razavi

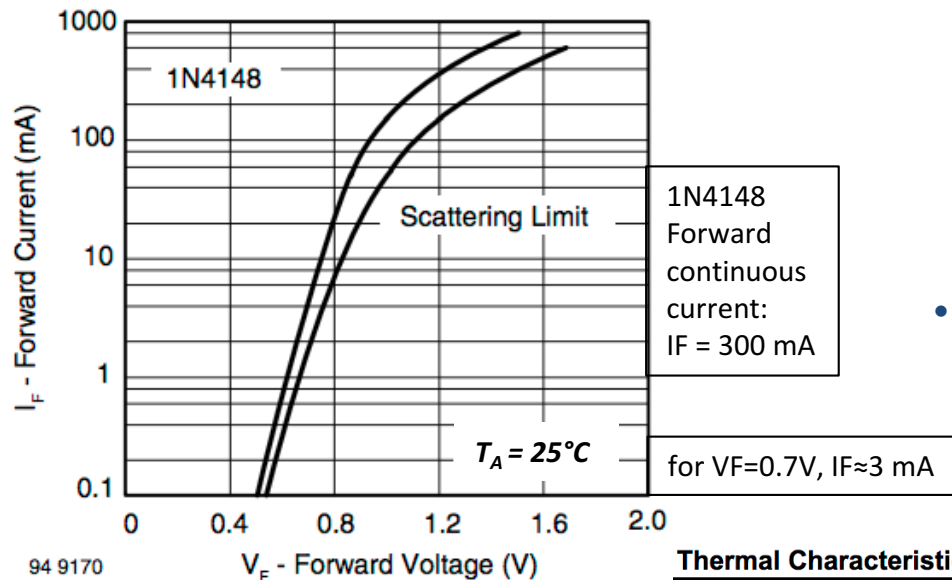
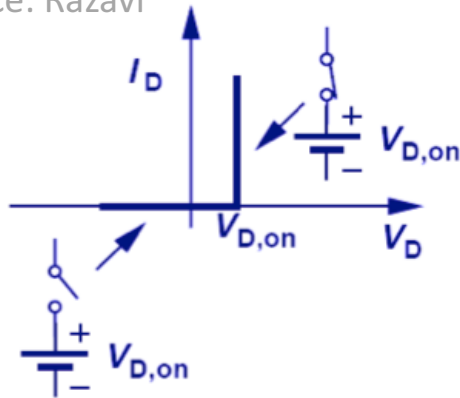


Fig. 2 - Forward Current vs. Forward Voltage

- Constant voltage model:
 - the constant voltage is called cut-in voltage, turn-on voltage, or threshold voltage and is usually denoted as $V_{D,on}$ or V_Y
- This model is based on the observation that a forward-conducting diode has a voltage drop that varies in a relatively narrow range (e.g. 0.6 to 0.8). We'll assume $V_Y \approx 0.7V$
- Below V_Y the current is very small (less than 1% of the maximum rated value).

$$\text{for } T > 25^\circ\text{C} \Rightarrow P_{D,max} = 500 - 1.68 \times (T - 25) [mW]$$



$$T_J = T_A + R_{\theta JA} \times P_D$$

Thermal Characteristics

Characteristic	Symbol	Value	Unit
Power Dissipation (Note 1)	P_D	500	mW
Derate Above 25°C		1.68	mW/°C
Thermal Resistance, Junction to Ambient Air (Note 1)	$R_{\theta JA}$	300	°C/W
Operating and Storage Temperature Range	T_J, T_{STG}	-65 to +175	°C

Ideal diode with voltage offset

source: Neamen

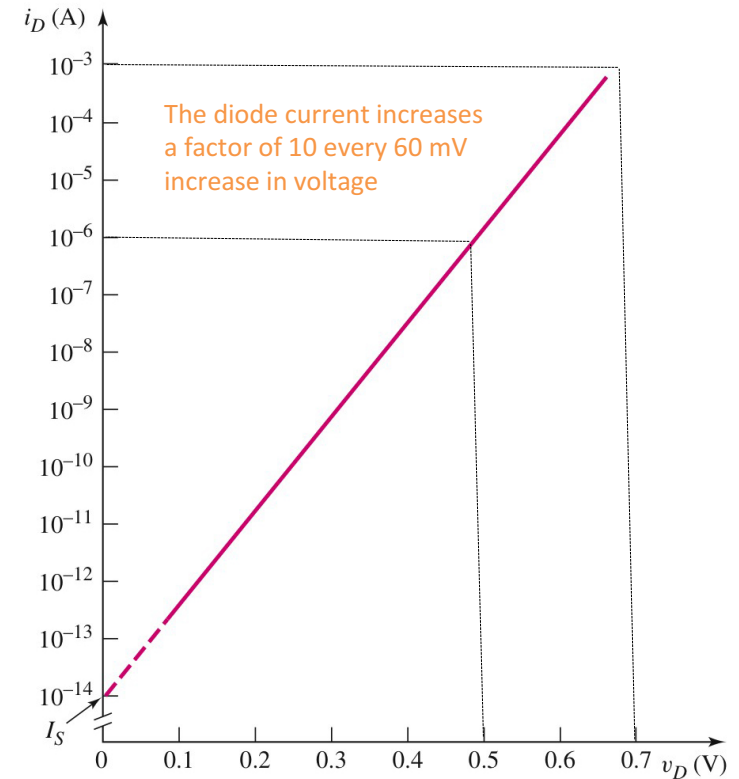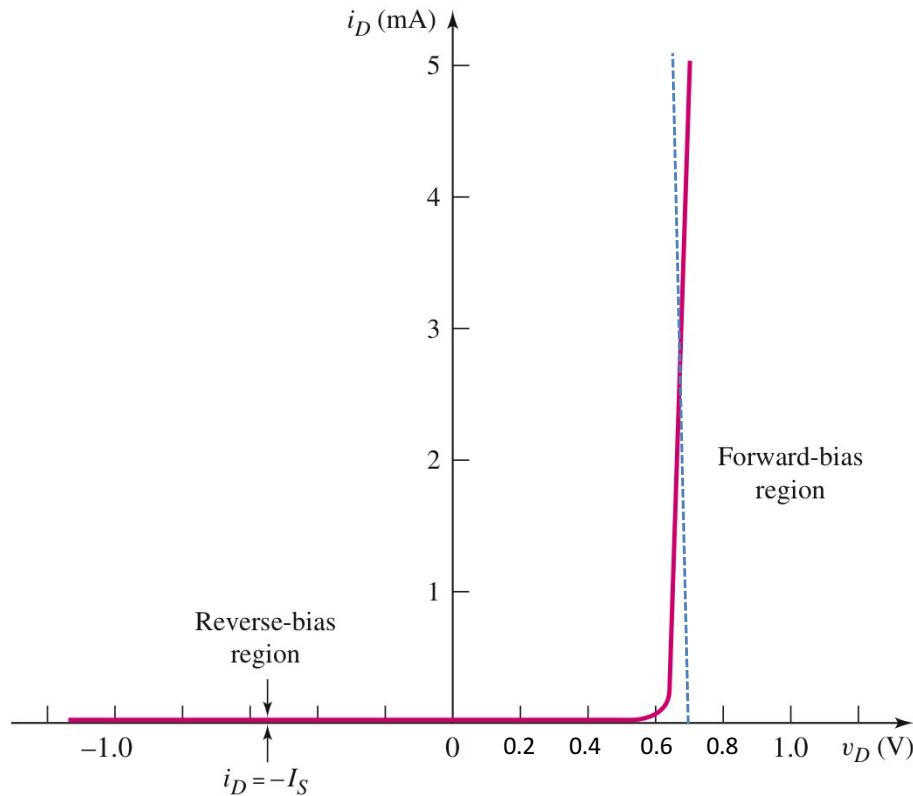

- I/V characteristic of a theoretical diode with $I_S = 10^{-14} \text{ A} = 10 \text{ fA}$

- Forward-bias part of the characteristics with current plotted on a log scale

NOTE: real diodes exhibit reverse currents that are considerably larger than I_S (this is mainly due to holes and electrons being generated within the space charge region). A typical value of reverse-bias current maybe 1nA (still small and negligible in most cases)

Is the model good enough ?

- Should we worry about the fact that the diode has resistance ?

$$r_{diode} = \left(\frac{dI_D}{dV_D} \right)^{-1} = \frac{d}{dV_D} \left[I_S \left(e^{\frac{V_D}{V_T}} - 1 \right) \right]^{-1} = \left(\frac{I_S}{V_T} e^{\frac{V_D}{V_T}} \right)^{-1} = \left(\frac{I_S e^{\frac{V_D}{V_T}} - I_S + I_S}{V_T} \right)^{-1} = \frac{V_T}{I_D + I_S}$$

- Forward Region: $r_{diode} = \frac{V_T}{I_D + I_S} \approx \frac{V_T}{I_D}$ V_T/I_D is only a few Ω
 $I_D \gg I_S$


Example:

$$I_S \approx 10 \text{ fA} \Rightarrow I_D \approx I_S \exp(V_D/V_T) = 10^{-14} \exp(0.7/26\text{m}) \approx 4.9 \text{ mA} \Rightarrow V_T/I_D = 26/4.9 \approx 5.3 \Omega$$

- Reverse Region: $r_{diode} = \frac{V_T}{I_D + I_S} \approx \infty [\Omega]$
 $I_D \approx -I_S$

Ideal Diode


source: Razavi

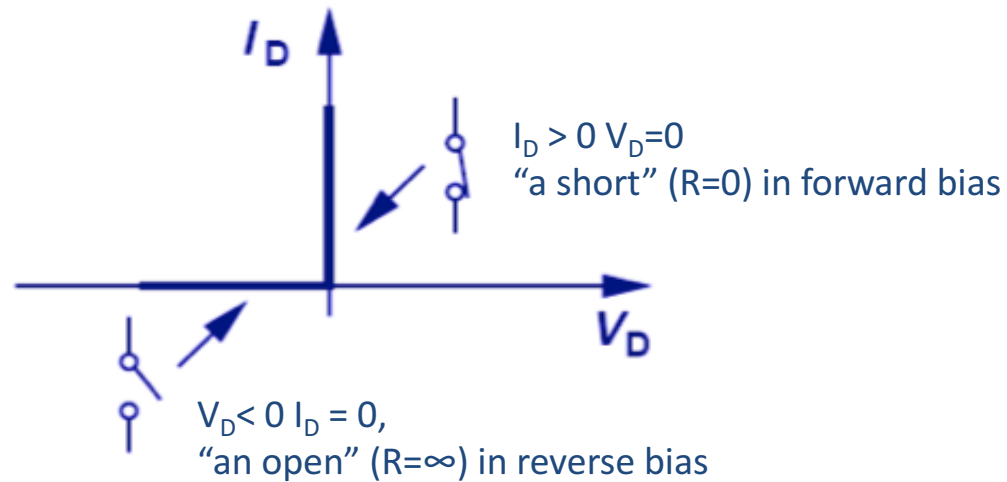

- In applications that involve voltages much greater than the diode voltage drop (0.6V-0.8V) we may neglect the diode voltage drop altogether.

Piecewise linear model

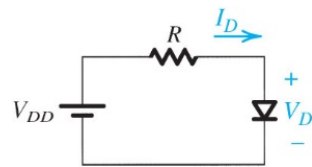- This model is useful when there is a small varying signal superimposed to the biasing voltage
- Let's say we want to forward bias a diode so that it operates at a given value of I_D , we need to find the corresponding V_D (Q = operating point = (I_D, V_D))




$$\begin{cases} I_D = \frac{V_{DD} - V_D}{R} \Leftrightarrow I_D = \frac{V_{DD}}{R} - \frac{V_D}{R} \\ I_D \approx I_S e^{\frac{V_D}{V_T}} \end{cases}$$

KVL = topological eq.

constitutive eq. of device

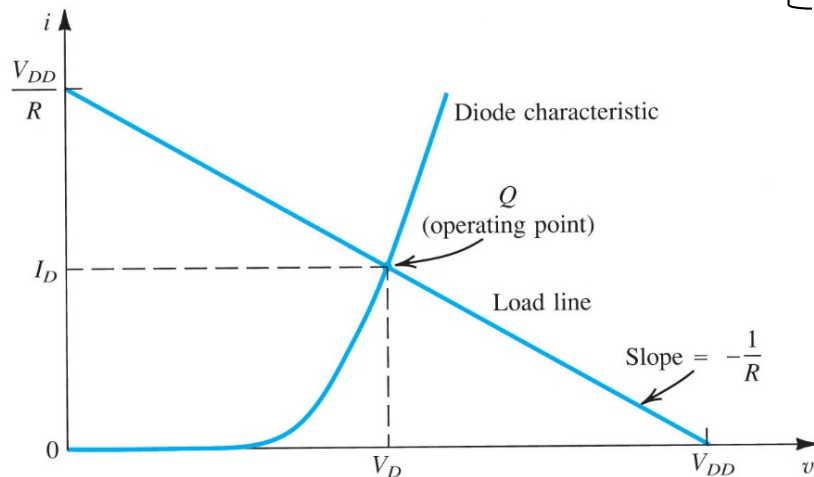This is the eq. of a line (I_D vs. V_D) with slope $-1/R$





NOTE: $\ln(x) = \alpha \cdot \text{Log}(x) \rightarrow \ln(e) = 1 = \alpha \cdot \text{Log}(e) = \alpha \cdot 0.43 \rightarrow \alpha \approx 2.3$

Piecewise linear model

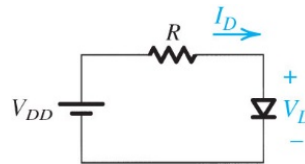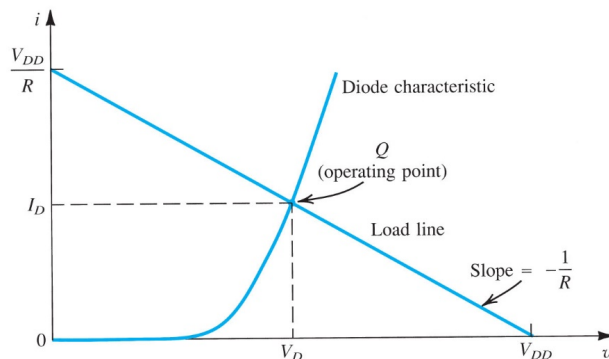Example

We have $V_{DD}=5V$ and the diode at $V_{D0}=0.7V$ has a current of $I_{D0}=1mA$. We want $I_D \approx 4.3mA$.

Let's assume $V_D \approx 0.7V$ (and iterate until we find the right value corresponding to I_D)



$$R = \frac{V_{DD} - V_D}{I_D} = \frac{5 - 0.7}{4.3m} = 1K\Omega$$


A voltage increase of 60 mV corresponds to a 10 x current increase

$$V_{D1} - V_{D0} = 2.3V_T \times \text{Log}\left(\frac{I_{D1}}{I_{D0}}\right) \Rightarrow V_{D1} = V_{D0} + 60mV \times \text{Log}\left(\frac{4.3m}{1m}\right) \approx 0.738V \quad (\text{iteration 1})$$

$$I_{D2} = \frac{V_{DD} - V_{D1}}{R} = \frac{5 - 0.738}{1K} = 4.262mA \quad V_{D2} = V_{D1} + 60mV \times \text{Log}\left(\frac{I_{D2}}{I_{D1}}\right) \approx 0.738 + 60mV \times \text{Log}\left(\frac{4.262m}{4.3m}\right) \approx 0.738V \quad (\text{iteration 2})$$

No further iterations are necessary. The circuit used gives $I_D \approx 4.262mA$ and $V_D \approx 0.738V$

Piecewise linear model

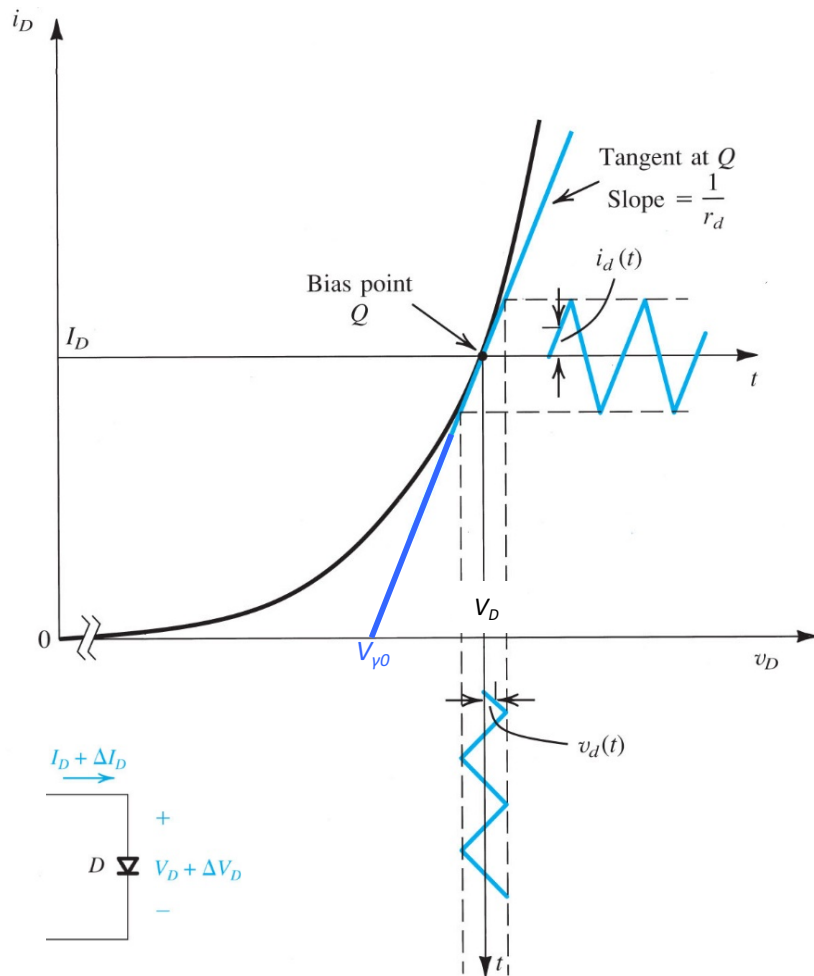

We have a signal superimposed to the bias voltage V_D :

$$v_D = V_D + v_d \Rightarrow v_d = v_D - V_D \equiv \Delta V_D \Rightarrow v_D = V_D + \Delta V_D$$



$$i_D \cong I_S e^{\frac{v_D}{V_T}} = I_S e^{\frac{V_D + \Delta V_D}{V_T}} = I_S e^{\frac{V_D}{V_T}} e^{\frac{\Delta V_D}{V_T}} = I_D e^{\frac{\Delta V_D}{V_T}}$$

If the max excursion of the signal is small (that is $\Delta V_D/V_T \ll 1$):

$$i_D = I_D e^{\frac{\Delta V_D}{V_T}} \approx I_D \left(1 + \frac{\Delta V_D}{V_T} \right)$$

*
$$e^x = 1 + x + \frac{x^2}{2!} + \frac{x^3}{3!} + \dots$$

for $x \ll 1$: $e^x \cong 1 + x$



$$\frac{\Delta V_D}{V_T} \ll 1$$

$$i_D \approx I_D + \frac{I_D}{V_T} \Delta V_D = I_D + g_d \Delta V_D = I_D + \Delta I_D = i_d$$

we find out that the response of the diode is about linear and it make sense to approximate the diode characteristic with the tangent line at Q:


$$\frac{1}{r_d} = g_d = \frac{\Delta I_D}{\Delta V_D} = \frac{i_d}{v_d} = \left. \frac{di_D}{dv_D} \right|_{@V_D}$$

Piecewise linear model

Equation of line
given two points:

$$y - y_0 = m(x - x_0)$$
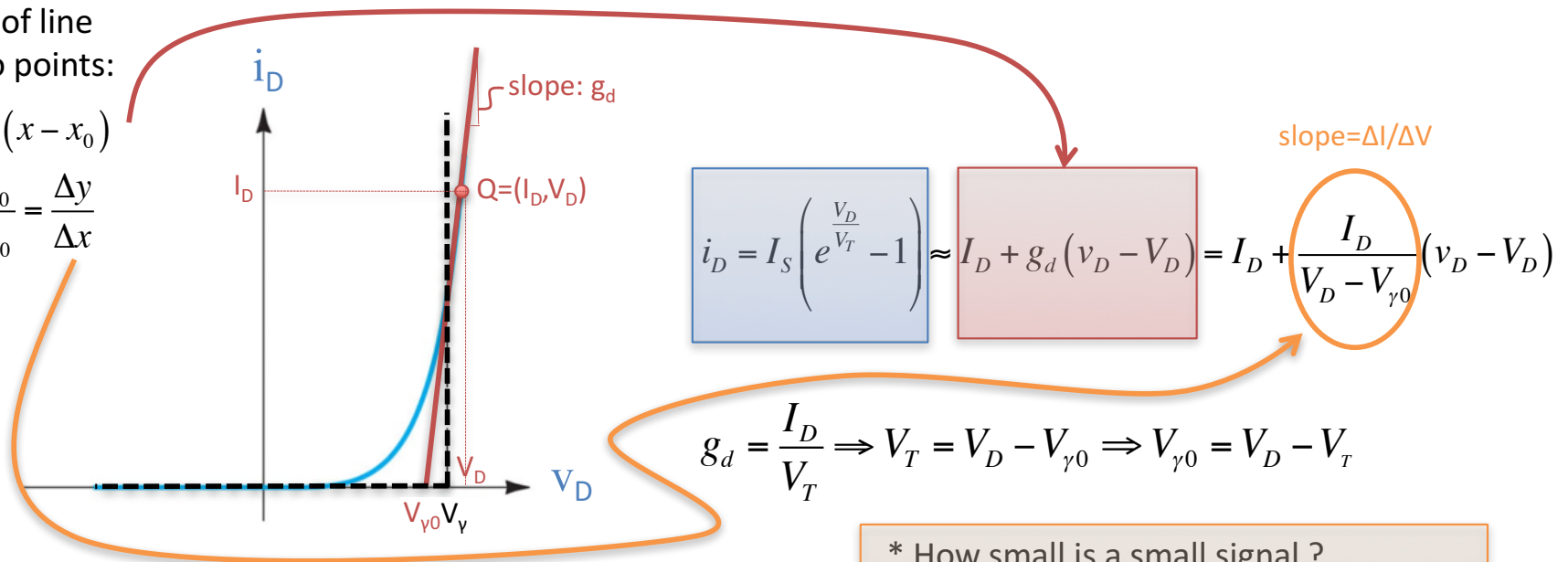
$$m = \frac{y_1 - y_0}{x_1 - x_0} = \frac{\Delta y}{\Delta x}$$



$$g_d = \frac{I_D}{V_T} \Rightarrow V_T = V_D - V_{\gamma 0} \Rightarrow V_{\gamma 0} = V_D - V_T$$

alternatively:

$$y = mx + n \Rightarrow i_D \approx \frac{v_D}{r_d} - \frac{V_{\gamma 0}}{r_d}$$

$$y(\bar{x}) \equiv 0 = m\bar{x} + n \Rightarrow n = -m\bar{x}$$

* How small is a small signal ?

$$e^x \approx 1 + x$$

The error of the approx. should
be $\leq 10\%$

$$\text{Error} = e^x - 1 - x \leq 0.1$$

Solving numerically we see that for
 $x \leq 0.4$ the error is ≤ 0.09

$$\frac{\Delta V_D}{V_T} \leq 0.4 \Rightarrow \Delta V_D \leq 26mV \times 0.4 \approx 10.4mV$$

Diode Circuits

- ... Finally let's start building some circuit
- Applications:
 - Rectifiers
 - Limiting Circuits (a.k.a. Clippers)
 - Level Shifters (a.k.a. Clampers)
 - Detectors
 - Voltage doublers
 - Regulators
 - Switches