
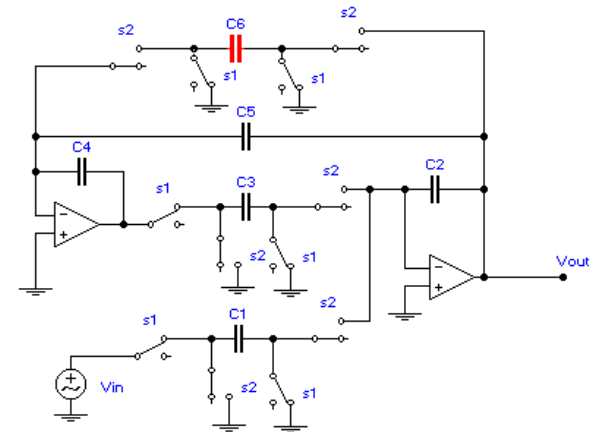
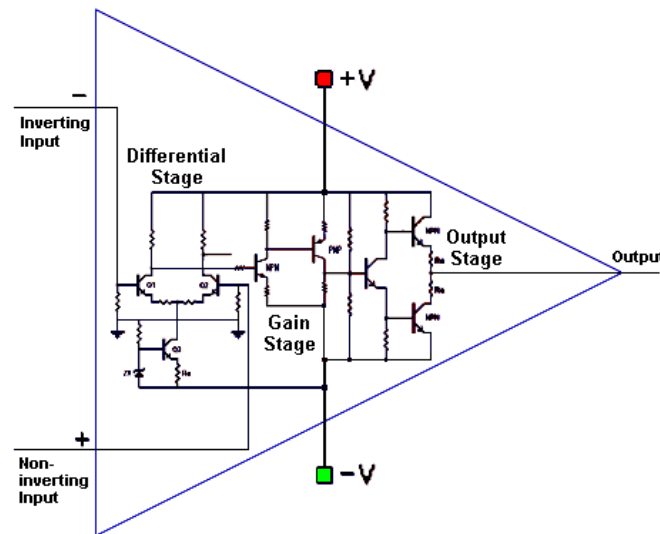


Differential Pair


**Claudio Talarico, Gonzaga University
Fall 2014**

Significance of the Differential Pair

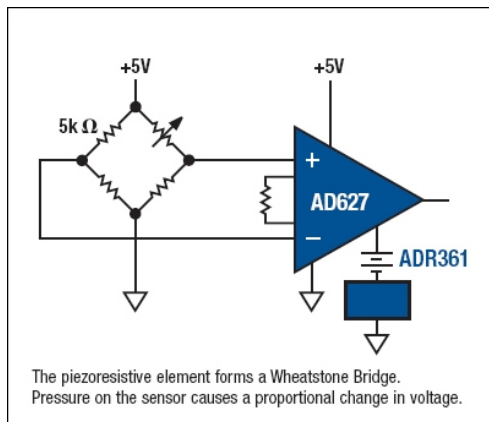- The differential pair is the most widely used two-transistor circuit in integrated circuits
 - Many circuits rely on the “computation” of the difference between two voltages



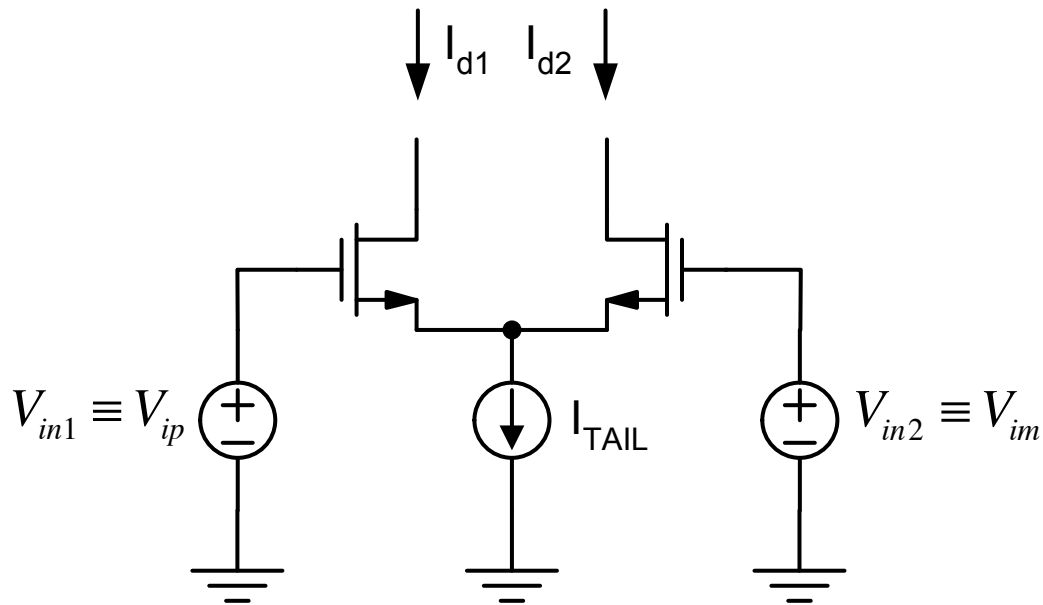General Analysis of the Differential Pair




- When $V_{ip} = V_{im}$, and both transistors are identical, we must have $I_{d1} = I_{d2} = I_{TAIL}/2$
- How about $V_{ip} = V_{im} = 1V$ versus $V_{ip} = V_{im} = 2V$?
 - Makes no difference !
- From a signal perspective, we care only about the difference of the applied voltages
 - Makes sense to introduce a new variable:
 - $V_{id} = V_{ip} - V_{im}$


Differential Mode and Common Mode (1)

- Differential Mode \longleftrightarrow Signal
- Common Mode \longleftrightarrow Bias

source: Razavi

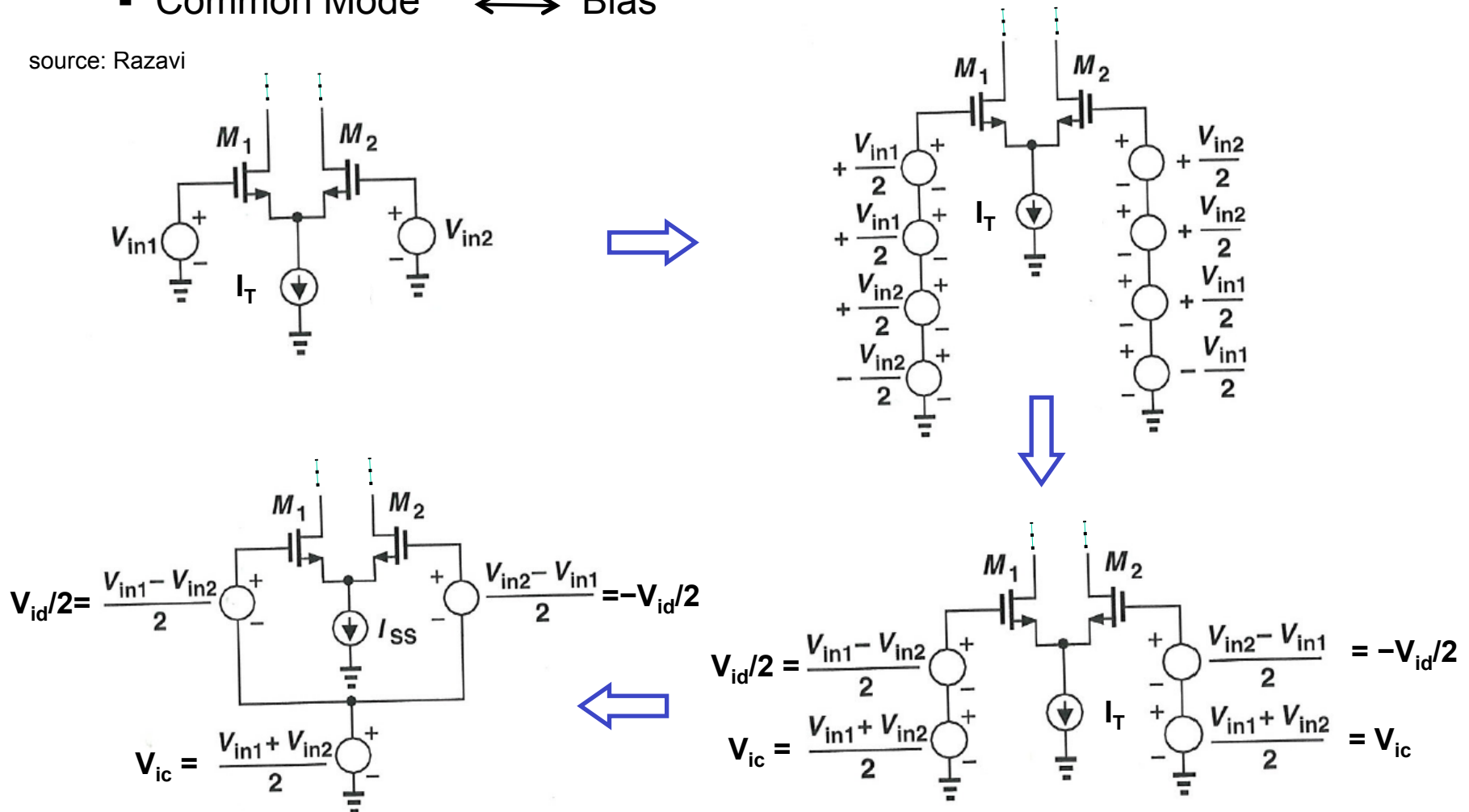

Differential Mode and Common Mode (2)

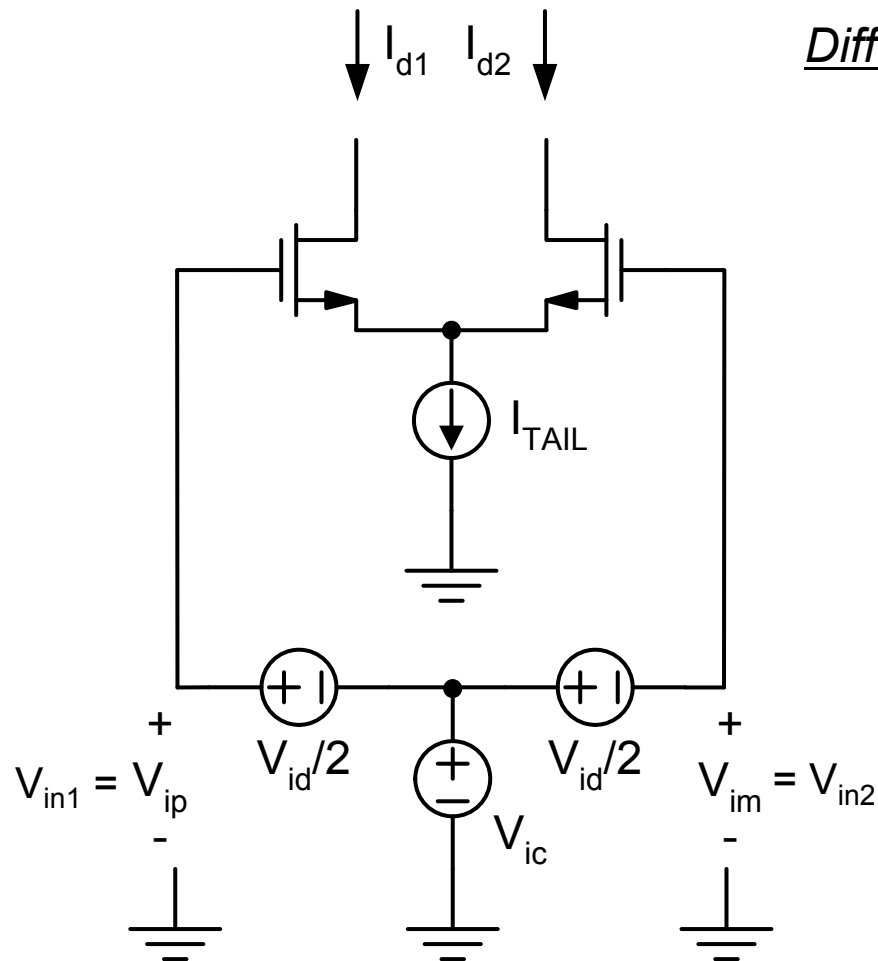

Difference

$$V_{id} = V_{ip} - V_{im}$$

$$V_{ip} = V_{ic} + \frac{V_{id}}{2}$$


$$V_{im} = V_{ic} - \frac{V_{id}}{2}$$

Average


$$V_{ic} = \frac{V_{ip} + V_{im}}{2}$$

Differential Signaling and Coupling Noise Immunity

Single Ended Signaling

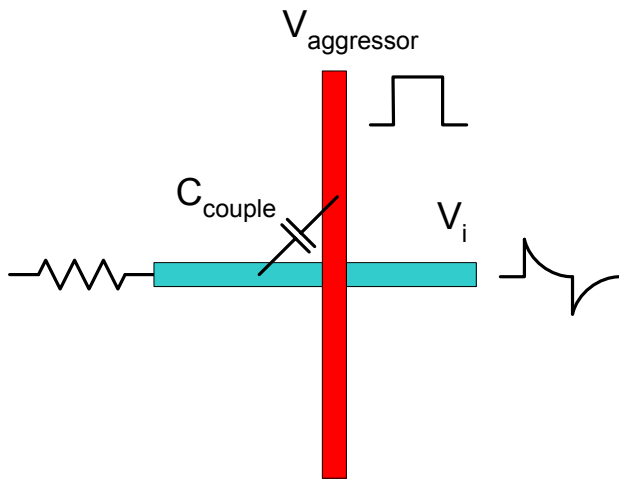


Differential Signaling

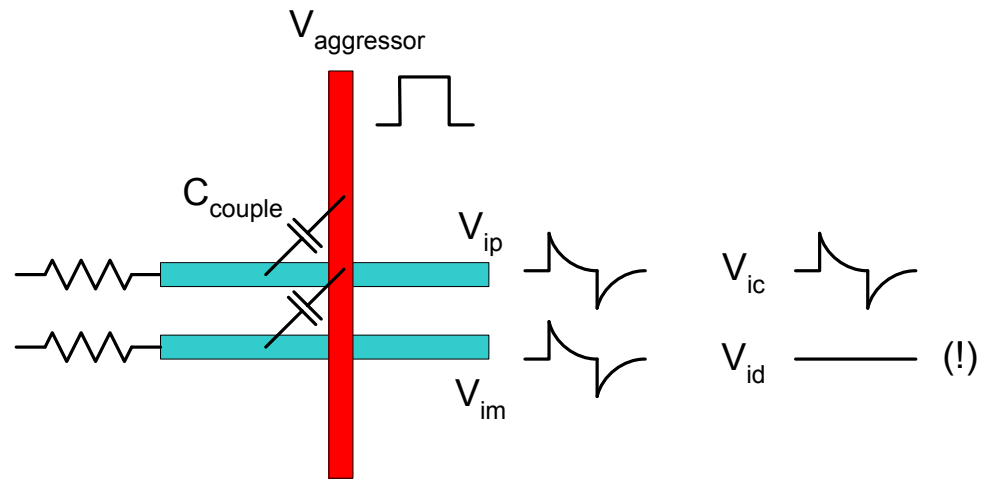

Similar arguments can be made regarding the rejection of supply variation, ground bounce, etc.

Differential Pair Bias (Common Mode Bias)

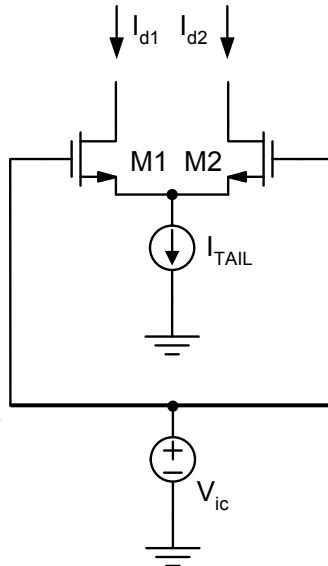- We are interested in the range of input DC bias (V_{IC}) over which the differential pair operates properly



- The highest value of V_{IC} ($= V_{ICmax}$) is limited by the requirement that M_1 and M_2 remain in saturation

$$V_{GS} - V_t < V_{DS} = V_D - V_{IC} + V_{GS} \iff V_{IC} < V_t + V_D$$

$$V_{IC} < V_t + V_{DD} - \frac{I_{TAIL}}{2} R$$


- The lowest value of V_{IC} ($= V_{ICmin}$) is determined by the need to have sufficient voltage across the tail current source for it to operate properly (M_{TAIL} in saturation)

$$V_{IC} > V_t + V_{OV} + V_{OVTAIL}$$

Large Signal Transfer Function (1)

$$V_{ip} - V_{gs1} = V_{im} - V_{gs2} \Leftrightarrow V_{id} \equiv V_{ip} - V_{im} = V_{gs1} - V_{gs2}$$

$$I_{d1} + I_{d2} = I_{TAIL}$$

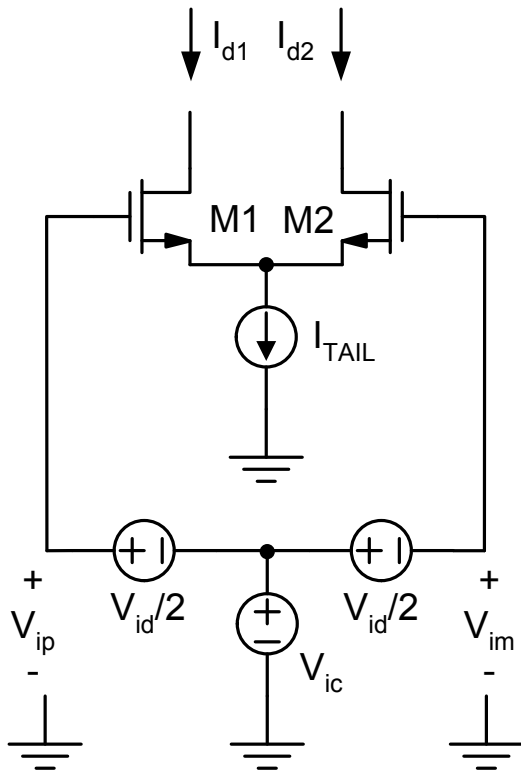

$$V_{gs1} = V_t + \underbrace{\sqrt{\frac{2I_{d1}}{\mu C_{ox} \frac{W}{L}}}}_{= V_{OV1}}$$

$$V_{gs2} = V_t + \underbrace{\sqrt{\frac{2I_{d2}}{\mu C_{ox} \frac{W}{L}}}}_{= V_{OV2}}$$

$$V_{id} = \frac{\sqrt{I_{d1}} - \sqrt{I_{d2}}}{\sqrt{\frac{\mu C_{ox} W}{2L}}}$$

* see aside for the "algebra"

$$I_{od} = I_{d1} - I_{d2} = \frac{1}{2} \mu C_{ox} \frac{W}{L} V_{id} \sqrt{\frac{4I_{TAIL}}{\mu C_{ox} \frac{W}{L}} - V_{id}^2}$$

Aside *

Square both terms of the following equation and solve the resulting second order equation (for the unknown $\sqrt{I_{d1}}$)

$$V_{id} = \frac{\sqrt{I_{d1}} - \sqrt{I_{d2}}}{\sqrt{\frac{\mu C_{ox} W}{2L}}}$$

$$I_{d2} = I_{TAIL} - I_{d1}$$

➔

$$I_{d1} = \frac{I_{TAIL}}{2} + \frac{\mu C_{ox} W}{4L} V_{id} \sqrt{\frac{4I_{TAIL}}{\mu C_{ox} W} - V_{id}^2}$$

$$I_{d2} = \frac{I_{TAIL}}{2} - \frac{\mu C_{ox} W}{4L} V_{id} \sqrt{\frac{4I_{TAIL}}{\mu C_{ox} W} - V_{id}^2}$$

for $V_{id} > 0 \rightarrow I_{d1}$ must be $> I_{TAIL}/2$ (and I_{d2} must be $<$ than $I_{TAIL}/2$ by the same amount)

for $V_{id} = 0 \rightarrow I_{d1} = I_{d2} = I_{TAIL}/2$

Large Signal Transfer Function (2)

- We can turn this into a more elegant expression by using

$$\frac{I_{TAIL}}{2} = \frac{1}{2} \mu C_{ox} \frac{W}{L} V_{OV}^2$$

where V_{OV} is the quiescent point gate overdrive with $V_{id}=0$

$$\frac{I_{od}}{I_{TAIL}} = \frac{I_{d1} - I_{d2}}{I_{TAIL}} = \frac{V_{id}}{V_{OV}} \sqrt{1 - \left(\frac{V_{id}}{2V_{OV}} \right)^2}$$


↓

With $V_{id}=0$:
 $I_{d1}=I_{d2}=I_{TAIL}/2$
 $V_{OV} \equiv \sqrt{\frac{I_{TAIL}}{\mu C_{ox} \frac{W}{L}}}$

- This equation predicts
 - $I_{od}/I_{TAIL} = 0$ when $V_{id}=0$, as expected
 - Complete current steering ($I_{od}/I_{TAIL} = \pm 1$) takes place when $V_{id} = \pm V_{OV} \sqrt{2}$

Large Signal Plot

- Note that the equation on previous slide is only valid in the center of this transfer function (that is for $|V_{id}| \leq \sqrt{2} V_{OV}$)
 - The equation assume both M_1 and M_2 are in saturation

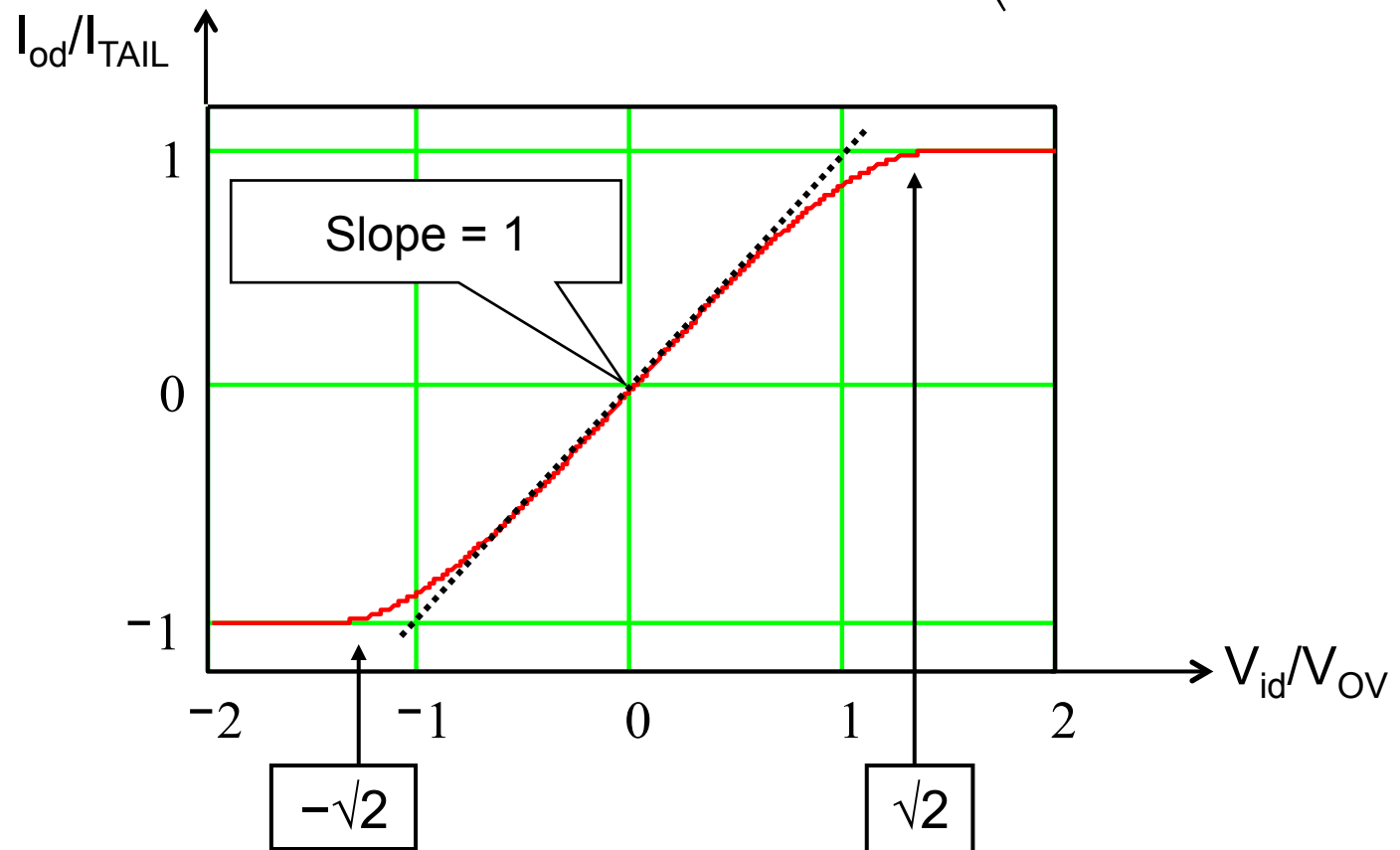

Observations

- The large Signal TF Looks like something we have seen before
 - A transfer function that is somewhat linear as long as $V_{id} \ll 2 V_{OV}$

$$\frac{I_{od}}{I_{TAIL}} = \frac{I_{d1} - I_{d2}}{I_{TAIL}} = \frac{V_{id}}{V_{OV}} \sqrt{1 - \left(\frac{V_{id}}{2V_{OV}}\right)^2} \approx \frac{V_{id}}{V_{OV}}$$

- For small signal analysis, we can find an equivalent transconductance by differentiation at the operating point

$$G_m = \left. \frac{dI_{od}}{dV_{id}} \right|_{V_{id}=0} = \frac{I_{TAIL}}{V_{OV}}$$


- Note that the transconductance of M_1 and M_2 is given by

$$g_{m1,2} = \frac{2I_D}{V_{OV}} = \frac{2 \frac{I_{TAIL}}{2}}{V_{OV}} = \frac{I_{TAIL}}{V_{OV}}$$

Linearity range of the differential pair

- To increase the linearity range ($V_{id} \ll 2 V_{OV}$) of a differential pair we need to increase V_{OV}
 - V_{OV} can be adjusted by changing W/L ratio or I_{TAIL}
 - For a fixed I_{TAIL} to increase V_{OV} we have to reduce the W/L ratio \rightarrow the price is a reduction in g_m ($g_m = \text{slope of } I_{od} \text{ vs. } V_{id} \text{ T.F. plot}$). A reduction in g_m causes a reduction in gain
 - For obtaining a higher g_m the bias current I_{TAIL} can be increased \rightarrow the cost is an increase in power consumption

source: GHLM p. 219

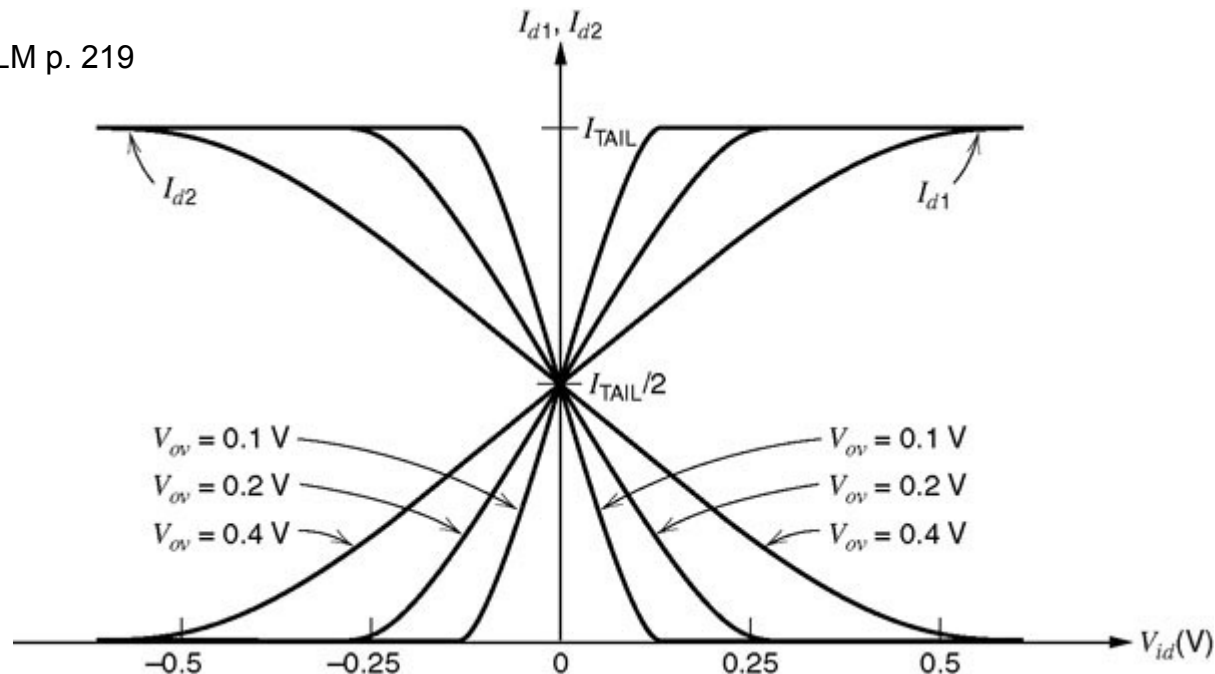

“Linear” Region of Transfer Function

- The requirement for “linear” T.F. can be generalized as follows to capture both long and short channel cases simultaneously:

$$V_{id} \ll \frac{2}{\left(\frac{g_m}{I_{TAIL}}\right)}$$

- A few approximate rule of thumbs:
 - For ~ 1.5% non linearity error

$$V_{id} < 0.5 \frac{2}{\left(\frac{g_m}{I_{TAIL}}\right)}$$

- For ~ 0.1% non linearity error

$$V_{id} < 0.2 \frac{2}{\left(\frac{g_m}{I_{TAIL}}\right)}$$

Another convenient property of the differential pair


- If M_1 and M_2 are identical and identical resistors are connected to the drains of M_1 and M_2 when $V_{id}=0$ then $I_{d1} - I_{d2} = 0$. This shows that when $V_{id}=0$ (no signal applied) then $V_{od}=0$ ($V_{od1} = V_{od2} = V_{DD} - R \cdot I_{TAIL}/2$)
- This property allows direct coupling (no coupling capacitors) and biasing of cascaded MOS differential pairs

Does the Tail Node X Move?

$$KVL@V_X \Rightarrow V_X = V_{ic} + \frac{V_{id}}{2} - V_{gs1} = V_{ic} + \frac{V_{id}}{2} - V_t - \sqrt{\frac{2I_{d1}}{\mu C_{ox} \frac{W}{L}}}$$

Can show that:
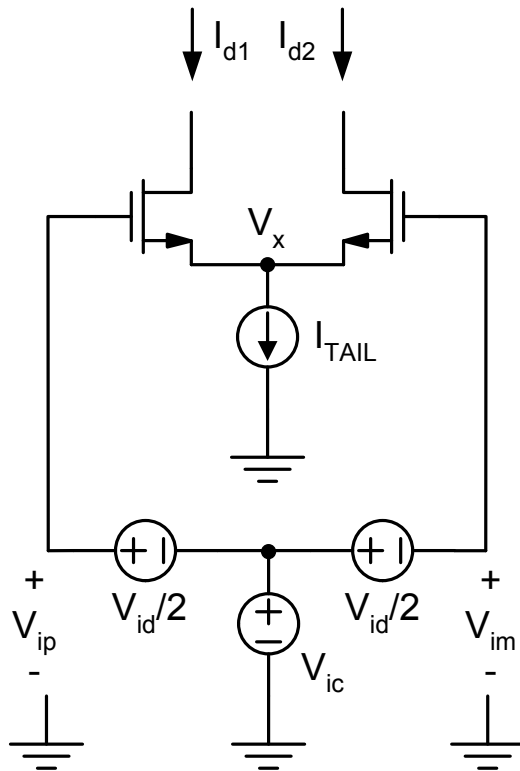
$$V_x = V_{ic} - V_t - V_{OV} \sqrt{1 - \left(\frac{V_{id}}{2V_{OV}}\right)^2}$$




- From this expression, we see that from a small signal perspective the tail node is pinned at $V_{ic} - V_t - V_{OV}$ – "AC ground"

Aside: A detailed look at the large signal DM TF (1)

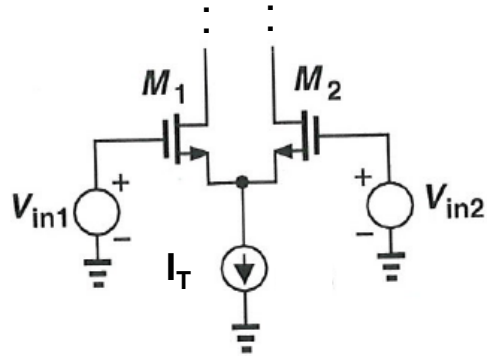Example:


$V_{DD} = 5V$; $I_T = 600\mu A$;
 $W/L = 21.33\mu m / 1\mu m$;
 $R_L = 5K\Omega$; ($V_{IC} = 2.5V$)




- $V_{id} = V_{in1} - V_{in2}$
- $V_{ic} = (V_{in1} + V_{in2})/2$
- $V_{od} = V_{o1} - V_{o2}$

Vid	M1	M2
$V_{id} < -1.19$	off	lin.
$-1.19 < V_{id} < -0.65$	sat	lin.
$-0.65 < V_{id} < 0.65$	sat.	sat.
$0.65 < V_{id} < 1.19$	lin.	sat
$V_{id} > 1.19$	lin.	off

M1, M2 operation – 1um Technology

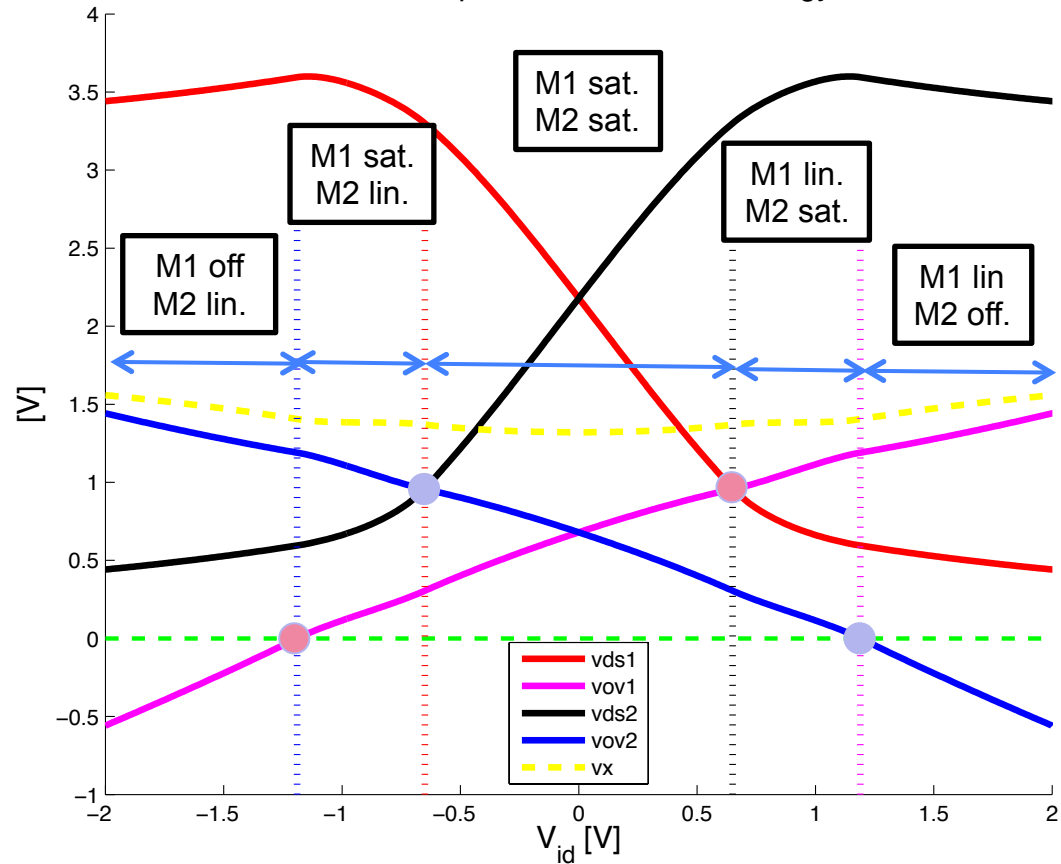

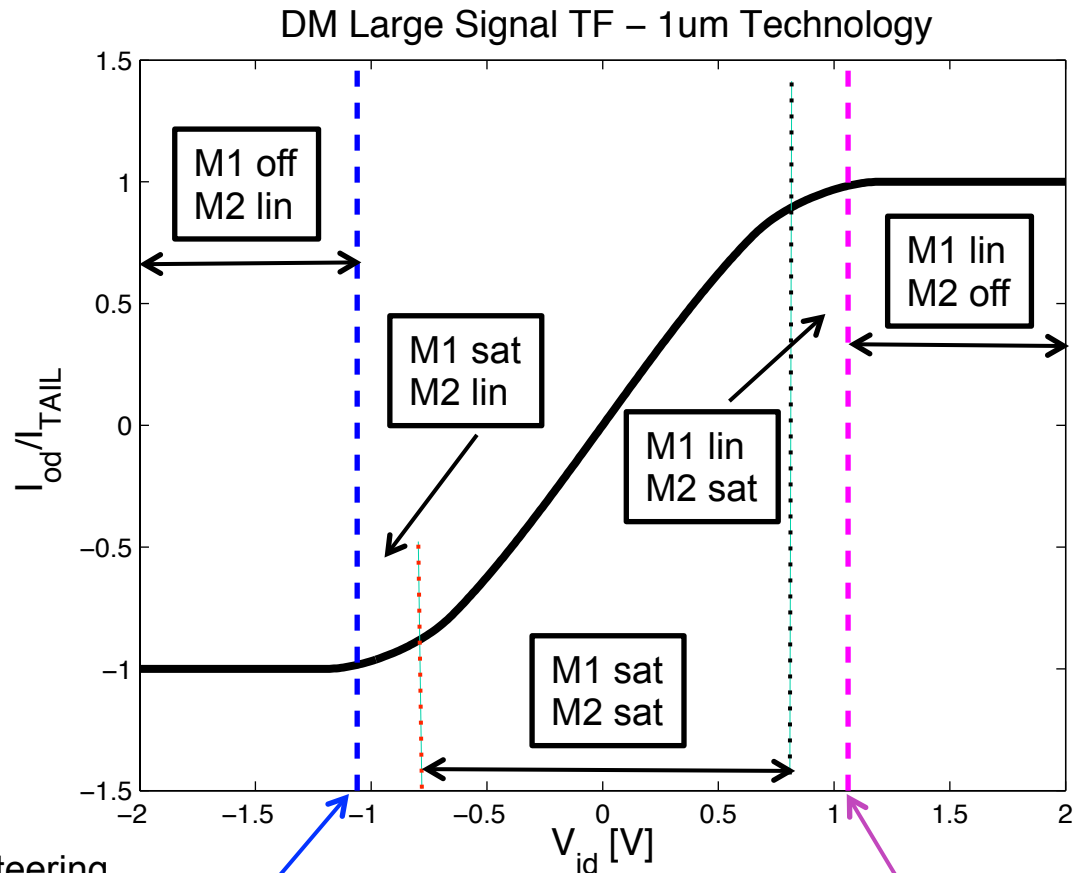Aside: A detailed look at the large signal DM TF (2)



$\approx -V_{OV,eq} \sqrt{2} (= -1.1V)$

$\approx +V_{OV,eq} \sqrt{2} (= +1.1V)$

complete current steering ($I_{od}/I_{TAIL} = \pm 1$) takes place when $V_{id} \approx \pm V_{OV,eq} \sqrt{2}$

approximate assumption:
 one MOST is in sat.,
 and the other one is
 at the edge of cut off

$$V_{OV,eq} = (V_{GS} - V_{TH})|_{V_{id}=0} = \sqrt{\frac{I_{TAIL}}{\mu C_{OX} \frac{W}{L}}} \quad (= 750mV)$$

Aside: spice netlist

```
*
* ideal_dp.sp
* no backgate effect and ideal tail
*

* include models
.include ~/hspice_libs/ee114_hspice.mod

.option post brief accurate

* ideal balun
* example instantiation
* x1 vdm vcm vp vm balun
.subckt balun vdm vcm vp vm
e1 vp vcm transformer vdm 0 2
e2 vcm vm transformer vdm 0 2
.ends balun

* circuit
vdd vdd 0 5
vic vic 0 DC 2.5
vid vid 0 AC 1 DC=0

x1 vid vic vip vim balun
x2 vod voc vop vom balun
rdum vod 0 1gig * cannot leave the node floating

it vx 0 600u

m1 vop vgp vx vx nmos114 W=21.33u L=1u
m2 vom vgm vx vx nmos114 W=21.33u L=1u
RLp vdd vop 5K
RLm vdd vom 5K
CLp vop 0 50f
CLm vom 0 50f
RSp vip vgp 10k
RSm vim vgm 10k
```

```
* analysis and measurements
.OP
.ac dec 100 1e6 1e12
.pz v(vod) vid
.dc vid -5 5 0.01

.measure AC GDC find VDB(vod) at 1Meg
.measure AC ADC find V(vod) at 1Meg
.measure AC F3DB when VDB(vod)='GDC - 3'

.probe i(m1) i(m2) vth(m1) vth(m2) vdsat(m1) vdsat(m2)
.probe vgs(m1) vgs(m2) vds(m1) vds(m2)

* double check transistors' regions of operation
.alter
vid vid 0 AC=1 DC=-2 * M1 off, M2 linear
.alter
vid vid 0 AC=1 DC=-900m * M1 sat, M2 linear

.end
```

Aside: script to plot the simulation results (1)

```
%
% file: plot_ideal_dp.m
%
clear all; close all;
format short eng

addpath('/usr/local/MATLAB/HspiceToolbox');

% technology
RL = 5e3; IT=600e-6; vdd = 5; vt0 = 0.5;
W = 21.33e-6; L=1e-6; KP=50e-6;

figure(1)
y = loadsig('./spiceout/ideal_dp.sw0');
lssig(y)
vid = evalsig(y, 'v_vid');
vod = evalsig(y, 'v_vod');
vds1 = evalsig(y, 'vds_m1');
vds2 = evalsig(y, 'vds_m2');
vth1 = evalsig(y, 'vth_m1');
vth2 = evalsig(y, 'vth_m2');
vgs1 = evalsig(y, 'vgs_m1');
vgs2 = evalsig(y, 'vgs_m2');
vov1 = vgs1 - vth1;
vov2 = vgs2 - vth2;
vx = evalsig(y, 'v_vx');
i1 = evalsig(y, 'i_m1');
i2 = evalsig(y, 'i_m2');
iod = i1-i2;
iod_it = iod/IT;
VOV_eq = sqrt(L*IT/KP/W)
plot(vid, iod_it, 'linewidth',3, 'color', 'k', 'linestyle', '-');
xlim([-2 2]);
pointA = -sqrt(2)*VOV_eq
pointB = sqrt(2)*VOV_eq
% vertical lines
line([pointA pointA], [-1.5 1.5], 'linestyle', '--', ...
     'linewidth', 2, 'color', 'b');
line([pointB pointB], [-1.5 1.5], 'linestyle', '--', ...
     'linewidth', 2, 'color', 'm');
xlabel('V_{id} [V]', 'FontSize', 14);
ylabel('I_{od}/I_{TAIL} ', 'FontSize', 14);
title('DM Large Signal TF - 1um Technology', 'fontsize', 14);

figure(2)
hold on;
xlim([-2 2]);
plot(vid, vds1, 'linewidth',3, 'color', 'r', 'linestyle', '-');
plot(vid, vov1, 'linewidth',3, 'color', 'm', 'linestyle', '-');
plot(vid, vds2, 'linewidth',3, 'color', 'k', 'linestyle', '-');
plot(vid, vov2, 'linewidth',3, 'color', 'b', 'linestyle', '-');
plot(vid, vx, 'linewidth',3, 'color', 'y', 'linestyle', '--');
% horizontal line at 0
line([-2 2], [0 0], 'linestyle', '--', ...
     'linewidth', 2, 'color', 'g');
legend('vds1', 'vov1', 'vds2', 'vov2', 'vx', 'location', 'south');
xlabel('V_{id} [V]', 'FontSize', 14);
ylabel(' [V]', 'FontSize', 14);
title('M1, M2 operation - 1um Technology', 'fontsize', 14);
```


to be continued ...

Aside: script to plot the simulation results (2)

```
% compute operating regions for M1
for i=1:length(vid)
    if vov1(i) > 0
        index = i;
        break
    end
end
% M1 exit cut off and enters saturation
M1off2sat = vid(index-1)
for i=1:length(vid)
    if vds1(i) < vov1(i)
        index = i;
        break
    end
end
% M1 exit saturation and enters triode
M1sat2triode = vid(index-1)
% vertical lines for M1
line([M1off2sat M1off2sat], [-1 3], 'linestyle', ':', ...
     'linewidth', 3, 'color', 'b');
line([M1sat2triode M1sat2triode], [-1 3], 'linestyle', ':', ...
     'linewidth', 3, 'color', 'k');


% compute operating regions for M2
for i=1:length(vid)
    if vds2(i) > vov2(i)
        index = i;
        break
    end
end
% M2 exit triode and enters saturation
M2triode2sat = vid(index)
for i=1:length(vid)
    if vov2(i) < 0
        index = i;
        break
    end
end
% M2 exit saturation and enters triode
M2sat2off = vid(index)
% vertical lines for M2
line([M2triode2sat M2triode2sat], [-1 3], 'linestyle', ':', ...
     'linewidth', 3, 'color', 'r');
line([M2sat2off M2sat2off], [-1 3], 'linestyle', ':', ...
     'linewidth', 3, 'color', 'm');
```

Small Signal Equivalent

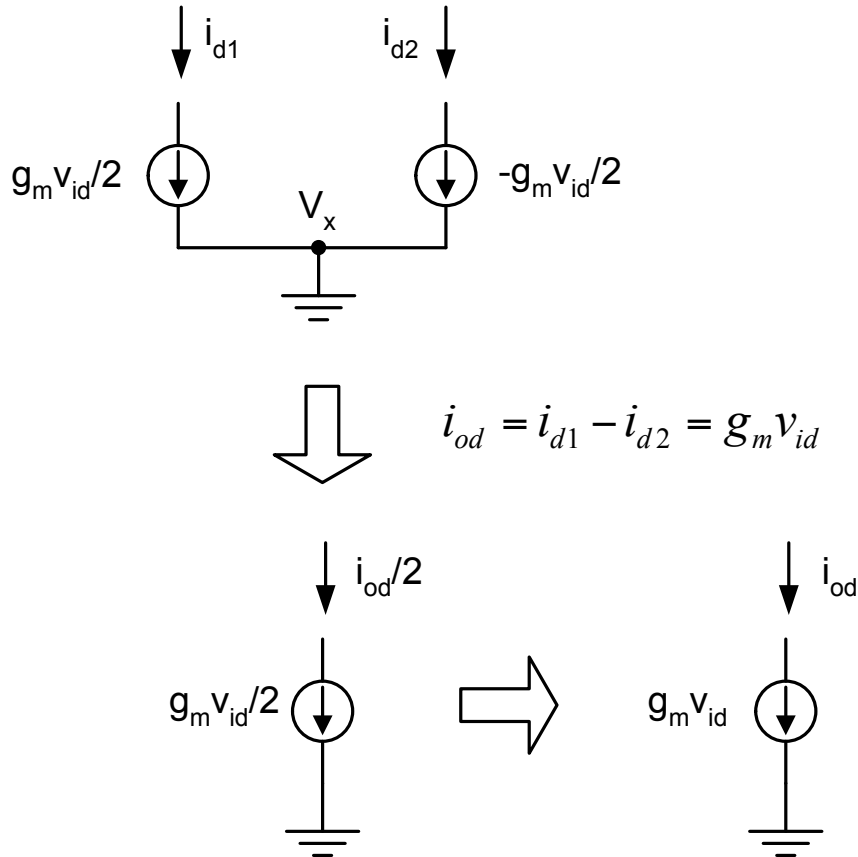

- It is sufficient to work with half circuit!
 - Can directly apply everything we've learned about single transistor stage
- Half circuit caveats
 - Cannot analyze nonlinearity using half circuits
 - Assumes that M_1 and M_2 are identical

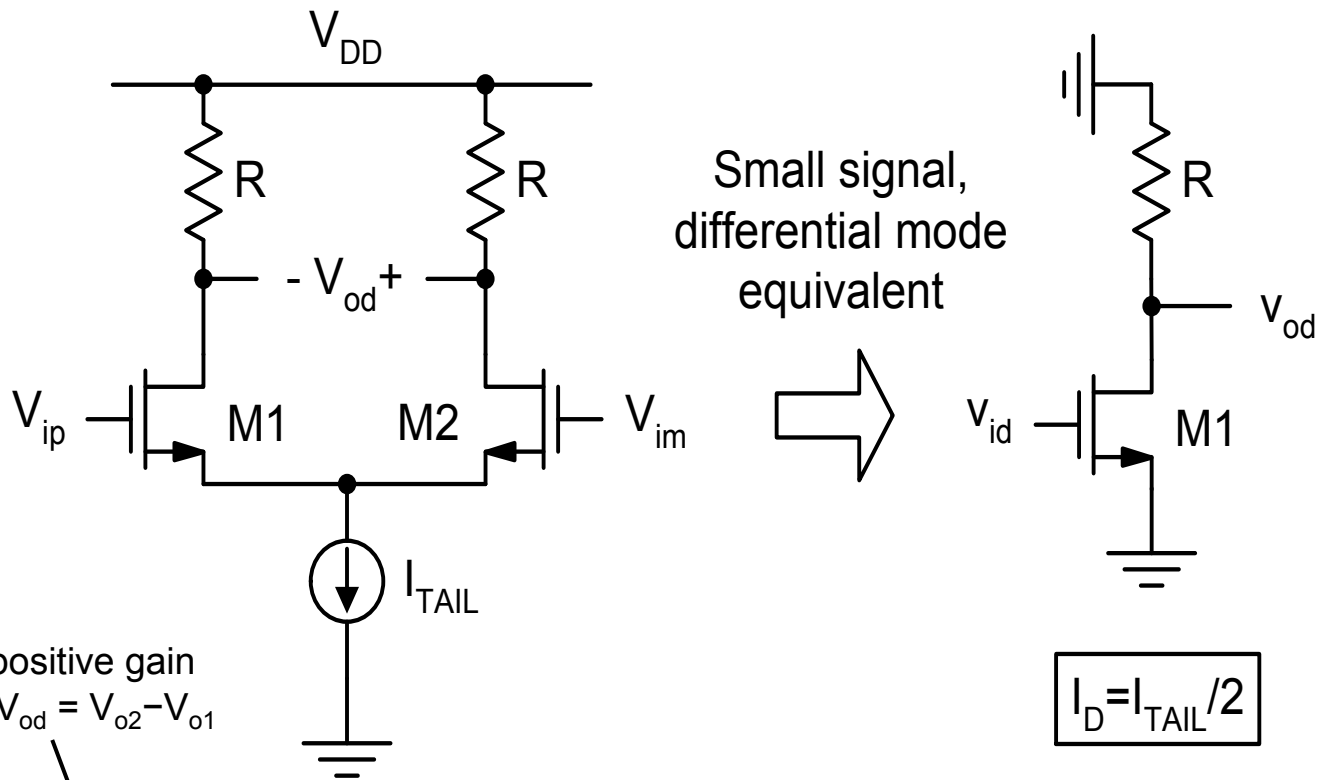Basic Differential Voltage Amplifier Example



NOTE:
to get positive gain
chose $V_{od} = V_{o2} - V_{o1}$

$$A_{dm} = \frac{v_{od}}{v_{id}} = g_m (R \parallel r_o) \approx g_m R$$


$$R_{in-dm} = \infty$$

$$R_{out-dm} = 2 \cdot (R \parallel r_o)$$

Observations

- Obtained same amount of gain as a CS stage
- Used twice as many “components” as we used for a CS stage (not a big deal since we plan to build the amplifier inside an IC)
- Used twice as much current
 - To get the same g_m a CS stage need to spend only $I_{TAIL}/2$
- The use of the tail current source makes $I_{D1}+I_{D2}$ independent of V_{IC}
 - The role of the tail current source is to suppress the effect of input common level variations on the operation of M_1 and M_2 and the output levels ($V_{O1} = V_{O2} = V_{DD} - R * I_{TAIL}/2$)
 - The circuit rejects input CM variations (the node V_X absorbs the changes !)
- In the case the output is taken between the two drains, the resulting differential output is entirely a signal component (0 DC component → $V_{OD} = 0$ V)
- The differential pair has high immunity to noise and fluctuations

Differential Pair: Design Example

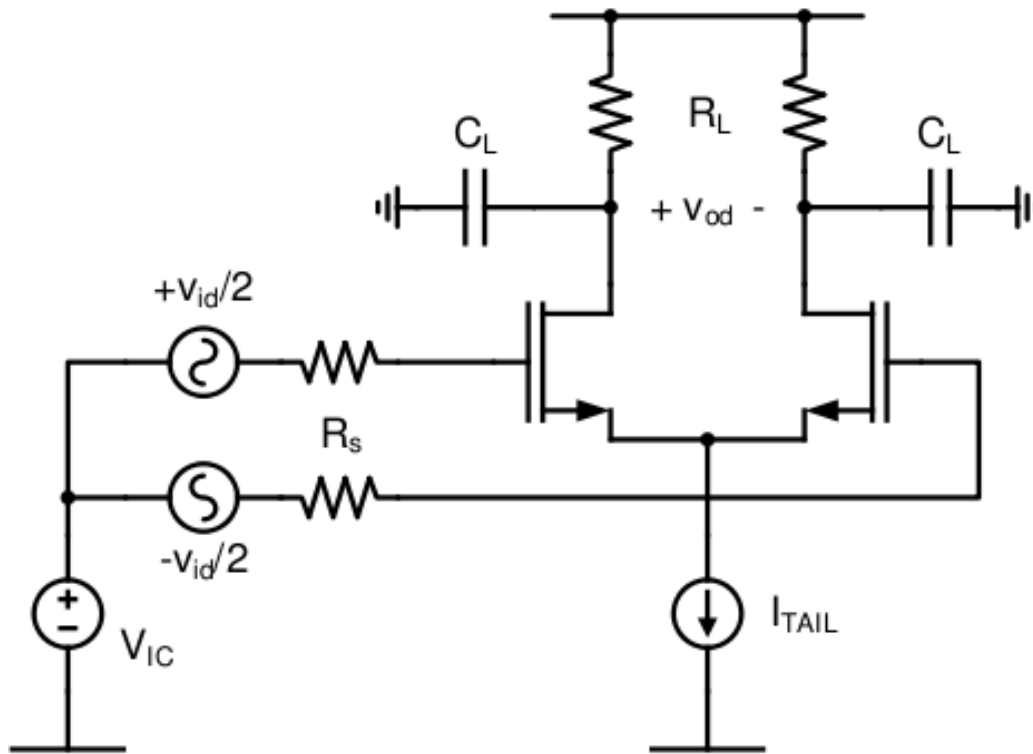

- Specifications:
 - 0.18 μm technology
 - $A_{v0} = -4$
 - $R_L = 1\text{K}\Omega$
 - $R_S = 10\text{K}\Omega$
 - $C_L = 50\text{fF}$
 - $I_{TAIL} \leq 600\mu\text{A}$
 - ($V_{IC} = 1\text{V}$)
- Maximize BW

MATLAB design script – 180nm technology

```

%
% gm/ID design of diff pair
% file: design_gmid_dp.m
%
clear all; close all;
addpath('~\gmid_starterkit_2014');
load 180n.mat;

% Specs.
Av0 = 4; RL=1e3; CL=50e-15; RS=10e3; IT=600e-6;
VDD=1.8;
% DC spec.
VIC = 1

% Calculations
VOUT = VDD - RL*IT/2
gm = Av0/RL
gm_id = gm/(IT/2)
wT = lookup(nch, 'GM_CGG', 'GM_ID', gm_id)
cgd_cgg = lookup(nch, 'CGD_CGG', 'GM_ID', gm_id)
cdd_cgg = lookup(nch, 'CDD_CGG', 'GM_ID', gm_id)
cgg = gm/wT
cgd = cgd_cgg*cgg
cdd = cdd_cgg*cgg
cdb = cdd - cgd
cgs = cgg - cgd

% pole calculations
b1 = RL*CL + cgs*RS + cgd*(RS+RL+gm*RL*RS)
% b1 = coeff of s in den. of Av(s)
fp1 = 1/b1/2/pi
b2 = RS*RL*(cgs*CL + cgs*cgd + CL*cgd)
% b2 = coeff of s^2 in den. of Av(s)
fp2 = 1/2/pi*b1/b2

% device sizing
id_w = lookup(nch, 'ID_W', 'GM_ID', gm_id)
W = IT/2 / id_w

```

```

%
% tail design sizing
%
% Relevant Equations:
%  $V_x = V_{IC} - V_{TH} - V_{OV}\sqrt{1-0.25*(V_{id}/V_{OV})^2}$ 
%  $VX = V_{IC} - V_{TH} - V_{OV}$  (=  $V_{IC} - V_{GS}$ )

% Lookup VGS with unknown source voltage
% transistor sits on the tail node
VDB1 = VOUT;
VGB1 = VIC;
VGS1 = lookupVGS(nch, 'GM_ID', gm_id, 'VDB', VDB1, 'VGB', VGB1)
VX = VIC - VGS1
VDS1 = VOUT - VX


LT = 0.36e-6;
VDST = VX
VSBT = 0;
% pick gm_id such that vod-vdsat = 10%*vod
for gm_id = 5:0.5:20
    VGST = lookupVGS(nch, 'GM_ID', gm_id, 'VDS', VDST, 'VSB',
VSBT, 'L', LT);
    VTHT= lookup(nch, 'VT', 'VGS', VGST, 'VDS', VDST, 'VSB',
VSBT, 'L', LT);
    VODT = VGST - VTHT;
    VDSATT = lookup(nch, 'VDSAT', 'VGS', VGST, 'VDS', VDST,
'VSB', VSBT, 'L', LT);
    ERROR = VODT - VDSATT;
    if ERROR <= 0.1*VODT
        ERROR
        gm_idT = gm_id - 0.5
        break
    end
end

VGST = lookupVGS(nch, 'GM_ID', gm_idT, 'VDS', VDST, 'VSB',
VSBT, 'L', LT)
id_wT = lookup(nch, 'ID_W', 'GM_ID', gm_idT, 'L', LT)
WT = IT/id_wT


```

Aside: Ideal Balun

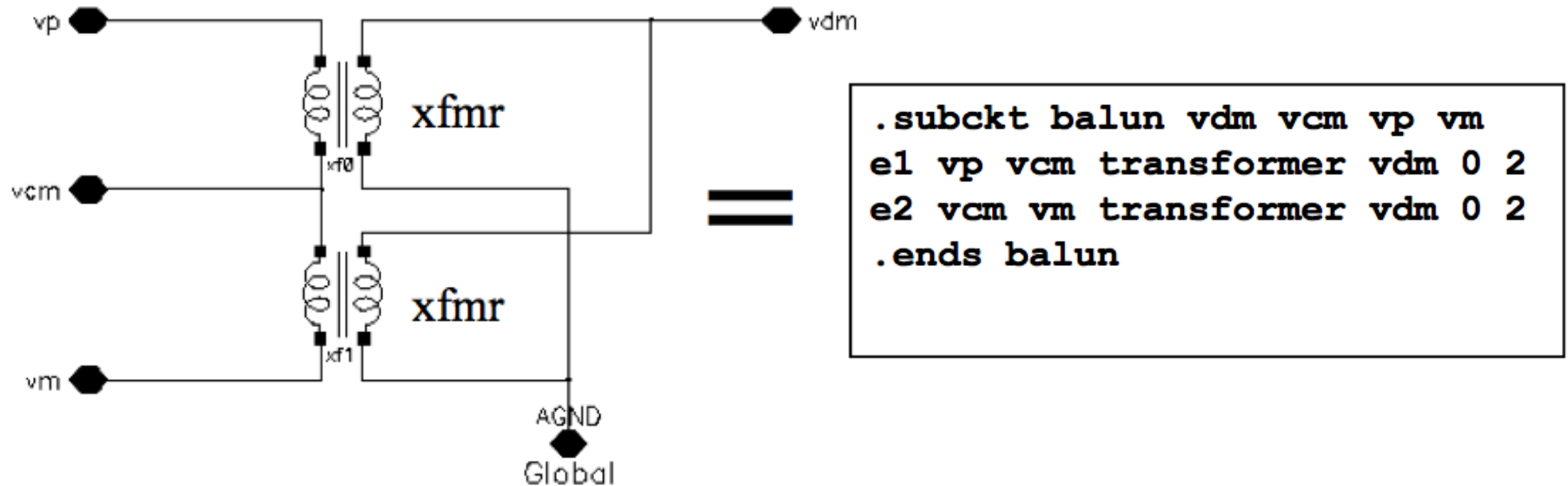- Useful for separating CM and DM signal components
- Bidirectional, preserves port impedance
- Uses ideal, inductor-less transformers that works down to DC



Circuit

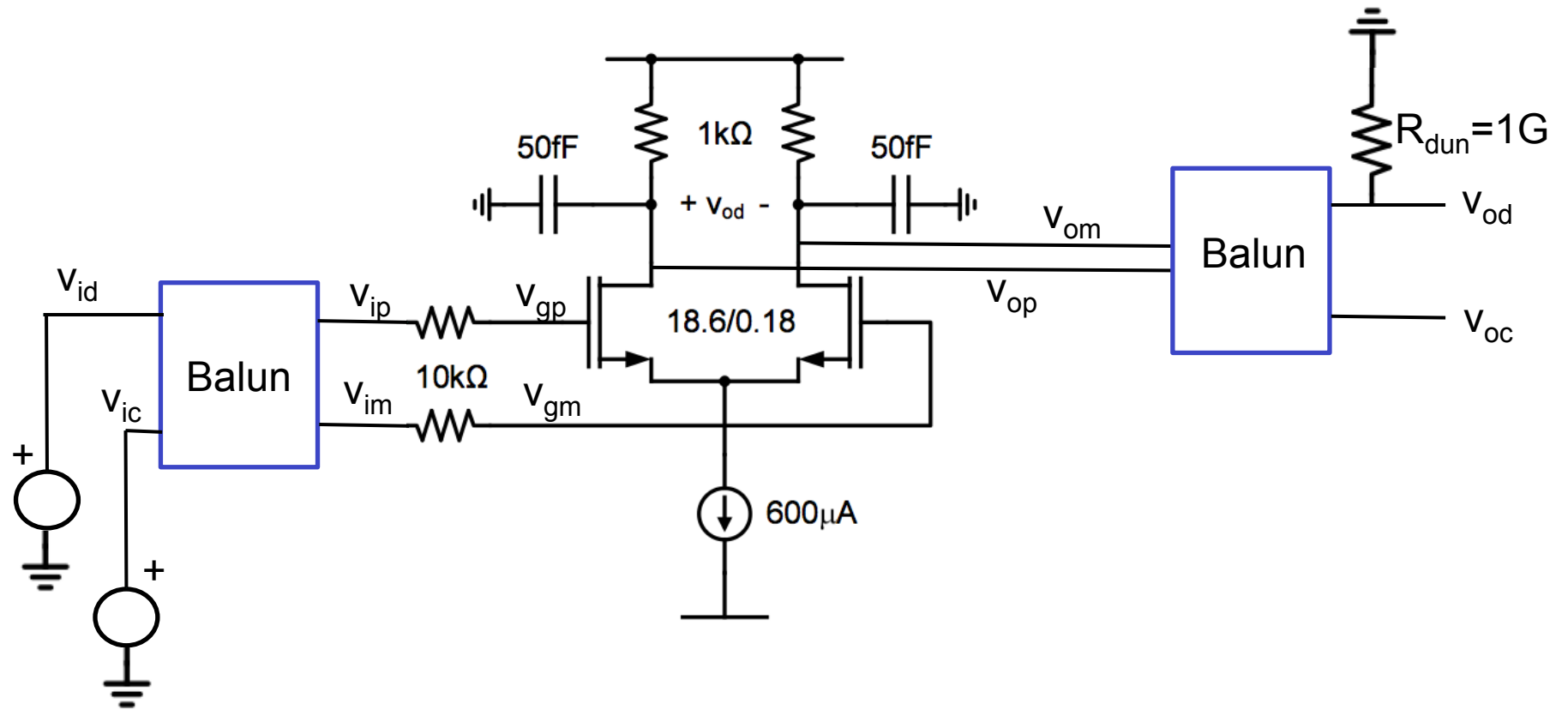

Circuit Netlist

```
* gmid_dp.sp

* include models
.include ~/hspice_libs/ee214_hspice.mod

.option post brief accurate

* circuit
vdd vdd 0 1.8
vic vic 0 DC 1
vid vid 0 AC 1
x1 vid vic vip vim balun
x2 vod voc vop vom balun
rdun vod 0 1gig * cannot leave the node floating
it vx 0 600u

m1p vop vgp vx 0 nmos214 W=18.64u L=0.18u
m1m vom vgm vx 0 nmos214 W=18.64u L=0.18u
RLp vdd vop 1K
RLm vdd vom 1K
CLp vop 0 50f
CLm vom 0 50f
RSp vip vgp 10K
RSm vim vgm 10K

* analysis and measurements
.OP
.ac dec 100 1e6 1e12
.pz v(vod) vid

.measure AC GDC find VDB(vod) at 1Meg
.measure AC ADC find V(vod) at 1Meg
.measure AC F3DB when VDB(vod)='GDC - 3'

.alter tail_transistor
vb vb 0 DC 569m
it vx 0 0
MT vx vb 0 0 nmos214 W=150.25u L=0.36u

.end
```

Simulated Operating Point (w/ ideal tail)

```
vx = 317.6774m
element  0:m1p      0:m1m
model    0:nmos214 0:nmos214
region   Saturati Saturati
id       300.0000u 300.0000u
ibs      0.        0.
ibd      0.        0.
vgs      682.3226m 682.3226m
vds      1.1823    1.1823
vbs      -317.6774m -317.6774m
vth      564.5355m 564.5355m
vdsat    109.0106m 109.0106m
vod      117.7872m 117.7872m
beta     37.3394m  37.3394m
gam eff  583.8502m 583.8502m
gm       4.0749m   4.0749m
gds      101.0427u  101.0427u
gmb      887.8890u   887.8890u
cdtot    20.8733f   20.8733f
cgtot    37.5590f   37.5590f
cstot    42.3251f   42.3251f
cbtot    31.5833f   31.5833f
cgs      26.8412f   26.8412f
cgd      8.9865f   8.9865f
```

Good Agreement !

Computed Values:

$$g_m = 4\text{mS}$$

$$c_{dd} = 22.71\text{ fF}$$

$$c_{gg} = 37.91\text{ fF}$$

$$c_{gd} = 8.98\text{ fF}$$

$$W = 18.66\text{ }\mu\text{m}$$

Simulated Operating Point (w/ MOST tail)

vx = 319.5041m

element	0:m1p	0:m1m	0:mt
model	0:nmos214	0:nmos214	0:nmos214
region	Saturati	Saturati	Saturati
id	291.6595u	291.6595u	583.3190u
ibs	0.	0.	0.
ibd	0.	0.	0.
vgs	680.4959m	680.4959m	569.0000m
vds	1.1888	1.1888	319.5041m
vbs	-319.5041m	-319.5041m	0.
vth	564.9171m	564.9171m	464.3768m
vdsat	107.7501m	107.7501m	94.1598m
vod	115.5789m	115.5789m	104.6232m
beta	37.3394m	37.3394m	132.1440m
gam eff	583.8442m	583.8442m	585.5913m
gm	4.0091m	4.0091m	9.6468m
gds	99.0495u	99.0495u	151.6471u
gmb	873.4055u	873.4055u	2.6084m
cdtot	20.8607f	20.8607f	190.2633f
cgtot	37.5273f	37.5273f	487.0294f
cstot	42.2759f	42.2759f	544.7463f
cbtot	31.5606f	31.5606f	353.6086f
cgs	26.8026f	26.8026f	385.1031f
cgd	8.9867f	8.9867f	71.5793f

Good Agreement !

Computed Values:

ID1 = 300 uA

IDT = 600 uA

gm1 = 4mS

cdd1 = 22.71 fF

cgg1 = 37.91 fF

cgd1 = 8.98 fF

W1 = 18.66 um

WT = 150.25 um

Plotting HSPICE results in MATLAB

```
%
% file: plot_gmid_dp.m
%
clear all; close all;
format short eng

addpath('/usr/local/MATLAB/HspiceToolbox');
y = loadsig('./spiceout/gmid_dp.ac0');
lssig(y)

figure(1);
freq = evalsig(y, 'HERTZ');
vod = evalsig(y, 'v_vod');
magdb = 20*log10(abs(vod));
phase = 180*unwrap(angle(vod))/pi;
semilogx(freq, magdb, 'linewidth', 2, 'color', 'b',
'linestyle', '-');
grid on;
ylabel(' Magnitude [dB]', 'FontSize', 16);
xlabel(' Frequency [Hz]', 'FontSize', 16);
xmin = 1e6;
xmax = 1e12;
xlim([xmin xmax]);
av0 = abs(vod(1))
av0db = magdb(1)
f3db = interp1(magdb, freq, magdb(1)-3, 'spline')
% Annotate title
str1 = sprintf('AC Response (ideal tail)\n');
str2 = sprintf('|gain| = %0.3g dB (%0.3g); f_{3db}
= %3.2f MHz', av0db, av0, f3db*1e-6);
str = {str1, str2};
title(str, 'fontsize', 16);
```


```
x = loadsig('./spiceout/gmid_dp.ac1');
lssig(x)

figure(2);
freq = evalsig(x, 'HERTZ');
vod = evalsig(x, 'v_vod');
magdb = 20*log10(abs(vod));
phase = 180*unwrap(angle(vod))/pi;
semilogx(freq, magdb, 'linewidth', 2, 'color', 'b',
'linestyle', '-');
grid on;
ylabel(' Magnitude [dB]', 'FontSize', 16);
xlabel(' Frequency [Hz]', 'FontSize', 16);
xmin = 1e6;
xmax = 1e12;
xlim([xmin xmax]);
av0 = abs(vod(1))
av0db = magdb(1)
f3db = interp1(magdb, freq, magdb(1)-3, 'spline')
% Annotate title
str1 = sprintf('AC Response (with tail transistor)
\n');
str2 = sprintf('|gain| = %0.3g dB (%0.3g); f_{3db}
= %3.2f MHz', av0db, av0, f3db*1e-6);
str = {str1, str2};
title(str, 'fontsize', 16);
```


Simulated AC Response (w/ ideal tail)

AC Response (ideal tail)

|gain| = 11.4 dB (3.7); $f_{3db} = 213.92$ MHz

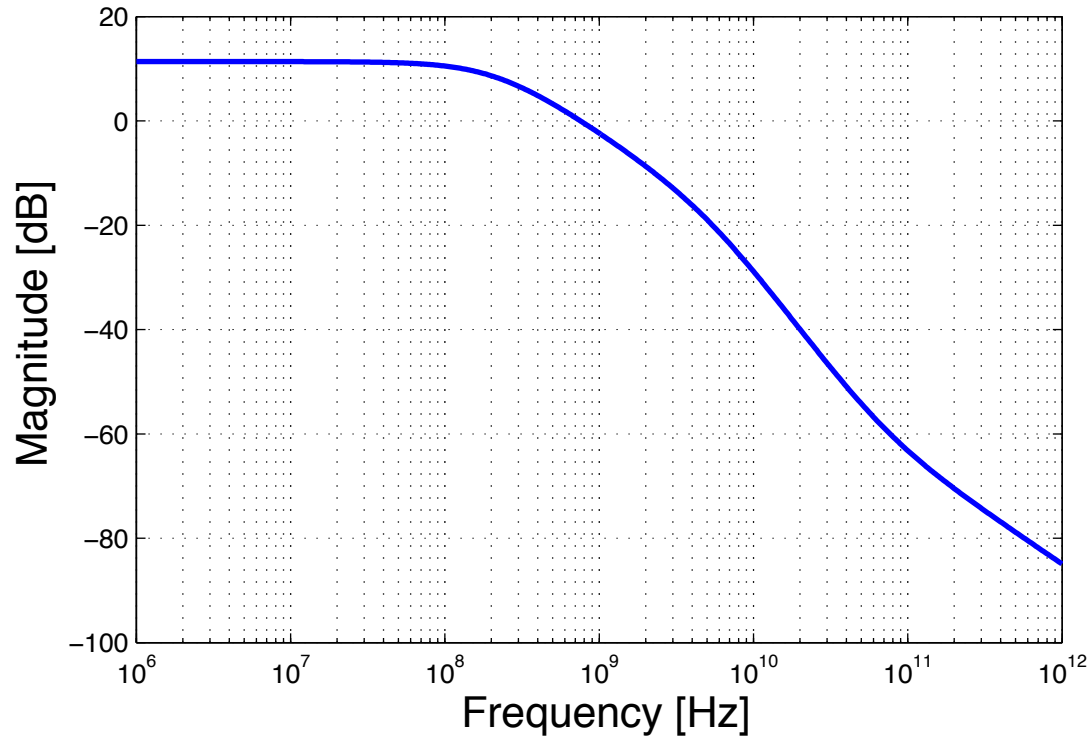


poles (hertz)	
real	imag
-214.807x	0.
-5.03309g	0.

- Calculated values:
|gain|=12 dB (=4); fp1=199.66 MHz; fp2=5.89GHz

Simulated AC Response (w/ MOST tail)

AC Response (with tail transistor)

|gain| = 11.2 dB (3.65); $f_{3db} = 215.43$ MHz

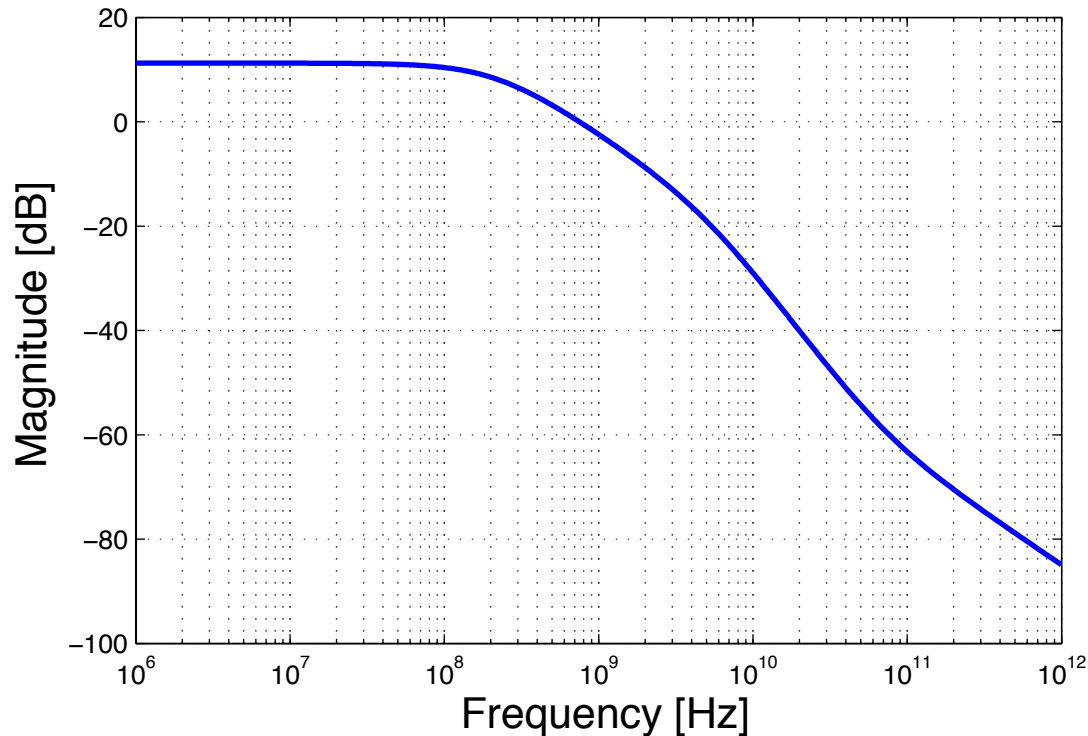


poles (hertz)	
real	imag
-216.335x	0.
-4.99376g	0.

- Calculated values:
|gain|=12 dB (=4); fp1=199.66 MHz; fp2=5.89GHz

Voltage Amplifier Transfer Functions

NOTE: $V_{od} = V_{o2} - V_{o1}$

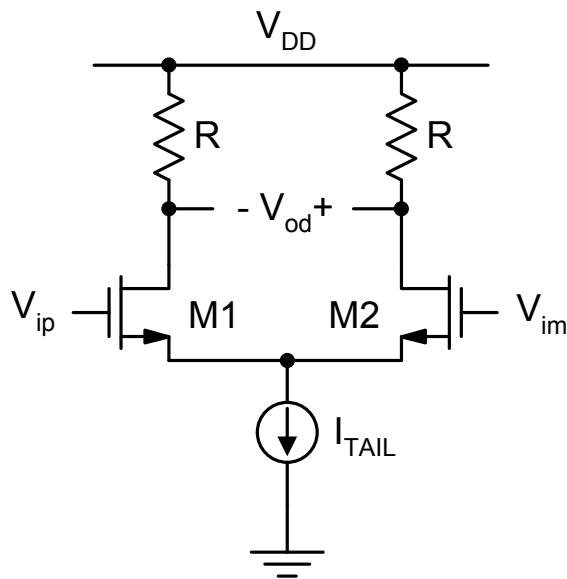


- In a differential amplifier, we primarily want to have large gain that links only the two differential variables

$$A_{dm} = \frac{V_{od}}{V_{id}}$$

- Unfortunately, circuit non-idealities will also cause nonzero "parasitic" gain terms

$$A_{cm} = \frac{V_{oc}}{V_{ic}} \quad A_{dm-cm} = \frac{V_{oc}}{V_{id}} \quad A_{cm-dm} = \frac{V_{od}}{V_{ic}}$$

Common Mode Gain

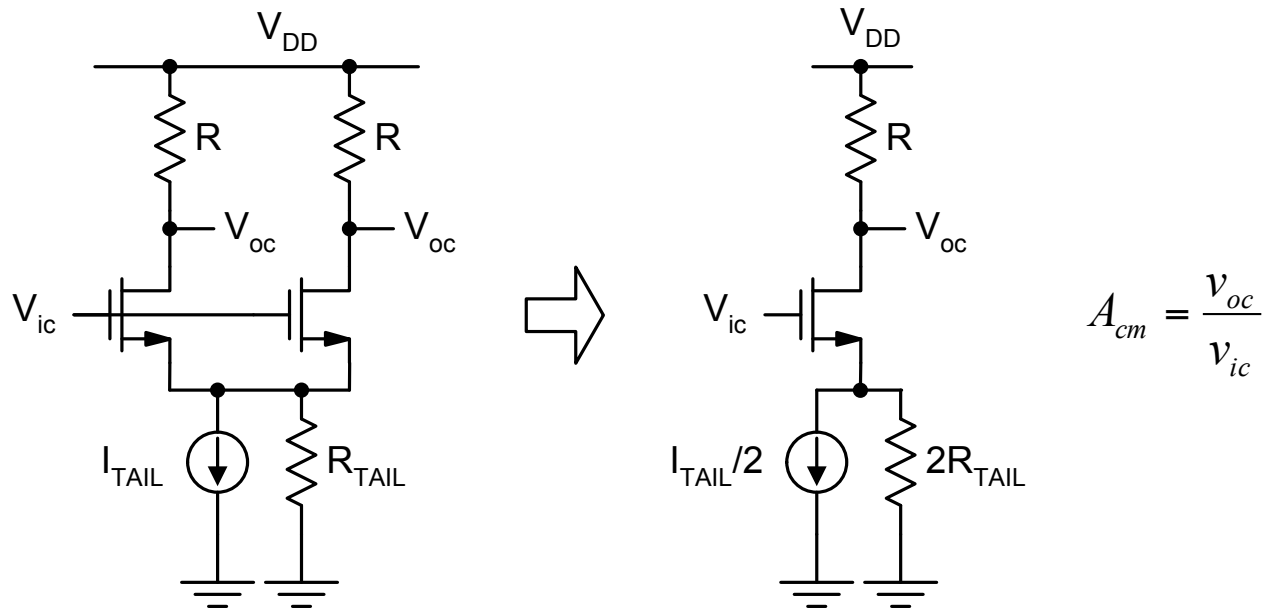

- Ideally zero ($R_{TAIL} = \infty$)

- With finite R_{TAIL} :
$$A_{cm} \approx -\frac{g_m}{1 + g'_m \cdot 2R_{TAIL}} (R \parallel r_o (1 + g'_m \cdot 2R_{TAIL})) \approx -\frac{g_m R}{1 + g'_m \cdot 2R_{TAIL}}$$

Since degeneration reduces the effective transconductance, and since degeneration occurs only in the CM case, the differential pair is more sensitive to differential inputs than to common-mode inputs ($|A_{cm}| < |A_{dm}|$)

Common Mode Rejection Ratio

- Figure of merit that quantifies ratio of desired/undesired gain
 - Ideally infinite

$$CMRR \triangleq \left| \frac{A_{dm}}{A_{cm}} \right|$$

- For our simple resistively loaded differential pair, this becomes (assuming $R \ll r_o$ and ignoring body effect)

$$CMRR = \left| \frac{A_{dm}}{A_{cm}} \right| \cong \frac{g_m \cdot R}{\frac{g_m}{1 + g_m \cdot 2R_{TAIL}} \cdot R} = 1 + g_m \cdot 2R_{TAIL}$$

- Other important figures of merit

$$\left| \frac{A_{dm}}{A_{cm-dm}} \right|$$

$$\left| \frac{A_{dm}}{A_{dm-cm}} \right|$$

Common Mode Rejection Ratio

- Considering mismatches:

$$\left| \frac{A_{dm}}{A_{cm-dm}} \right| \cong \frac{1 + g_m \cdot 2R_{TAIL}}{\frac{|\Delta g_m|}{g_m} + \frac{|\Delta R|}{R}}$$

NOTE:

when considering mismatches the circuit become asymmetric; half-circuit cannot be used to analyze the effect of CM fluctuations on the output


$$g_m \triangleq \frac{g_{m1} + g_{m2}}{2}; \Delta g_m = g_{m1} - g_{m2} \Leftrightarrow g_{m1} = g_m + \frac{\Delta g_m}{2}; g_{m2} = g_m - \frac{\Delta g_m}{2}$$

$$R_1 = R$$

$$R_2 = R + \Delta R$$

- Ratio between desired gain and undesired gain can be improved by
 - matching well the transistors and the drain resistances
 - increasing the output resistance of the tail current
- Best option: increase R_{TAIL}
 - Use a large tail transistor
 - Use a cascode for the tail current source

Power Supply Rejection Ratio

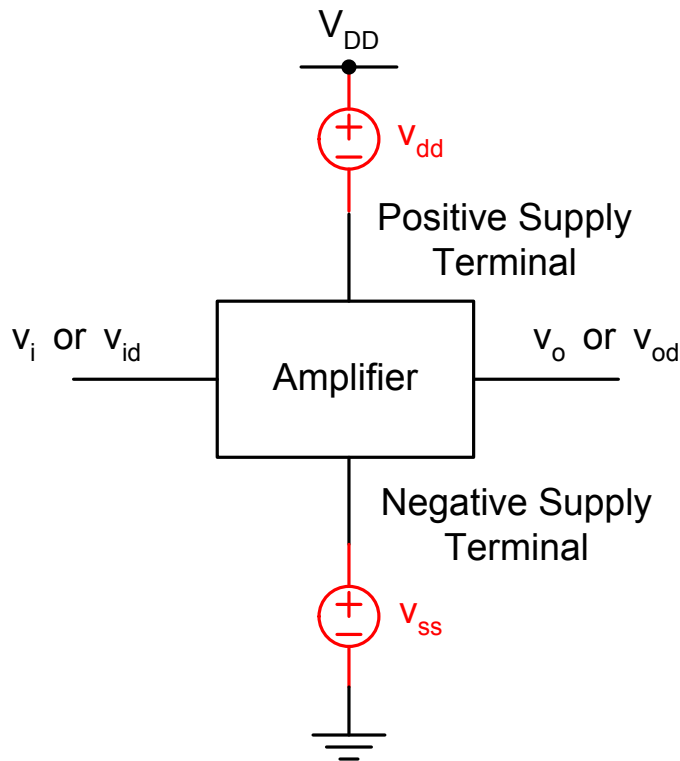


- In practice, "noise" on the supplies will also propagate to the output
 - In a differential system usually due to (half-) circuit imbalance
- Define

$$A_+ = \frac{v_{od}}{v_{dd}} \quad A_- = \frac{v_{od}}{v_{ss}}$$

$$PSRR_+ = \left| \frac{A_{dm}}{A_+} \right| \quad PSRR_- = \left| \frac{A_{dm}}{A_-} \right|$$

Input Referred Interpretation

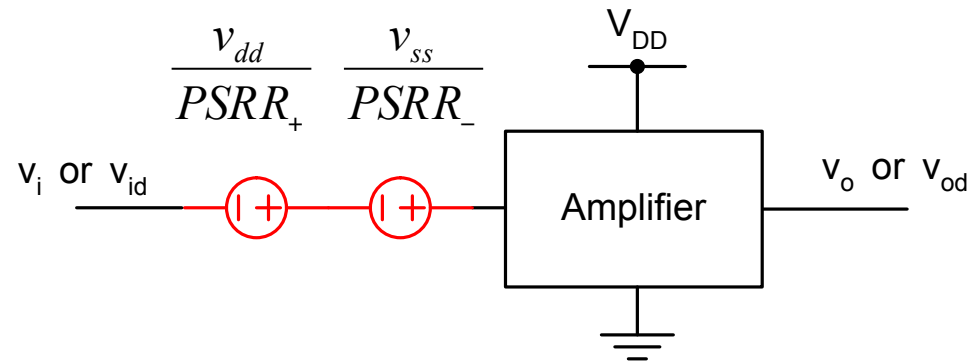


- E.g. 1mV input signal, 100mV supply noise
 - Need $PSRR \gg 100$ (40dB)
- PSRR can be a very critical issue in highly integrated, complex integrated circuits
 - Lots of potential supply noise sources
 - E.g. cross-talk between analog and digital sections

I/O DC characteristics (w/ ideal tail) (1)


Common Mode:

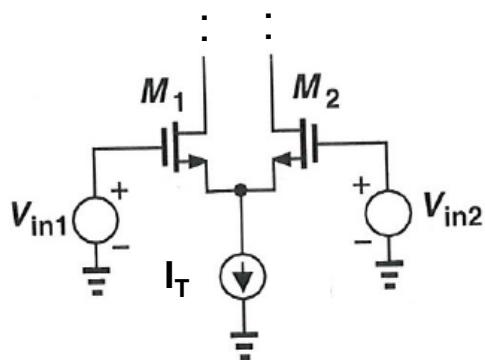$V_{DD} = 5V$; $I_T = 600\mu A$;
 $W/L = 21.33\mu m/1\mu m$;
 $R_L = 5K\Omega$



Math "artifact":
 Because of the ideal tail the voltage V_x across the tail can take any value (even negative values)

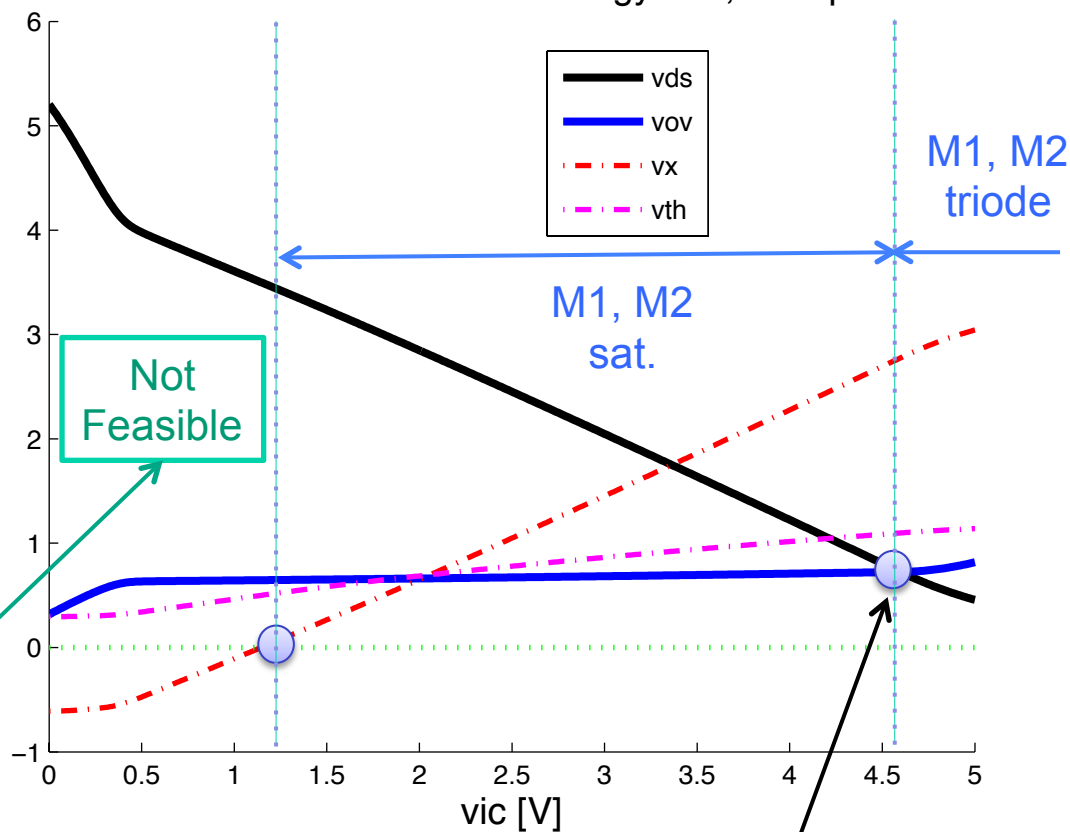Common Mode – 1um Technology: M1, M2 operation




- M_1 and M_2 end up in triode for $V_{IC(max)} \approx V_{DD} + V_{TH} - R_L I_{TAIL} / 2 \approx 4.6 V$

I/O DC characteristics (w/ ideal tail) (2)


Differential Mode:

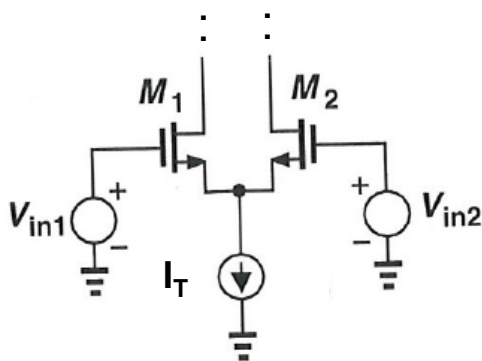$V_{DD} = 5V$; $I_T = 600\mu A$;
 $W/L = 21.33\mu m/1\mu m$;
 $R_L = 5K\Omega$ ($V_{IC} = 2.5$)




- $V_{id} = V_{in1} - V_{in2}$
- $V_{od} = V_{o1} - V_{o2}$
- $|V_{od}| < R_L I_{TAIL}$

Diff. Mode – 1um Technology

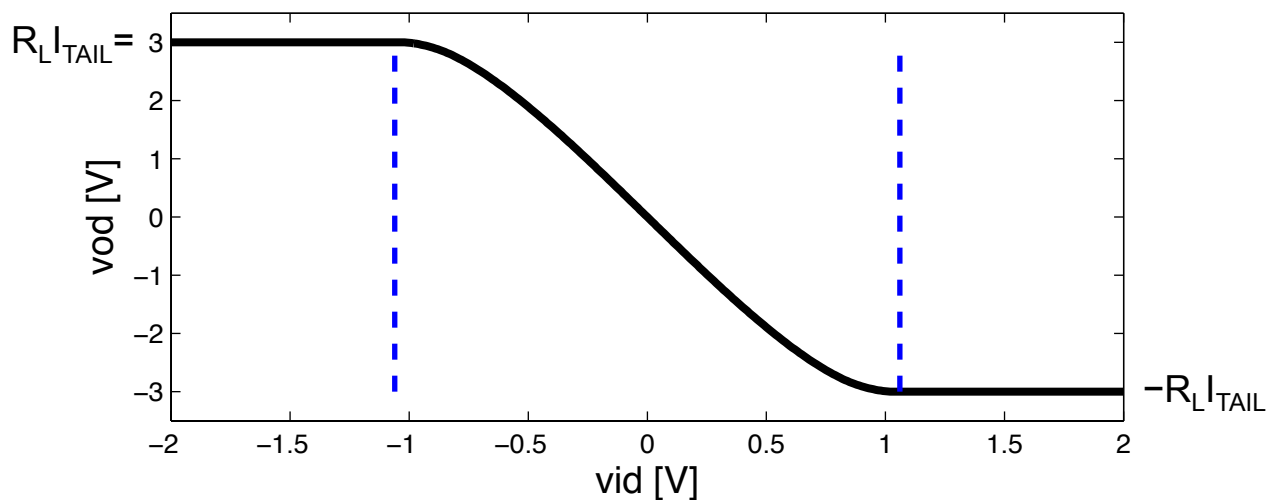


M2 operation (M1 is symmetric)

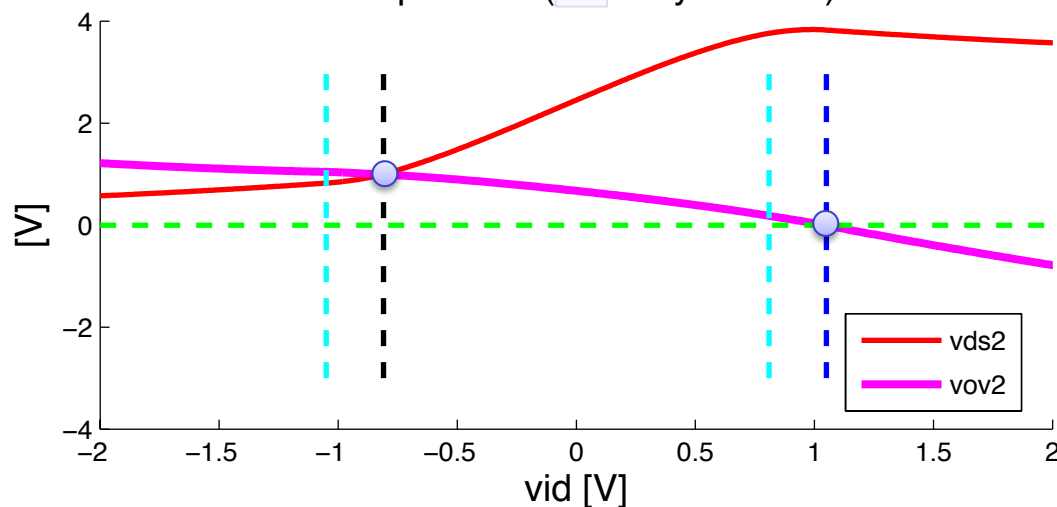

I/O DC characteristics (w/ ideal tail) (3)

output signal swing:

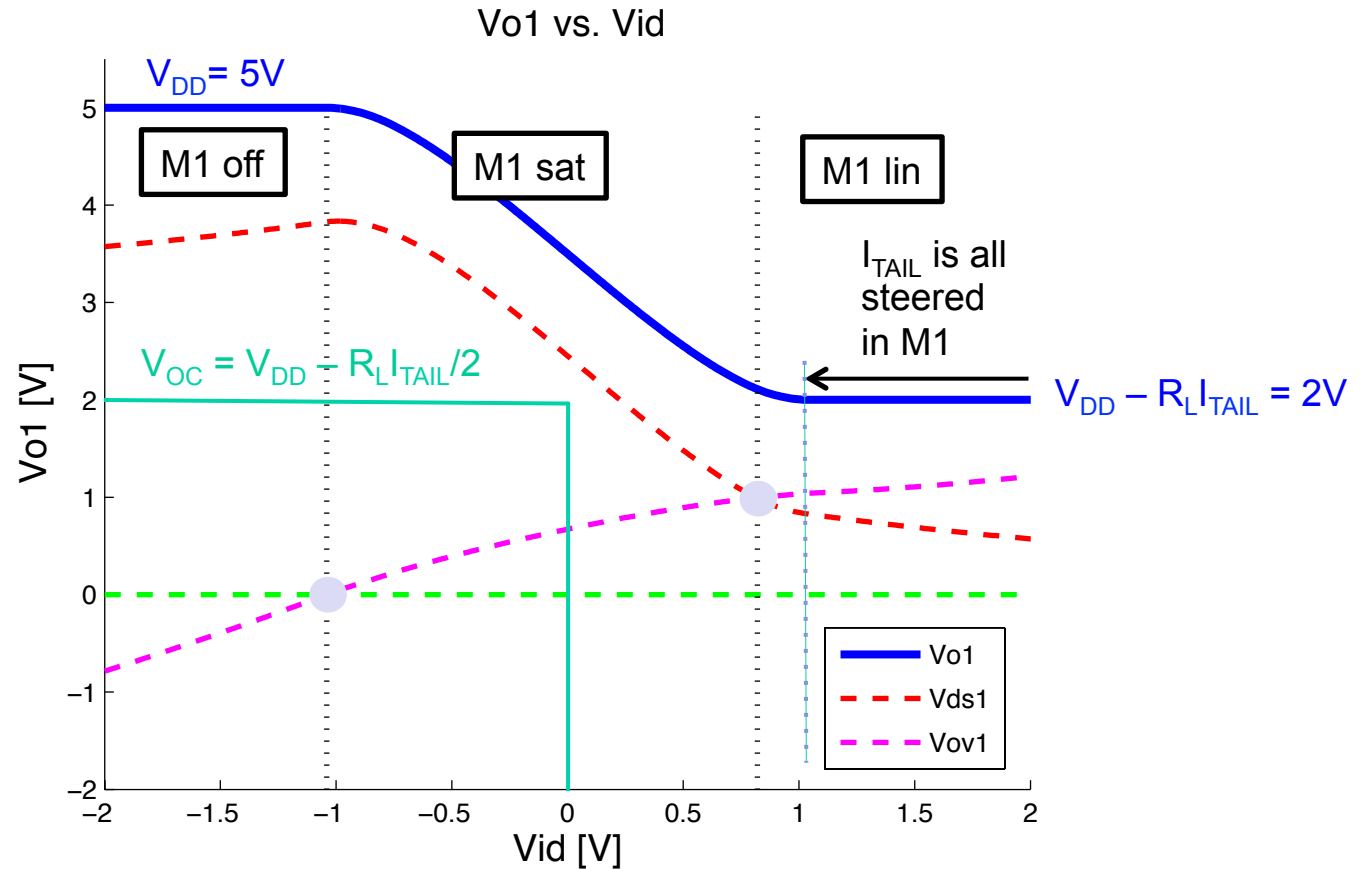


- $V_{o1}(\max) = V_{DD}$
 - $V_{o1}(\min) = V_{OV1} + V_X = V_{IC} - V_{TH} \approx V_{DD} - R_L I_{TAIL}$
 - $V_X = V_{IC} - V_{GS1} = V_{IC} - V_{OV1} - V_{TH}$
- } $\Rightarrow |V_{od}| < V_{DD} - V_{IC} + V_{TH} < R_L I_{TAIL}$

I/O DC characteristics (w/ MOST tail) (1)


Common Mode:

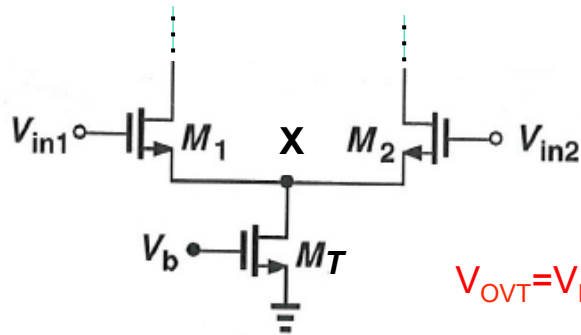$V_{DD} = 5V$; $I_T = 600\mu A$;
 $W/L = 21.33\mu m/1\mu m$;
 $R_L = 5K\Omega$;
 $(W/L)_T = 61.07\mu m/1\mu m$



M1 off
M2 off
MT lin.

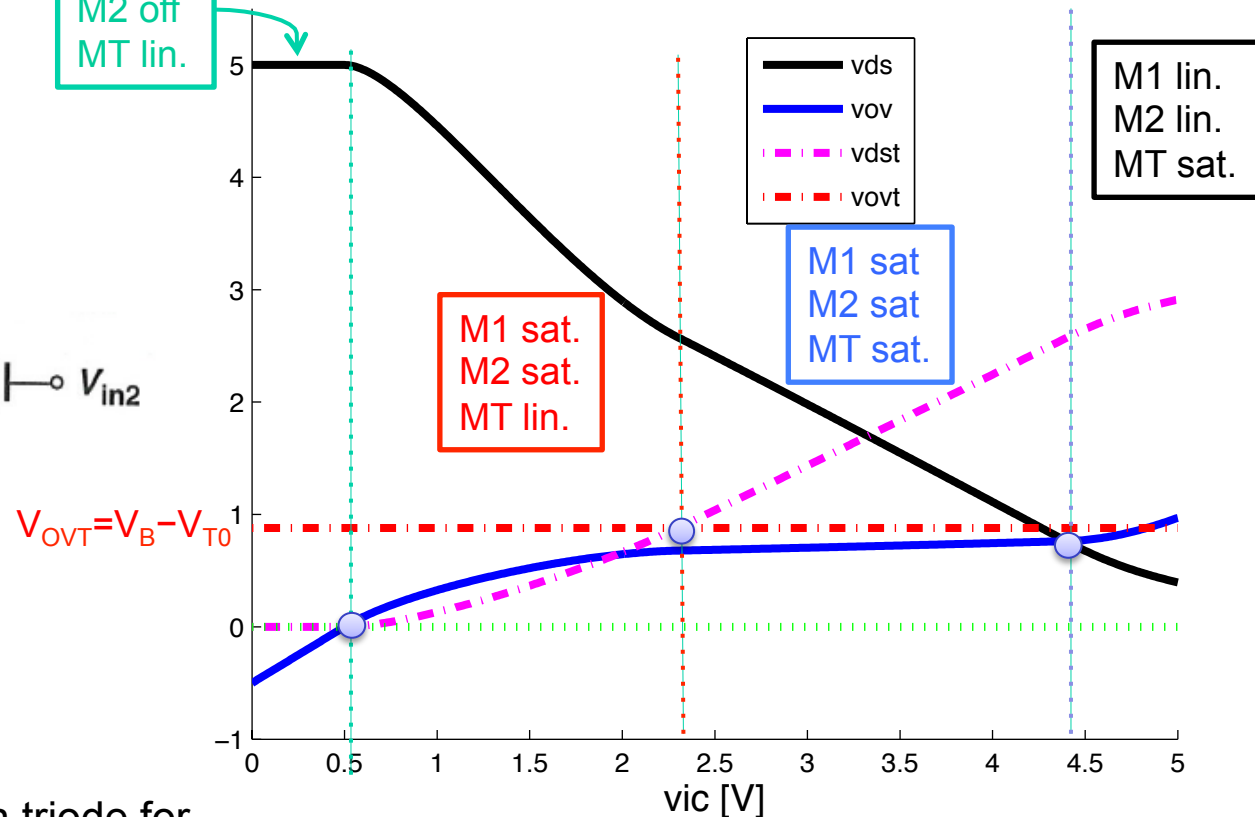Common Mode – 1um Technology: M1, M2, MT operation



- M_1 and M_2 end up in triode for $V_{IC}(\max) \approx V_{DD} + V_{TH} - R_L I_{TAIL} / 2 \approx 4.4 V$
- M_T doesn't operate in sat. until $V_{IC}(\min) \approx V_{TH} + V_{OV} + V_{OVT} \approx 2.3V$


NOTE:

V_{TH} depends on V_X (a MOST tail provides a "different" V_X than an ideal current source)




I/O DC characteristics (w/ MOST tail) (2)

Differential Mode:

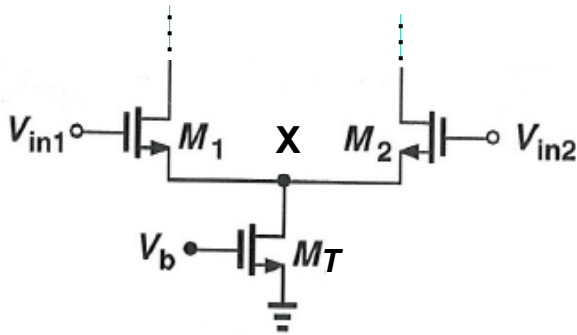$V_{DD} = 5V$; $I_T = 600\mu A$;
 $W/L = 21.33\mu m/1\mu m$;
 $R_L = 5K\Omega$; ($V_{IC} = 2.5V$)
 $(W/L)_T = 61.07\mu m/1\mu m$



NOTE:
 The tail MOST
 operates in sat.
 for all feasible
 values of V_{id}
 $(|V_{id}| < V_{OV,eq}\sqrt{2})$

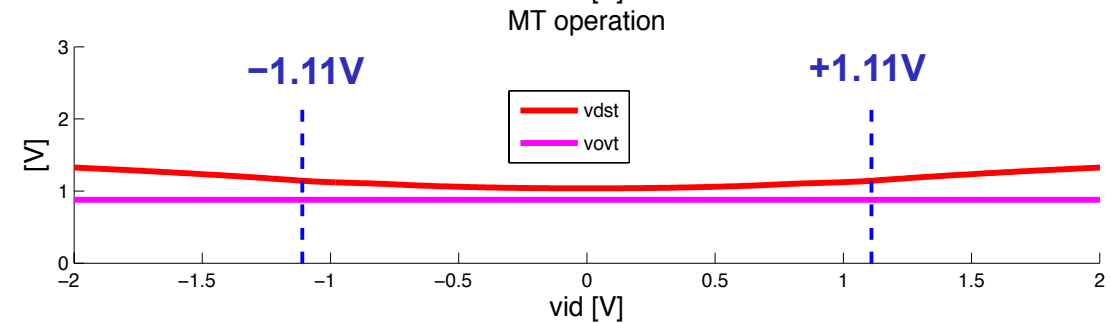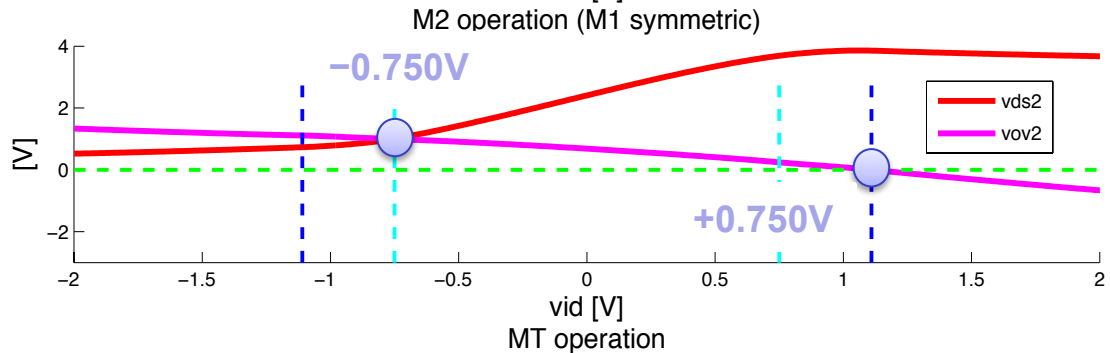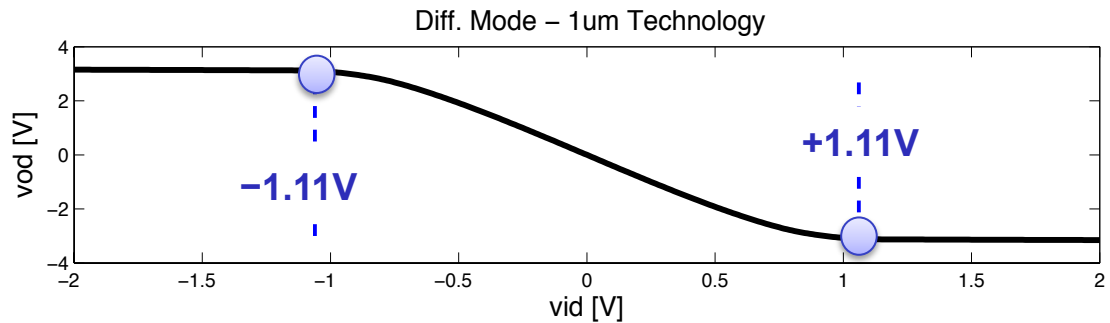

MATLAB design script - 1um technology

```

%
% Design of diff pair - 1 um technology
% file: design_dp.m
%
clear all; close all;

% Specs.
Av0 = 4; RL=5e3; CL=50e-15; RS=10e3; IT=600e-6; VDD=5;
% DC spec.
VIC = 2.5;

% technology
Cox = 2.3e-3; KP=50e-6; L=1e-6; VT0=0.5;
gamma=0.6; PHI=0.8; Ldiff=3e-6; PB=0.95; MJ=0.5; MJSW=0.33;
CJ0 = 0.5e-3; CJSW0=0.5e-9; Cov = 0.5e-9; lambda=0.1;

% Calculations
ID = IT/2;
VOUT = VDD - RL*ID
gm = Av0/RL
VOV = 2*ID/gm
VTH = VT0; % first pass: neglect body effect
for i=1:10 % iterate a few times
    VGS = VOV + VTH;
    VX = VIC - VGS; % VX = VIC - VTH - VOV (= VIC - VGS)
    VTH = VT0 + gamma*(sqrt(PHI+VX)-sqrt(PHI));
end
VGS
VX
VTH
W = L*2*ID/KP/VOV^2
gm_id = gm/ID
VDS = VOUT - VX

cgd = Cov*W
cgs = Cov*W + 2*Cox*W*L/3
cgg = cgs + cgd;
% neglect cdb and csb

fT = gm/2/pi/cgg
% pole calculations
b1 = RL*CL + cgs*RS + cgd*(RS+RL+gm*RL*RS);
% b1 = coeff of s in den. of Av(s)
fp1 = 1/b1/2/pi
b2 = RS*RL*(cgs*CL + cgs*cgd + CL*cgd);
% b2 = coeff of s^2 in den. of Av(s)
fp2 = 1/2/pi*b1/b2

```

```

%
% tail design sizing
%
LT = 2e-6;
VDST = VX
VOVT_max = VDST % for tail to stay in sat VDST > VOVT
VOVT = 0.9*VOVT_max
WT_LT = 2*IT/VOVT^2/KP
WT = WT_LT*LT
VGST = VOVT + VT0
VB = VGST

```

HSPICE netlist – 1um Technology

```
*
* biasdp.sp
*
* include models
.include ~/hspice_libs/ee114_hspice.mod
.option post brief accurate

* ideal balun
* example instantiation
* x1 vdm vcm vp vm balun
.subckt balun vdm vcm vp vm
e1 vp vcm transformer vdm 0 2
e2 vcm vm transformer vdm 0 2
.ends balun

* circuit
vdd vdd 0 5
vic vic 0 DC 2.5
vid vid 0 AC 1 DC=0

x1 vid vic vip vim balun
x2 vod voc vop vom balun
rdum vod 0 1gig * cannot leave the node floating

it vx 0 600u

m1p vop vgp vx 0 nmos114 W=21.33u L=1u * M1
m1m vom vgm vx 0 nmos114 W=21.33u L=1u * M2
RLp vdd vop 5K
RLm vdd vom 5K
CLp vop 0 50f
CLm vom 0 50f
RSp vip vgp 10k
RSm vim vgm 10k

* analysis and measurements
.OP
.ac dec 100 1e6 1e12
.pz v(vod) vid
.dc vic -5 5 0.01
.dc vid -5 5 0.01

.probe i(m1m) i(m1p) vth(m1m) vth(m1p) vdsat(m1m) vdsat(m1p)
.probe vgs(m1m) vgs(m1p) vds(m1m) vds(m1p)
.probe vgs(mt) vds(mt) vth(mt) vdsat(mt) i(mt)

.measure AC GDC find VDB(vod) at 1Meg
.measure AC ADC find V(vod) at 1Meg
.measure AC F3DB when VDB(vod)='GDC - 3'

.alter most_tail
it vx 0 0
vb vb 0 1.38
mt vx vb 0 0 nmos114 W=61.07u L=2u

.end
```

Script to plot simulation results (w/ ideal tail) (1)

```
%
% file: plot_biasdp.m
%
clear all; close all;
format short eng

addpath('/usr/local/MATLAB/HspiceToolbox');
x = loadsig('./spiceout/biasdp.sw0');
lssig(x)

vic = evalsig(x,'v_vic');
voc = evalsig(x,'v_voc');
vdsat = evalsig(x,'vdsat_m1m');
vds = evalsig(x,'vds_m1m');
vx = evalsig(x,'v_vx');
vov = evalsig(x,'vgs_m1m') - evalsig(x,'vth_m1m');
vth = evalsig(x,'vth_m1m');

% long channel transistors vov=vdsat
figure(1)
xlim([0 5]);
hold on;
plot(vic,vds,'linewidth',3, 'color', 'k', 'linestyle', '-');
plot(vic,vov,'linewidth',3, 'color', 'b', 'linestyle', '-');
plot(vic,vx,'linewidth',2, 'color', 'r', 'linestyle', '-');
plot(vic,vth,'linewidth',2, 'color', 'm', 'linestyle', '-');
% horizontal line across zero
line([0 5], [0 0], 'linestyle', ':', ...
      'linewidth', 2, 'color', 'g');
xlabel('vic [V]', 'FontSize', 14);
title('Common Mode - 1um Technology: M1, M2 operation', 'fontsize', 14);
legend('vds', 'vov', 'vx', 'vth', 'location', 'best');

% compute vic_max
for i=1:length(vic)
    if vds(i) < vov(i)
        index = i;
        break
    end
end
% margin: index -1
vic_max_num = vic(index-1)
RL = 5e3; IT=600e-6;vdd = 5; vt0 = 0.5; W = 21.33e-6; L=1e-6; KP=50e-6;
vic_max_an_approx = vdd + vt0 - RL*IT/2 % neglect back gate
vth = vth(index-1)
vic_max_an_precise = vdd + vth - RL*IT/2 % with back gate

figure(2)
y = loadsig('./spiceout/biasdp.sw1');
lssig(y)

vid = evalsig(y,'v_vid');
vod = evalsig(y,'v_vod');
vdsat = evalsig(y,'vdsat_m1m'); % M2
vds = evalsig(y,'vds_m1m');
vx = evalsig(y,'v_vx');
vgs = evalsig(y,'vgs_m1m');
vth = evalsig(y,'vth_m1m');
vov = vgs - vth;

subplot(2,1,1);
plot(vid,vod,'linewidth',3, 'color', 'k', 'linestyle', '-');
% ideal (no body effect, both MOST in sat)
VOV_eq = sqrt(IT/KP/(W/L))
pointA = sqrt(2)*VOV_eq
pointB = -sqrt(2)*VOV_eq
% ideal vertical lines (no body effect, both MOST in sat)
line([pointA pointA], [-3 3], 'linestyle', '--', ...
      'linewidth', 2, 'color', 'b');
line([pointB pointB], [-3 3], 'linestyle', '--', ...
      'linewidth', 2, 'color', 'b');
xlim([-2 2]);
ylim([-3.5 3.5]);
xlabel('vid [V]', 'FontSize', 14);
ylabel('vod [V]', 'FontSize', 14);
title('Diff. Mode - 1um Technology', 'fontsize', 14);

subplot(2,1,2)
hold on;
plot(vid,vds,'linewidth',2, 'color', 'r', 'linestyle', '-');
plot(vid,vov,'linewidth',3, 'color', 'm', 'linestyle', '-');
xlim([-2 2]);
% horizontal line across zero
line([-2 2], [0 0], 'linestyle', '--', ...
      'linewidth', 2, 'color', 'g');
legend('vds2', 'vov2', 'location', 'best');
xlabel('vid [V]', 'FontSize', 14);
ylabel('vov [V]', 'FontSize', 14);
title('M2 operation (M1 is symmetric)', 'fontsize', 14);
```

to be continued ...

Script to plot simulation results (w/ ideal tail) (2)

```
% compute M2 operation
for i=1:length(vid)
    if vov(i) < 0
        index = i;
        break
    end
end
M2cutoff = vid(index)
line([M2cutoff M2cutoff], [-3 3], 'linestyle', '--', ...
     'linewidth', 2, 'color', 'b');
for i=1:length(vid)
    if vds(i) > vov(i)
        index = i;
        break
    end
end
M2sat = vid(index)
line([M2sat M2sat], [-3 3], 'linestyle', '--', ...
     'linewidth', 2, 'color', 'k');
% M1 operation (symmetric)
line([-M2cutoff -M2cutoff], [-3 3], 'linestyle', '--', ...
     'linewidth', 2, 'color', 'c');
line([-M2sat -M2sat], [-3 3], 'linestyle', '--', ...
     'linewidth', 2, 'color', 'c');
```

```
figure(3);
hold on;
vout1 = evalsig(y,'v_vop');
vgs1 = evalsig(y,'vgs_m1p');
vth1 = evalsig(y,'vth_m1p');
vds1 = evalsig(y,'vds_m1p');
vov1 = vgs1 - vth1;
plot(vid,vout1,'linewidth',3, 'color', 'b', 'linestyle', '-');
plot(vid,vds1,'linewidth',2, 'color', 'r', 'linestyle', '--');
plot(vid,vov1,'linewidth',2, 'color', 'm', 'linestyle', '--');
% horizontal line across zero
line([-2 2], [0 0], 'linestyle', '--', ...
     'linewidth', 2, 'color', 'g');
xlim([-2 2]);
ylim([-2 5.5]);
xlabel('Vid [V]', 'FontSize', 14);
ylabel('Vo1 [V]', 'FontSize', 14);
title('Vo1 vs. Vid', 'fontSize', 14);
legend('Vo1','Vds1','Vov1','location', 'best')
% compute M1 operation
for i=1:length(vid)
    if vov1(i) > 0
        index = i;
        break
    end
end
M1sat = vid(index)
line([M1sat M1sat], [-3 5], 'linestyle', ':', ...
     'linewidth', 2, 'color', 'k');
for i=1:length(vid)
    if vds1(i) < vov1(i)
        index = i;
        break
    end
end
M1triode = vid(index)
line([M1triode M1triode], [-3 5], 'linestyle', ':', ...
     'linewidth', 2, 'color', 'k');
```

Script to plot simulation results (w/ MOST tail) (1)

```
%
% file: plot_biasdp_wtail.m
%
clear all; close all;
format short eng

addpath('/usr/local/MATLAB/HspiceToolbox');
x = loadsig('./spiceout/biasdp.sw2');
lssig(x)

vic = evalsig(x,'v_vic');
voc = evalsig(x,'v_voc');
vgs = evalsig(x,'vgs_m1m');
vds = evalsig(x,'vds_m1m');
vth = evalsig(x,'vth_m1m');
vov = vgs - vth;
vx = evalsig(x,'v_vx');
vgst = evalsig(x,'vgs_mt');
vdst = evalsig(x,'vds_mt');
vtht = evalsig(x,'vth_mt');
vovt = vgst - vtht;

% long channel transistors vov=vdsat
figure(1)
xlim([0 5]);
ylim([-1 5.5]);
hold on;
plot(vic,vds,'linewidth',3,'color','k','linestyle','-');
plot(vic,vov,'linewidth',3,'color','b','linestyle','-');
plot(vic,vdst,'linewidth',3,'color','m','linestyle','-');
plot(vic,vovt,'linewidth',3,'color','r','linestyle','-');
% horizontal line across zero
line([0 5],[0 0],'linestyle',':', ...
      'linewidth',3,'color','g');
xlabel('vic [V]','FontSize',14);
title('Common Mode - 1um Technology: M1, M2, MT operation','fontsize',14);
legend('vds','vov','vdst','vovt','location','best');

% compute vic_max
for i=1:length(vic)
    if vds(i) < vov(i)
        index = i;
        break
    end
end
% margin: index -1
vic_max_num = vic(index-1)
RL = 5e3; IT=600e-6;vdd = 5; vt0 = 0.5; W = 21.33e-6; L=1e-6; KP=50e-6;
vic_max_an_approx = vdd + vt0 - RL*IT/2 % neglect back gate
vth = vth(index-1)
vic_max_an_precise = vdd + vth - RL*IT/2 % with back gate
% compute vic_min
for i=1:length(vic)
    if vdst(i) > vovt(i)
        index = i;
        break
    end
end
vic_min_num = vic(index)
```

```
figure(2)
y = loadsig('./spiceout/biasdp.sw3');
lssig(y)

vid = evalsig(y,'v_vid');
vod = evalsig(y,'v_vod');
vx = evalsig(y,'v_vx');
vdsat = evalsig(y,'vdsat_m1m'); % M2
vds = evalsig(y,'vds_m1m');
vgs = evalsig(y,'vgs_m1m');
vth = evalsig(y,'vth_m1m');
vov = vgs - vth;
vgst = evalsig(y,'vgs_mt');
vdst = evalsig(y,'vds_mt');
vtht = evalsig(y,'vth_mt');
vovt = vgst - vtht;

subplot(3,1,1);
plot(vid,vod,'linewidth',3,'color','k','linestyle','-');
% ideal (no body effect, both MOST in sat)
VOV_eq = sqrt(IT/KP/(W/L))
pointA = sqrt(2)*VOV_eq
pointB = -sqrt(2)*VOV_eq
% ideal vertical lines (no body effect, both MOST in sat)
line([pointA pointA],[ -3 3], 'linestyle', '--', ...
      'linewidth', 2, 'color', 'b');
line([pointB pointB],[ -3 3], 'linestyle', '--', ...
      'linewidth', 2, 'color', 'b');
xlim([-2 2]);
ylim([-4 4]);
xlabel('vid [V]','FontSize',14);
ylabel('vod [V]','FontSize',14);
title('Diff. Mode - 1um Technology','fontsize',14);
```

to be continued ...

Script to plot simulation results (w/ MOST tail) (2)

```
subplot(3,1,2)
hold on;
plot(vid,vds,'linewidth',3,'color','r','linestyle','-');
plot(vid,vov,'linewidth',3,'color','m','linestyle','-');
xlim([-2 2]);
ylim([-3 4]);
% horizontal line across zero
line([-2 2],[0 0],'linestyle','--',...
     'linewidth',2,'color','g');
legend('vds2','vov2','location','best');
xlabel('vid [V]','FontSize',14);
ylabel('V','FontSize',14);
title('M2 operation (M1 symmetric)','fontsize',14);
% compute M2 operation
for i=1:length(vid)
    if vov(i) < 0
        index = i;
        break
    end
end
M2cutoff = vid(index-1)
line([M2cutoff M2cutoff],[-3 3],'linestyle','--',...
     'linewidth',2,'color','b');
for i=1:length(vid)
    if vds(i) > vov(i)
        index = i;
        break
    end
end
M2sat = vid(index)
line([M2sat M2sat],[-3 3],'linestyle','--',...
     'linewidth',2,'color','c');
% M1 operation (symmetric)
line([-M2cutoff -M2cutoff],[-3 3],'linestyle','--',...
     'linewidth',2,'color','b');
line([M2sat M2sat],[-3 3],'linestyle','--',...
     'linewidth',2,'color','c');

subplot(3,1,3)
hold on;
plot(vid,vdst,'linewidth',3,'color','r','linestyle','-');
plot(vid,vovt,'linewidth',3,'color','m','linestyle','-');
xlim([-2 2]);
ylim([0 3]);
legend('vdst','vovt','location','best');
xlabel('vid [V]','FontSize',14);
ylabel('V','FontSize',14);
title('MT operation','fontsize',14);
line([-M2cutoff -M2cutoff],[-3 3],'linestyle','--',...
     'linewidth',2,'color','b');
line([M2cutoff M2cutoff],[-3 3],'linestyle','--',...
     'linewidth',2,'color','b');
```