
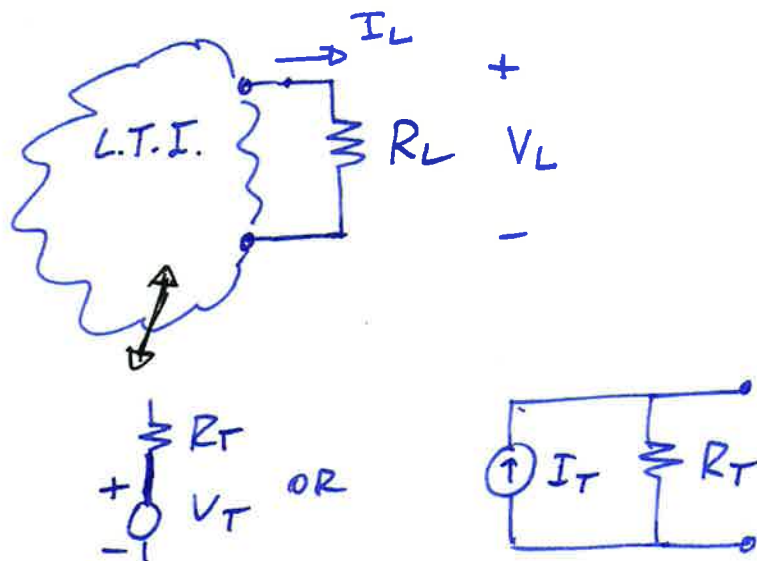


THEVENIN AND NORTON TRANSFORMATIONS

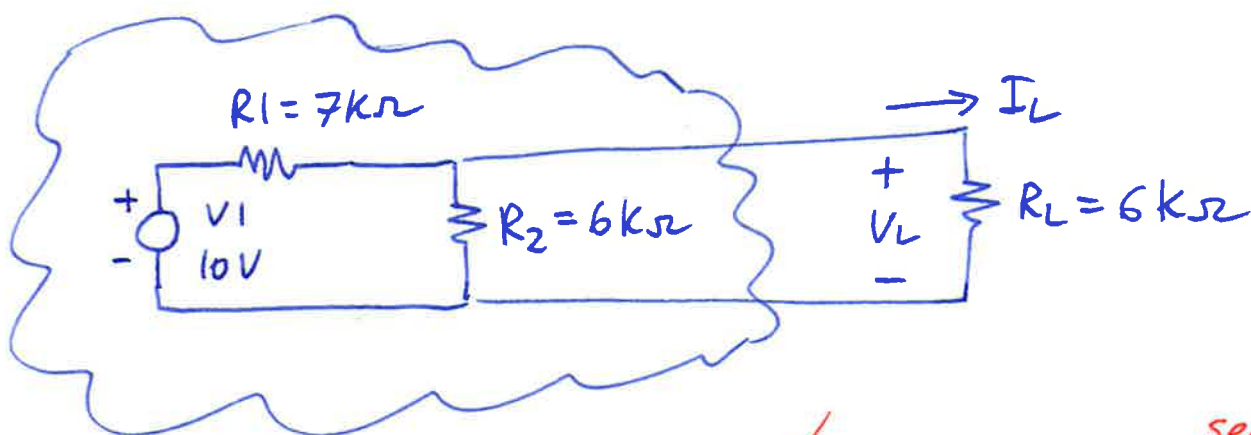


Example



How we model the stuff inside the "bubble" does not matter, as long as the voltage and the current on the load are correct! However, we want a model that is general enough that once it is built, it works for any R_L we attach to it!


First attempt

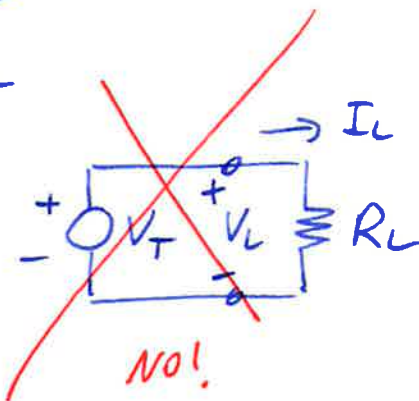Let's try to set the voltage across the load by applying an ideal voltage source. The value of V_T we need is exactly V_L



Then if I change R_L I also need to change V_T so I would have to change the model based on R_L

second attempt

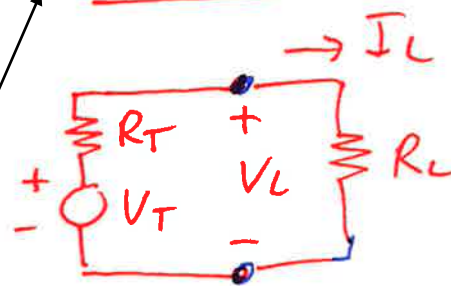


1. I need a voltage V_T different from V_L

2. But then I need to add some resistance that when "traversed" by I_L drops just the right amount of voltage to get V_L on the load

→ 2 cases (extremes)


• $R_L = \infty$

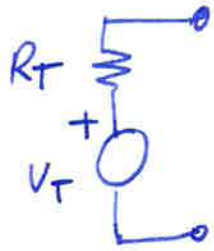

$$V_{open} = V_T$$


$$I_L = 0$$

• $R_L = 0$

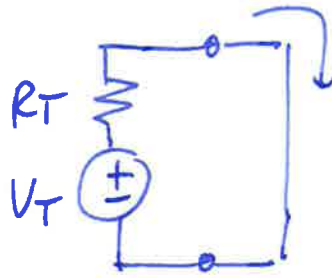

$$I_{short} = \frac{V_T}{R_T} \rightarrow R_T = V_{OPEN} / I_{SHORT}$$

$$V_L = 0$$

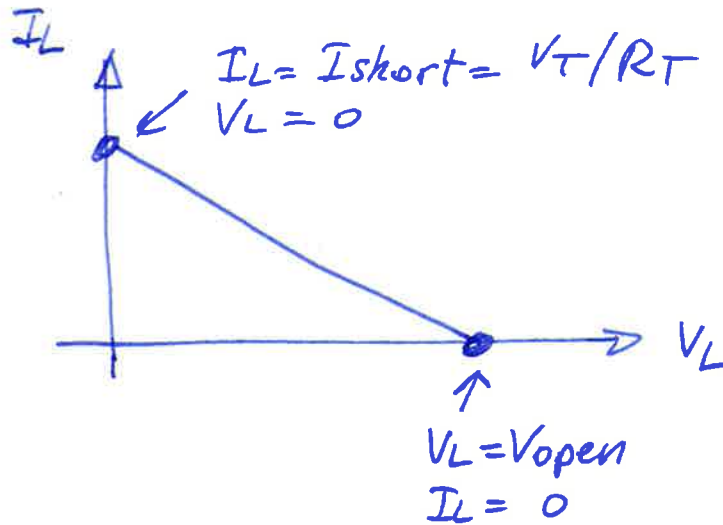

straight line between two points:


$$I_L - \frac{V_T}{R_T} = -\frac{1}{R_T} \cdot V_L$$

↓


$$I_L = -\frac{1}{R_T} V_L + \frac{V_T}{R_T}$$

$$(y = m \cdot x + n)$$

back to the example:

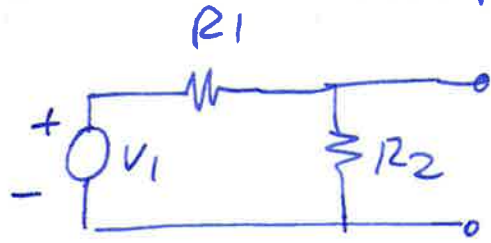

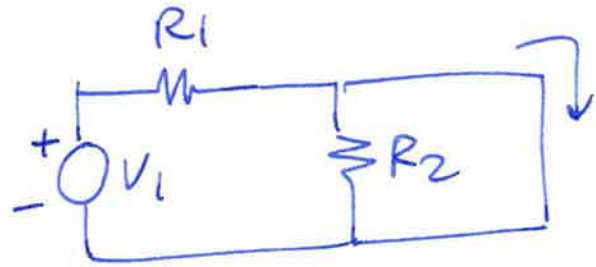
$$V_T = V_{open} = \frac{V_1}{R_1 + R_2} \cdot R_2 = 4.62 \text{ V}$$





$$I_{short} = \frac{V_T}{R_T} = \frac{V_1}{R_1} = \frac{10 \text{ V}}{7 \text{ k}\Omega} \approx 1.43 \text{ mA}$$

$$R_T = \frac{V_T}{I_{short}} = \frac{4.62 \text{ V}}{1.43 \text{ mA}} \approx 3.23 \text{ k}\Omega$$


Thevenin/Norton Transf. rules

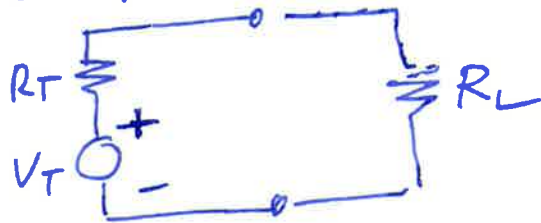


→ remove R_L to find out V_T

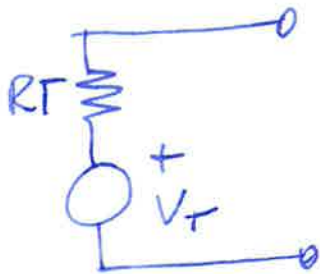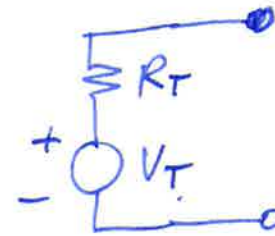

→ remove V_T and apply test voltage

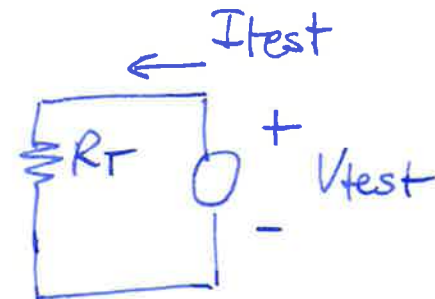

$$\frac{V_{test}}{I_{test}} = R_T$$

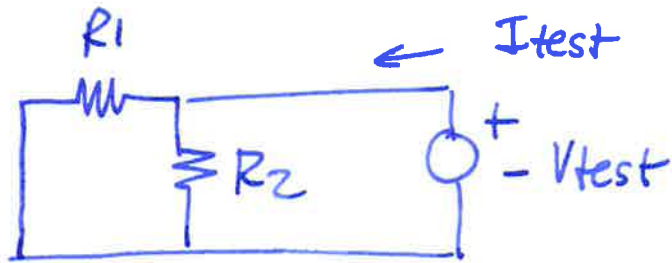

$V=0 \rightarrow$ replace indep. voltage source short

$I=0 \rightarrow$ replace indep. current source open

$$\frac{V_{test}}{I_{test}} = R_T = R_1 \parallel R_2 =$$

$$= 7k\Omega \parallel 6k\Omega \approx 3.23k\Omega$$

same as using ~~multimeter~~ a multimeter in a lab.
(shutdown the supply of the board)