

Problem 1

Given the circuit in Figure 1 hand derive the symbolic expressions for

1. $A_s = v_{out}/v_s$
2. R_{in} , that is the Thevenin equivalent resistance looking into terminals 1 and 0 (in the direction shown by the arrow)
3. R_{out} , that is the Thevenin equivalent resistance looking into terminals 2 and 0 (in the direction shown by the arrow)

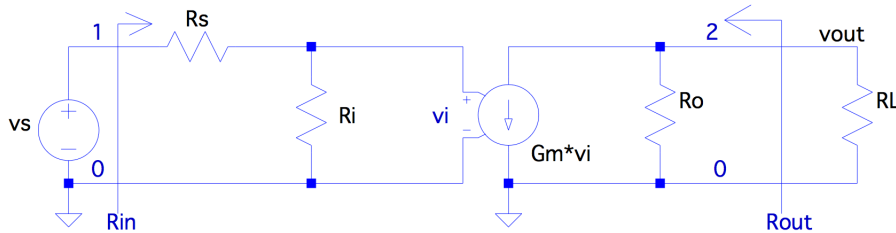


Figure 1

4. Verify your results by simulating the given circuit with LTSPICE. Assume the following values $v_s=1V$, $R_s=1\Omega$, $R_i=1K\Omega$, $G_m=1mS$, $R_o=1M\Omega$, $R_L=10K\Omega$. Hint: take a look at the .TF analysis. Make sure to 1) attach your LTSPICE schematic and your simulation results, and 2) explain any discrepancies.

Problem 2

Given the circuit in Figure 2 use matlab symbolic toolbox to derive an expression for

1. $A_s = v_{out}/v_s$
2. R_{in} , that is the Thevenin equivalent resistance looking into terminals 1 and 0
3. R_{out} , that is the Thevenin equivalent resistance looking into terminals 2 and 0
4. Find the practical conditions under which v_{out}/v_s , R_{in} , and R_{out} are approximately the same as you derived for the circuit in Figure 1

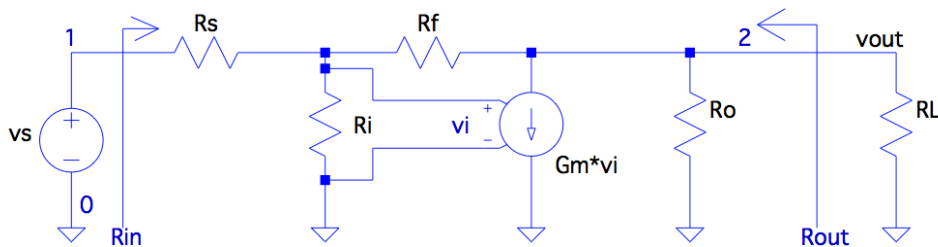


Figure 2

Make sure to attach you matlab script and its output.

Problem 3

Given the RC circuit in Figure 3 find out:

1. The transfer function $T(j\omega) = V_{out}(j\omega)/V_{in}(j\omega)$.
Note: for a given value of R, C, and ω the transfer function is simply a complex number
2. The expression of the magnitude of the transfer function $M = |T(j\omega)|$
3. The expression of the phase of the transfer function $\Phi = \text{angle}[T(j\omega)]$
4. What is the approximate value of M for very small values of ω (that is $\omega \rightarrow 0$)
5. What is the value of M for $\omega = 1/(RC)$
6. What is the approximate value of M for very large values of ω (that is $\omega \rightarrow \infty$)
7. What is the approximate value of Φ for very small values of ω (that is $\omega \rightarrow 0$)
8. What is the value of Φ for $\omega = 1/(RC)$
9. What is the approximate value of Φ for very large values of ω (that is $\omega \rightarrow \infty$)

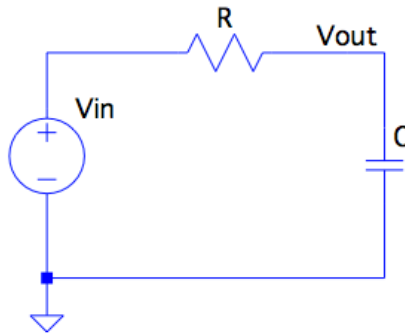


Figure 3

Problem 4

Assuming the input to the RC circuit in Figure 3 is $v_{in}(t) = V_{DD} \times [u(t) - u(t-T)]$ and $T \gg \tau = RC$:

1. Draw v_{in} vs. t and v_{out} vs. t
2. What is the equation of $v_{out}(t)$ for $-\infty \leq t \leq T$
3. What is the equation of $v_{out}(t)$ for $t > T$