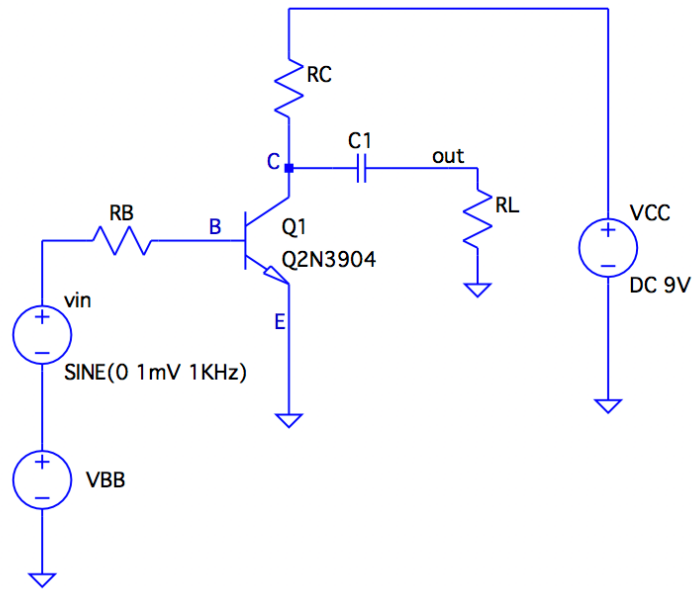


## Objectives:

- Performing DC and small signal AC analysis of the circuit
- Implementing the circuit in an experimental setting, taking measurements and comparing the circuit behavior with theoretical results

## Pre-Lab



Consider the amplifying circuit provided in figure. Select adequate values for  $R_B$ ,  $R_C$  and  $V_{BB}$  so that the DC bias point is set at  $V_{CE}=4.5V$  and  $I_C=10\text{ mA}$ .

Use SPICE to infer the  $\beta$  of the BJT. Hint: plot of the transistor's  $\beta=I_c(Q1)/I_b(Q1)$  vs.  $V_{CE}$  curve using the model of the 2N3904 provided by LTSPICE. Extract the value of  $\beta$  for a DC bias point reasonably close to  $I_C=10\text{ mA}$ ,  $V_{CE}=4.5V$

$\beta =$

Provide the symbolic equations and numerical values of the following quantities:

$R_C =$

$I_B =$

$V_{BB} =$

$R_B =$

$g_m =$

$r_{\pi} =$

$A_V = v_c/v_{in}$  with  $R_L$  not connected =

## EE 303 - Laboratory

---

### Lab

Use the DC offset in your AWG for generating VBB.

1. Before applying the AC input signal to the base, adjust its DC offset (that is VBB) until VC=4.5V. Measure the value of VBB required to set VC at 4.5V, and measure the value of VBE.

VBB =

VBE =

2. Now, apply also the AC sinusoidal input signal. Measure the gain of the amplifier at a frequency of 10KHz with RL not connected ( $AV = v_c/v_{in}$ ). Compare your measurement with your theoretical prediction from the prelab.

amplitude of the AC signal applied =

AV =

Parameter	Theoretical prediction	Measurement	% Error
AV =			

3. Measure the maximum output swing you can achieve.

- a. Maximum output swing

\_\_\_\_\_

- b. Corresponding maximum input swing

\_\_\_\_\_

- c. When clipping, does the transistor go in saturation or cut off? \_\_\_\_\_

Explain shortly your conclusion:

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

4. Connect a load of 100  $\Omega$  to the collector via capacitive coupling. Measure the gain again

## EE 303 - Laboratory

---

- a.  $A_V$  with  $R_L$  connected = \_\_\_\_\_
- b. Did the gain increase, decrease or remain the same? \_\_\_\_\_

Increase the input voltage until clipping occurs.

- c. What is the maximum output swing: \_\_\_\_\_
- d. Does the transistor go into saturation or cut-off first? \_\_\_\_\_
5. Use SPICE .OP and .AC analysis to simulate the circuit you have built (use the version with  $R_L$  not connected). Lookup the values of  $\beta_{DC}$  (hFE),  $\beta_{AC}$  (hfe),  $r_{\pi}$  (hie) and  $r_o$  (1/ho) provided on the data sheet of the transistor.
- a. Compare the quantities provided on the data sheet with the quantities obtained using SPICE

Quantity	SPICE	Data Sheet	% Error
$\beta_{DC}$			
$\beta_{AC}$			
$r_{\pi}$			
$r_o$			

$$\% \text{ Error} = 100 \times (\text{SPICE} - \text{DataSheet}) / \text{SPICE}$$

- b. Circle the value of  $\beta$  you used for computing  $|A_V|$ ?

$\beta_{DC}$

$\beta_{AC}$

Was it the best choice? \_\_\_\_\_

- c. Estimate the importance of choosing the correct value of  $\beta$ .

$$100 \times (\beta_{DC,SPICE} - \beta_{AC,SPICE}) / \beta_{AC,SPICE} =$$

$$100 \times (\beta_{DC,DATASHEET} - \beta_{AC,DATASHEET}) / \beta_{AC,DATASHEET} =$$

- d. If you used  $\beta_{DC}$  compute  $|A_V|$  again, but this time using  $\beta_{AC}$
- e. Compare the gain measured, the gain estimated and the gain obtained with SPICE (use the version with  $R_L$  not connected)

Quantity	SPICE	Measured	Estimated
$ A_V $			