


The purpose of this laboratory is

- 1) Show that the basic functionality needed to build amplification is a controlled (aka dependent) source
- 2) How the various performance parameters (R_i , R_o , A_0 and BW) of the amplifier affect its overall operation w.r.t to the driving signal V_{sig} and the driven load R_L
- 3) Show that the output signal issued by a practical amplifier is limited by its supply

Pre-Lab:

Given the following simplified single pole amplifier's model:
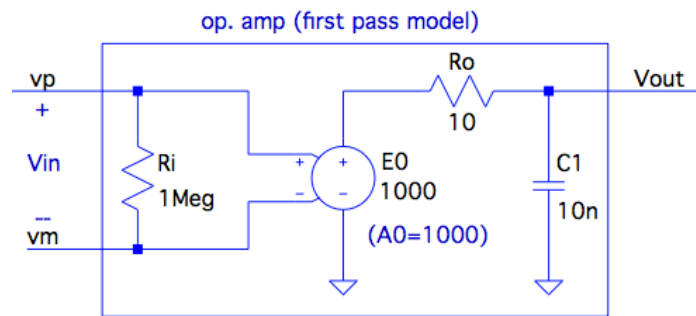
$$T(s) = \frac{A_0}{1 + \frac{s}{\omega_p}}$$



1. What are the values of:

$R_i =$ _____


$R_o =$ _____

$A_0 =$ _____

$BW = \omega_p =$ _____

2. Plot the “asymptotic” transfer function of the amplifier (both magnitude $M = |T(s)|$ and phase $\Theta = \angle T(s)$):

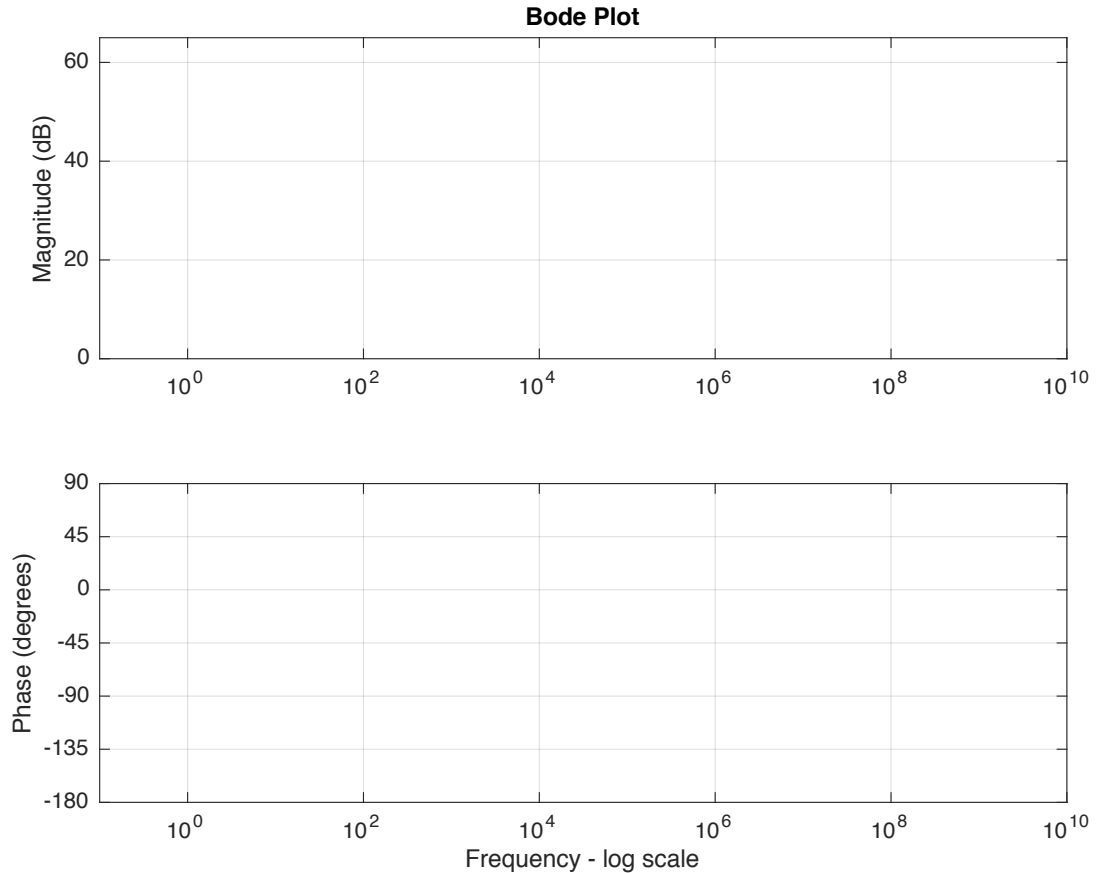
$$T(s) = \frac{A0}{1 + \frac{s}{\omega_p}}$$



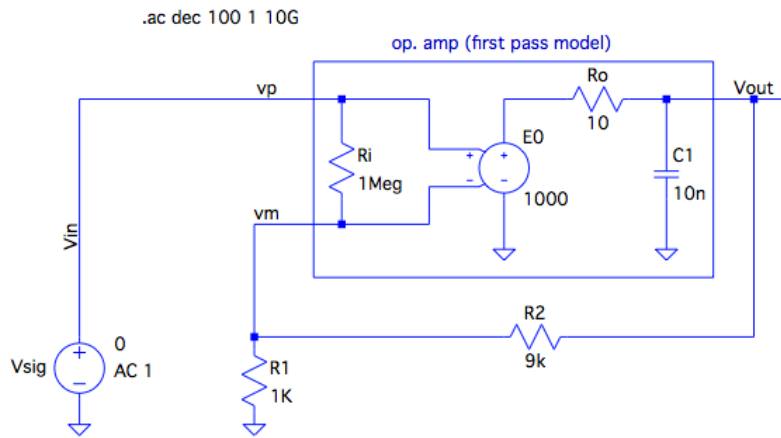3. Verify the Bode Plot you have just drawn is correct by using LTSPICE. Connect vp to an AC voltage source of 1V and vm to ground. Simulate your circuit by running an LTSPICE’s AC analysis. Run the AC analysis command sweeping the frequency in decades by using 100 points per decade. Start the sweep at 1 Hz and stop it at 10GHz.
Have LTSPICE plot magnitude and phase on two separate panes, and bring the printout with you to lab.
4. Go through the Lab. and answer all the theoretical/analytical questions.

Lab. - Part A

Modify your circuit to build a non-inverting op amp based amplifier, and run again the AC analysis.



Analytical expression of gain = _____

Using your analytical expression, compute the gain in dB = _____

LTSPICE gain in dB = _____

Bandwidth in Hz = _____


(hint: the gain-BW product must stay the same as the one you had for the open-loop op amp you analyzed in the prelab (open loop means the op amp is without the R1, R2 feedback network wrapped around it).

LTSPICE bandwidth in Hz = _____

Attach your LTSPICE magnitude plot.

Lab. - Part B

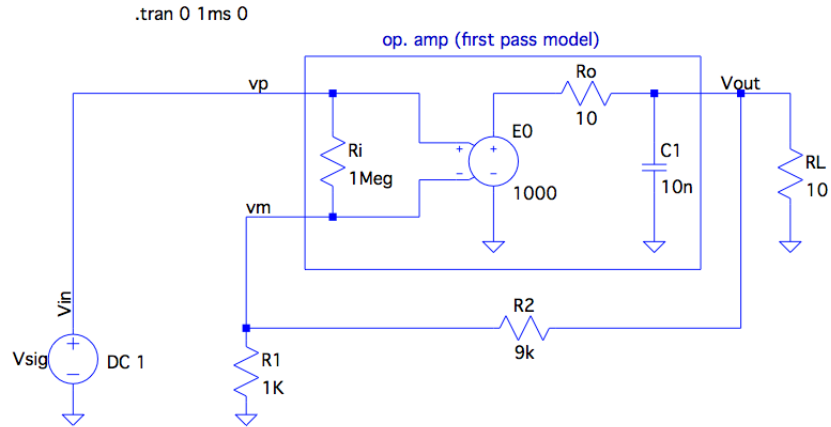Modify the previous circuit as follows. Change Vsig into a DC voltage of 1V. Add a load $R_L = 10 \Omega$ between the node Vout and ground. Change your simulation to be a TRAN analysis running for 1ms.



Calculate the following quantities (show the symbolic expressions you used). For simplicity in your derivations assume R_i is infinite.

$V_{out} =$

$V(v_m) =$

$I(R_i) =$

$I(R_o) =$

$I(R_1) = I(R_2) =$

$I(R_L) =$

Do the values simulated with LTSPICE match reasonably well? (is it within 10-20 %?) _____

$V_{out} =$

$V(v_m) =$

$I(R_i) =$

$I(R_o) =$

$I(R_1) =$

$I(R_2) =$

$I(R_L) =$

How do you expect V_{out} to change if R_o increases to 100Ω ?


$V_{out} =$

Does the value simulated with LTSPICE match reasonably well? (is it within 10-20 %?) _____

$V_{out} =$

Lab. - Part C

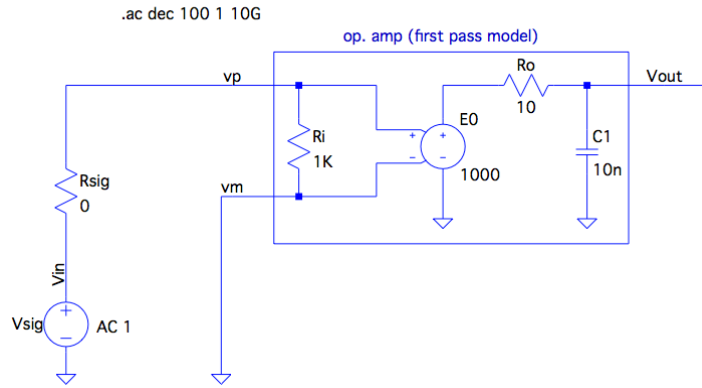Modify the op amp model by reducing its input resistance to $1\text{K}\Omega$.



Do you expect V_{out}/V_{in} to change? _____

Why? _____

Run the AC analysis command and **attach the plot of the magnitude?**

LTSPICE V_{out}/V_{in} in dB = _____

Let's now change R_{sig} to $1\text{K}\Omega$.

Do you expect V_{out}/V_{in} to change? _____

Why? _____


Compute the value of V_{out}/V_{in} and show the symbolic expression you used:

V_{out}/V_{in} in dB = _____

LTSPICE V_{out}/V_{in} in dB = _____

Lab. - Part D

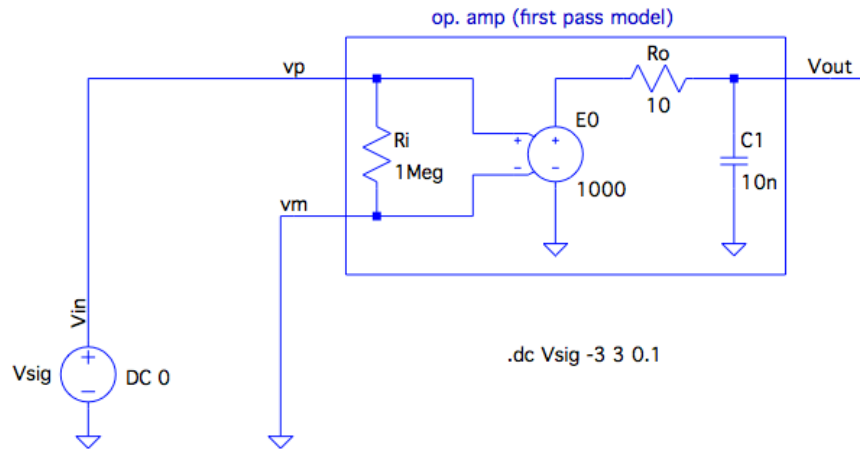Use LTSPICE to sweep the DC signal applied to the input of the open-loop op. amp from -3V to 3V.



Run the DC sweep analysis command and plot V_{out} vs. V_{in} simulation obtained. **Attach the plot.** What are the max and min values V_{out} according to the LTSPICE simulation?

LTSPICE $V_{out}(\max) =$


LTSPICE $V_{out}(\min) =$

Assuming the op-amp has a positive supply rail of +10V and a negative supply rail of -10V what are the max and min values of V_{in} that can be applied to the op-amp without having the output saturating to the supply rail values

$V_{in}(\max) =$


$V_{in}(\min) =$

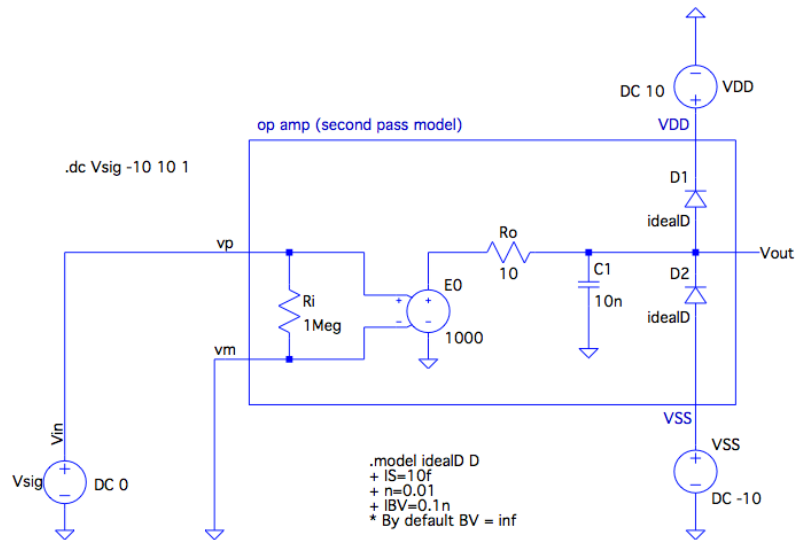Modify the op amp model as follows to make the V_{out} vs. V_{in} DC transfer characteristic saturate at the supply rails.



Run the DC sweep analysis command and plot the V_{out} vs. V_{in} DC transfer characteristic. **Attach the plot.**

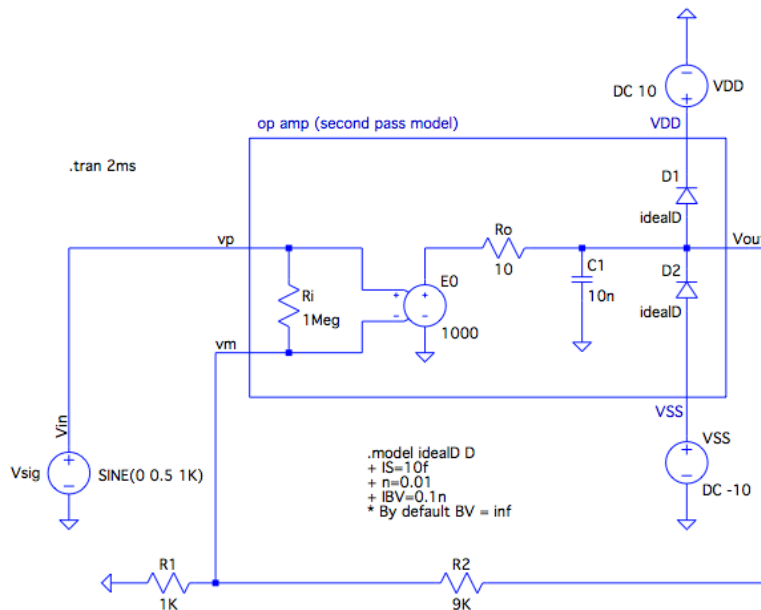Modify your circuit to build a non-inverting op amp based amplifier. This time apply at the input a sinusoidal signal with 0.5 peak voltage and 1KHz frequency.



What is the max voltage at the output?

$V_{out(max)} =$ _____

What is the frequency of V_{out} ?

$f =$ _____

Run a TRAN analysis simulation and plot the V_{out} vs. time. Select the run time of the simulation to show exactly two full cycles of the V_{out} sinusoid.

Stop time = _____

Attach the plot.

What happen to V_{out} if you increase the peak voltage of V_{sig} to 2V?

$V_{out(max)} =$

$V_{out(min)} =$

Run the TRAN analysis simulation and plot the V_{out} vs. time. **Attach the plot.**

Modify the peak voltage of V_{sig} back to 0.5V, but this time increase the frequency to 1GHz. Run a TRAN analysis simulation and plot the V_{out} vs. time. Run the simulation for 12ns, but start saving the data only at 10ns

Attach the plot.

Why is $V_{out(max)}$ smaller than 0.5V times the amplifier gain?
