


The purpose of this laboratory is:

Model and simulate the DC characteristic of diodes and observe and quantify how the diode's behavior is affected by temperature.

Pre-Lab:

Using the 1N4148 diode model provided by LTSPICE, plot the I_D vs. V_D curve of the diode in FORWARD and REVERSE region at room temperature.

Room temperature = _____

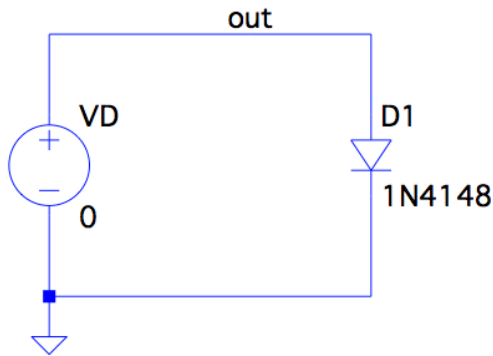

What is the default temperature (TNOM) used by SPICE simulation? _____

What is the unit of temperature used by SPICE? _____

What type of Analysis do you need to use for plotting the I_D vs. V_D curve of the diode? _____

Write down the SPICE directive you used to obtain your plot. _____

What is a reasonable range of V_D values over which plot the I_D characteristic? _____

Write down the SPICE directive you used to obtain your plot. _____

Compare qualitatively your plots with the information provided by the diode Data Sheet:

Does the model provided seem to capture the forward region behavior adequately? _____

Does the model provided seem to capture the reverse region behavior adequately? _____

Does the model provided seem to capture the reverse breakdown region behavior adequately? _____

Lab:

Modify your Prelab circuit to use the following model rather than the default one provided by LTSPICE:

```
.model D1N4148 D (IS=0.1PA, RS=16 CJO=2PF TT=12N BV=100 IBV=0.1PA)
```

Plot the ID vs. VD characteristic of the diode in forward region, reverse region, and reverse breakdown region at three different temperatures: -50 centigrade, 25 centigrade and 50 centigrade.
HINT: to change temperature use the parametric analysis command .STEP

1. Attach the plot. Make sure to clearly label the three curves with the corresponding temperature.
2. Determine the forward temperature coefficient $dV_o/dT \approx \Delta V_o/\Delta T$.

What is the forward temperature coefficient of the diode?

| Diode | Temperature coeff. [units] | I_o [units] | ΔV_o [units] | ΔT [units] |
|--------|----------------------------|---------------|----------------------|--------------------|
| 1N4148 | | | | |

Shortly explain/show how it was computed using your graphs.

Compare your graphically determined results to the well-known theoretical equation:

$$dV_o/dT \approx -2 \text{ mV}/^\circ\text{C}$$

%Error = 100 x (measured - theoretical) / theoretical =

3. Measure the reverse breakdown voltage. Does the breakdown voltage increase, decrease, or remain constant when temperature increases? _____

| Diode Type | V_{RR} [units] at $-50\text{ }^{\circ}\text{C}$ | V_{RR} [units] at $25\text{ }^{\circ}\text{C}$ | V_{RR} [units] at $50\text{ }^{\circ}\text{C}$ |
|------------|---|--|--|
| 1N4148 | | | |