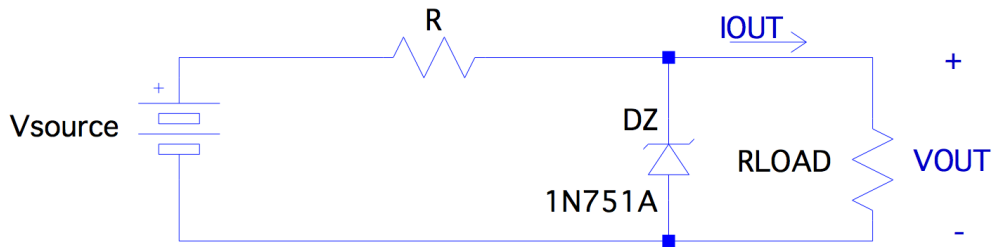


Objectives


To design, construct, and test a Zener diode voltage regulator.

Instructions

Your regulator requires a 1N751A and thus has a nominal zener voltage of 5.1V. Your design should resemble the following Figure.



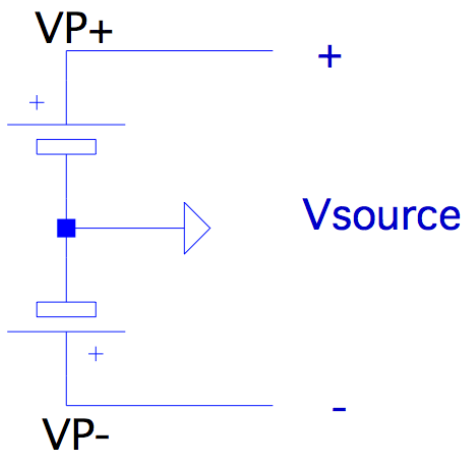NOTE: Use the programmable voltage supplies $VP+$ and $VP-$ to generate the required V_{source}



DESIGN TIPS:

Make sure the diode will remain in the breakdown region over the specified range of operation ($10V \leq V_{source} \leq 15V$). In addition, make sure the regulator will not get damaged under any possible loading condition (loads can range from $R_{LOAD}=0 \Omega$ to $R_{LOAD} = \infty \Omega$).

The nominal load is $R_{LOAD} = 250 \Omega$.

Pre-Lab:

1. Calculate the expected range of output voltages and currents (extremes) using a piecewise linear circuit model for the diode. Assume the load is nominal. Show your work.

_____ $\leq I_{out} \leq$ _____

_____ $\leq V_{out} \leq$ _____

2. Show the piecewise model you used for your zener diode (plot I_D vs. V_D)

Lab:

3. With a load of 250 ohm, vary the DC source voltage from 10V to 15 V and measure the output voltage at several points. Plot the output voltage as a function of the source voltage.

$$R_{\text{LOAD}} = 250 \, \Omega$$

V_{source} [V]	V_{OUT} [V]
10	
11	
12	
13	
14	
15	

V_{OUT} vs. V_{source} Plot:

Repeat for $R_{LOAD} = \infty \Omega$

V_{source} [V]	V_{OUT} [V]
10	
11	
12	
13	
14	
15	

V_{OUT} vs. V_{source} Plot:

Determine the line regulation: (Line regulation $\equiv \Delta V_{out}/\Delta V_{source} \times 100$)

4. With a source voltage of 15 V, vary the load current from 0 to 20 mA by changing the load resistor R_{LOAD} from _____ to _____ (Fill the blanks)

For $V_{source} = 15V$

$R_{LOAD} [\Omega]$	$I_{OUT} [mA]$	$V_{OUT} [V]$
	0	
	20	

Plot the output current vs. the output voltage.

Repeat for $V_{\text{source}} = 10 \text{ V}$

$R_{\text{LOAD}} [\Omega]$	$I_{\text{OUT}} [\text{mA}]$	$V_{\text{OUT}} [\text{V}]$
	0	
	20	

Plot the output current vs. the output voltage.

Determine the load regulation:

$$\text{Load regulation} \equiv 100 \times (V_{\text{out, no load}} - V_{\text{out, full load}}) / (I_{\text{L, no load}} - I_{\text{L, full load}}) = 100 \times \Delta V_{\text{out}} / \Delta I_{\text{L}}$$

5. Did the Zener diode stay in breakdown the whole time? _____

6. If not indicate on your plots where the diode was not in breakdown and explain why the diode was not in breakdown.