

Name: _____

Solution

EE303 - Final Exam

Closed Book:

Two 8.5"x11" sheet of handwritten notes permitted
Calculator permitted


Important Notes:

- Read each problem completely and thoroughly
- Summarize all your answers in the boxes provided on these exam sheets
- Make sure to mark the units on your answers!
- Do all your work on the exams sheets provided. If you use any additional sheets, please turn them in, so we can consider all work for partial credit
- Do not forget to put your name in the space above

Problem #	Points	Score
1	10	
2	20	
3	20	
4	20	
5	20	
TOTAL	90	



solution - problem 1

(b) differential half circuit

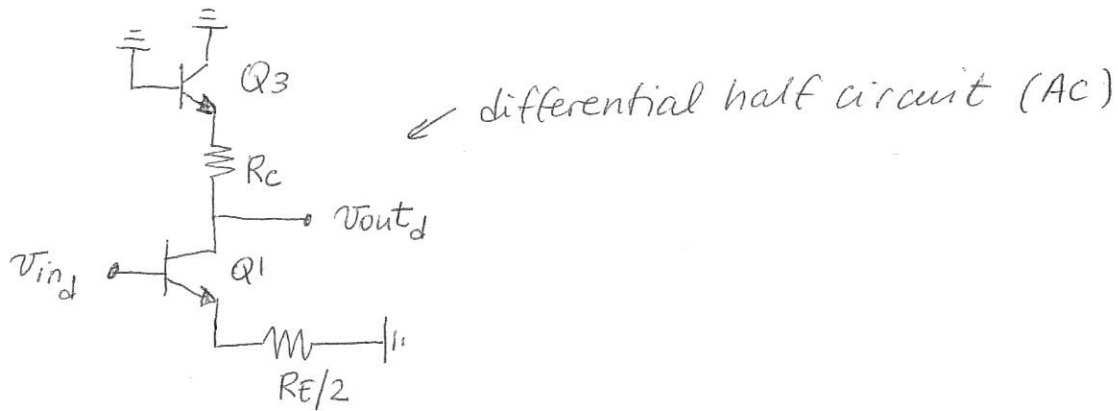

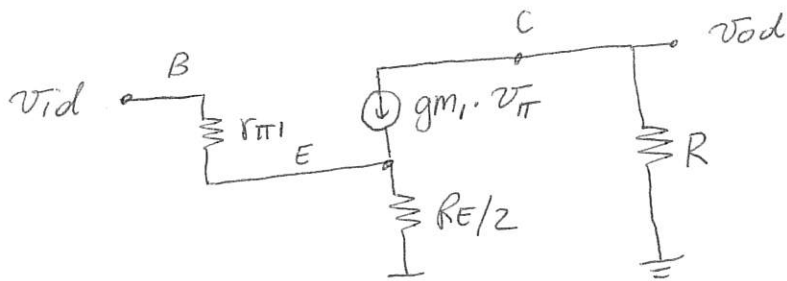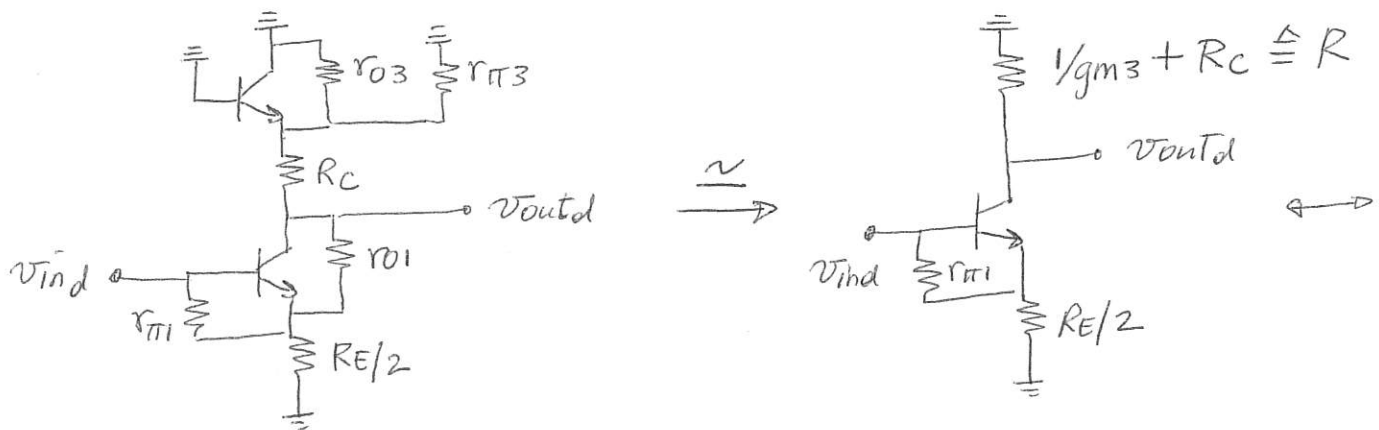(a) assume $r_o = \infty$ and $\beta = g_m \cdot r_{\pi} \gg 1 \Leftrightarrow r_{\pi} \gg \frac{1}{g_m}$

$$\frac{v_{out,d}}{v_{ind}} = \frac{-R}{\frac{1}{g_{m1}} + \frac{R_E}{2} + \frac{R_E}{2 \cdot \beta_1}} \approx \frac{-R}{\frac{1}{g_{m1}} + \frac{R_E}{2}} \quad \beta \gg 1$$



$$v_{out,d} = -g_{m1} \cdot v_{\pi} \cdot R$$

$$v_{\pi} = v_{id} - \frac{R_E}{2} \left(g_{m1} \cdot v_{\pi} + \frac{v_{\pi}}{r_{\pi 1}} \right)$$

$$v_{\pi} \left(1 + g_{m1} \frac{R_E}{2} + \frac{R_E}{2 r_{\pi 1}} \right) = v_{id}$$

$$v_{out,d} = -g_{m1} \cdot R \cdot \frac{v_{id}}{1 + g_{m1} \frac{R_E}{2} + \frac{R_E}{2 r_{\pi 1}}}$$

Name: _____

Problem 1 [10 pts]

Consider the differential pair illustrated in Fig. 10.70. Assuming perfect symmetry and $V_A = \infty$, and $\beta \gg 1$.

- (a) Determine the voltage gain.
- (b) Draw the differential AC half circuit


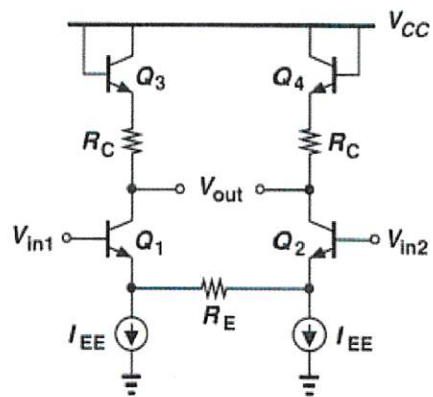


Figure 10.70

$V_{out}/(V_{in1}-V_{in2})$	
-----------------------------	--

solution - problem 2

(a)

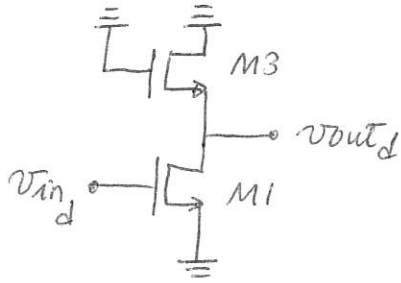


assume finite r_o

← differential half AC circuit

$$\frac{v_{od}}{v_{id}} = -g_{m1} \cdot (r_{o1} \parallel r_{o3} \parallel \frac{1}{g_{m3}})$$

(b) assume finite r_o

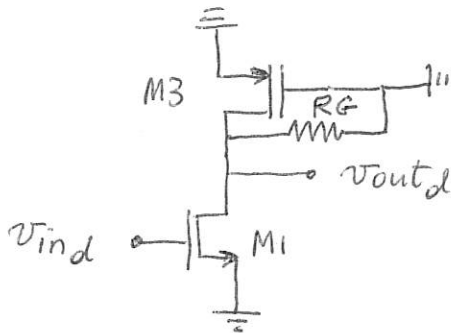

$$R_G \triangleq R_1 = R_2$$

$$\frac{v_{out,d}}{v_{in,d}} = -g_{m1} (r_{o1} \parallel R_G \parallel r_{o3})$$

Name: _____

Problem 2 [20 pts]

Calculate the differential voltage gain of the circuits depicted in Fig. 10.76. Assume perfect symmetry and $\lambda > 0$.

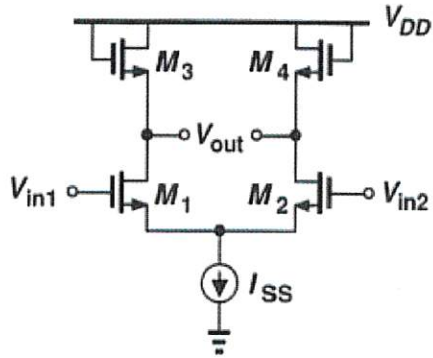


Fig. 10.76 (a)


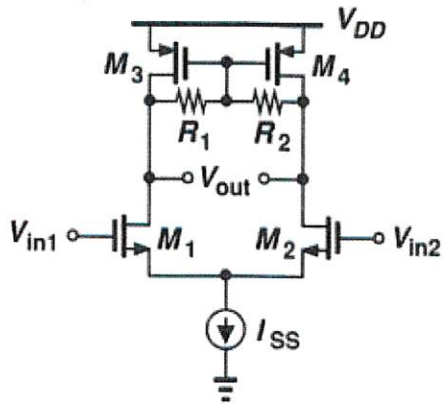


Fig. 10.76 (b)

(a) $V_{out}/(V_{in1}-V_{in2}) =$	
(b) $V_{out}/(V_{in1}-V_{in2}) =$	


solution problem 3

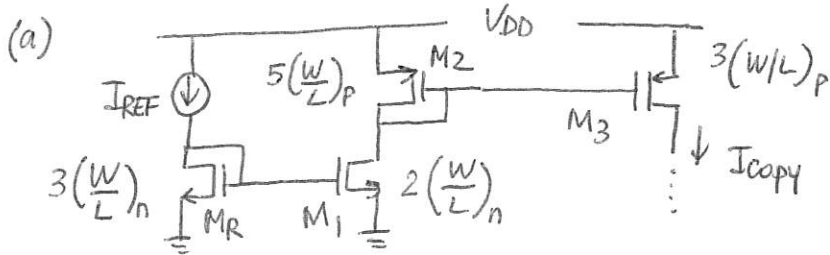

$$V_{GS_R} = V_{GS_1} \rightarrow I_{D1} = \frac{2}{3} I_{REF} \quad I_{D1} = I_{D2}$$

$$V_{GS2} = V_{GS3} \rightarrow \frac{I_{COPY}}{I_{D1}} = \frac{3(W/L)_P}{5(W/L)_P} = \frac{3}{5}$$
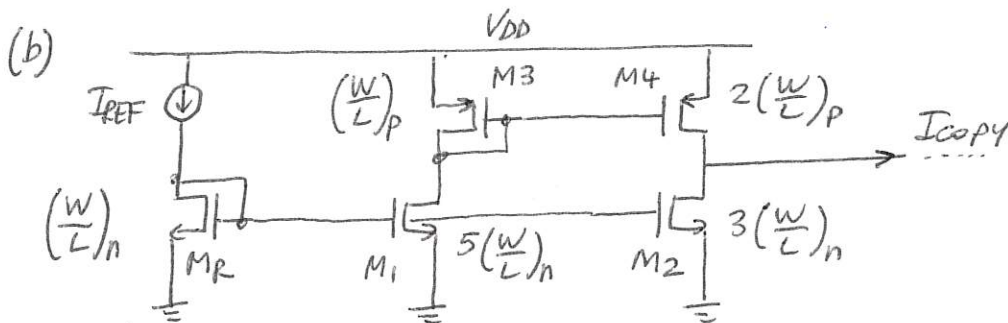
$$I_{COPY} = \frac{3}{5} I_{D1} = \frac{3}{5} \cdot \frac{2}{3} I_{REF} = \frac{2}{5} I_{REF}$$



$$I_{COPY} = I_{D4} - I_{D2}$$

$$I_{D1} = I_{D3} = I_{REF} \cdot 5 \quad \leftarrow \text{since: } V_{GS_R} = V_{GS1}$$

$$V_{GS3} = V_{GS4} \rightarrow \frac{I_{D4}}{I_{D3}} = \frac{2(W/L)_P}{(W/L)_P} \rightarrow I_{D4} = 2 I_{D3} = 10 I_{REF}$$

$$V_{GS_R} = V_{GS2} \rightarrow \frac{I_{D2}}{I_{REF}} = \frac{3(W/L)_n}{(W/L)_n} \rightarrow I_{D2} = 3 I_{REF}$$

In conclusion:

$$I_{COPY} = 10 I_{REF} - 3 I_{REF} = 7 I_{REF}$$

Name: _____

Problem 3 [15 pts]

Calculate I_{copy} in each of the circuits shown in Fig. 9.71. Assume all of the transistors operate in saturation.

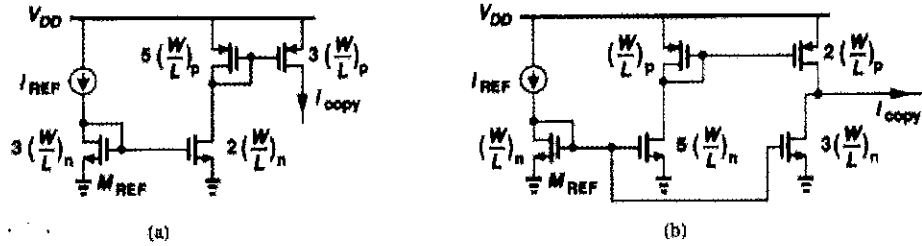




Figure 9.71

a) $I_{copy} =$	
b) $I_{copy} =$	

Solution problem 4

assume $g_m r_o \gg 1$

(a)

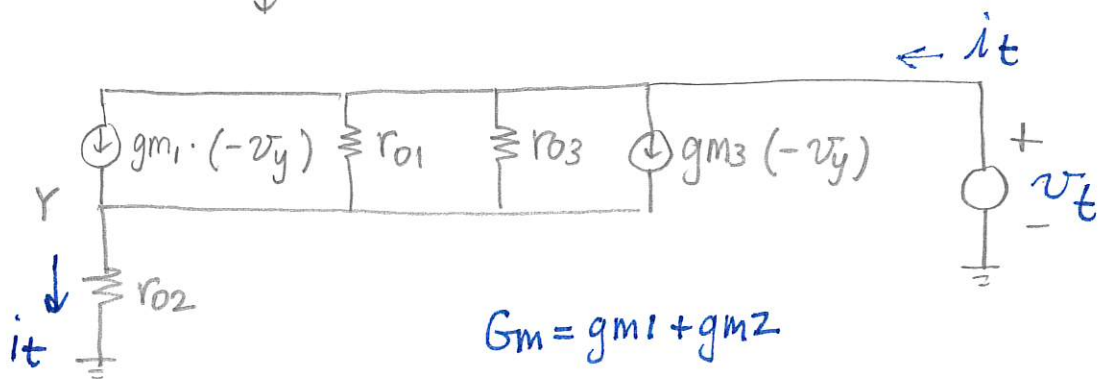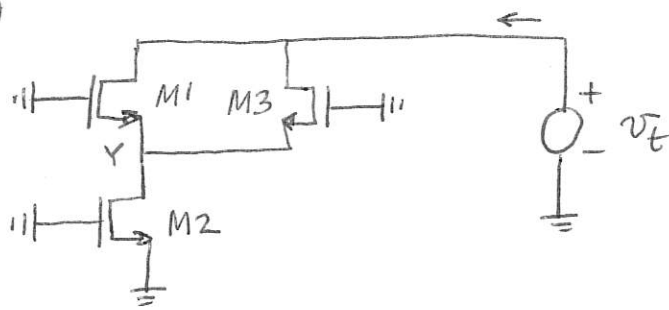

$$v_y = r_{o2} \cdot i_t$$

$$i_t = \frac{(v_t - v_y)}{r_{o1}} + \frac{(v_t - v_y)}{r_{o3}} - v_y (g_{m1} + g_{m3})$$

$$i_t = \frac{v_t}{r_{o1}} + \frac{v_t}{r_{o3}} - \frac{r_{o2}}{r_{o1}} i_t - \frac{r_{o2}}{r_{o3}} i_t - r_{o2} i_t \cdot G_m$$



$$i_t \left(1 + \frac{r_{o2}}{r_{o1}} + \frac{r_{o2}}{r_{o3}} + r_{o2} G_m \right) = v_t \left(\frac{1}{r_{o1}} + \frac{1}{r_{o3}} \right)$$

$$\frac{v_t}{i_t} = (r_{o1} \parallel r_{o3}) \cdot \left[1 + r_{o2} / (r_{o1} \parallel r_{o3}) + r_{o2} G_m \right] =$$

$$= (r_{o1} \parallel r_{o3}) + r_{o2} + r_{o2} (r_{o1} \parallel r_{o3}) G_m =$$

$$\approx r_{o2} (r_{o1} \parallel r_{o3}) G_m$$

(b)

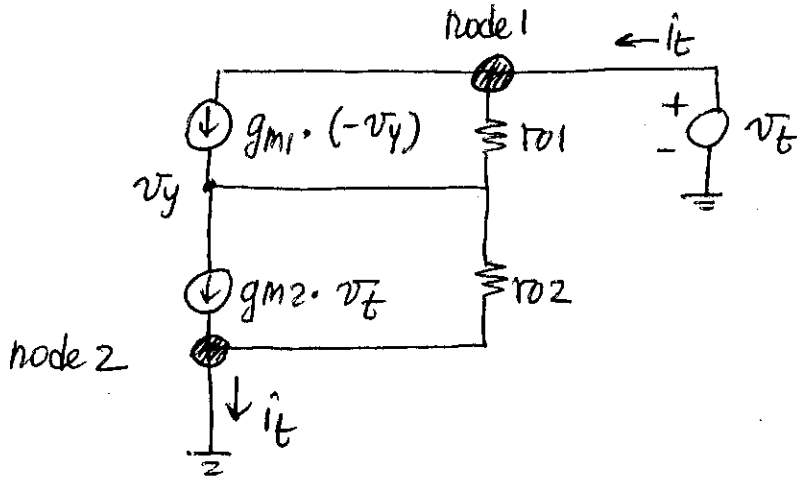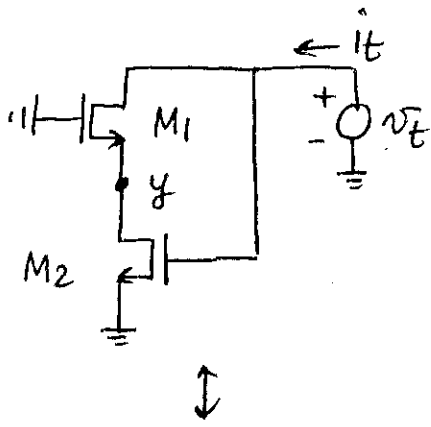

KCL at node 1 :

$$i_t = -g_{m1} v_y + \frac{v_t - v_y}{r_{o1}} \rightarrow$$

$$i_t = -g_{m1} v_y + \frac{v_t}{r_{o1}} - \frac{v_y}{r_{o1}} \rightarrow i_t = \frac{v_t}{r_{o1}} - v_y \left(g_{m1} + \frac{1}{r_{o1}} \right)$$

KCL at node 2 :

$$i_t = g_{m2} v_t + \frac{v_y}{r_{o2}} \rightarrow v_y = r_{o2} \left(i_t - g_{m2} v_t \right) \rightarrow$$

$$v_y = r_{o2} \cdot i_t - g_{m2} r_{o2} \cdot v_t$$

let's take the result from KCL at node 1 and right away assume $r_{o1} g_{m1} \gg 1$:

$$i_t = \frac{v_t}{r_{o1}} - v_y \left(\frac{g_{m1} r_{o1} + 1}{r_{o1}} \right) \approx \frac{v_t}{r_{o1}} - v_y \frac{g_{m1} r_{o1}}{r_{o1}}$$

replace the value of v_y found applying KCL at node 2 :

$$i_t \approx \frac{v_t}{r_{o1}} - \frac{g_{m1} r_{o1}}{r_{o1}} [r_{o2} i_t - g_{m2} r_{o2} v_t] \rightarrow$$

$$i_t \approx \frac{v_t}{r_{o1}} - g_{m1} r_{o2} i_t + g_{m1} g_{m2} r_{o2} v_t \rightarrow$$

$$i_t (1 + g_{m1} r_{o2}) = v_t \left(\frac{1}{r_{o1}} + g_{m1} g_{m2} r_{o2} \right)$$

$$\frac{v_t}{i_t} \approx \frac{1 + g_{m1} r_{o2}}{\frac{1}{r_{o1}} + g_{m1} g_{m2} r_{o2}}$$

$$\frac{v_t}{i_t} \approx \frac{r_{o1} (1 + g_{m1} r_{o2})}{1 + g_{m1} g_{m2} r_{o1} r_{o2}} \approx \leftarrow g_{m1} r_{o1} \gg 1$$

$$\approx \frac{r_{o1} (1 + g_{m1} r_{o2})}{g_{m1} g_{m2} r_{o1} r_{o2}} = \frac{1 + g_{m1} r_{o2}}{g_{m1} g_{m2} r_{o2}} \approx$$

$$\approx \frac{g_{m1} r_{o2}}{g_{m1} g_{m2} r_{o2}} \approx \frac{1}{g_{m2}}$$

Name: _____

Problem 4 [20 pts]

Compute the output resistance of the circuits depicted in Fig. 9.50. Assume all of the transistors operate in saturation and $g_{mfo} \gg 1$.

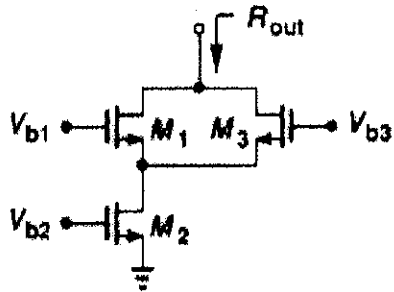


Fig 9.50 (a)


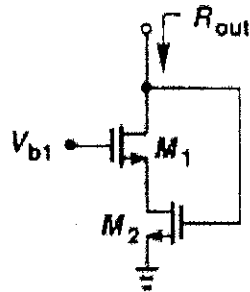


Fig 9.50 (b)

a) $R_{out} =$	
b) $R_{out} =$	

solution problem 5

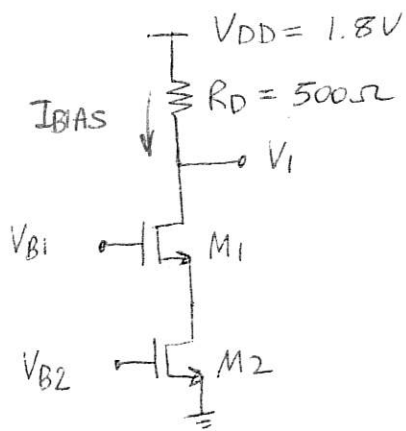

$$(W/L)_1 = \frac{20}{0.18}$$

$$(W/L)_2 = \frac{40}{0.18}$$

$$\mu C_{ox} = 100 \mu\text{A}/\text{V}^2$$

$$V_{TH} = 0.4 \text{ V}$$

$$I_{BIAS} = 1 \text{ mA}$$

(a) highest allowable value of V_{B1}

$$I_{BIAS} = \frac{\mu C_{ox}}{2} \left(\frac{W}{L}\right)_2 V_{OV2}^2$$

$$V_{OV2}^2 = \frac{2 I_{BIAS}}{\mu C_{ox} (W/L)_2} \rightarrow V_{OV2} = \sqrt{\frac{2 \text{ m} \cdot 0.18}{100 \mu \cdot 40}} =$$

$$\approx 300 \text{ mV}$$

$$V_{B2} = V_{GS2} = V_{OV2} + V_{TH} = 700 \text{ mV}$$

$$V_1 = V_{DD} - R_D \cdot I_{BIAS} = 1.8 - 500 \cdot 1 \text{ m} = 1.3 \text{ V}$$

$$V_{OV1} = \sqrt{\frac{2 I_{BIAS}}{\mu C_{ox} (W/L)_1}} = \sqrt{\frac{2 \text{ m} \cdot 0.18}{100 \mu \cdot 20}} \approx 424.26 \text{ mV}$$

$$V_{GS1} = V_{OV1} + V_{TH} = 824.26 \text{ mV}$$

$$\underbrace{V_1 = V_{S1}}_{V_{DS1}} \geq \underbrace{V_{GS1} - V_{TH}}_{V_{OV1}} = V_{B1} - V_{S1} - V_{TH}$$

$$V_{B1} \leq V_1 + V_{TH} = 1.3 \text{ V} + 0.4 \text{ V} = 1.7 \text{ V}$$

Name: _____

Problem 5 [10 pts]

Consider the circuit shown in Fig. 9.49, where $V_{DD} = 1.8$ V, $(W/L)_1 = 20/0.18$, and $(W/L)_2 = 40/0.18$. Assume $\mu_n C_{ox} = 100 \mu\text{A}/\text{V}^2$ and $V_{TH} = 0.4$ V.

- (a) If we require a bias current of 1 mA and $R_D = 500 \Omega$, what is the highest allowable value of V_{b1} ?
 (b) With such a value chosen for V_{b1} , what is the value of V_X ?

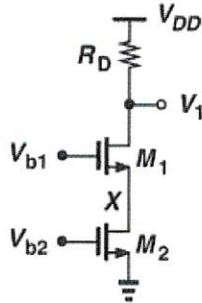


Figure 9.49

(a) $V_{b1}(\text{max}) =$	
(b) $V_X =$	

(b) $V_{B1} = 1.7\text{V}$

$$I_{BIAS} = \frac{\mu_n C_{ox}}{2} \left(\frac{W}{L}\right)_1 \underbrace{(V_{B1} - V_X - V_{TH})}_{V_{GS1}}^2$$

$$V_{B1} - V_X - V_{TH} = \underbrace{V_{GS1}}_{V_{OV1}}$$

$$V_X = V_{B1} - V_{OV1} - V_{TH} = 1.7 - 424\text{m} - 0.4 \approx 0.88\text{V}$$

