

EE303 - Problem Set

Problem 1

Consider the differential pair illustrated in Fig. 10.70. Assuming perfect symmetry and $V_A = \infty$,

- Determine the voltage gain.
- Under what condition does the gain become *independent* of the tail currents? This is an example of a very linear circuit because the gain does not vary with the input or output signal levels.

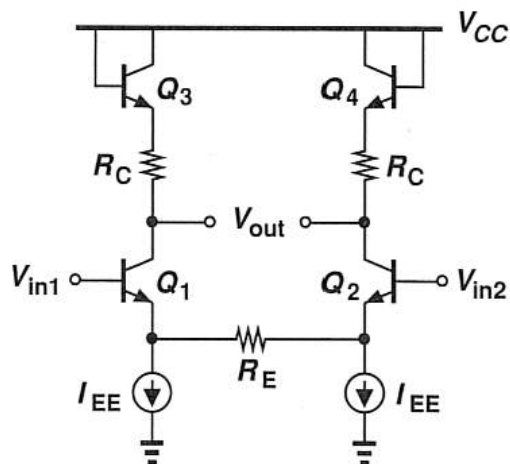


Figure 10.70

Problem 2

Consider the MOS differential pair of Fig. 10.24. What happens to the tail node voltage if (a) the width of M_1 and M_2 is doubled, (b) I_{SS} is doubled, (c) the gate oxide thickness is doubled?

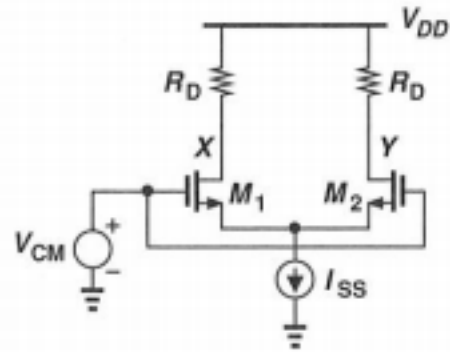


Figure 10.24 Response of MOS differential pair to input CM variation.

Problem 3

Calculate the differential voltage gain of the circuits depicted in Fig. 10.76. Assume perfect symmetry and $\lambda > 0$.

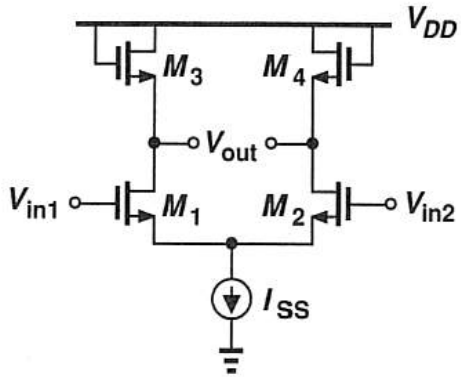


Fig. 10.76 (a)

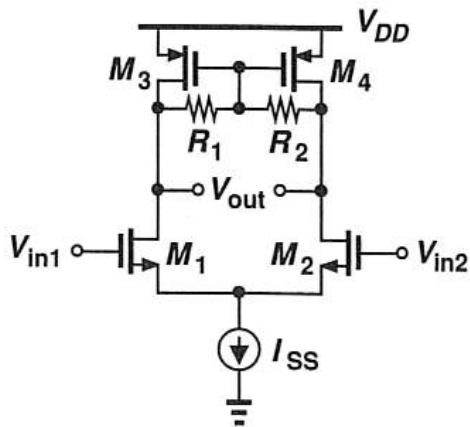


Fig. 10.76 (b)

Problem 4

Design an nMOST differential pair with the following parameters:

$I_{TAIL} = 0.4 \text{ mA}$, $V_{TH} = 0.5 \text{ V}$, $\mu C_{ox}(W/L) = 4 \text{ mA/V}^2$, $V_{DD} = 1.5 \text{ V}$, $V_{SS} = -1.5 \text{ V}$, $R_D = 2.5 \text{ K}\Omega$

Neglect channel length modulation:

Analytically:

- Find V_{OV} and V_{GS} at equilibrium
- For $V_{CM} = 0$ find the values of V_S , I_{D1} , I_{D2} , V_{D1} , V_{D2}
- Repeat (b) for $V_{CM} = 1 \text{ V}$
- Repeat (b) for $V_{CM} = 0.2 \text{ V}$
- What is the highest value of V_{CM} for which M_1 and M_2 remain in saturation?
- If the current source I_{TAIL} requires a minimum voltage of 0.4 V to operate properly, what is the lowest value allowed for V_{CM} ?
- What is the range of differential mode operation (i.e. the range of $V_{id} = V_{in1} - V_{in2}$ for which M_1 and M_2 are "ON")
- Assuming the output differential pair is taken single-ended, plot the differential voltage amplification $A_{Vd} = v_{out1}/v_{id}$ and the common mode voltage amplification $A_{Vc} = v_{oc}/v_{ic}$.

