

EE303 - Problem Set

In the following problems, unless otherwise stated, assume $\mu_n C_{ox} = 200 \mu\text{A}/\text{V}^2$, $\mu_p C_{ox} = 100 \mu\text{A}/\text{V}^2$, $\lambda = 0$, and $V_{TH} = 0.4 \text{ V}$ for NMOS devices and -0.4 V for PMOS devices.

Problem 1

We wish to design the circuit of Fig. 7.40 for a drain current of 1 mA . If $W/L = 20/0.18$, compute R_1 and R_2 such that the input impedance is at least $20 \text{ k}\Omega$.

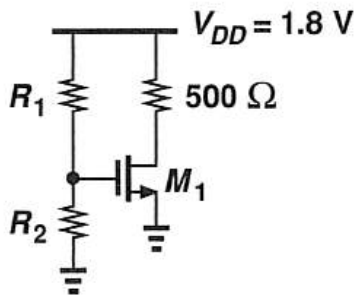


Figure 7.40

Problem 2

Consider the circuit shown in Fig. 7.41. Calculate the maximum transconductance that M_1 can provide (without going into the triode region.)

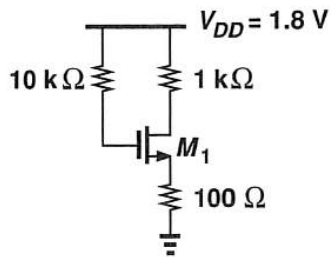


Figure 7.41

Problem 3

- The circuit of Fig. 7.42 must be designed for a voltage drop of 200 mV across R_S .
- Calculate the minimum allowable value of W/L if M_1 must remain in saturation.
 - What are the required values of R_1 and R_2 if the input impedance must be at least 30 k Ω ?

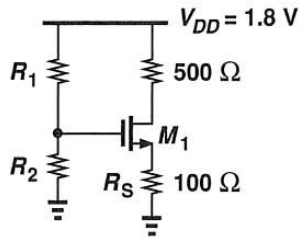


Figure 7.42

Problem 4

The self-biased stage of Fig. 7.44 must be designed for a drain current of 1 mA. If M_1 is to provide a transconductance of $1/(100 \Omega)$, calculate the required value of R_D .

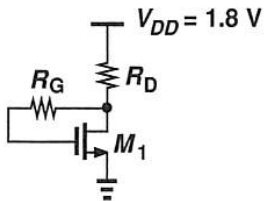


Figure 7.44

Problem 5

The CS stage of Fig. 7.56 must provide a voltage gain of 10 with a bias current of 0.5 mA. Assume $\lambda_1 = 0.1 \text{ V}^{-1}$, and $\lambda_2 = 0.15 \text{ V}^{-1}$.

- (a) Compute the required value of $(W/L)_1$.
- (b) If $(W/L)_2 = 20/0.18$, calculate the required value of V_B .

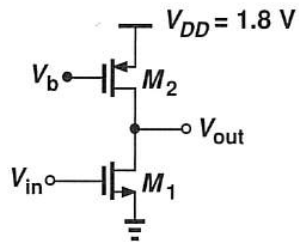


Figure 7.56