

## EE303 - Problem Set

In the following problems, unless otherwise stated, assume  $\mu_n C_{ox} = 200 \mu\text{A}/\text{V}^2$ ,  $\mu_p C_{ox} = 100 \mu\text{A}/\text{V}^2$ ,  $\lambda = 0$ , and  $V_{TH} = 0.4 \text{ V}$  for NMOS devices and  $-0.4 \text{ V}$  for PMOS devices.

### Problem 1

In the common-source stage of Fig. 7.54,  $W/L = 30/0.18$  and  $\lambda = 0$ .

- (a) What gate voltage yields a drain current of  $0.5 \text{ mA}$ ? (Verify that  $M_1$  operates in saturation.)

 


Figure 7.54

- (b) With such a drain bias current, calculate the voltage gain of the stage.

### Problem 2

We wish to design the circuit shown in Fig. 7.59 for a voltage gain of 3. If  $(W/L)_1 = 20/0.18$ , determine  $(W/L)_2$ . Assume  $\lambda = 0$ .

 


Figure 7.59

Problem 3

The degenerated CS stage of Fig. 7.61 must provide a voltage gain of 4 with a bias current of 1 mA. Assume a drop of 200 mV across  $R_S$  and  $\lambda = 0$ .

 



Figure 7.61

- (a) If  $R_D = 1 \text{ k}\Omega$ , determine the required value of  $W/L$ . Does the transistor operate in saturation for this choice of  $W/L$ ?
- (b) If  $W/L = 50/0.18$ , determine the required value of  $R_D$ . Does the transistor operate in saturation for this choice of  $R_D$ ?

Problem 4

Calculate the voltage gain, the input impedance and the output impedance of the circuit depicted in fig. Assume channel length modulation is negligible.

NOTE:  $V_b$  is a DC bias voltage.

 

Problem 5

Consider the circuit of Fig. 7.72, where a common-source stage ( $M_1$  and  $R_{D1}$ ) is followed by a common-gate stage ( $M_2$  and  $R_{D2}$ ).

- (a) Writing  $v_{out}/v_{in} = (v_X/v_{in})(v_{out}/v_X)$  and assuming  $\lambda = 0$ , compute the overall voltage gain.
- (b) Simplify the result obtained in (a) if  $R_{D1} \rightarrow \infty$ . Explain why this result is to be expected.

 


Figure 7.72

NOTE:  $V_b$  is a DC bias voltage.

Problem 6

We wish to design the source follower shown in Fig. 7.77 for a voltage gain of 0.8. If  $W/L = 30/0.18$  and  $\lambda = 0$ , determine the required gate bias voltage.

 


Figure 7.77

Problem 7

We wish to design the source follower of Fig. 7.79 for a voltage gain of 0.8 with a power budget of 3 mW. Compute the required value of  $W/L$ . Assume  $C_1$  is very large and  $\lambda = 0$ .

 


Figure 7.79