

Name: Solution

EE303 - Midterm Exam #1

Closed Book:

One 8.5"x11" sheet of handwritten notes permitted
Calculator permitted

Important Notes:

- Read each problem completely and thoroughly
- Summarize all your answers in the boxes provided on these exam sheets
- Make sure to mark the units on your answers!
- Do all your work on the exams sheets provided. If you use any additional sheets, please turn them in, so we can consider all work for partial credit
- Do not forget to put your name in the space above

Problem #	Points	Score
1	20	
2	5	
3	5	
4	15	
5	10	
6	5	
7	20	
8	20	
TOTAL	100	

Name: _____

Problem 1 [20 pts]

Given the circuit in Figure 1 find an expression for R_{in} and R_{out}


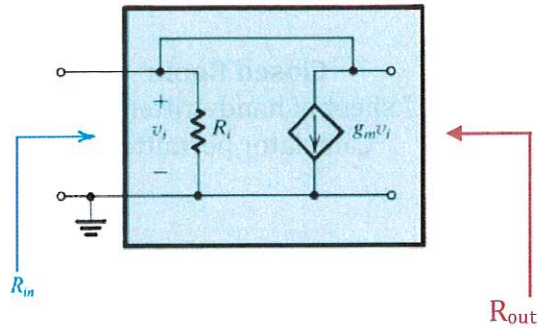


Figure 1

$R_{in} =$	$R_i \parallel \frac{1}{g_m}$
$R_{out} =$	0


①

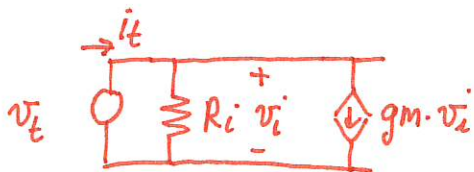

$$v_i = v_T$$

$$R_{in} = \frac{v_T}{i_T} = R_i \parallel \frac{1}{g_m}$$

②

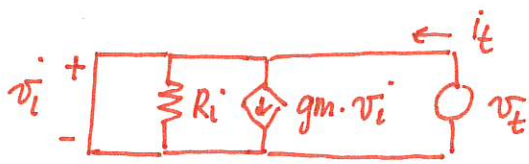

$$v_i = 0$$

$$R_{out} = \frac{v_T}{i_T} = 0$$

Name: _____

Problem 2 [5 pts]

A silicon wafer is doped with donors at a concentration of $N_D = 10^{15} \text{ cm}^{-3}$. Assume the mobility for the doped silicon is $\mu_n = 1000 \text{ cm}^2/(\text{V}\cdot\text{s})$ and $\mu_p = 500 \text{ cm}^2/(\text{V}\cdot\text{s})$ and n_i at room temperature is 10^{10} cm^{-3} . What is the drift current density

- (a) What type is material (n or p)?
- (b) Find the resistivity of the material at room temperature?
- (c) Calculate the drift current density for an applied electric field of 100 V/cm

Type of material =	N-TYPE
$1/\sigma =$	$6.25 \ \Omega \text{ cm}$
$J_{\text{drift}} =$	16 A/cm^2

$$\sigma = q (\mu_n \cdot n + \mu_p \cdot p)$$

$$n = 10^{15} \text{ cm}^{-3} \quad p = \frac{n_i^2}{n} = \frac{10^{20}}{10^{15}} = 10^5 \text{ cm}^{-3}$$

$$\sigma = 1.6 \times 10^{-19} (1000 \times 10^{15} + 500 \times 10^5) \approx 0.16 \ \Omega \cdot \text{cm}$$

$$J_{\text{drift}} = \sigma \cdot E = 0.16 \times 100 = 16 \text{ A/cm}^2$$

Problem 3 [5 pts]

Find the change in diode voltage if the current changes from 0.1 mA to 1 mA

$\Delta V_D =$	60 mV
----------------	-----------------

$$I_D \approx I_S e^{V_D/V_T}$$

$$I_{D1} = 0.1 \text{ mA} \quad I_{D2} = 1 \text{ mA}$$

$$\frac{I_{D1}}{I_{D2}} = e^{(V_{D1} - V_{D2})/V_T} \rightarrow \ln \frac{I_{D1}}{I_{D2}} = \frac{V_{D1} - V_{D2}}{V_T}$$

$$-\ln \frac{I_{D1}}{I_{D2}} = \frac{V_{D2} - V_{D1}}{V_T} \rightarrow \Delta V_D \triangleq V_{D2} - V_{D1} = V_T \cdot \ln \frac{I_{D2}}{I_{D1}} =$$

$$\approx 60 \text{ mV}$$

Name: _____

Problem 4 [15 pts]

Consider the circuit shown in Figure 2. A string of three diodes is used to provide a constant voltage of about 2.4 V. We want to calculate the percentage change in the regulated voltage caused by:

- (a) A 10% change in the power-supply voltage without the load
- (b) A 10% change in the power-supply voltage with a load of 1-k Ω connected

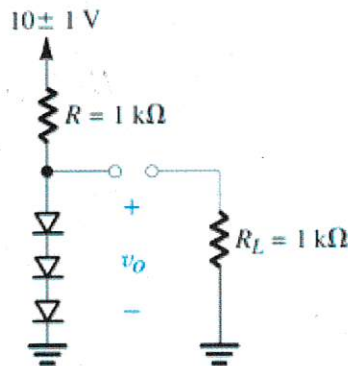


Figure 2

(a) $\Delta V_o / \Delta V_{\text{supply}} =$	1.02 %
(b) $\Delta V_o / \Delta V_{\text{supply}} =$	1.46 %

a)
$$I_D = \frac{V_{SS} - V_o}{R} = \frac{10 - 2.4}{1K} = 7.6 \text{ mA} \quad r_d = \frac{V_T}{I_D} = \frac{26 \text{ mV}}{7.6 \text{ mA}} \approx 3.42 \Omega$$

$$\frac{\Delta V_o}{\Delta V_{\text{supply}}} = \frac{3 \times r_d}{3r_d + R} = \frac{3 \times 3.42}{3.42 \times 3 + 1000} \approx 10.16 \times 10^{-3} \approx 1.02 \%$$

b)
$$I_{RL} = \frac{V_o}{R_L} = \frac{2.4}{1K} = 2.4 \text{ mA}$$

$$I_R = \frac{V_{SS} - V_o}{R} = 7.6 \text{ mA} \quad I_D = I_R - I_{RL} = 5.2 \text{ mA}$$

$$r_d = V_T / I_D = 26 \text{ mV} / 5.2 \text{ mA} \approx 5 \Omega$$

$$\frac{\Delta V_o}{\Delta V_{\text{supply}}} = \frac{(3 \times r_d) \parallel R_L}{R_L \parallel (3 \times r_d) + R} \approx 0.146 = 1.46 \%$$

$$3r_d \parallel R_L = 15 \Omega \parallel 1K \Omega \approx 14.78 \Omega$$

Name: _____

Problem 5 [10 pts]

Plot the input output characteristics for the circuit shown in figure 3. Assume the diode to be ideal. Label carefully the slope(s) of the input/output characteristics.


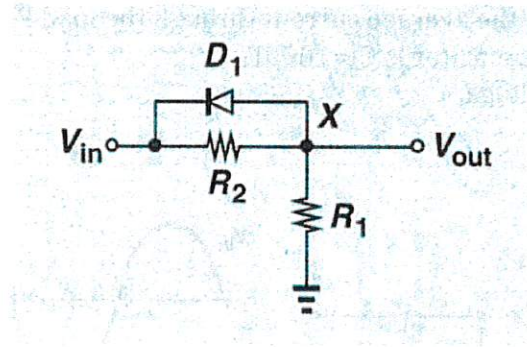


Figure 3.

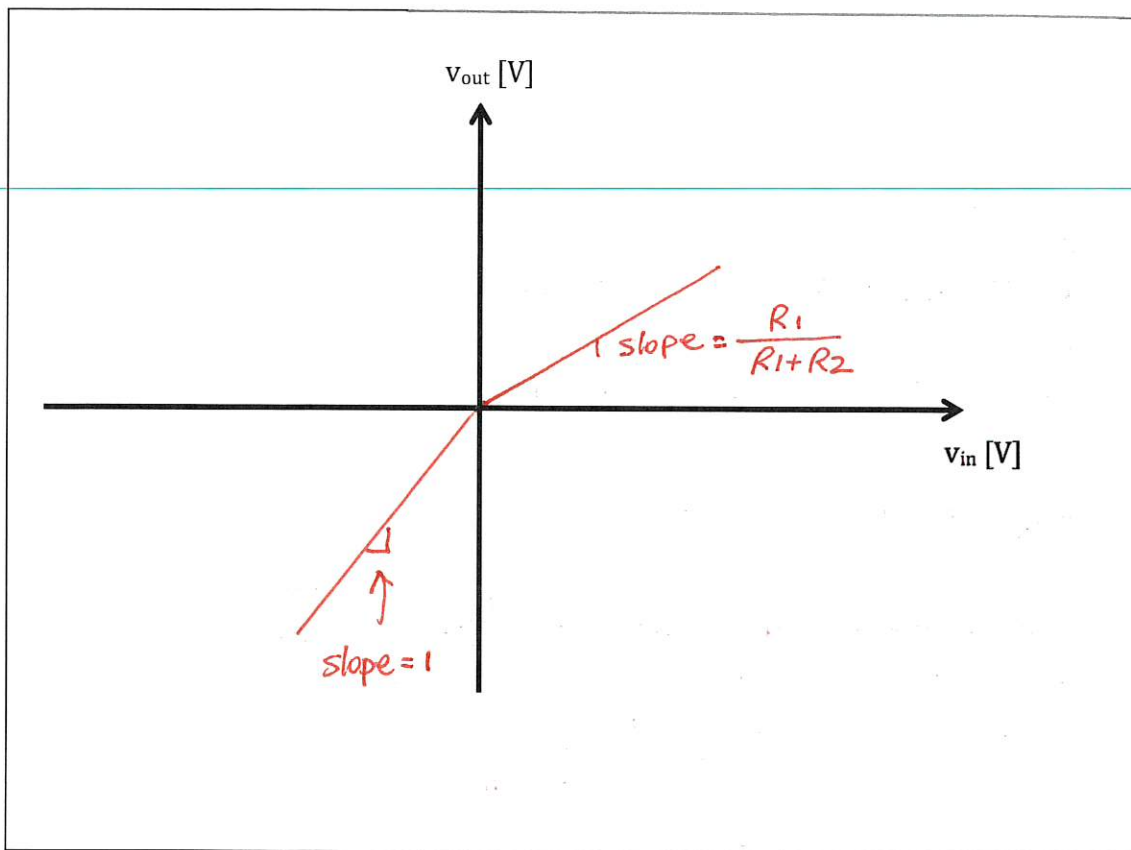



for $V_{in} > 0$ the diode is OFF $\rightarrow V_{out} = \frac{R_1}{R_1 + R_2} \cdot V_{in}$

for $V_{in} < 0$ the diode is ON $\rightarrow V_{out} = V_{in}$

Name: _____

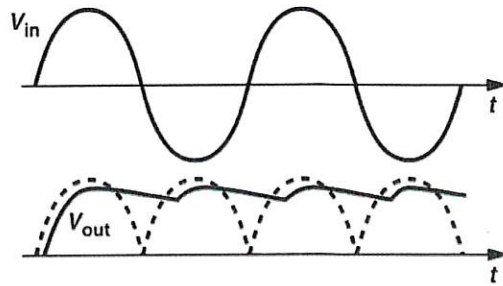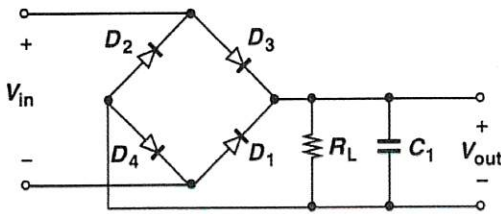Problem 6 [5 pts]

Given the following circuit where: 1) the input signal V_{in} is a sinusoidal waveform with $V_{in,rms} = 3.96V$ and with frequency $f_{in} = 50$ Hz, 2) the diodes have a turn on voltage $V_{D,ON} = 0.8V$, 3) the average current through the load R_L is equal to $I_{RL} = 5mA$ and 4) the smoothing capacitor is $C_1 = 100\mu F$. Compute the ripple voltage.



$V_{RIPPLE} =$	$0.5V$
----------------	--------

$$\hat{V}_{out} = \hat{V}_{in} - 2 \cdot V_{D,ON} = 4V$$

$$\hat{V}_{in} = V_{in,rms} \cdot \sqrt{2} = 5.6V$$

$$I_{RL,avg} \approx \frac{\hat{V}_{out}}{R_L} = 5mA$$

$$Q_{discharged} = C_1 \cdot V_{RIPPLE} \approx I_{RL,avg} \cdot \frac{T}{2}$$


$$V_{RIPPLE} \approx \left(\frac{\hat{V}_{out}}{R_L} \right) \frac{1}{2 \cdot C_1 \cdot f_{in}} =$$

$$= \frac{5mA}{2 \times 100 \times 10^{-6}} \cdot \frac{1}{50} \approx 0.5V$$

Name: _____

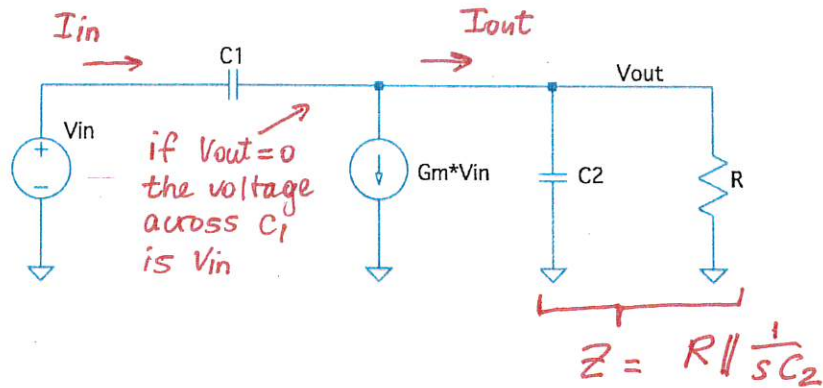Problem 7 [20 pts]

Given the following circuit derive its transfer function:



$T(s) = V_{out}(s)/V_{in}(s) =$	$-G_m R \frac{1 - s C_1 / G_m}{1 + s R (C_1 + C_2)}$
---------------------------------	--

- Pole is independent of the excitation (i.e. V_{in}):

$$s_p = -\frac{1}{R(C_1 + C_2)} \quad \{ \text{LHP pole} \}$$

- DC gain (open the caps) $A_0 = \frac{V_{out}}{V_{in}}(s=0) = -G_m \cdot R$

- Zero (frequency at which $V_{out} = 0$)

$$I_{in} = C_1 \cdot s V_{in} \quad I_{out} = I_{in} - G_m \cdot V_{in}$$

$$V_{out} = I_{out} \cdot \frac{R \cdot \frac{1}{sC_2}}{R + \frac{1}{sC_2}} = I_{out} \frac{R}{1 + sRC_2}$$

$$V_{out} = (C_1 s V_{in} - G_m \cdot V_{in}) \cdot \frac{R}{1 + sRC_2}$$

$$\frac{V_{out}}{V_{in}} = \frac{R (sC_1 - G_m)}{1 + sRC_2}$$

$V_{out} = 0$ for s such that:

$$C_1 \cdot s - G_m = 0 \iff s_z = \frac{G_m}{C_1} \quad \{ \text{RHP } \overset{\text{zero}}{\cancel{\text{pole}}} \}$$

Name: _____

Problem 8 [20 pts]

Draw the Asymptotic Bode plots for the following $T(j\omega)$:



$A_0 = -1000, G_1 = 1\text{mS}, C_1 = 1\text{fF}, R = 1\text{k}\Omega, C_2 = 1\text{pF}$

$DC\ gain = -1000 \rightarrow 60\text{ dB}$

$\omega_p = \frac{1}{RC_2} = 10^9\text{ rad/s}$

$\omega_z = \frac{G_1}{C_1} = 10^{12}\text{ rad/s}$

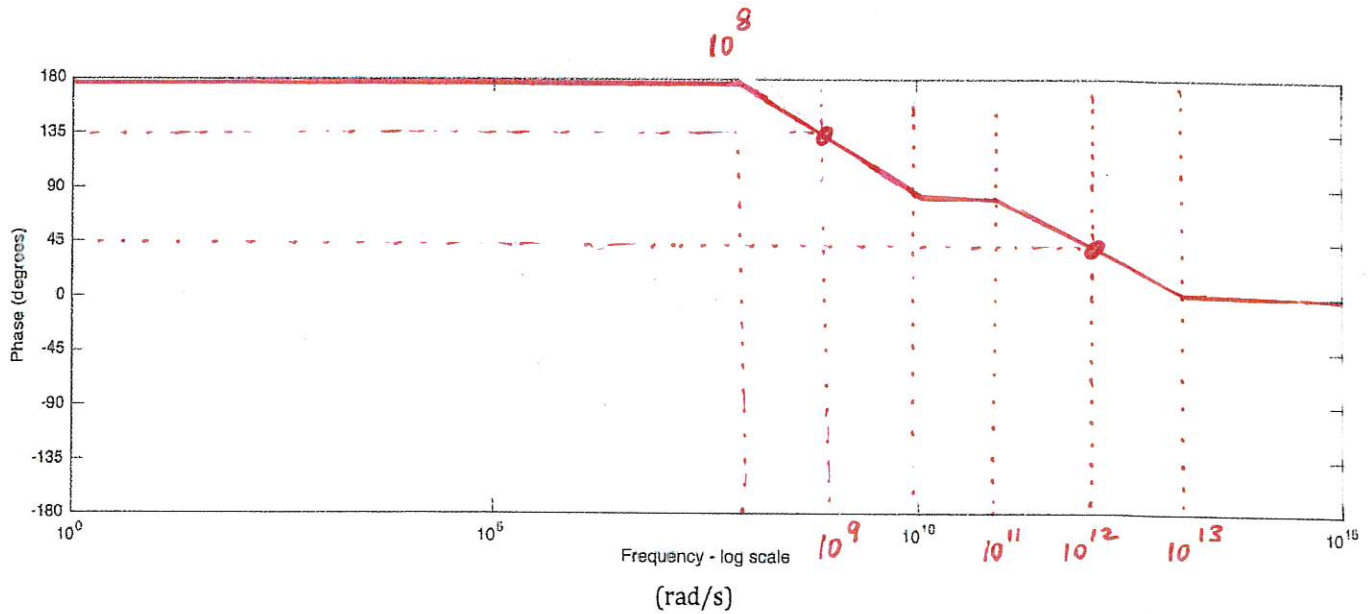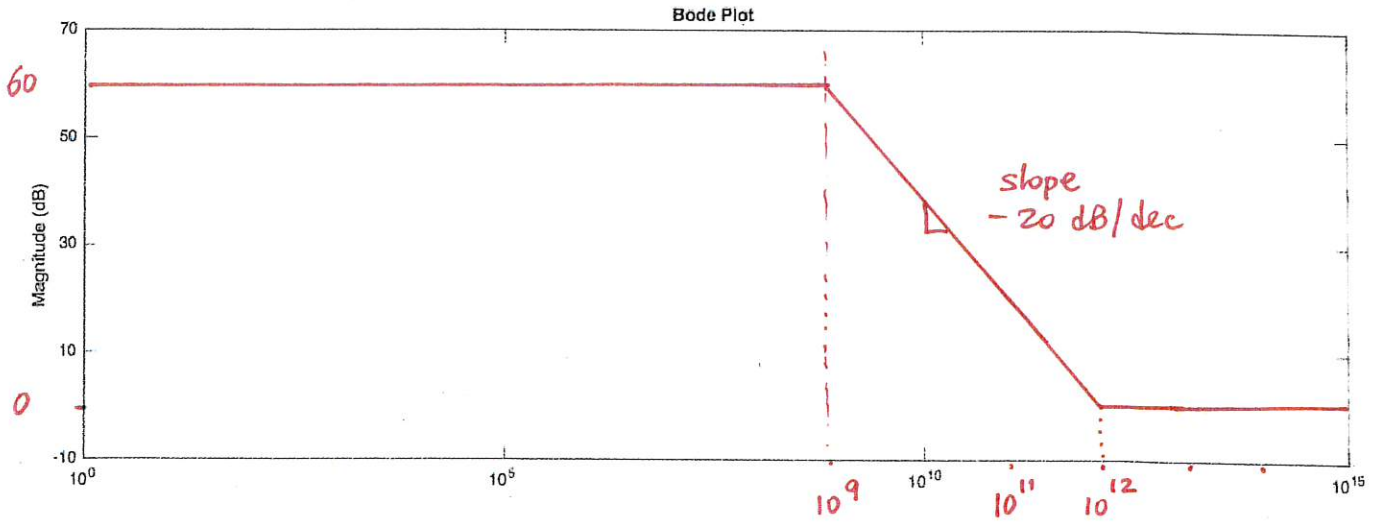$T(j\omega) = A_0 \frac{1 - \frac{j\omega C_1}{G_1}}{1 + j\omega RC_2}$
← RHP zero
← LHP pole




```

% MT1_2017_pb8.m
clc; clear all; close all;
s = tf('s');
A0 = -1000;
G1 = 1e-3;
C1 = 1e-15;
R = 1e3;
C2 = 1e-12;
N = A0*(1 - s*C1/G1);
D = 1 + s*R*C2;
T = N/D;
w = logspace(0,15,100*10); % divide the range from 0 to 4 in 100 points
opts = bodeoptions('cstprefs');
opts.Title.FontSize = 16;
opts.Title.Color = 'b';
opts.Xlabel.FontSize = 14;
opts.Ylabel.FontSize = 14;
opts.TickLabel.FontSize = 12;
opts.PhaseVisible = 'on';
opts.Grid = 'on';
opts.GridColor = 'b';
bodeplot(w,T,opts);
T0dB = 20*log10(abs(dcgain(T)));
fprintf('\nThe DC gain of the T.F. is: %.2g dB\n',T0dB);

sys = zpkm(T)
K = sys.k;
[P,Z] = pzmap(sys);
fprintf('\nThe coefficient K of the T.F. is: %.2g',K);
np = length(P); %number of poles
nz = length(Z); %number of zeros
fprintf('\nThe T.F. has %d pole(s) and %d zero(s)',np,nz);
if np >= 1
    for i=1:np
        fprintf('\nThe pole(s) are at P(%d): %.2g (rad/s)',i,P(i));
    end
end
if nz >= 1
    for i=1:nz
        fprintf('\nThe zero(s) are at Z(%d): %.2g (rad/s)',i,Z(i));
    end
end
end

```

The DC gain of the T.F. is: 60 dB

sys =

```

(s-1e12)
-----
(s+1e09)

```

Continuous-time zero/pole/gain model.

```

The coefficient K of the T.F. is: 1
The T.F. has 1 pole(s) and 1 zero(s)
The pole(s) are at P(1): -1e+09 (rad/s)
The zero(s) are at Z(1): 1e+12 (rad/s)

```

Bode Diagram

