



Semiconductors and Diodes

Table 3.1 Summary of Important Equations		
Quantity	Relationship	Values of Constants and Parameters (for Intrinsic Si at $T = 300$ K)
Carrier concentration in intrinsic silicon (cm^{-3})	$n_i = BT^{3/2} e^{-E_g/2kT}$	$B = 7.3 \times 10^{15} \text{ cm}^{-3} \text{ K}^{-3/2}$ $E_g = 1.12 \text{ eV}$ $k = 8.62 \times 10^{-5} \text{ eV/K}$ $n_i = 1.5 \times 10^{10} / \text{cm}^3$
Diffusion current density (A/cm^2)	$J_p = -qD_p \frac{dp}{dx}$ $J_n = qD_n \frac{dn}{dx}$	$q = 1.60 \times 10^{-19} \text{ coulomb}$ $D_p = 12 \text{ cm}^2/\text{s}$ $D_n = 34 \text{ cm}^2/\text{s}$
Drift current density (A/cm^2)	$J_{\text{drift}} = q(p\mu_p + n\mu_n)E$	$\mu_p = 480 \text{ cm}^2/\text{V} \cdot \text{s}$ $\mu_n = 1350 \text{ cm}^2/\text{V} \cdot \text{s}$
Resistivity ($\Omega \cdot \text{cm}$)	$\rho = 1/[q(p\mu_p + n\mu_n)]$	μ_p and μ_n decrease with the increase in doping concentration
Relationship between mobility and diffusivity	$\frac{D_n}{\mu_n} = \frac{D_p}{\mu_p} = V_T$	$V_T = kT/q \simeq 25.9 \text{ mV}$
Carrier concentration in n -type silicon (cm^{-3})	$n_{n0} \simeq N_D$ $p_{n0} = n_i^2/N_D$	
Carrier concentration in p -type silicon (cm^{-3})	$p_{p0} \simeq N_A$ $n_{p0} = n_i^2/N_A$	
PN junctions (diodes)	Junction built-in voltage (V)	$V_0 = V_T \ln\left(\frac{N_A N_D}{n_i^2}\right)$
	Width of depletion region (cm)	$\frac{x_n}{x_p} = \frac{N_A}{N_D}$ $W = x_n + x_p$ $= \sqrt{\frac{2\epsilon_s}{q} \left(\frac{1}{N_A} + \frac{1}{N_D}\right) (V_0 + V_R)}$

$$\epsilon_s = 11.7\epsilon_0$$

$$\epsilon_0 = 8.854 \times 10^{-14} \text{ F/cm}$$

Table 3.1 continued		
Quantity	Relationship	Values of Constants and Parameters (for Intrinsic Si at $T = 300$ K)
Charge stored in depletion layer (coulomb)	$Q_J = q \frac{N_A N_D}{N_A + N_D} AW$	
Forward current (A)	$I = I_p + I_n$ $I_p = Aq n_i^2 \frac{D_p}{L_p N_D} (e^{V/V_T} - 1)$ $I_n = Aq n_i^2 \frac{D_n}{L_n N_A} (e^{V/V_T} - 1)$	
Saturation current (A)	$I_S = Aq n_i^2 \left(\frac{D_p}{L_p N_D} + \frac{D_n}{L_n N_A} \right)$	
I - V relationship	$I = I_S (e^{V/V_T} - 1)$	
Minority-carrier lifetime (s)	$\tau_p = L_p^2 / D_p \quad \tau_n = L_n^2 / D_n$	$L_p, L_n = 1 \mu\text{m to } 100 \mu\text{m}$ $\tau_p, \tau_n = 1 \text{ ns to } 10^4 \text{ ns}$
Minority-carrier charge storage (coulomb)	$Q_p = \tau_p I_p \quad Q_n = \tau_n I_n$ $Q = Q_p + Q_n = \tau_T I$	
Depletion capacitance (F)	$C_{j0} = A \sqrt{\left(\frac{\epsilon_s q}{2} \right) \left(\frac{N_A N_D}{N_A + N_D} \right) \frac{1}{V_0}}$ $C_j = C_{j0} / \left(1 + \frac{V_R}{V_0} \right)^m$	$m = \frac{1}{3} \text{ to } \frac{1}{2}$
Diffusion capacitance (F)	$C_d = \left(\frac{\tau_T}{V_T} \right) I$	

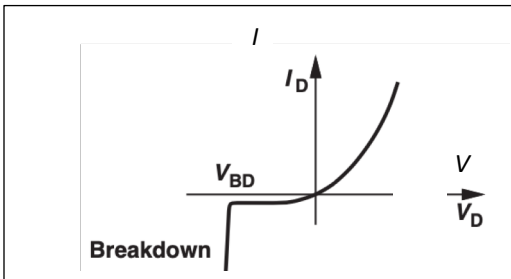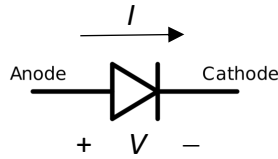

I vs. V equation for diode in forward and reverse region:

$$I = I_S(e^{V/V_T} - 1)$$

V is the voltage across the diode from anode to cathode

I is the current through the diode from anode to cathode

$$V_T = \frac{kT}{q}$$

V_T = 25.9 mV at room temperature (= 300 degree Kelvin)


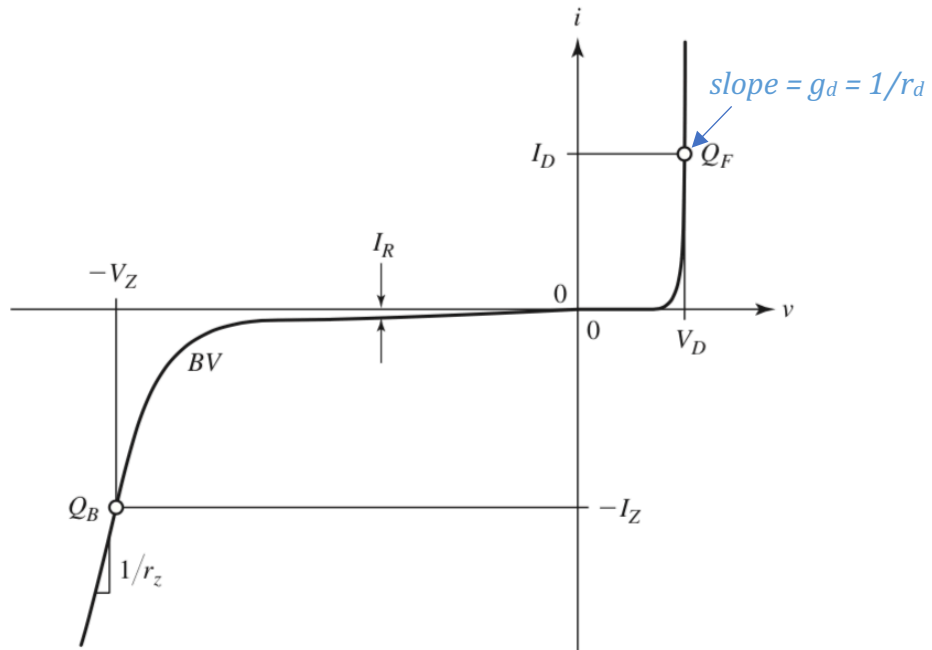


FIGURE 1.46 The complete *i-v* characteristic of a *pn* junction.

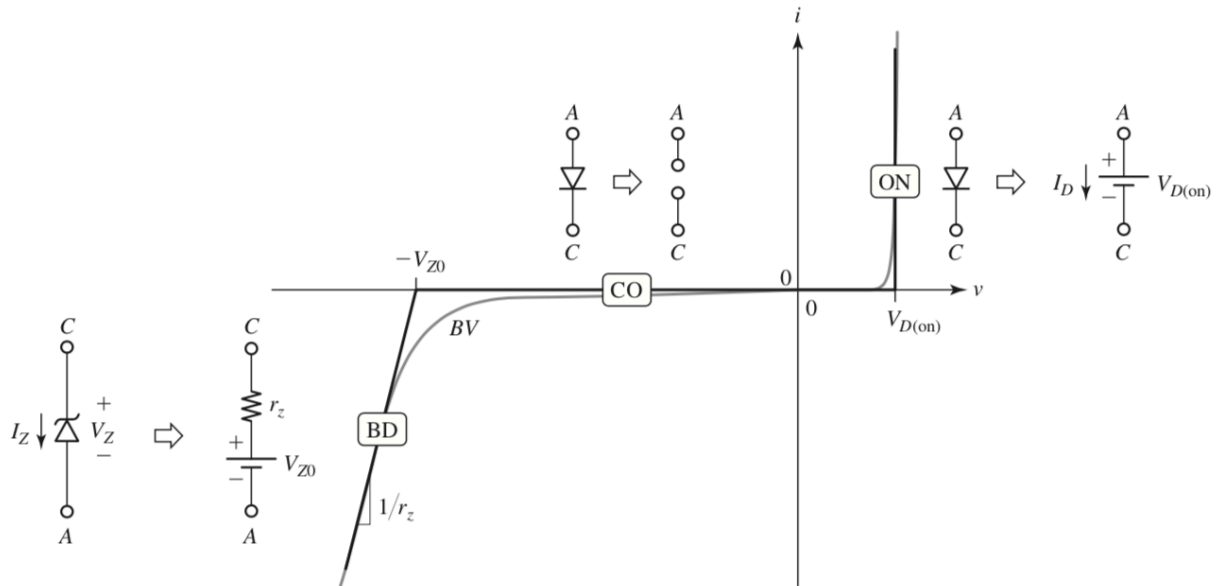Approximations of the diode three regions of operation



The *slope* of the diode curve at a given operating current I_D in the forward-bias region is:

$$g_d = \frac{I_D}{V_T}$$

In forward region to cause a *decade* change in I_D we need to change V_D by 60 mV.

Temperature affects the forward region as follows:

$$V_D(T) \cong V_D(T_0) - (2 \text{ mV}) \times (T - T_0)$$

and the reverse region as follows:

$$I_R(T) \cong I_R(T_0) \times 2^{(T-T_0)/10}$$

MOSFET in saturation mode ($V_{GS} > V_{TH}$ and $V_{DS} > V_{GS} - V_{TH}$)

$$I_D = \frac{1}{2} \mu C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$$

Key Small Signal Parameters for the MOSFET in saturation mode:

$$g_m = \mu C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) = \frac{2I_D}{V_{GS} - V_{TH}}$$

$$r_o \approx \frac{1}{\lambda I_D}$$

BIPOLAR in active mode ($V_{BE} \approx 0.7$ V and $V_{CE} > V_{CE,sat} \approx 1$ V)

$$I_C \approx I_S e^{V_{BE}/V_T}$$

$$V_T = \frac{kT}{q}$$

$V_T = 25.9$ mV at room temperature (= 300 degree Kelvin)

$$I_E = I_B + I_C = (\beta + 1)I_B$$

$$\beta = I_C/I_B$$

Key Small Signal Parameters for the BIPOLAR in active mode


$$g_m = \frac{I_C}{V_T}$$

$$r_\pi = \frac{\beta}{g_m}$$

$$r_o = \frac{V_A}{I_C}$$

Small signal model for MOSFET in saturation mode

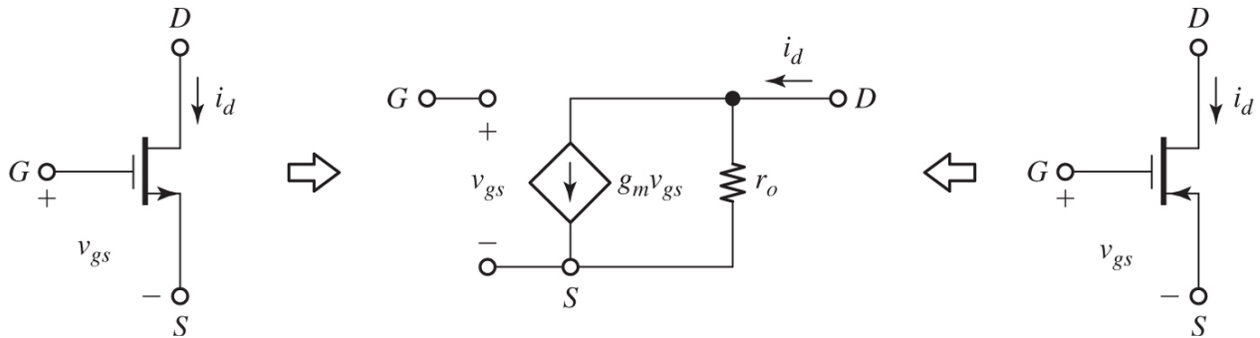
Copyright © McGraw-Hill Education. All rights reserved. No reproduction or distribution without the prior written consent of McGraw-Hill Education.



Small-signal MOSFET model. This model applies to both *n*MOSFETs and pMOSFETs

Small signal model for BIPOLAR in active mode

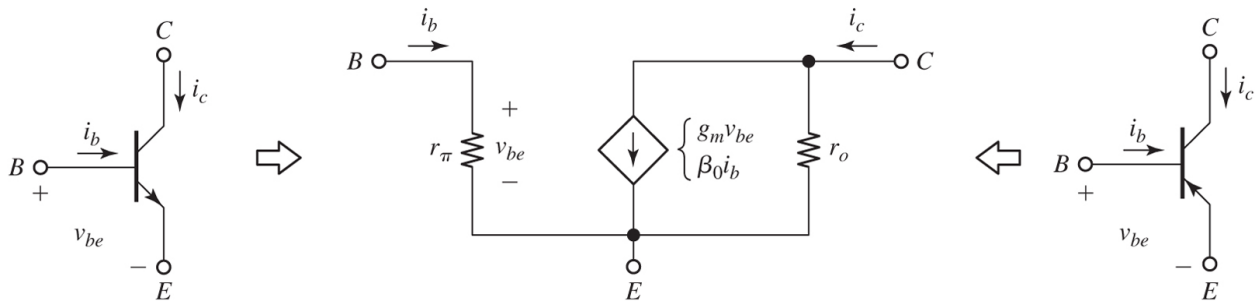
Copyright © McGraw-Hill Education. All rights reserved. No reproduction or distribution without the prior written consent of McGraw-Hill Education.



Small-signal BJT model. This model applies to both *n*pn and *p*np BJTs.


Small signal resistances looking into the BJT's terminals

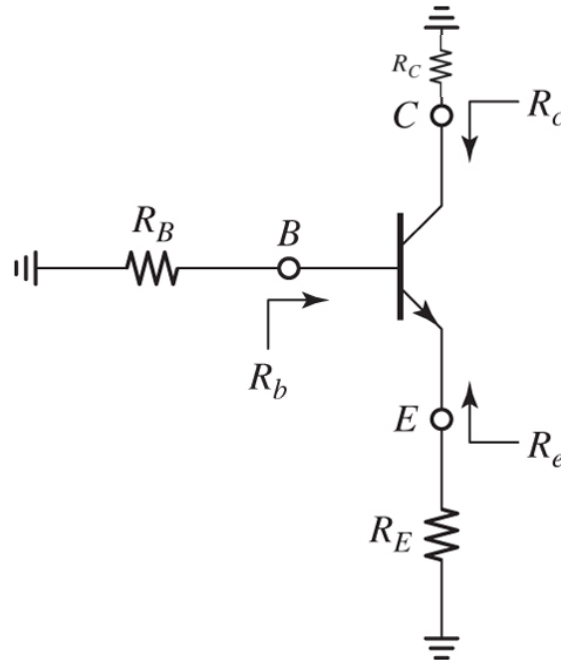Copyright © McGraw-Hill Education. All rights reserved. No reproduction or distribution without the prior written consent of McGraw-Hill Education.



Exact	Approximate
$R_b = r_\pi + (\beta + 1)R_E \left(\frac{r_o + \frac{R_C}{\beta + 1}}{r_o + R_C + R_E} \right) [GHLM]$	$R_b \approx r_\pi + (\beta + 1)R_E \quad (r_o \gg R_E, r_o \gg R_C)$
$R_e = \left[\frac{(r_o + R_C)(r_\pi + R_B)}{r_\pi + R_B + \beta r_o} \right] (r_\pi + R_B)$	$R_e \approx \left[\frac{(r_\pi + R_B)}{\beta + 1} \right] \quad (r_o \gg R_C; g_m r_o \gg 1; r_o \gg \frac{R_B}{\beta})$
$R_c = r_o \left[1 + \frac{g_m r_\pi R_E}{r_\pi + R_B + R_E} \right] + (r_\pi + R_B) R_E$	$R_c \approx r_o [1 + g_m (r_\pi R_E)] \quad (r_\pi \gg R_B; g_m r_o \gg 1)$

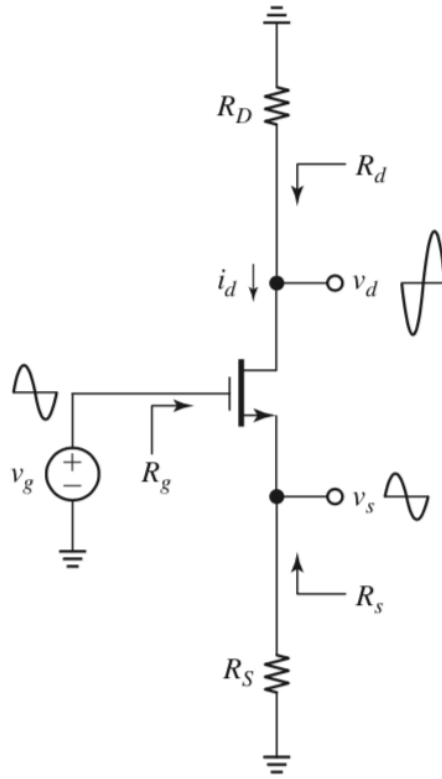Small signal terminal resistances for the MOSFET




Exact	Approximate
$R_g = \infty$	$R_g = \infty$
$R_s = \left(\frac{1}{g_m} \parallel r_o \right) + \frac{R_D}{1 + g_m r_o}$	$R_s \cong \frac{1}{g_m}$
$R_d = r_o(1 + g_m R_S) + R_S$	$R_d \cong r_o(1 + g_m R_S)$

NOTE: $R_s = \left(\frac{1}{g_m} \parallel r_o \right) + \frac{R_D}{(1 + g_m r_o)} = \frac{R_D + r_o}{(1 + g_m r_o)}$


Summary of small signal gains for BJT based topologies

(A)

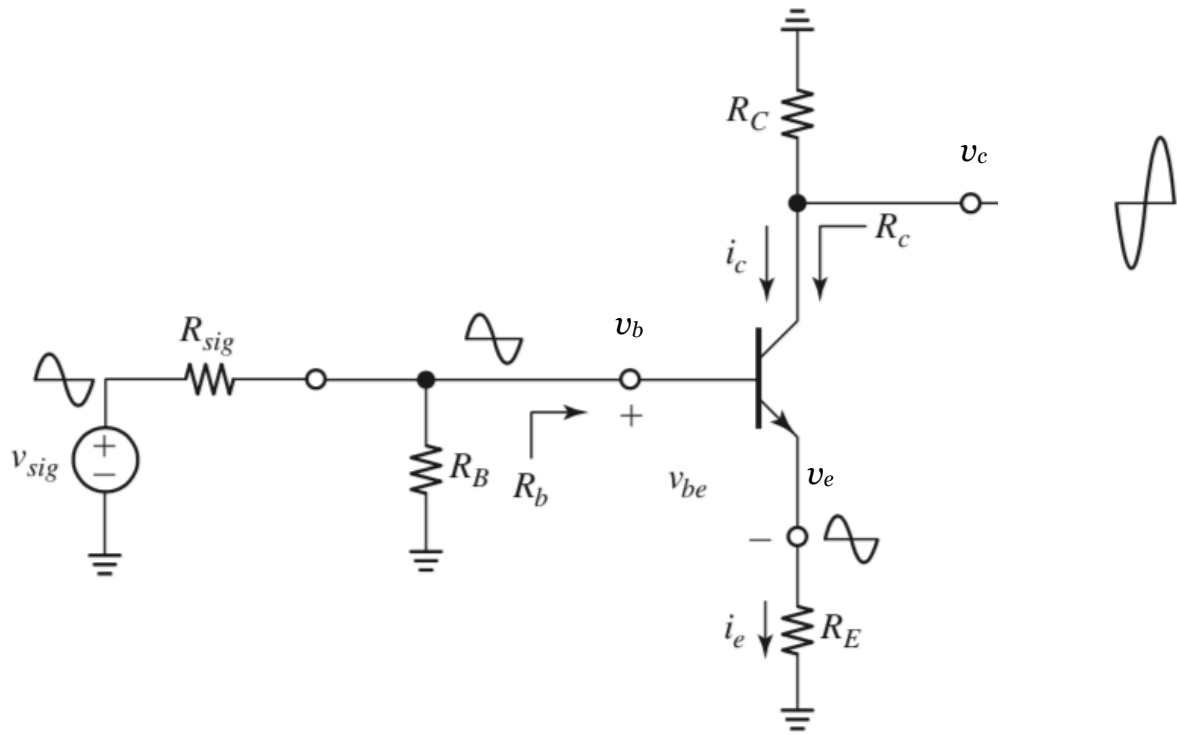

Exact	Approximate
<p>with $R_E \neq 0$ [GHLM]:</p> $\frac{v_c}{v_b} = -\frac{R_C(\beta r_o - R_E)}{R_E[R_C + r_o(\beta + 1)] + r_\pi(R_C + R_E + r_o)}$	<p>with $R_E \neq 0$:</p> $\frac{v_c}{v_b} = -\frac{g_m R_C}{1 + g_m R_E}$ <p>$r_o \gg R_C + R_E; \beta \gg 1$</p>
<p>with $R_E = 0$:</p> $\frac{v_c}{v_b} = -g_m(R_C r_o)$	<p>with $R_E = 0$:</p> $\frac{v_c}{v_b} = -g_m R_C$ <p>$r_o \gg R_C$</p>
<p>with $R_C \neq 0$ [GHLM]:</p> $\frac{v_e}{v_b} = \frac{1}{1 + \frac{r_\pi(R_C + R_E + r_o)}{R_E[R_C + r_o(\beta + 1)]}}$	<p>with $R_C \neq 0$:</p> $\frac{v_e}{v_b} = \frac{g_m R_E}{g_m R_E + 1}$ <p>$r_o \gg R_C + R_E; \beta \gg 1$</p>
<p>with $R_C = 0$ [GHLM]:</p> $\frac{v_e}{v_b} = \frac{(\beta + 1)/r_\pi}{\frac{1}{R_E} + \frac{1}{r_o} + \frac{\beta + 1}{r_\pi}}$	<p>with $R_C = 0$ [GHLM]:</p> $\frac{v_e}{v_b} = \frac{g_m R_E}{g_m R_E + 1}$ <p>$g_m r_o \gg 1; \beta \gg 1$</p>

(B)

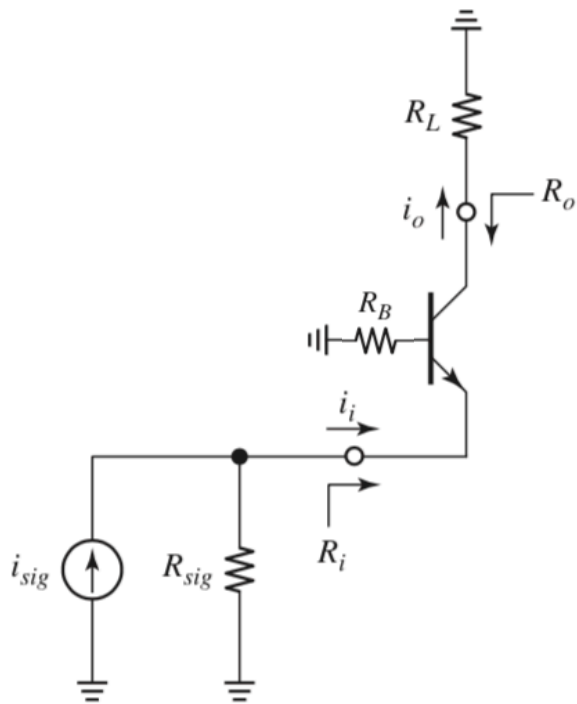

$$i_o = \alpha i_i = \frac{\beta}{\beta + 1} i_i$$

$$i_i = \frac{R_{sig}}{R_{sig} + R_i} i_{sig}$$

$$v_{be} = -v_e \frac{r_\pi}{r_\pi + R_B}$$

Exact:


$$\frac{v_c}{v_e} = \frac{g_m R_L \frac{r_\pi}{r_\pi + R_B} + \frac{R_L}{r_o}}{1 + \frac{R_L}{r_o}}$$

Approximate:

$$\frac{v_c}{v_e} = g_m (R_L || r_o) \quad r_\pi \gg R_B$$


Summary of small signal gains for MOSFET based topologies

(A)

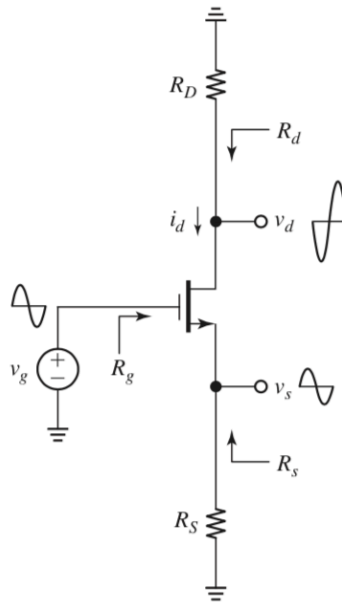

Exact	Approximate
$G_m = \frac{i_d}{v_g} = \frac{g_m}{1 + g_m R_S + (R_D + R_S)/r_o}$	$G_m \cong \frac{g_m}{1 + g_m R_S}$
$\frac{v_d}{v_g} = \frac{-g_m R_D}{1 + g_m R_S + (R_D + R_S)/r_o}$	$\frac{v_d}{v_g} \cong \frac{-g_m R_D}{1 + g_m R_S}$
$\frac{v_s}{v_g} = \frac{g_m R_S}{1 + g_m R_S + (R_D + R_S)/r_o}$	$\frac{v_s}{v_g} \cong \frac{1}{1 + 1/(g_m R_S)}$

(B)

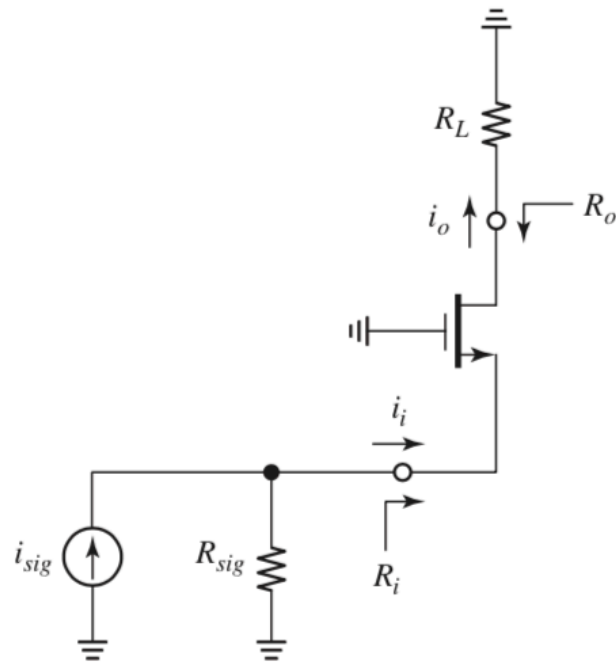


$$i_o = i_i$$

$$\frac{i_o}{i_{sig}} = \frac{1}{1 + \frac{r_o + R_L}{(1 + g_m r_o) R_{sig}}}$$

$$\frac{v_d}{v_s} = +g_m (R_L // r_o)$$

$$\frac{1}{g_m} || r_{\pi} \approx \frac{1}{g_m} \quad (\beta \gg 1)$$

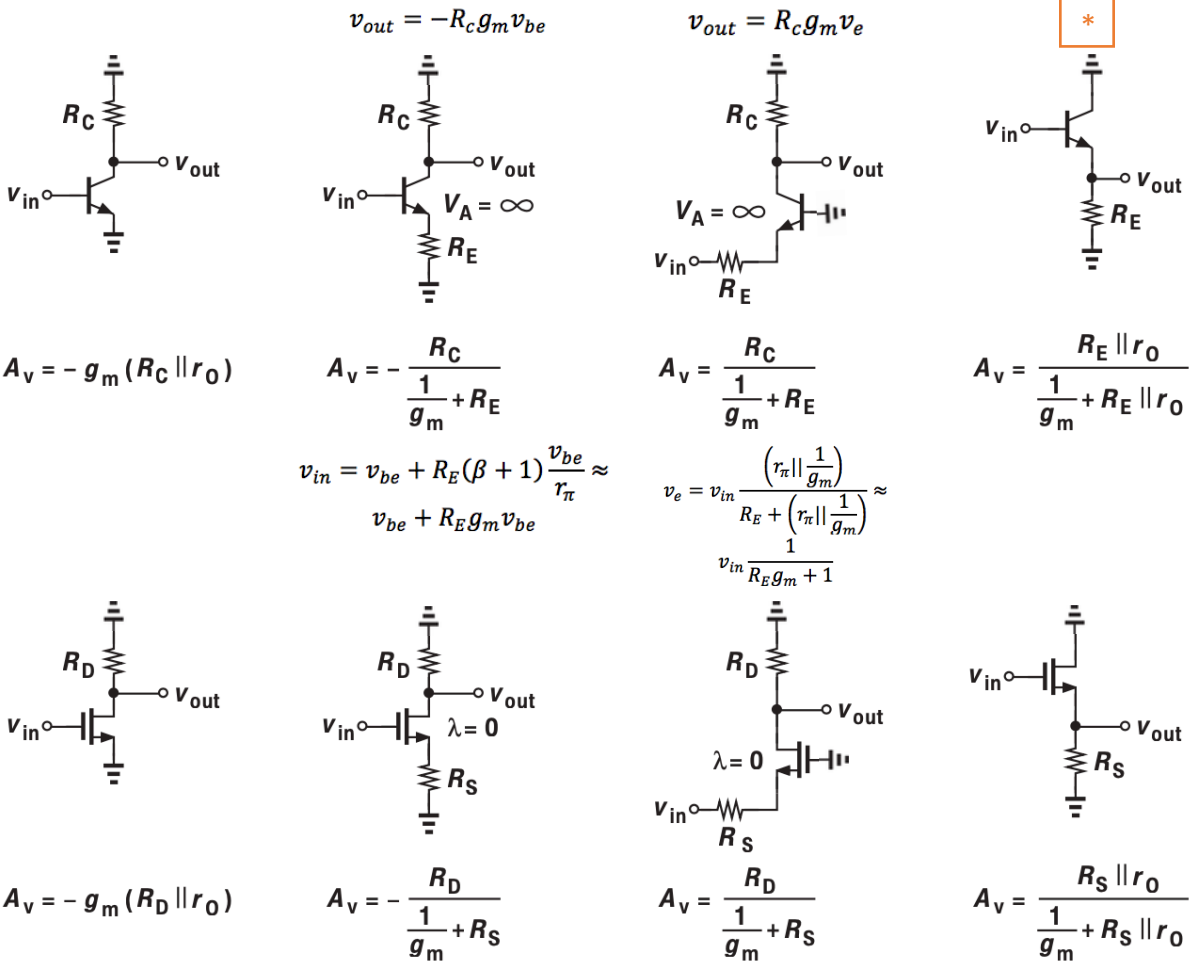Very Common Cases: Voltage Gain Equations for $\beta \gg 1 \rightarrow \left(r_{\pi} \parallel \frac{1}{g_m}\right) \approx \frac{1}{g_m}$









*

$$v_{out} = (R_E \parallel r_o) g_m v_{be} + (R_E \parallel r_o) \frac{v_{be}}{r_{\pi}} = \frac{R}{r_{\pi}} v_{be} (\beta + 1) \approx g_m R v_{be}$$

$$v_{in} = v_{be} + v_{out} \approx v_{be} (1 + g_m R)$$

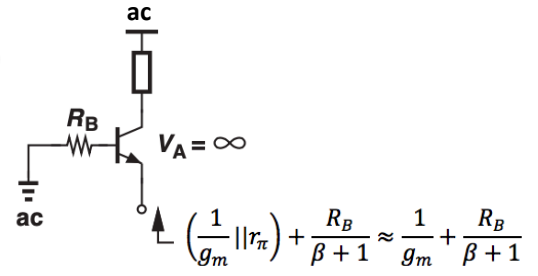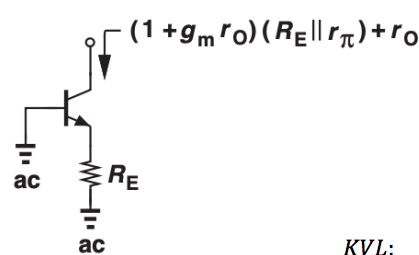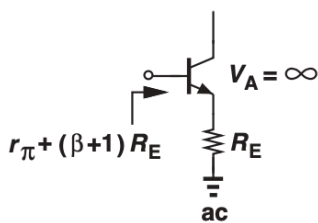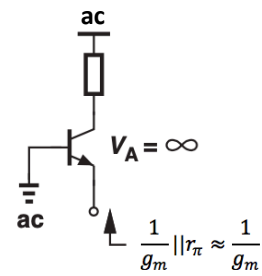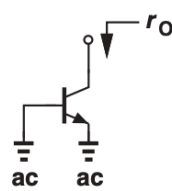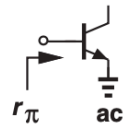Very Common Cases: Input and Output Impedances for $\beta \gg 1 \rightarrow \left(r_{\pi} \parallel \frac{1}{g_m}\right) \approx \frac{1}{g_m}$



KVL:
 $v_t = r_{\pi} i_t + R_E i_t (\beta + 1)$
 R_E can be "moved" in base as $R_B (\beta + 1)$ and E becomes ground

KVL:
 $v_e = -r_{\pi} i_b - R_B i_b = -r_{\pi} i_b - R_B \frac{i_e}{\beta + 1}$
 R_B can be "moved" in emitter as $R_E / (\beta + 1)$ and B becomes ground

