

### EE304 – Problem Set 1

#### Problem 3.1 [M]

Sketch the Bode Plots (magnitude and phase) for the following transfer functions.

Assume  $R_i C_i \gg R_k C_k$  if  $i > k$

(a)  $[1/(1 + j\omega R_1 C_1)][(1/(1 + j\omega R_2 C_2)]$


(b)  $(j\omega R_3 C_3)[(1 + j\omega R_4 C_4)/(1 + j\omega R_5 C_5)]$

(c)  $[(1 + j\omega R_6 C_6)/(1 + j\omega R_8 C_8)][(1 + j\omega R_7 C_7)/(1 + j\omega R_9 C_9)]$

**Problem 7.121 [S&S 7/e]**

**D \*7.121** The MOSFET in the circuit of Fig. P7.121 has  $V_t = 0.8\text{ V}$ ,  $k_n = 5\text{ mA/V}^2$ , and  $V_A = 40\text{ V}$ .

- Find the values of  $R_S$ ,  $R_D$ , and  $R_G$  so that  $I_D = 0.4\text{ mA}$ , the largest possible value for  $R_D$  is used while a maximum signal swing at the drain of  $\pm 0.8\text{ V}$  is possible, and the input resistance at the gate is  $10\text{ M}\Omega$ . Neglect the Early effect.
- Find the values of  $g_m$  and  $r_o$  at the bias point.
- If terminal Z is grounded, terminal X is connected to a signal source having a resistance of  $1\text{ M}\Omega$ , and terminal Y is connected to a load resistance of  $10\text{ k}\Omega$ , find the voltage gain from signal source to load.
- If terminal Y is grounded, find the voltage gain from X to Z with Z open-circuited. What is the output resistance of the source follower?

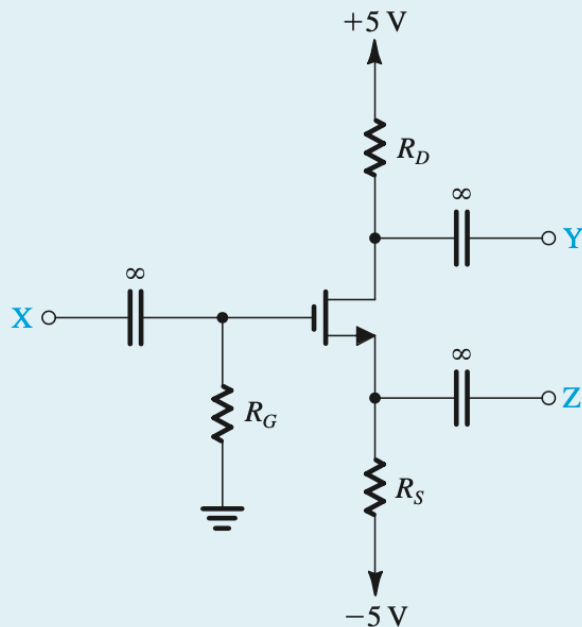


**Figure P7.121**

- If terminal X is grounded and terminal Z is connected to a current source delivering a signal current of  $50\text{ }\mu\text{A}$  and having a resistance of  $100\text{ k}\Omega$ , find the voltage signal that can be measured at Y. For simplicity, neglect the effect of  $r_o$ .

**Problem 7.130 [S&S 7/e]**

**\*7.130** The amplifier of Fig. P7.130 consists of two identical common-emitter amplifiers connected in cascade. Observe that the input resistance of the second stage,  $R_{in2}$ , constitutes the load resistance of the first stage.


- For  $V_{CC} = 15\text{ V}$ ,  $R_1 = 100\text{ k}\Omega$ ,  $R_2 = 47\text{ k}\Omega$ ,  $R_E = 3.9\text{ k}\Omega$ ,  $R_C = 6.8\text{ k}\Omega$ , and  $\beta = 100$ , determine the dc collector current and dc collector voltage of each transistor.
- Draw the small-signal equivalent circuit of the entire amplifier and give the values of all its components.
- Find  $R_{in1}$  and  $v_{b1}/v_{sig}$  for  $R_{sig} = 5\text{ k}\Omega$ .
- Find  $R_{in2}$  and  $v_{b2}/v_{b1}$ .
- For  $R_L = 2\text{ k}\Omega$ , find  $v_o/v_{b2}$ .
- Find the overall voltage gain  $v_o/v_{sig}$ .

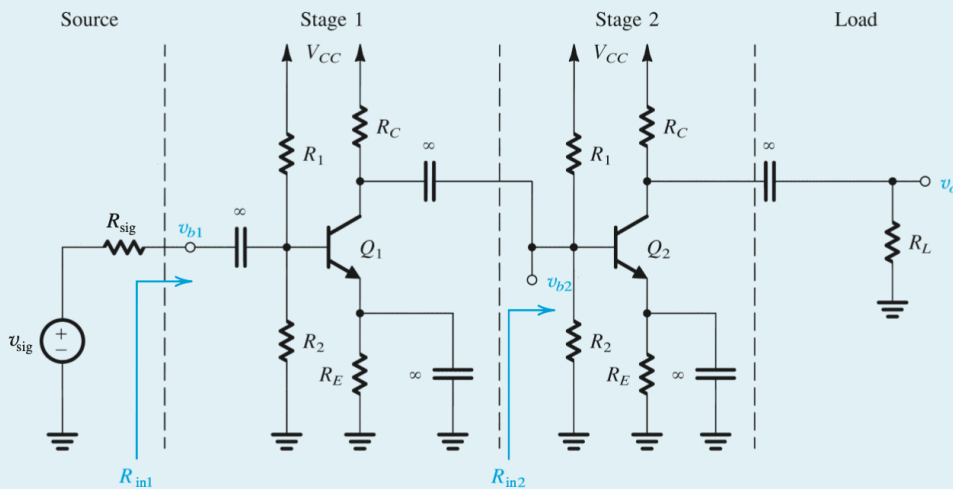

**Figure P7.130**

**Problem E6 [S&S]**

**E.6** Find the high-frequency gain, the 3-dB frequency  $f_0$ , and the gain at  $f = 1\text{ Hz}$  of the capacitively coupled amplifier shown in Fig. EE.6. Assume the voltage amplifier to be ideal.

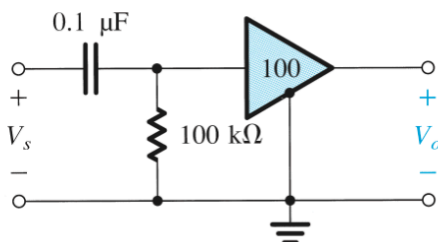


**Figure EE.6**

**Problem 10.27 [S&S]**

**D 10.27** In the circuit of Fig. P10.27, the voltage amplifier is ideal (i.e., it has an infinite input resistance and a zero output resistance).

- (a) Use the Miller approach to find an expression for the input capacitance  $C_{in}$  in terms of  $A$  and  $C$ .
- (b) Use the expression for  $C_{in}$  to obtain the transfer function  $V_o(s)/V_{sig}(s)$ .

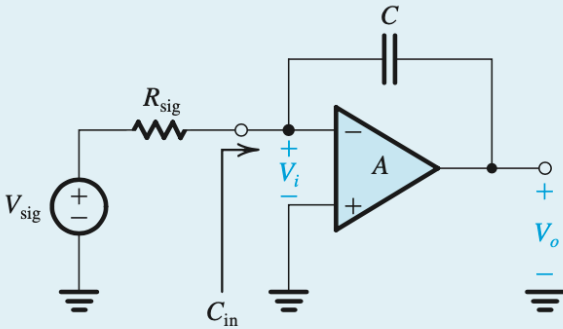

**Figure P10.27**

- (c) If  $R_{sig} = 1 \text{ k}\Omega$ , and the gain  $V_o/V_{sig}$  is to have a dc value of 40 dB and a 3-dB frequency of 100 kHz, find the values required for  $A$  and  $C$ .
- (d) Sketch a Bode plot for the gain and use it to determine the frequency at which its magnitude reduces to unity.