

EE304 – Problem Set 4

Problem 8.11 [S&S 7/e]

8.11 Consider the basic BJT current mirror of Fig. 8.7 when Q_1 and Q_2 are matched and $I_{\text{REF}} = 1 \text{ mA}$. Neglecting the effect of finite β , find the change in I_o , both as an absolute value and as a percentage, corresponding to V_o changing from 1 V to 10 V. The Early voltage is 90 V.

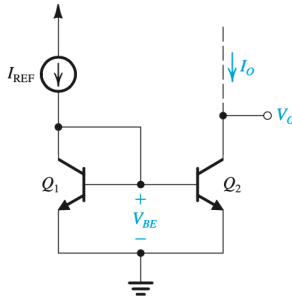


Figure 8.7 The basic BJT current mirror.

Problem 8.12 [S&S 7/e]

D 8.12 The current-source circuit of Fig. P8.12 utilizes a pair of matched *pn*p transistors having $I_s = 10^{-15} \text{ A}$, $\beta = 50$, and $|V_A| = 50 \text{ V}$. It is required to design the circuit to provide an output current $I_o = 1 \text{ mA}$ at $V_o = 1 \text{ V}$. What values of I_{REF} and R are needed? What is the maximum allowed value of V_o while the current source continues to operate properly? What change occurs in I_o corresponding to V_o changing from the

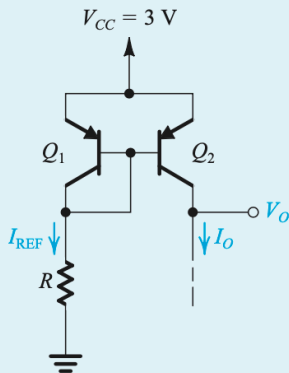


Figure P8.12

maximum positive value to -5 V ? *Hint:* Adapt Eq. (8.21) for this case as:

$$I_o = I_{\text{REF}} \left[\frac{1 + \frac{3 - V_o - V_{EB}}{|V_A|}}{1 + \frac{2}{\beta}} \right]$$

Problem 8.13 [S&S 7/e]

8.13 Find the voltages at all nodes and the currents through all branches in the circuit of Fig. P8.13. Assume $|V_{BE}| = 0.7 \text{ V}$ and $\beta = \infty$.

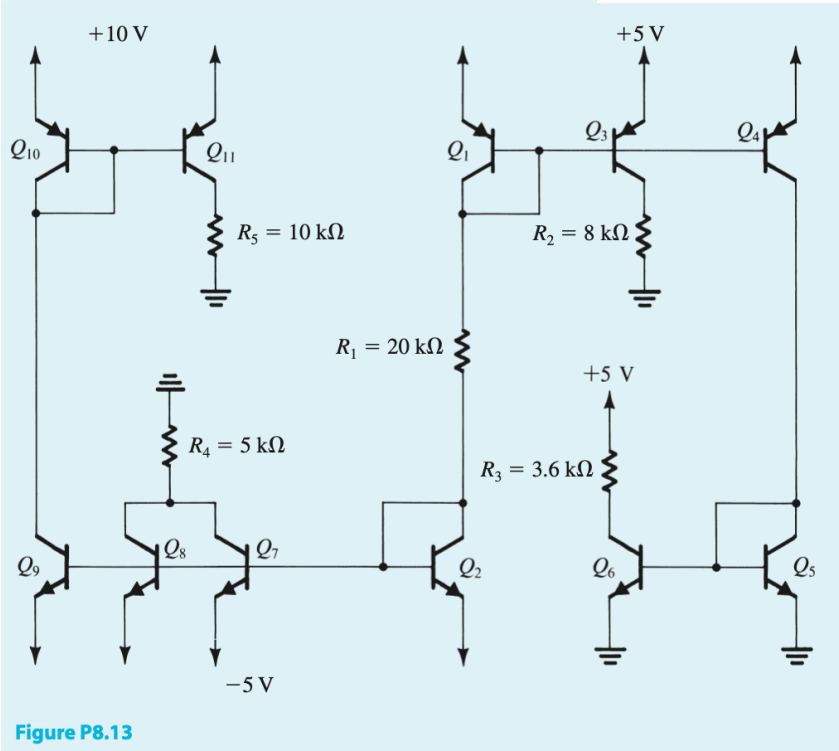


Figure P8.13

Problem 8.49 [S&S 7/e]

8.49 Transistor Q_1 in the circuit of Fig. P8.49 is operating as a CE amplifier with an active load provided by transistor Q_2 , which is the output transistor in a current mirror formed by Q_2 and Q_3 . (Note that the biasing arrangement for Q_1 is *not* shown.)

- Neglecting the finite base currents of Q_2 and Q_3 and assuming that their $V_{BE} \simeq 0.7$ V and that Q_2 has five times the area of Q_3 , find the value of I .
- If Q_1 and Q_2 are specified to have $|V_A| = 30$ V, find r_{o1} and r_{o2} and hence the total resistance at the collector of Q_1 .
- Find $r_{\pi1}$ and g_{m1} assuming that $\beta_1 = 50$.
- Find R_{in} , A_v , and R_o .

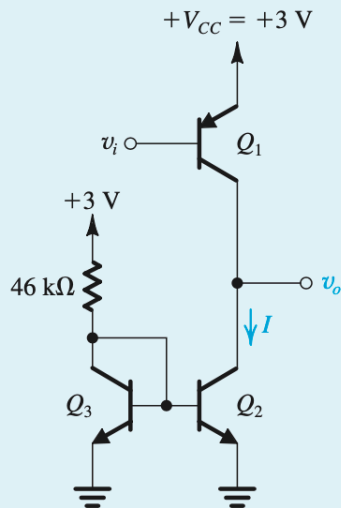


Figure P8.49