

*Problem set*

**P2.9** Consider the following logic function:

$$Y = \overline{A(BC + (D(E + F)))}$$

(a)

Draw the circuit schematic for a static gate that implements the function.

- (b) If each ideal switch has a resistor with a value of  $R$  in series with it, what is the largest resistance that will charge up the output?
- (c) If each ideal switch has a resistor with a value of  $R$  in series with it, what is the largest resistance that will discharge the output to ground?
- (d) If each ideal switch has a resistor with a value of  $R$  in series with it, what is the smallest resistance that will charge up the output?
- (e) If each ideal switch has a resistor with a value of  $R$  in series with it, what is the smallest resistance that will discharge the output to ground?

**P2.10** Consider the following logic function:

$$Y = \overline{A + BC(D + EF)}$$

- (a) draw the circuit  
schematic for a static gate that implements the function.
- (b) If each ideal switch has a resistor with a value of  $R$  in series with it, what is the largest resistance that will charge up the output?
- (c) If each ideal switch has a resistor with a value of  $R$  in series with it, what is the largest resistance that will discharge the output to ground?
- (d) If each ideal switch has a resistor with a value of  $R$  in series with it, what is the smallest resistance that will charge up the output?
- (e) If each ideal switch has a resistor with a value of  $R$  in series with it, what is the smallest resistance that will discharge the output to ground?