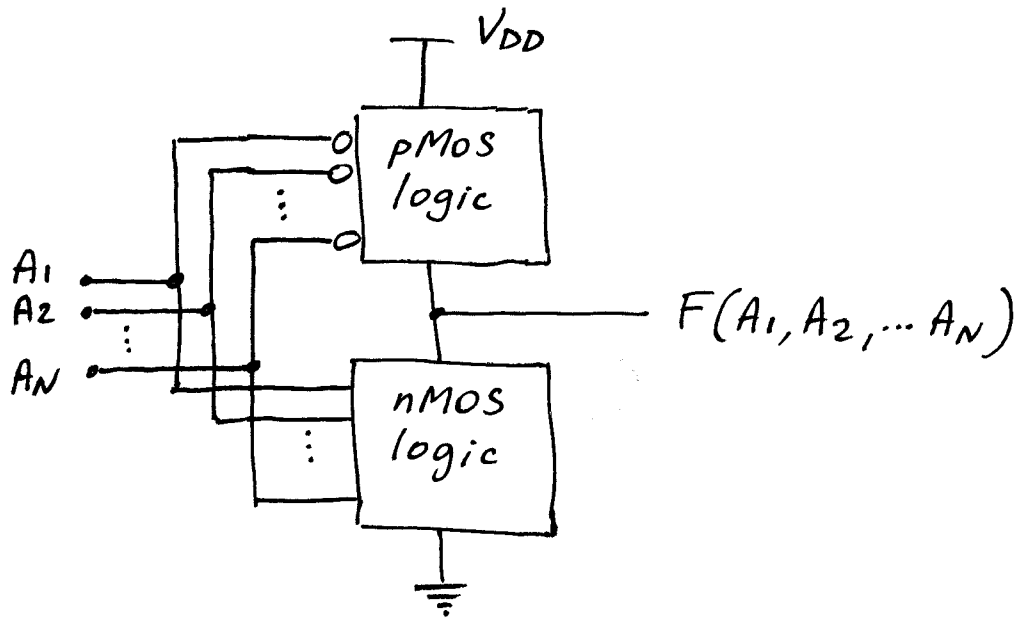


## CMOS combinational logic

CMOS logic gates are built from symmetric ("complementary") nMOS and pMOS transistors structures




Generic CMOS gate

Example : 2 inputs NAND gate


$A_1$	$A_2$	$F$
0	0	1
0	1	1
1	0	1
1	1	0

For  $F=0$  I need to create a path between  $F$  and ground (this is done through the nMOS transistors)

 
In order to put  $F=1$  I need to create a path between  $F$  and  $V_{DD}$  (this is done through the pMOS transistors)



 Once one of the 2 sections is built we can infer the other by symmetry ~~the other way~~ (no need of too much thinking)





 The "complementary" logic is built simply putting together the pMOS and nMOS sections.



Example : 2 inputs NOR gate

$A_1$	$A_2$	$F$
0	0	1
0	1	0
1	0	0
1	1	0

  

This time I start building the pMOS logic (I have less ones than zeros on the F column) and later I build the nMOS logic by symmetry

The switches connected serially on one section become connected in parallel in the other section, and vice versa.

Example

$$F = \overline{ABC + AD}$$

A	B	C	D	F
1	1	1	-	0
1	-	-	1	0
0	-	-	-	1
-	0	-	0	1
-	-	0	0	1

