 


Digital Systems: Quick Review

Digital System

- Transform signals that can be abstracted as discrete in range and domain



Analog & (vs.) Digital

- **Analog Circuits Advantages**
 - Require less devices
 - Better to deal with low signal amplitudes
 - Better to deal with high frequencies
- **Digital Circuits Advantages**
 - More “adaptable” (e.g. microprocessor)
 - Design can be done at a more abstract level
 - Better economic

Types of Digital Circuits

- **Combinational**
The value of the outputs at any time t depends only on the combination of the values applied at the inputs at time t (the system has no memory)
- **Sequential**
The value of the outputs at any time t depends not only on the values applied at the inputs at time t but also on the past sequence of inputs that have been applied to it (system with memory)

C.L.: effect of gate delays

- The analysis of combinational circuits ignoring delays can predict only the steady-state behavior of a circuits. That is they predict a circuit's output as a function of its inputs under the assumption that the inputs have been stable for a long time, relative to the delays into the circuit's electronics.
- Because of circuit delays, the transient behavior of a combinational logic circuit may differ from what is predicted by a steady-state analysis.
- In particular a circuit's output may produce a short pulse (often called a glitch) at a time when steady state analysis predicts that the output should not change.


C.L.: Timing Hazards

- A **glitch** is an unwanted pulse at the output of a combinational logic network – a momentary change in an output that should not have changed.
- A circuit with the potential for a glitch is said to have a **hazard**.
- An hazard is something **intrinsic** about a circuit; a circuit with hazard may or may not have a glitch depending on input patterns and the electric characteristics of the circuit.


When do C.L. circuits have Hazards ?

- Hazards are potential unwanted transients that occur in the output when different paths from input to output have different propagation delays

Types of Hazards (on an output)

 


(a) Static 1-hazard

 


 (b) Static 0-hazard

← The output undergoes a momentary transition when it is expected to remain unchanged






(c) Dynamic hazards

 

← The output changes multiple times as the result of a single input transition

Detection of Static 1-Hazards

 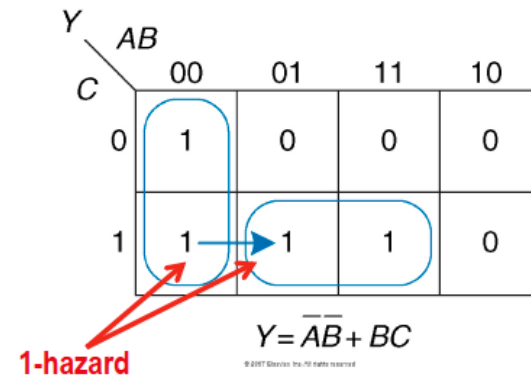
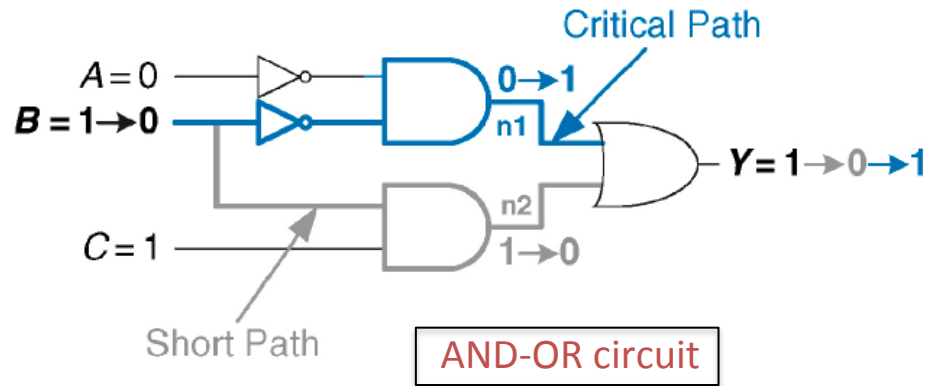


Basically because of gate delays for a moment when B changes is not true that $B + \bar{B} = 1$

Temporary violation of complementary law.

Removing Static Hazards

  
- The fundamental strategy for eliminating an hazard is to add redundant prime implicants (extra prime implicants won't change F, but can cause F to be asserted independently of the change to the input that cause the hazard).



circuit with hazard removed


Detection of static 0-Hazards

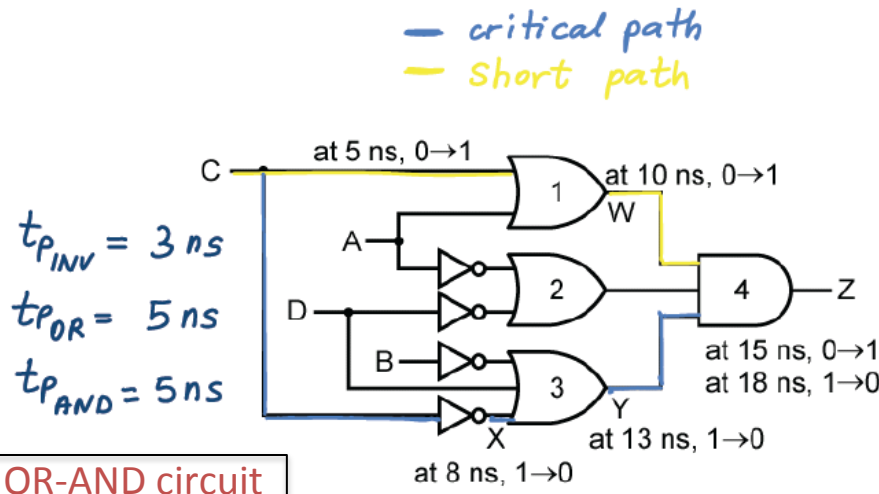example: $A=0, B=1, D=0, C=0 \rightarrow 1$



OR-AND circuit


(a) Circuit with a static 0-hazard

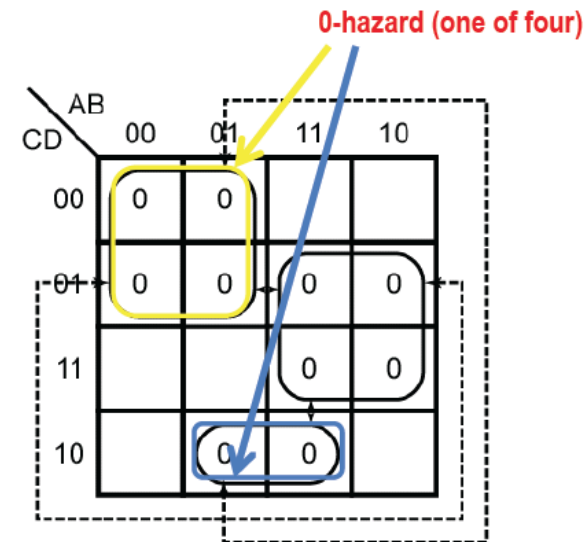

(b) Karnaugh map for circuit of (a)

Basically because of gate delays for a moment when C changes is not true that $C \cdot \bar{C} = 0$


Temporary violation of complementary law

 

(c) Timing diagram illustrating 0-hazard of (a)

$$F = (A+C) \cdot (\bar{A} + \bar{D}) \cdot (\bar{B} + \bar{C} + D)$$

Removing Static Hazards

 

The circuit has 4 potential sources of hazards that must be removed



$$F = (A+C) \cdot (\bar{A}+\bar{D}) \cdot (\bar{B}+\bar{C}+D) \cdot (C+\bar{D}) \cdot (A+\bar{B}+D) \cdot (\bar{A}+\bar{B}+\bar{C})$$


In theory: we need to focus only on one type of hazard !

- A **properly designed two level AND-OR circuit** has **no static 0-hazards**. A static 0-hazard would exist only if both a variable and its complement were connected to the same AND gate, which would be a nonsense ($A \cdot A' \cdot X=0$)
- A **properly designed two level OR-AND circuit** has **no static 1-hazards**. A static 1-hazard would exist only if both a variable and its complement were connected to the same OR gate, which would be a nonsense ($A+A'+X=1$)

Dynamic Hazards

- If there are 3 or more paths from an input or its complement to the output the circuit has the potential for a dynamic hazard.
- Three or more paths from an input or its complement to the output can exist only in a multi-level networks. This means that dynamic hazards do not occur in a properly designed two level AND-OR or OR-AND network.
- Analysis and elimination of dynamic hazards is a rather complicated process.
- If you need a hazard free network, it is best to use a 2-level network and use the techniques shown earlier to eliminate the static hazards.


Dynamic Hazard Example

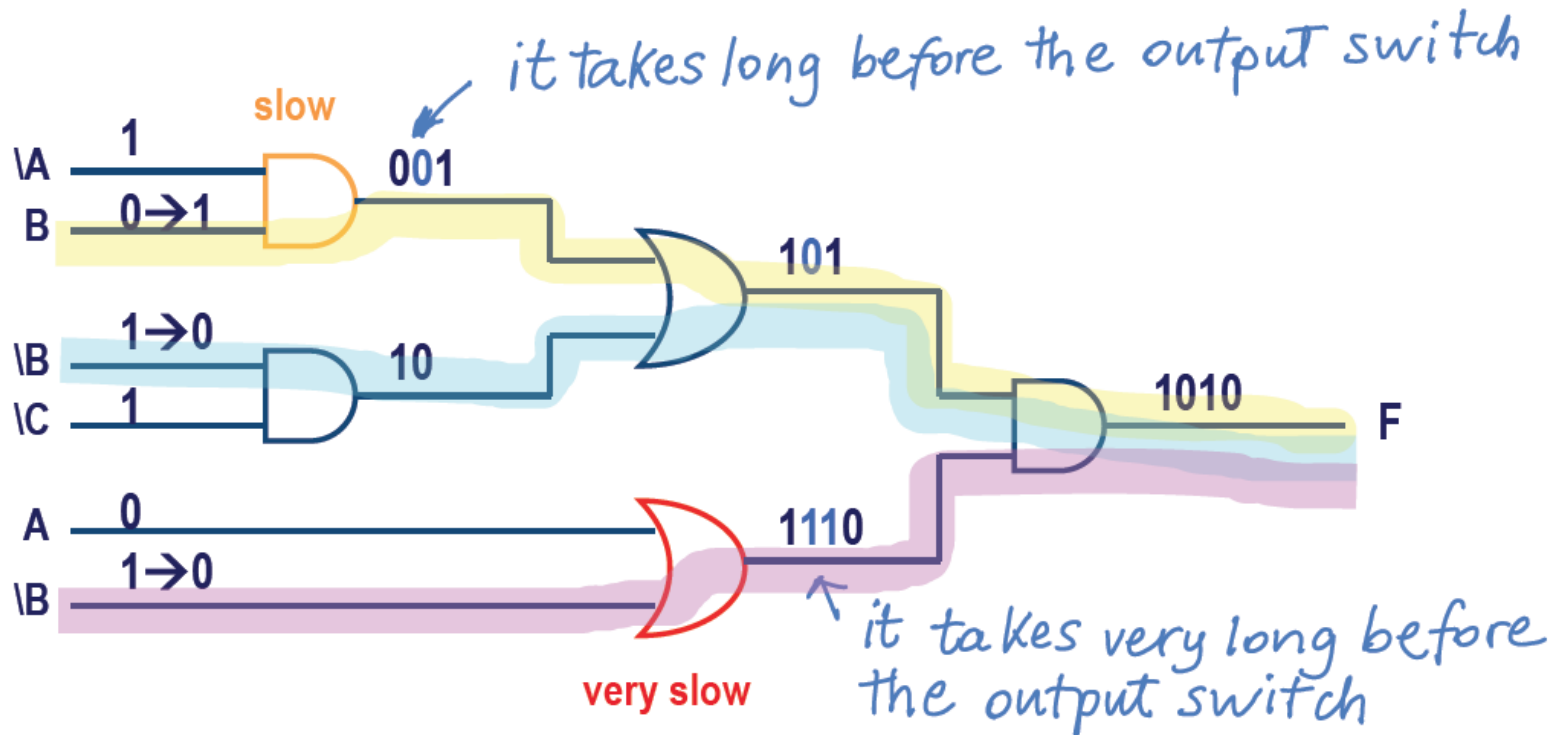

All gates are ideal (very fast) except a slow **AND** gate and a very slow **OR** gate

Hazard-Free Design

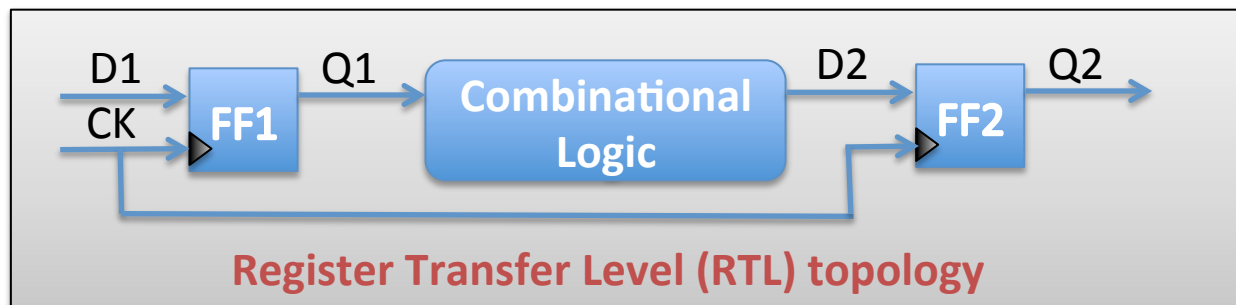- Best way to deal with hazards:
structure the design so that you do not have to worry about them !!!
- A well-designed, synchronous digital system is structured so that hazard analysis is not needed



- In a synchronous system, all the inputs to a combinational circuit are changed at a particular time, and the outputs are not looked at until they have time to settle to a steady-state value.

Timing Issues in S.L. circuits

- Set-up Time
- Hold Time
- Clock skew


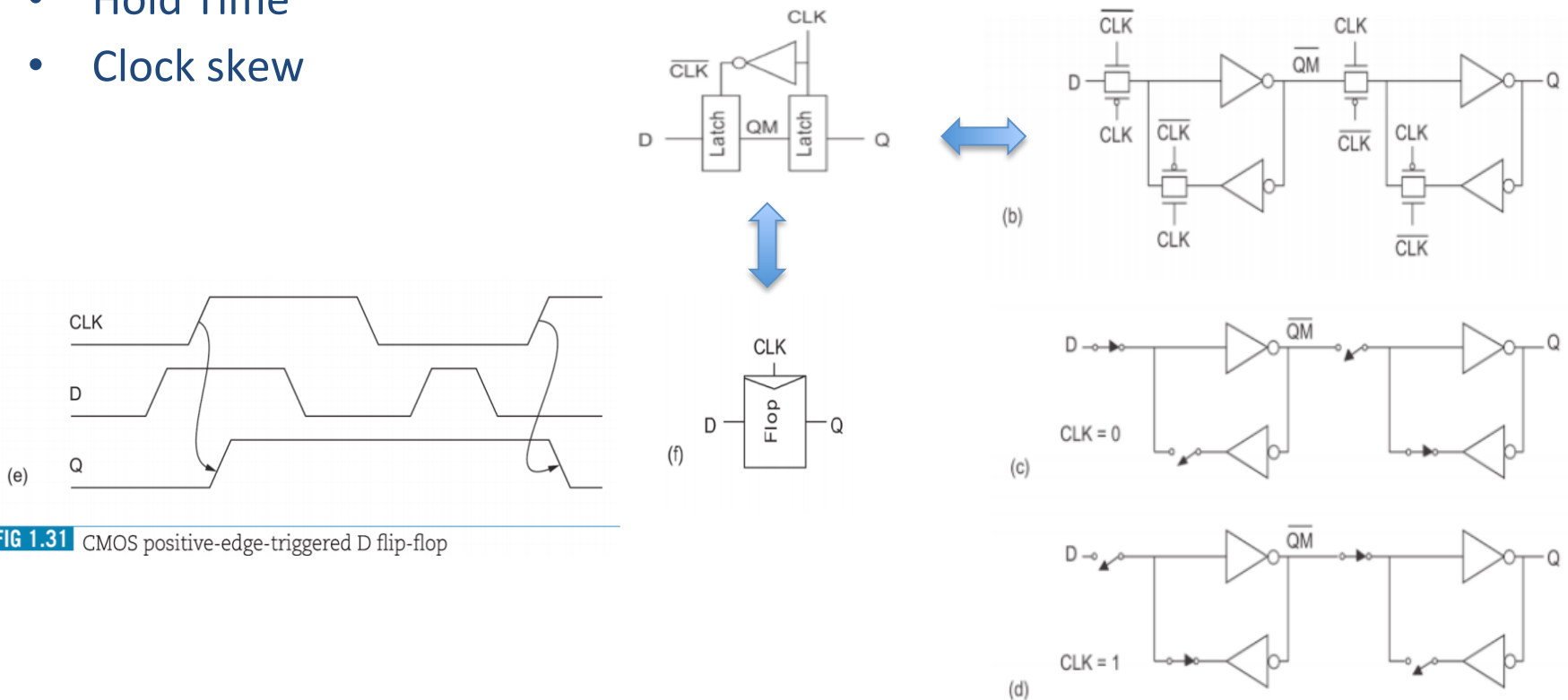


FIG 1.31 CMOS positive-edge-triggered D flip-flop


Setup/Hold Time

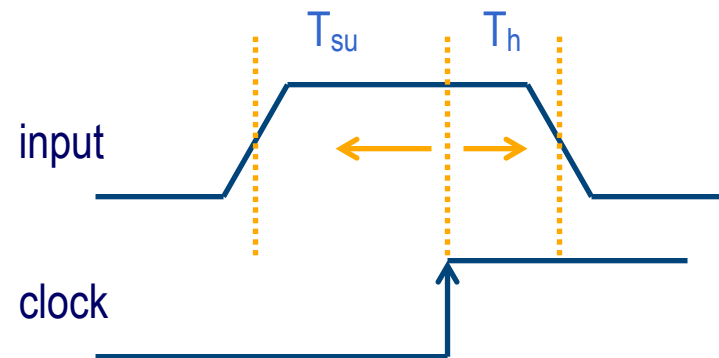


- An input to a flip flop can be validly recognized only if:
 - it is stable before the clocking event for a minimum time interval T_{setup} and
 - it is stable after the clocking event for a minimum time interval T_{hold}

Setup/Hold Time Violation

 - It is dangerous to allow input signals to change very close to the sampling event (that is the active clock edge)
- If setup or hold time constraints are not satisfied, the input maybe interpreted as a 1 or a 0 or some unrecognizable value between 0 and 1 (metastable value)




Timing Constraints in S.L. circuits

 

Let's assume d_{in} is applied in a way that satisfies setup and hold time for FF1, and let's examine what happens to FF2

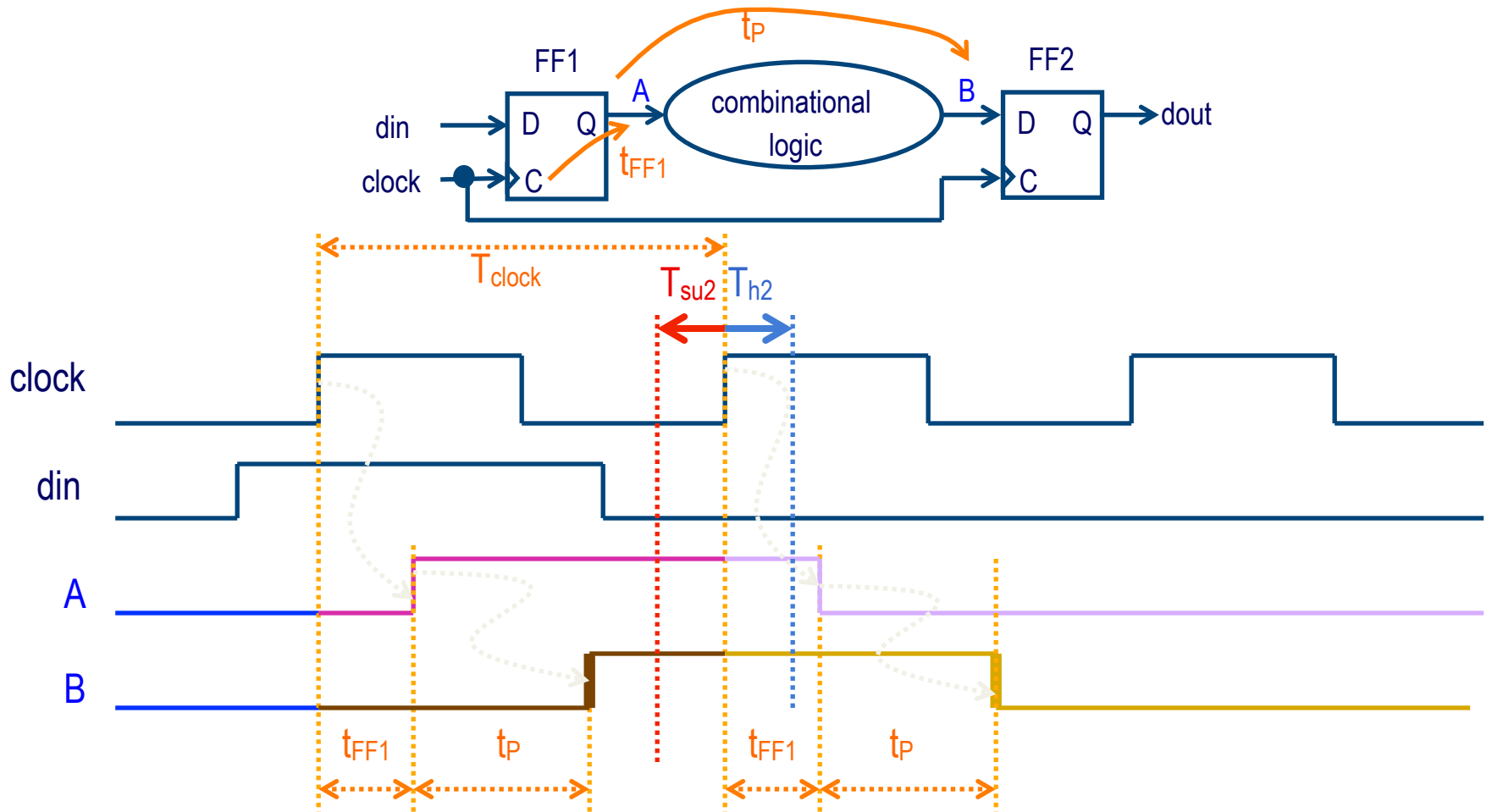Timing constraints in sequential circuits




Setup constraint

$$t_{FF1} + t_p < T_{clock} - T_{su2}$$

$$t_{FF1} + t_p > T_{h2}$$

Hold constraint

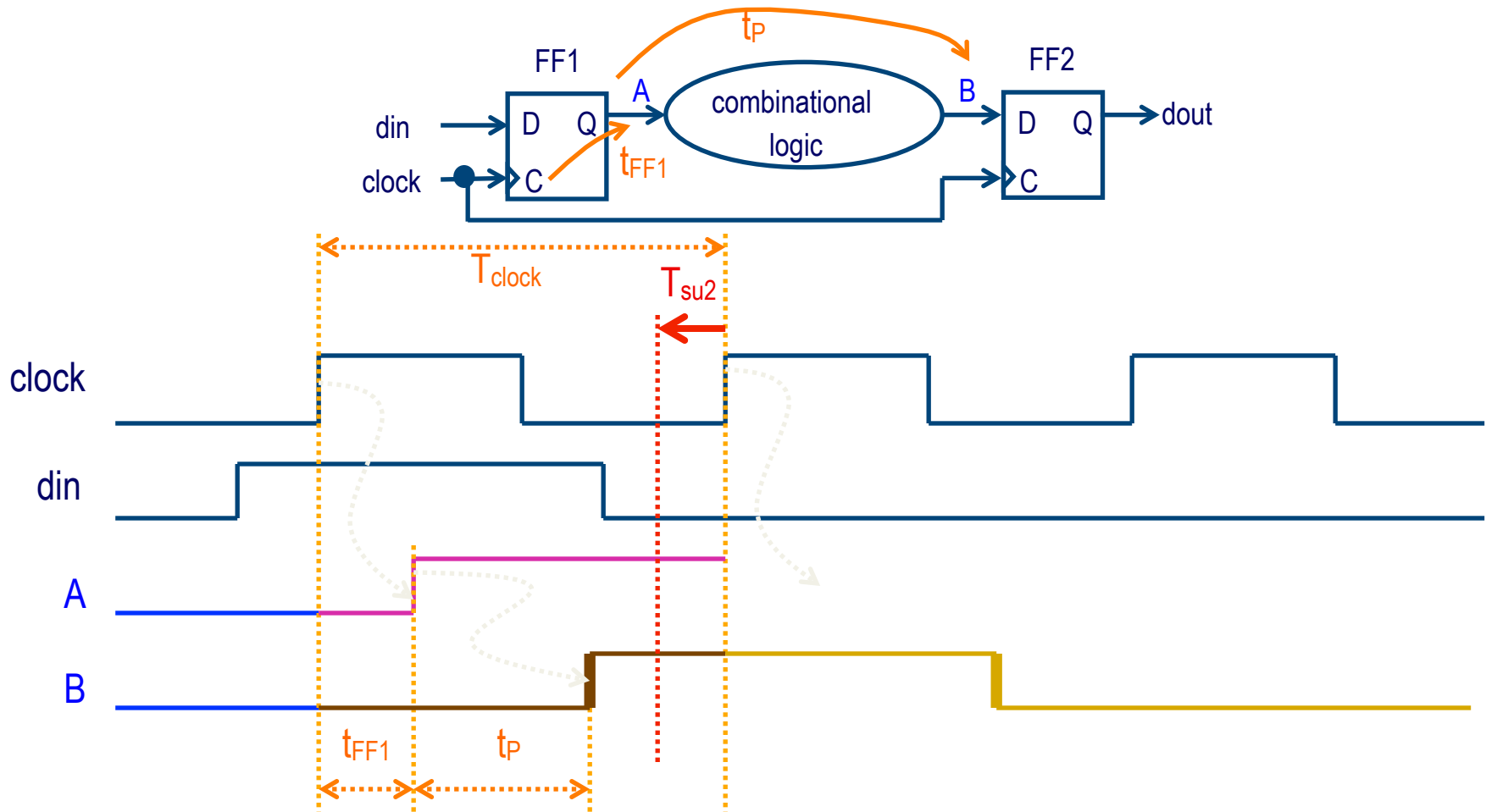
Timing constraints in sequential circuits




Setup constraint

$$t_{FF1} + t_p < T_{clock} - T_{su2}$$

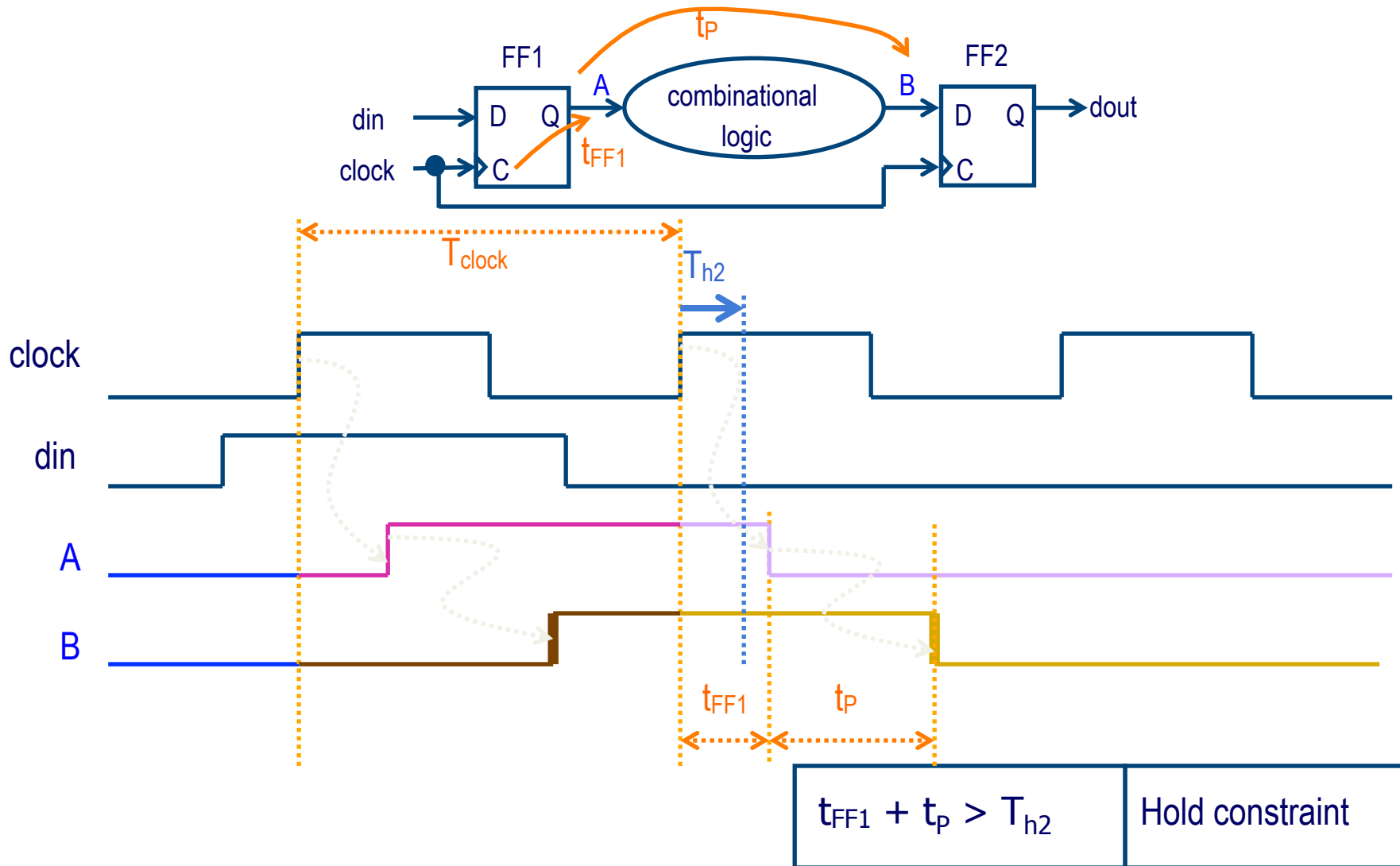Timing constraints in sequential circuits



Max/Min delays

 

Setup constraint	$t_{FF1} + t_p < T_{clock} - T_{su2}$	$t_{FF1} + t_p > T_{h2}$	Hold constraint
------------------	---------------------------------------	--------------------------	-----------------

- Unfortunately, delays through gates are not constant. Delays change with:
 - Supply Voltage, Temperature, and Manufacturing Process
- **Setup constraint** is more difficult to satisfy when delays are **max** ($V_{DD} \downarrow, T \uparrow, P \uparrow$)
- **Hold constraint** is more difficult to satisfy when delays are **min** ($V_{DD} \uparrow, T \downarrow, P \downarrow$)




$$I_{ds} = \beta(V_{gs} - VT)^2$$

$V_{DD} \downarrow \rightarrow V_{gs} \downarrow \rightarrow I_{ds} \downarrow \rightarrow$ it takes longer to charge C_L

$T \uparrow \rightarrow \mu \downarrow \rightarrow \beta \downarrow \rightarrow I_{ds} \downarrow \rightarrow$ it takes longer to charge C_L

Minimum Clock period for a Sequential circuit

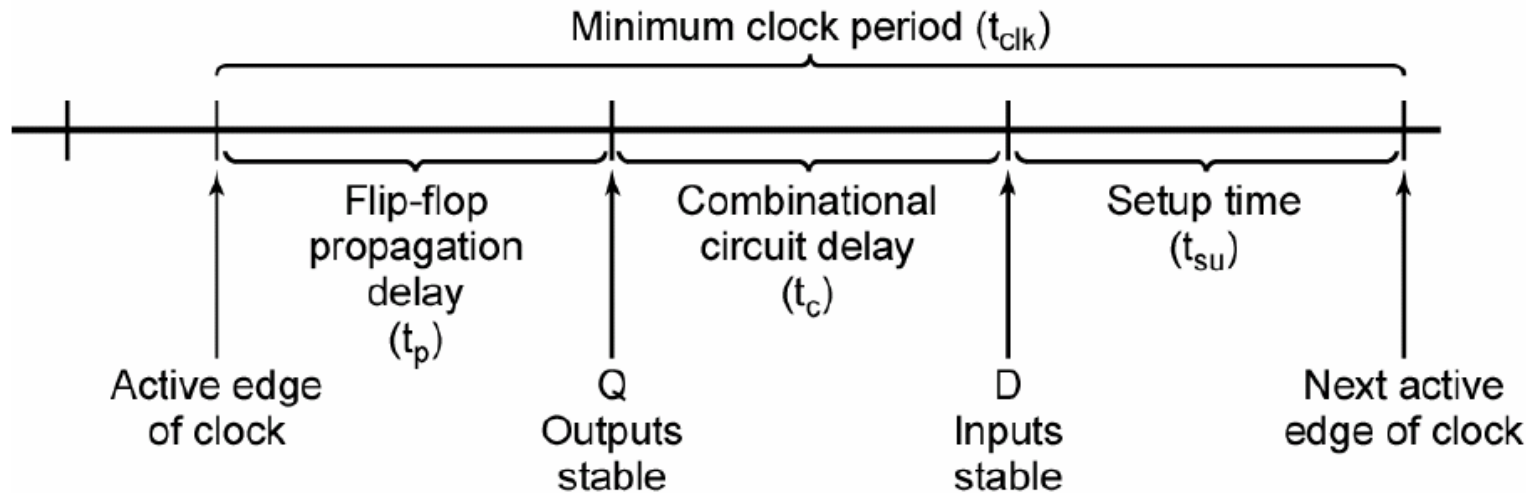max frequency
at which the
circuit can
operate





Minimum Clock Period for a Sequential Circuit

make sure to compute it with max delays

Clock skew

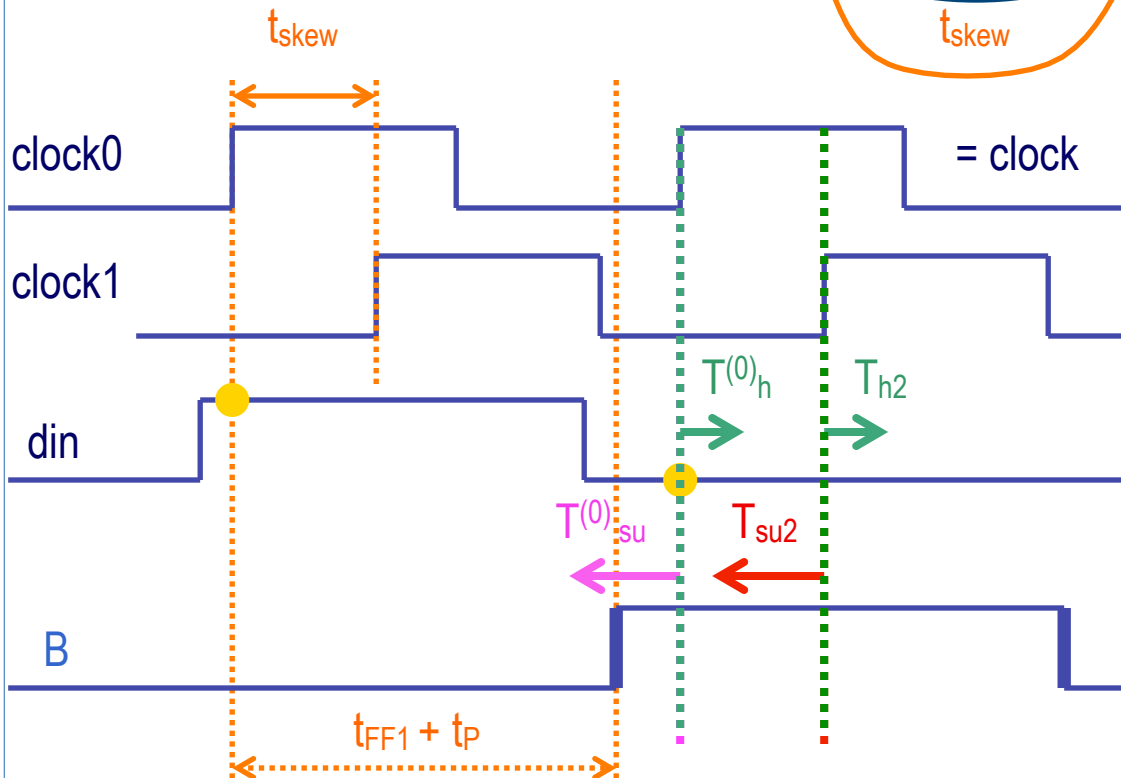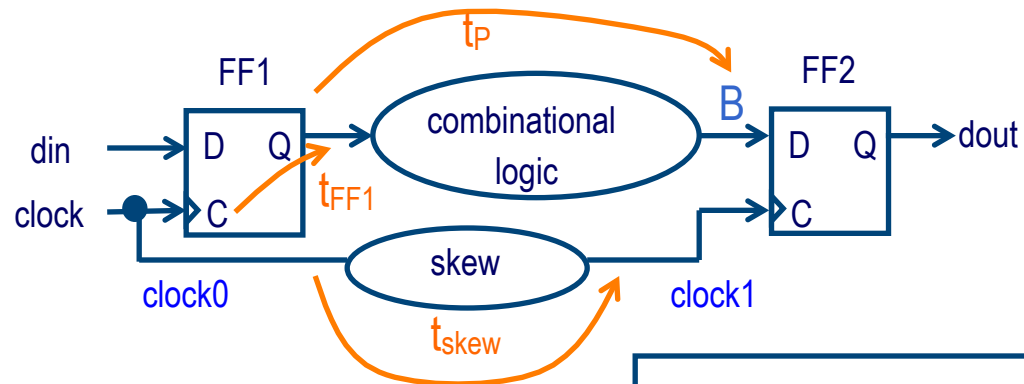
In this example if clock0=clock1 (no skew) setup at FF2 is violated



Positive skew makes easier to satisfy setup constraint:
 $t_{FF1} + t_P < T_{clock} - T_{su2} + t_{skew}$

Positive skew makes more difficult to satisfy hold constraint:
 $t_{FF1} + t_P > T_{h2} + t_{skew}$

Design Abstraction Levels

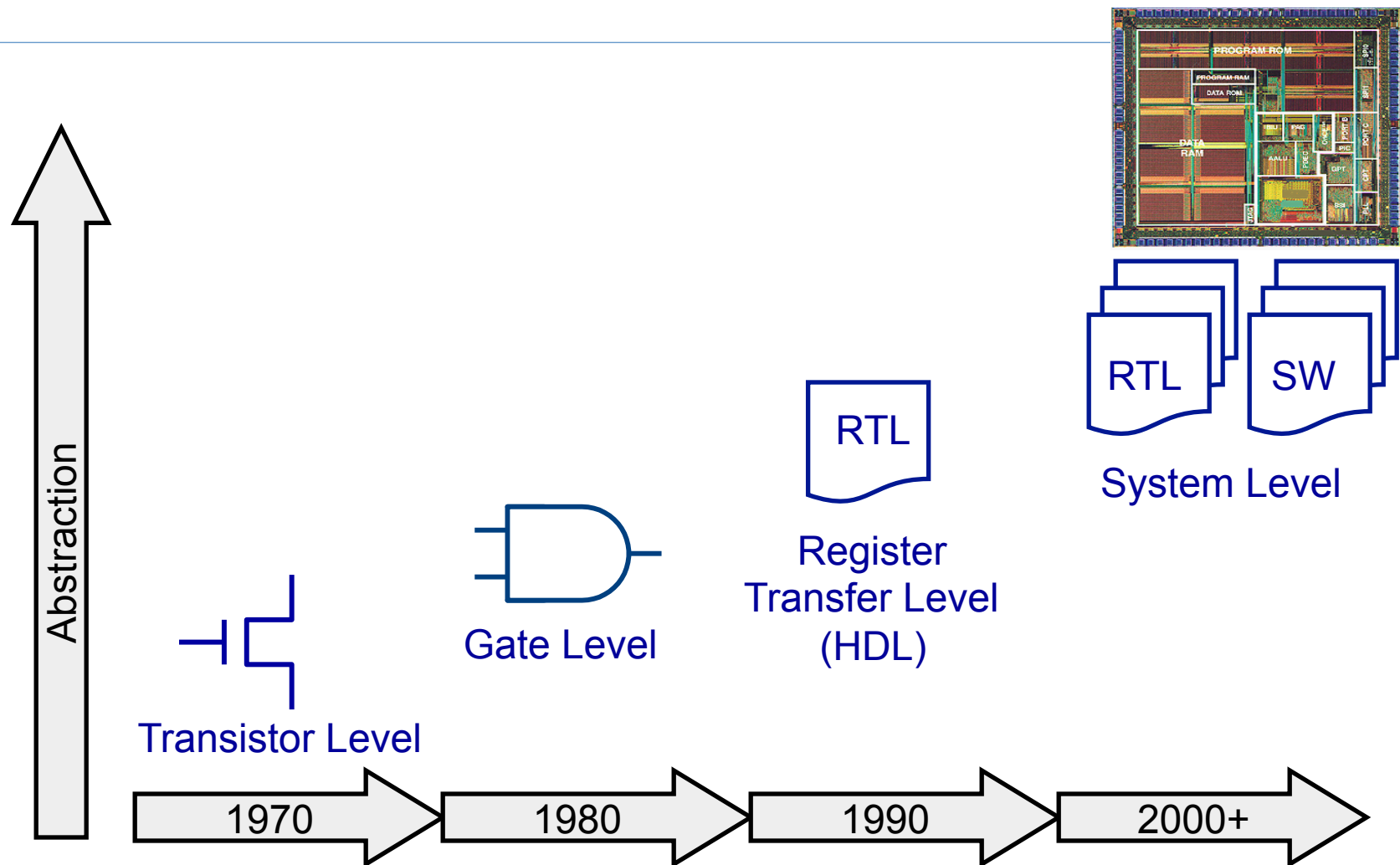


Moore's Law



- In 1963 Gordon Moore predicted that as a result of continuous miniaturization transistor count would double every 18 months
 - 53% compound annual growth rate over 45 years
 - No other technology has grown so fast so long
 - Transistors become smaller, faster, consume less power, and are cheaper to manufacture


The Design Productivity Gap

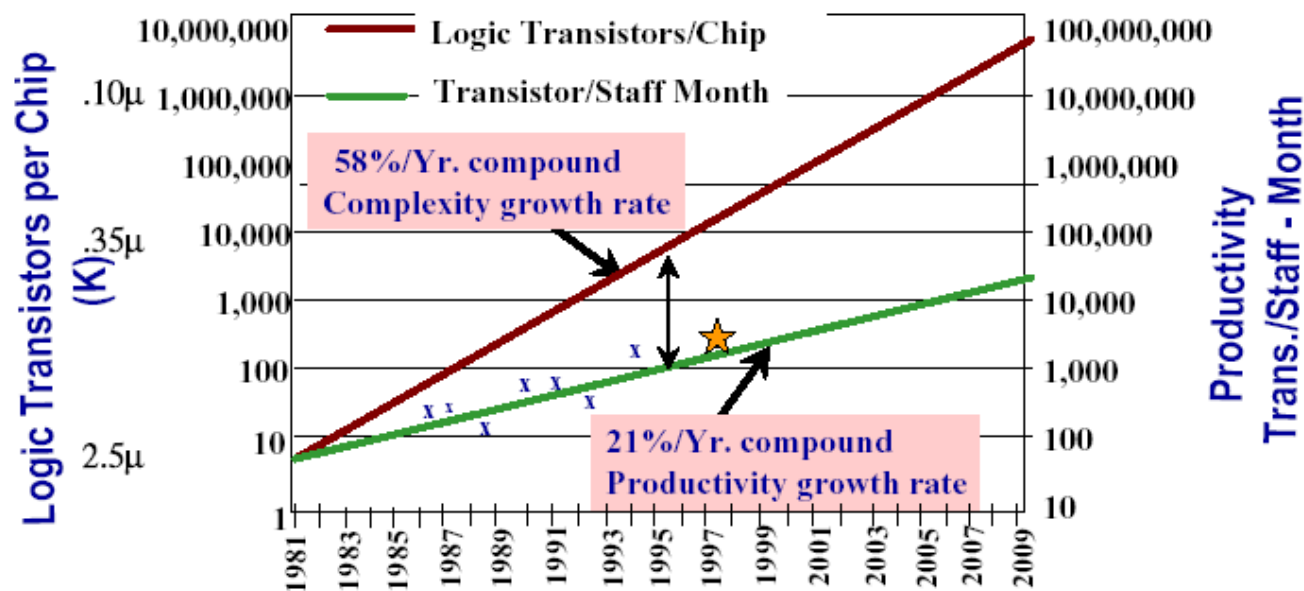

CAD Tools

- Designers rely on design automation software tools to seek productivity gains and to cope with increased complexity

Typical Design Flow

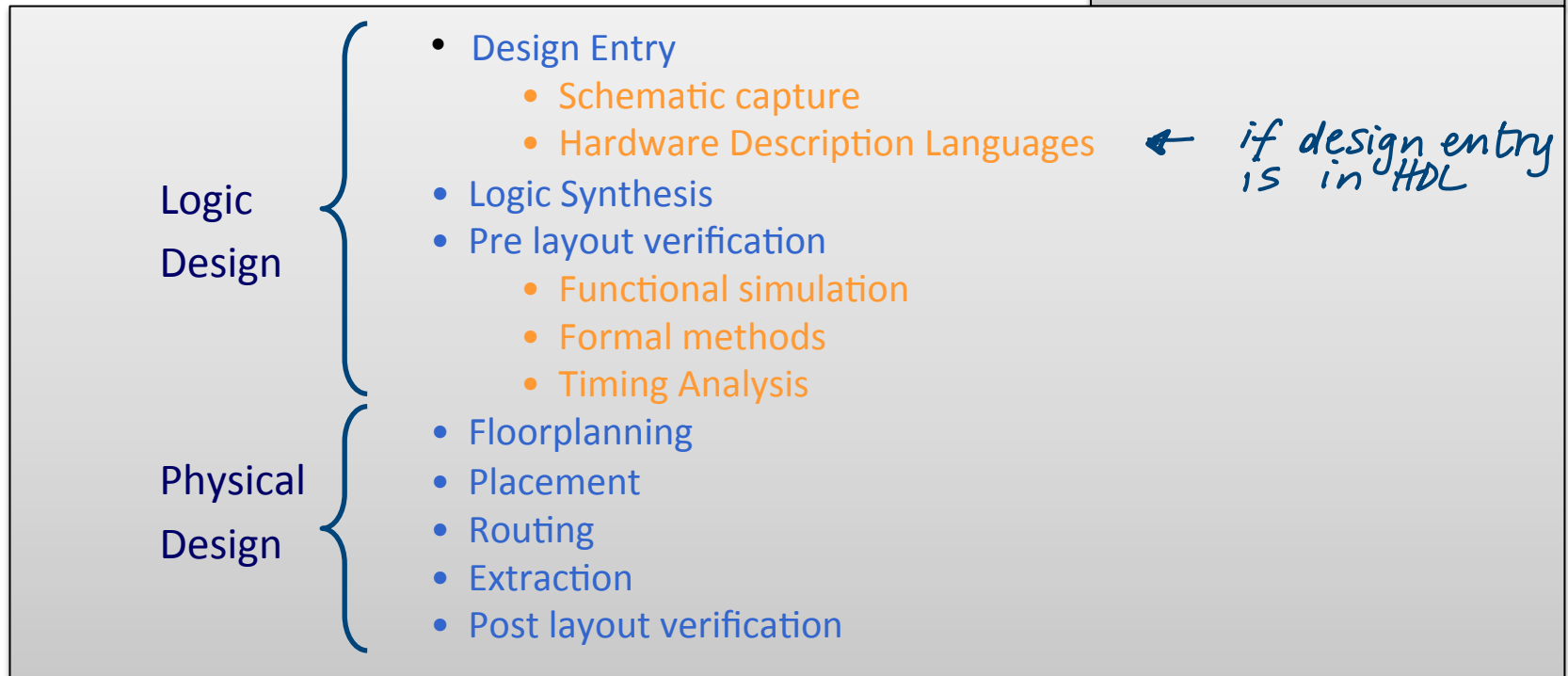

Types of ICs


Design Style




- * ASSP
- * ASIC

Use

 
- * Full-custom
- * Semi-custom
 - Cell Based
 - Gate Arrays
- * Programmable
 - CPLD and FPGA




Cell based

 

Gate Array


 


CPLD

 

FPGA

Back ... to Design Abstraction Levels

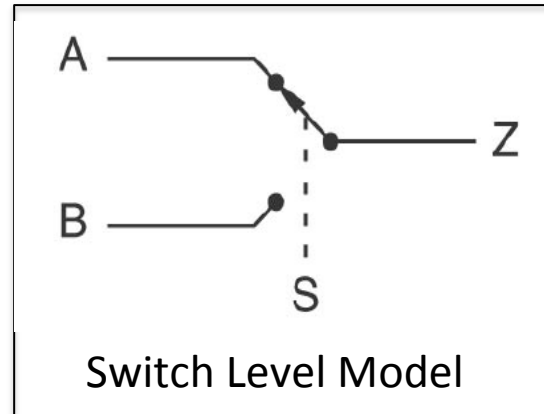 


$$Z = A \cdot \bar{S} + B \cdot S$$

Logic Equation




Truth Table

S	A	B	Z
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

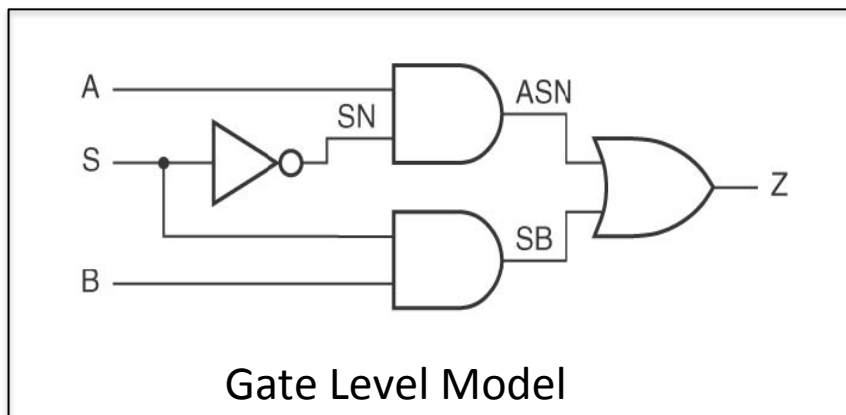Issues:
 - Level of
 Details
 - Portability
 - Physical
 mapping



... Design Abstraction Levels

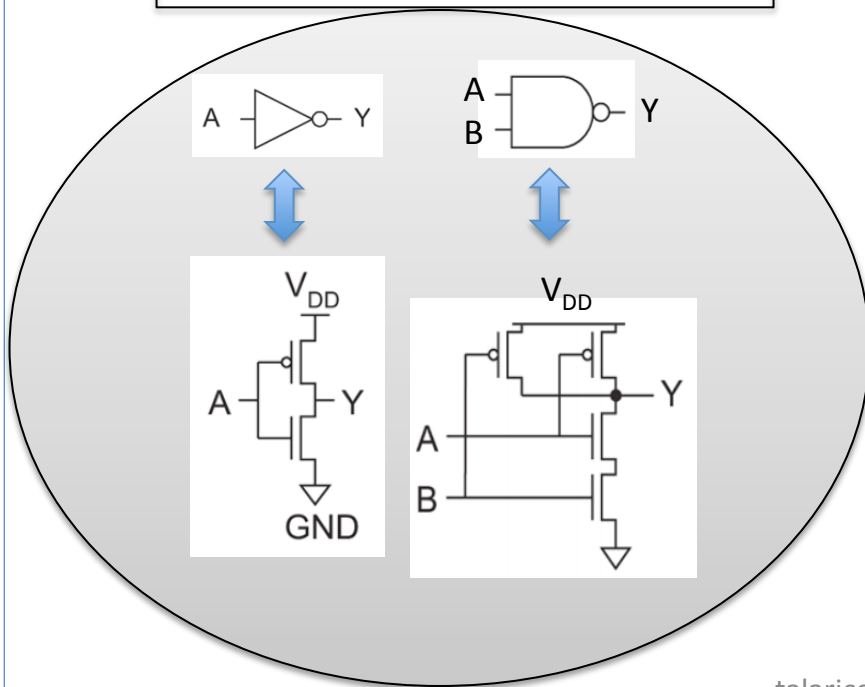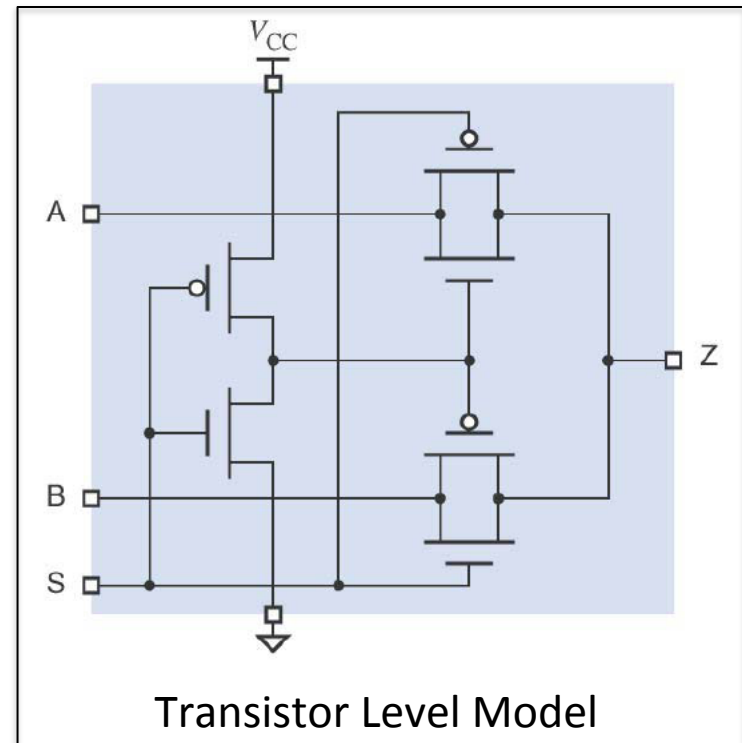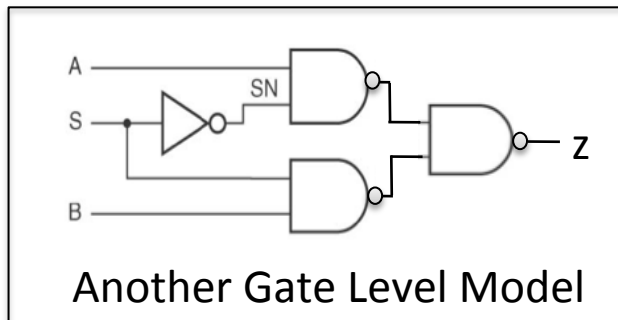

... Design Abstraction Levels: HDL

```
library ieee;
use ieee.std_logic_1164.all;
library altera;
use altera.altera_primitives_components.all;
```

```
entity mux is
port (A, B, S: in std_logic;
      Z: out std_logic);
end mux;
```


architecture struct of mux is

```
component INV is
port A: in std_logic;
      F: out std_logic);
end component;
component AND2 is:
port A, B: in std_logic;
      F: out std_logic);
end component;
component OR2 is:
port A, B: in std_logic;
      F: out std_logic);
end component;
```

```
signal SN, ASN, SB: std_logic;
```

```
begin
U1: port map INV (S, SN);
U2: port map AND2 (A, SN, ASN);
U3: port map AND2 (S, B, SB);
U4: port map OR2 (ASN, SB, Z);
end struct;
```

structural coding

 

Highly discouraged coding style except to:

- implement hierarchy
- infer “special” logic blocks (e.g. SRAM)

... Design Abstraction Levels: HDL

```
library ieee;  
use ieee.std_logic_1164.all;
```

```
entity mux is  
port (A, B, S: in std_logic;  
      Z: out std_logic);  
end mux;
```

```
architecture rtl_conc of mux is  
begin  
  Z <= A when S = '0' else B;  
end rtl_conc;
```

concurrent RTL coding

```
library ieee;  
use ieee.std_logic_1164.all;
```

```
entity mux is  
port (A, B, S: in std_logic;  
      Z: out std_logic);  
end mux;
```

```
architecture rtl of mux is  
begin  
  process mux_p (A, B, S)  
    if (S = '0') then  
      Z <= A;  
    else  
      Z <= B;  
    end if;  
  end process mux_p;  
end rtl;
```

sequential RTL coding

Preferred Style

