

The CMOS Inverter

Slides adapted from:

N. Weste and D. Harris, ***CMOS VLSI Design***

Addison-Wesley, 3/e, 2004

Outline

- Robustness of CMOS Inverter – The Static Behavior
 - Switching threshold
 - Noise Margins
- Performance of CMOS Inverter – Dynamic Behavior
 - Propagation delay
- Power Dissipation
 - Static dissipation
 - Dynamic dissipation

Q&A

1. If the width of a transistor increases, the current will
increase decrease not change
2. If the length of a transistor increases, the current will
increase decrease not change
3. If the supply voltage of a chip increases, the maximum transistor current will
increase decrease not change
4. If the width of a transistor increases, its gate capacitance will
increase decrease not change
5. If the length of a transistor decreases, its gate capacitance will
increase decrease not change
6. If the supply voltage of a chip increases, the gate capacitance of each transistor will
increase decrease not change

Q&A

1. If the width of a transistor increases, the current will
increase decrease not change
2. If the length of a transistor increases, the current will
increase **decrease** not change
3. If the supply voltage of a chip increases, the maximum transistor current will
increase decrease not change
4. If the width of a transistor increases, its gate capacitance will
increase decrease not change
5. If the length of a transistor decreases, its gate capacitance will
increase **decrease** not change
6. If the supply voltage of a chip increases, the gate capacitance of each transistor will
increase decrease **not change**

CMOS Inverter Static Behavior: DC Analysis

 


FIG 2.23 A CMOS inverter

CMOS Inverter: DC Analysis


- DC Response: V_{out} vs. V_{in} for a gate
- Inverter
 - When $V_{\text{in}} = 0 \rightarrow V_{\text{out}} = V_{\text{DD}}$
 - When $V_{\text{in}} = V_{\text{DD}} \rightarrow V_{\text{out}} = 0$
 - In between, V_{out} depends on transistor current
 - By KCL, must settle such that
 - $I_{\text{dsn}} = |I_{\text{dsp}}|$
 - We can solve equations
 - Graphical solution gives very good insight

Transistors operation regions

- Current depends on transistor's operation region
- For what V_{in} and V_{out} are nMOS and pMOS in
 - Cutoff ?
 - Linear ?
 - Saturation ?


nMOS and pMOS operation

Table 2.2 Relationships between voltages for the three regions of operation of a CMOS inverter			
	Cutoff	Linear	Saturated
nMOS	$V_{gsn} < V_{tn}$	$V_{gsn} > V_{tn}$	$V_{gsn} > V_{tn}$
	$V_{in} < V_{tn}$	$V_{in} > V_{tn}$	$V_{in} > V_{tn}$
		$V_{dsn} < V_{gsn} - V_{tn}$	$V_{dsn} > V_{gsn} - V_{tn}$
		$V_{out} < V_{in} - V_{tn}$	$V_{out} > V_{in} - V_{tn}$
pMOS	$V_{gsp} > V_{tp}$	$V_{gsp} < V_{tp}$	$V_{gsp} < V_{tp}$
	$V_{in} > V_{tp} + V_{DD}$	$V_{in} < V_{tp} + V_{DD}$	$V_{in} < V_{tp} + V_{DD}$
		$V_{dsp} > V_{gsp} - V_{tp}$	$V_{dsp} < V_{gsp} - V_{tp}$
		$V_{out} > V_{in} - V_{tp}$	$V_{out} < V_{in} - V_{tp}$

 

$$V_{gsn} = V_{in}$$

$$V_{dsn} = V_{out}$$

 


$$V_{gsp} = V_{in} - V_{DD}$$

$$V_{dsp} = V_{out} - V_{DD}$$


Graphical derivation of the inverter DC response: I-V Characteristics

 - Make pMOS wider than nMOS such that $\beta_n = \beta_p$
- For simplicity let's assume $V_{tn} = -V_{tp}$




Graphical derivation of the inverter DC response: current vs. V_{out} , V_{in}

- Load Line Analysis:
For a given V_{in} :
 - Plot I_{dsn} , I_{dsp} vs. V_{out}
 - V_{out} must be where $|currents|$ are equal

 


Graphical derivation of the inverter DC response: Load Line Analysis

- $V_{in} = 0$

 


Graphical derivation of the inverter DC response: Load Line Analysis

- $V_{in} = 0.2 V_{DD}$

 


Graphical derivation of the inverter DC response: Load Line Analysis

- $V_{in} = 0.4 V_{DD}$

 


Graphical derivation of the inverter DC response: Load Line Analysis

- $V_{in} = 0.6 V_{DD}$

 


Graphical derivation of the inverter DC response: Load Line Analysis

- $V_{in} = 0.8 V_{DD}$

 


Graphical derivation of the inverter DC response: Load Line Analysis

- $V_{in} = V_{DD}$

 

DC Transfer Curve

 - Transcribe points onto V_{in} vs. V_{out} plot



In region C both transistors are in saturation.
 Ideal transistors are only in region C for $V_{in} = \frac{V_{DD}}{2}$
 and the DC curve slope in C is $-\infty$.

The crossover point where $V_{in} = V_{out}$ is called input threshold.

DC transfer curve: operating regions


 
 
 


FIG 2.23 A CMOS inverter

Table 2.3 Summary of CMOS inverter operation				
Region	Condition	p-device	n-device	Output
A	$0 \leq V_{in} < V_{tn}$	linear	cutoff	$V_{out} = V_{DD}$
B	$V_{tn} \leq V_{in} < V_{DD}/2$	linear	saturated	$V_{out} > V_{DD}/2$
C	$V_{in} = V_{DD}/2$	saturated	saturated	V_{out} drops sharply
D	$V_{DD}/2 < V_{in} \leq V_{DD} - V_{tp} $	saturated	linear	$V_{out} < V_{DD}/2$
E	$V_{in} > V_{DD} - V_{tp} $	cutoff	linear	$V_{out} = 0$

Beta Ratio

 - If $\beta_p / \beta_n \neq 1$, switching point will move from $V_{DD}/2$
- Called *skewed gate*



- $\beta_p > \beta_n$
HIGH SKEWED inverter
 $V_{in} = \frac{V_{DD}}{2} \rightarrow V_{out} > \frac{V_{DD}}{2}$
- $\beta_p < \beta_n$
LOW SKEWED inverter
 $V_{in} = \frac{V_{DD}}{2} \rightarrow V_{out} < \frac{V_{DD}}{2}$

FIG 2.26 Transfer characteristics of skewed inverters

Noise Margins

- How much noise can a gate input see before it does not recognize the input ?

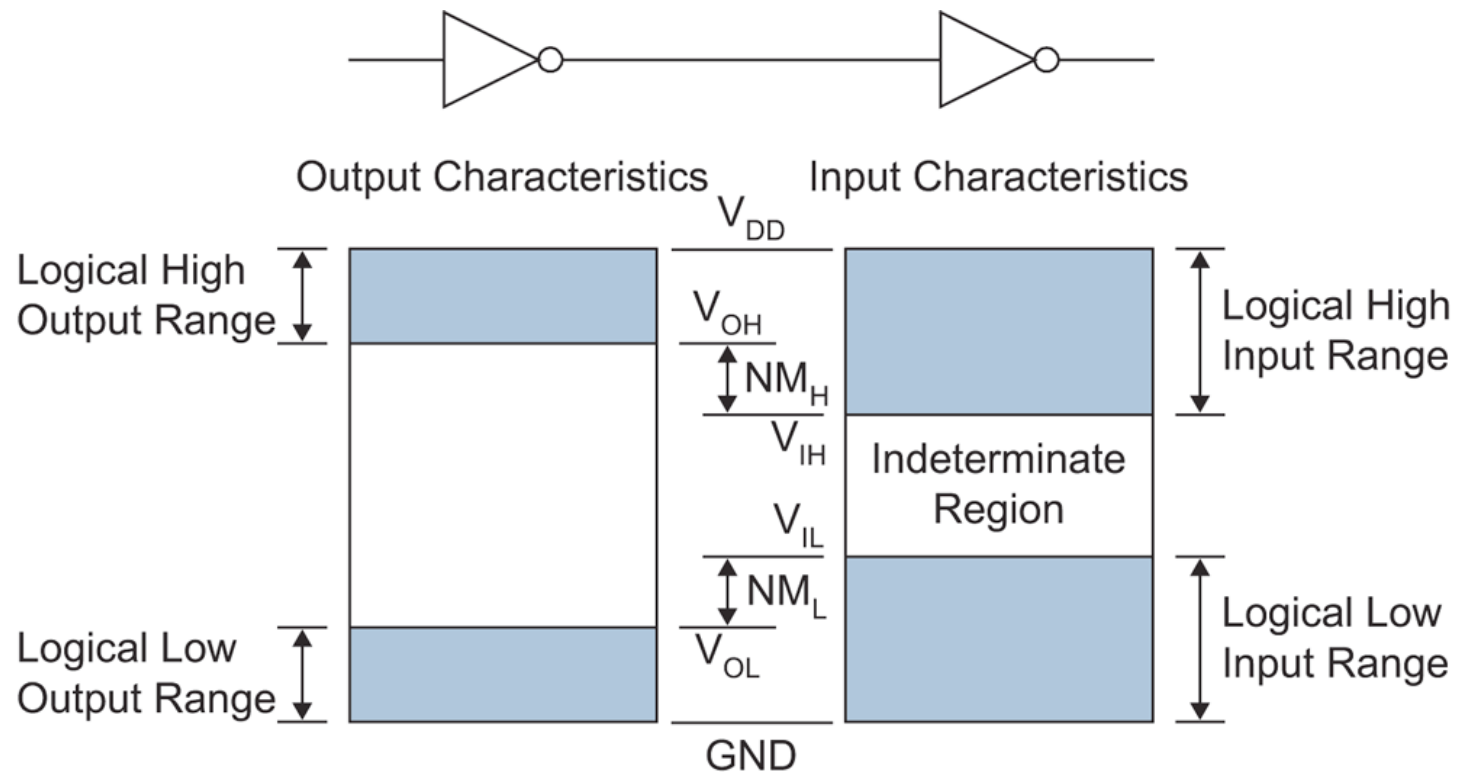


FIG 2.27 Noise margin definitions

Noise Margins

- To maximize noise margins, select logic levels at unity gain point of DC transfer characteristic

 


FIG 2.28 CMOS inverter noise margins

DC parameters

- Input switching threshold: V_{TH}
- Minimum high output voltage: V_{OH}
- Maximum low output voltage: V_{OL}
- Minimum HIGH input voltage: V_{IH}
- Maximum LOW input voltage: V_{IL}

} symmetry of the logic gate behavior

} quality of the logic values provided by the gate

} ability of the logic gate to tolerate noise


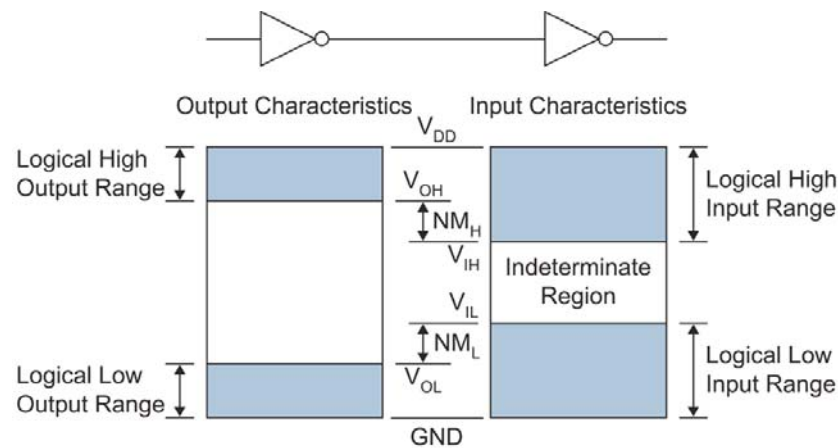


FIG 2.27 Noise margin definitions

 CMOS Inverter Dynamic Behavior: AC Analysis



- DC analysis tells V_{out} if V_{in} is constant
- AC analysis tells $V_{out}(t)$ if $V_{in}(t)$ changes
 - Requires solving differential equations
- Input is usually considered to be a step or ramp from 0 to V_{DD} or vice versa

FIG 2.23 A CMOS inverter

AC analysis = transient analysis = switching analysis = dynamic analysis

CMOS Inverter Dynamic Behavior: AC Analysis

- The switching characteristic ($V_{out}(t)$ given $V_{in}(t)$) of a logic gate tells the speed at which the gate can operate
- The switching speed of a logic gate can be measured in terms of the time required to charge and discharge a capacitive load
- Critical paths
- Timing Analyzers automatically finds the slowest paths in a logic design
- Critical paths can be affected at various levels:
 - Architecture/ Micro-architecture Level
 - Logic Level
 - Circuit Level
 - Layout level

Inverter Step Response



- Find step response of inverter driving load cap

$$V_{in}(t) = u(t - t_0)V_{DD}$$

$$V_{out}(t < t_0) = V_{DD}$$

$$\frac{dV_{out}(t)}{dt} = -\frac{I_{dsn}(t)}{C_{load}}$$
 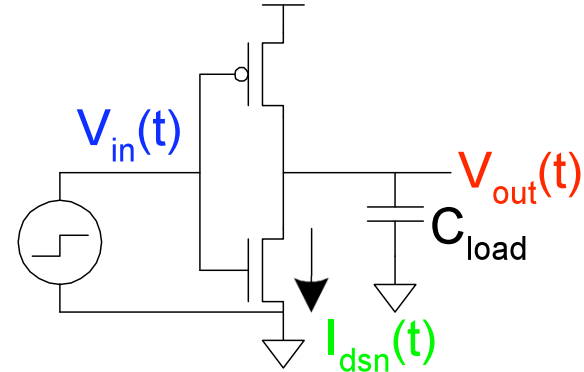
$$I_{dsn}(t) = \begin{cases} 0 & t \leq t_0 \\ \frac{\beta}{2}(V_{DD} - V_t)^2 & V_{out} > V_{DD} - V_t \\ \beta \left(V_{DD} - V_t - \frac{V_{out}(t)}{2} \right) V_{out}(t) & V_{out} < V_{DD} - V_t \end{cases}$$



Delay Parameters

- **t_r : rise time**
 - From output crossing $0.2 V_{DD}$ to $0.8 V_{DD}$
- **t_f : fall time**
 - From output crossing $0.8 V_{DD}$ to $0.2 V_{DD}$
- **t_{pdr} : rising propagation delay**
 - From input crossing $V_{DD}/2$ to rising output crossing $V_{DD}/2$
- **t_{pdf} : falling propagation delay**
 - From input crossing $V_{DD}/2$ to falling output crossing $V_{DD}/2$
- **t_{pd} : average propagation delay**
 - $t_{pd} = (t_{pdr} + t_{pdf})/2$

Delay Parameters cont.


- t_r, t_f
 - Tells how steep can be the waveform that the logic gate is able to provide at its output
- t_{pdr}, t_{pdf}
 - Input-to-output delay of the logic gate (time needed for the output to respond to a change in the input)

Factors affecting delay

- $C_{\text{LOAD}} (= C_{\text{intrinsic}} + C_{\text{extrinsic}})$
 - intrinsic capacitance
(parasitic capacitance of the driving logic gate)
 - extrinsic capacitance
(interconnect capacitance + capacitance of the stage driven)
- Slope of the input waveform
 - As the voltage on the gate terminal of a transistor change so does its capacitance

Simulated Inverter Delay

 - Solving differential equations by hand is too hard
- SPICE simulator solves the equations numerically
 - Uses more accurate I-V models too!
- But simulations take time to write
- It is important to develop back of the envelope techniques to rapidly estimate delay, understand its origin, and figure out how it can be reduced





Delay Estimation (*Revisited*)

- We would like to be able to easily estimate delay
 - Not as accurate as simulation
 - But easier to ask “What if ?”
- The step response usually looks like a 1st order RC response with a decaying exponential.
- Use RC delay models to estimate delay
 - C = total capacitance on output node
 - Use *effective resistance* R
 - So that $t_{pd} = RC$
- Characterize transistors by finding their effective R
 - Depends on average current as gate switches

$$R = \ln 2 \cdot \mathfrak{R}$$

RC Delay Models

  - Use equivalent circuits for MOS transistors
 - Ideal switch + capacitance and ON resistance
 - Unit nMOS has resistance R , capacitance C
 - Unit pMOS has resistance $2R$, capacitance C
- Capacitance proportional to width
- Resistance inversely proportional to width



Power Dissipation

- Static CMOS gates are very power-efficient because they dissipate nearly zero power while idle

- Instantaneous power: $P = i_{DD}(t) \cdot V_{DD}$

- Energy consumed: $E = \int_0^T i_{DD} \cdot V_{DD} dt$

- Average power: $P_{avg} = \frac{1}{T} \int_0^T i_{DD} \cdot V_{DD} dt$

Power Dissipation

- Power dissipation in CMOS circuits comes from two components:
 - Static Dissipation
 - Subthreshold conduction
 - Tunneling current
 - Leakage through reverse biased diodes
 - Dynamic Dissipation
 - Charging and discharging (switching) of the load capacitance
 - “Short-Circuit” current while both pMOS and nMOS networks are partially ON

Assume $I_{leakage} \approx \text{constant}$

Static Dissipation

$$P_{\text{static}} = V_{\text{DD}} \cdot I_{\text{leakage}}$$

- OFF transistors still conduct a certain amount of current :
 - Sub threshold current
 - Current through reverse biased diodes
 - gate tunneling current

 


FIG 4.26 CMOS inverter model for static power dissipation evaluation

- In 130 nm processes and beyond leakage is becoming a major design issue and vendors now provide leakage data (often in the form of nA/ μm of gate length)

Dynamic Dissipation

$$P_{\text{dynamic}} = P_{\text{sw}} + P_{\text{sc}} = \frac{1}{T} \int_0^T i_{\text{DD}}(t) \cdot V_{\text{DD}} dt = \frac{V_{\text{DD}}}{T} \int_0^T i_{\text{DD}}(t) dt$$

Assuming a logic gate goes through one complete charge/discharge cycle every clock cycle:

$$P_{\text{sw}} = C \cdot V_{\text{DD}}^2 \cdot f_{\text{clock}}$$

Because most gates do not switch every clock cycle, we introduce a corrective activity factor α :

$$P_{\text{sw}} = \alpha \cdot C \cdot V_{\text{DD}}^2 \cdot f_{\text{clock}}$$

A clock has $\alpha=1$ because it rises and fall every cycle, but most data have a maximum activity factor $\alpha=0.5$ because they transition only once every cycle

Dynamic Dissipation

- Because, input rise/fall time is greater than zero, both nMOS and pMOS will be ON for a short period of time (while the input is between V_{tn} and $VDD - |V_{tp}|$)
- This results in a “short-circuit” current pulse from VDD to GND
- Typically this increases power dissipation by about 10%

Low Power Design

- Power Dissipation is a major problem !!!

 
 


FIG 4.69 Intel processor power consumption. © IEEE 2001.

FIG 4.70 Dynamic and static power trends. © IEEE 2003.

Dynamic Power Reduction

- Decrease activity factor
 - Selective clock gating
 - Drawback: if the system transitions rapidly from an idle mode to a fully active mode a large di/dt spike will occur
- Decrease switching capacitance
 - Small transistors
 - Careful floor planning to reduce interconnect
- Decrease power supply
 - Adjust voltage depending on the operating mode
- Decrease operating frequency

Static Power Reduction

- Subthreshold current can be reduced by increasing V_t
 - Selective application of multiple threshold (low- V_t transistors on critical paths, high V_t transistors on other paths)
 - Control V_t through the body voltage

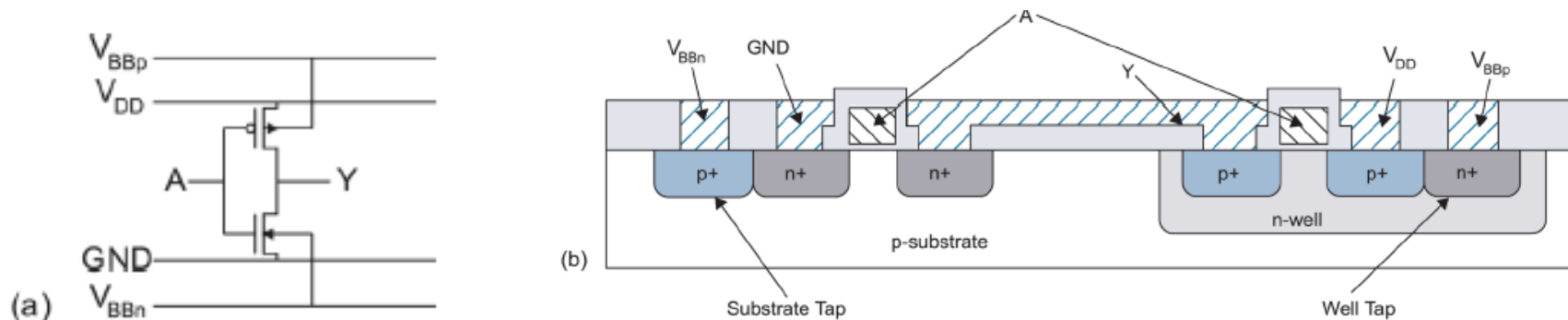


FIG 4.27 Body bias

Static Power Reduction cont.

- Turn off the power supply entirely. MTCMOS circuits use low V_t transistors for computation and high V_t transistor as a switch to disconnect the power supply during idle mode

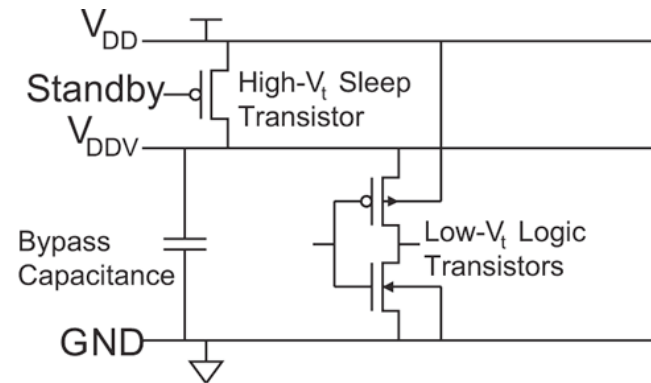


FIG 4.28 MTCMOS

- The leakage through two series OFF transistor is much lower (10-20x) than that of a single transistor (stack effect)

 


FIG 4.29 Leakage stack effect

Energy Delay Product (1/2)

- Delay is proportional to CV_{DD}/I_{dsat} ($\tau = Q/I$)

$$\tau = \kappa \frac{C \cdot V_{DD}}{(V_{DD} - V_T)^\eta}$$



κ reflect technology parameters

η account for velocity saturation

- Switching energy is proportional to CV_{DD}^2

$$E_{sw} = \alpha \cdot C \cdot V_{DD}^2$$

Energy Delay Product (2/2)

$$EDP = K \frac{C^2 \cdot V_{DD}^3}{(V_{DD} - V_T)^\eta}$$

- **BUT** ... unfortunately there is also the leakage energy:

$$E_{leak} = I_{leak} \cdot \frac{V_{DD}}{f} = \underbrace{I_{off} \cdot e^{\frac{V_{gs} - V_T}{nv_{TH}}} (1 - e^{-V_{ds}/v_{TH}})}_{\text{leakage current}} \cdot \frac{V_{DD}}{f}$$

Source: Kaushik Roy



I_{off} is the subthreshold current at $V_{gs}=0$ and $V_{ds}=V_{DD}$

v_{TH} is the thermal voltage