 


C10



**Verilog Coding Guidelines**  
for  
**High Performance**

**QUICK REFERENCE GUIDE**  
Version 1.0



**Synopsys, Inc.**  
**700 E. Middlefield Road**  
**Mt. View, CA 94043**

## Contents

---

<b>General Purpose Functions</b>	<b>5</b>
<b>If Statement</b>	
Priority encoded	6
Parallel encoded	8
Cascaded Select Logic	10
<b>Logic Replication</b>	
Pre-computing Values	12
<b>Case Statement</b>	
Embedded If	14
Late-arriving Selector	16
<b>Operand Reordering</b>	18
<b>Carry-in Speedup</b>	20
<b>Eliminating Common Subexpressions</b>	
Reducing Area	22
<b>Linear Structures</b>	
Reduce XOR function	24
MUXes	26

## General Purpose Functions

---

```
function even;
input [31:0] num;
begin
    even = ~num[0];
end
endfunction

function mux_2_1;
input sel;
input [1:0]data;
begin
    if (sel)
        mux_2_1 = data[0];
    else
        mux_2_1 = data[1];
    end
end
endfunction

function [N-1:0] log2N;
input [31:0] num;

integer I;
reg[31:0] M;

begin
    M = 1;
    for (I=0; I<=31; I=I+1)
        begin : iterate
            if (M >= num)
                begin
                    log2N = I;
                    disable iterate;
                end
            else
                M = M << 1;
            end
        end
    end
end
endfunction
```

---

*If Statement  
Priority encoded*

---

*Original Design*

```
module mult_if(a, b_is_late_arriving, c, d, e, sel, z);
input  [3:0] sel;
input   a,
        b_is_late_arriving,
        c,
        d,
        e;
output  z;
reg     z;

    always @ (sel or a or b_is_late_arriving or c or d
              or e)
begin
    z = e;
    if (sel[0])
        z = a;
    if (sel[1])
        z = b_is_late_arriving;
    if (sel[2])
        z = c;
    if (sel[3])
        z = d;
end
endmodule
```

---

## Improved Design

```
module mult_if(a, b_is_late_arriving, c, d, e, sel, z);
input [3:0] sel;
input  a,
       b_is_late_arriving,
       c,
       d,
       e;
output z;
reg    z;

wire high_priority_cond;
assign high_priority_cond = (sel[2] | sel[3]);

always @ (sel or a or b_is_late_arriving or c or d
          or e or high_priority_cond)
begin
  if (sel[1] & ~high_priority_cond)
    z = b_is_late_arriving;
  else
  begin
    z = e;
    if (sel[0])
      z = a;
    if (sel[2])
      z = c;
    if (sel[3])
      z = d;
  end
end
endmodule
```

late arrival signal must be moved as close to the output as possible

---

*If Statement  
Parallel encoded*

---

*Original Design*

```
module single_if(A, C, CTRL_is_late_arriving, Z);
input  [6:1] A;
input  [5:1] C;
input          CTRL_is_late_arriving;
output  Z;
//
reg      Z;

    always @(C or A or CTRL_is_late_arriving)
begin
    if (C[1] == 1'b1)
        Z = A[1];
    else if (C[2] == 1'b0)
        Z = A[2];
    else if (C[3] == 1'b1)
        Z = A[3];
    else if (C[4] == 1'b1 &&
            CTRL_is_late_arriving == 1'b0)
        Z = A[4];
    else if (C[5] == 1'b0)
        Z = A[5];
    else
        Z = A[6];
end
endmodule
```

---

## Improved Design

```
module single_if(A, C, CTRL_is_late_arriving, Z);
input  [6:1]  A;
input  [5:1]  C;
input  CTRL_is_late_arriving;
output  Z;
reg    Z;
//
    reg    Z1;
    wire  Z2;
    wire  prev_cond;
//
    always @(C or A)
    begin
        if (C[1] == 1'b1)
            Z1 = A[1];
        else if (C[2] == 1'b0)
            Z1 = A[2];
        else if (C[3] == 1'b1)
            Z1 = A[3];
        else if (C[5] == 1'b0)
            Z1 = A[5];
        else
            Z1 = A[6];
    end

    assign Z2 = A[4];
    assign prev_cond = (C[1] == 1'b1) ||
                       (C[2] == 1'b0) || (C[3] == 1'b1);

    always @(C or A or prev_cond or
            CTRL_is_late_arriving or Z1 or Z2)
    begin
        if (C[4] == 1'b1 &&
            CTRL_is_late_arriving == 1'b0)
            if (prev_cond)
                Z = Z1;
            else
                Z = Z2;
        else
            Z = Z1;
    end
endmodule
```

---

*If Statement*  
*Cascaded Select Logic*

---

*Original Design*

```
module ctrl_cascade(sel_is_late_arriving,
                    A,
                    B,
                    C,
                    D,
                    Z);
input  sel_is_late_arriving;
input  A, B, C, D;
output Z;
reg    Z;

    reg i_sel;

    always @(sel_is_late_arriving or A or B or C or D or
            i_sel)
    begin
        if (sel_is_late_arriving)
            i_sel = C;
        else
            i_sel = D;
        if (i_sel)
            Z = A;
        else
            Z = B;
    end
endmodule
```



---

## Improved Design

```
module ctrl_cascade(sel_is_late_arriving,
                   A,
                   B,
                   C,
                   D,
                   Z);
input  sel_is_late_arriving;
input  A, B, C, D;
output Z;
reg    Z;

    reg C_Z, D_Z;

    always @(sel_is_late_arriving or A or B or C or D
            or C_Z or D_Z)
    begin
        if (C)
            C_Z = A;
        else
            C_Z = B;

        if (D)
            D_Z = A;
        else
            D_Z = B;

        if (sel_is_late_arriving)
            Z = C_Z;
        else
            Z = D_Z;
    end
endmodule
```

---

*Logic Replication*  
*Pre-computing Values*

---

*Original Design*

```
module reorder(addr, sel_is_late_arriving, P1, P2, Z);
  parameter      N = 8;
  input  [N-1:0] addr;
  input          sel_is_late_arriving;
  input  [N-1:0] P1, P2;
  output [N-1:0] Z;

  reg[N-1:0] temp;

  always @(P1 or P2 or sel_is_late_arriving)
  begin
    if (sel_is_late_arriving)
      temp = P1;
    else
      temp = P2;
    end

  comp U1(addr, temp, Z);

endmodule
```

---

## *Improved Design*

```
module reorder(addr, sel_is_late_arriving, P1, P2, Z);
parameter      N = 8;
input  [N-1:0] addr;
input                sel_is_late_arriving;
input  [N-1:0] P1, P2;
output [N-1:0] Z;

    wire[N-1:0] Z1, Z2;

    comp U1(addr, P1, Z1);
    comp U2(addr, P2, Z2);

    assign Z = sel_is_late_arriving ? Z1 : Z2;
endmodule
```

---

## Case Statement Embedded If

---

### Original Design

```
module case_with_if(sel,
                    X,
                    A,
                    B,
                    C_is_late_arriving,
                    D_is_late_arriving,
                    Z);
input  [2:0] sel;
input    X;
input    A,
         B,
         C_is_late_arriving,
         D_is_late_arriving;
output   Z;
reg      Z;

    always @(sel or X or A or B or C_is_late_arriving or
            D_is_late_arriving)
begin
    case (sel)
        3'b000:    Z = A;
        3'b001:    Z = B;
        3'b010:
            if (X)
                Z = C_is_late_arriving;
            else
                Z = D_is_late_arriving;
        3'b100:    Z = A ^ B;
        3'b101:    Z = A & B;
        3'b111:    Z = ~A;
        default:   Z = ~B;
    endcase
end
endmodule
```

---

## Improved Design

```
module case_with_if(sel,
                    X,
                    A,
                    B,
                    C_is_late_arriving,
                    D_is_late_arriving,
                    Z);
input [2:0] sel;
input      X;
input      A,
          B,
          C_is_late_arriving,
          D_is_late_arriving;
output     Z;
reg        Z;

    reg Z1;

    always @(sel or A or B)
    begin
        case (sel)
            3'b000: Z1 = A;
            3'b001: Z1 = B;
            3'b100: Z1 = A ^ B;
            3'b101: Z1 = A & B;
            3'b111: Z1 = ~A;
            default: Z1 = ~B;
        endcase
    end

    always @(Z1 or sel or X or C_is_late_arriving or
            D_is_late_arriving)
    begin
        if (sel == 3'b010)
            if (X)
                Z = C_is_late_arriving;
            else
                Z = D_is_late_arriving;
        else
            Z = Z1;
        end
    end
endmodule
```

---

## Case Statement Late-arriving Selector

---

### Original Design

```
module split_case(sel0, sel1_is_late_arriving, sel2,
                  X, A, B, C, D, Z);
input sel0;
input sel1_is_late_arriving;
input sel2;
input X;
input A,
      B,
      C,
      D;
output Z;
reg Z;

    wire[2:0]sel = {sel2, sel1_is_late_arriving, sel0};

    always @(sel or X or A or B or C or D)
    begin
        case (sel)
            3'b000: Z = A;
            3'b001: Z = B;
            3'b010:
                if (X)
                    Z = C;
                else
                    Z = D;
            3'b100: Z = A ^ B;
            3'b101: Z = A | B;
            3'b111: Z = ~A;
            default: Z = ~B;
        endcase
    end
endmodule
```

---

## Improved Design

```
module split_case(sel0, sell_is_late_arriving, sel2,
                  X, A, B, C, D, Z);
    input sel0;
    input sell_is_late_arriving;
    input sel2;
    input X;
    input A,
           B,
           C,
           D;
    output Z;
    reg Z;

    wire [1:0] sel = {sel2, sel0};
    reg Z1, Z2;

    always @(sel or sell_is_late_arriving or X or A or B
            or C or D)
    begin
        case (sel) // sell_is_late_arriving == 1'b0
            3'b00: Z1 = A;
            3'b01: Z1 = B;
            3'b10: Z1 = A ^ B;
            3'b11: Z1 = A | B;
            default: Z1 = ~B;
        endcase

        case (sel) // sell_is_late_arriving == 1'b1
            3'b00:
                if (X)
                    Z2 = C;
                else
                    Z2 = D;
            3'b11: Z2 = ~A;
            default: Z2 = ~B;
        endcase

        if (sell_is_late_arriving)
            Z = Z2;
        else
            Z = Z1;
    end
endmodule
```

---

## Operand Reordering

---

### Original Design

```
module reorder(A_is_late_arriving, B, C, D, Z);
parameter N = 8;
input [N-1:0] A_is_late_arriving, B;
input [N-1:0] C, D;
output [N-1:0] Z;
reg [N-1:0] Z;

    always @(A_is_late_arriving or B or C or D)
    begin
        if (A_is_late_arriving + B < 24)
            Z = C;
        else
            Z = D;
        end
    endmodule
```



---

## *Improved Design*

```
module reorder(A_is_late_arriving, B, C, D, Z);
parameter N = 8;
input [N-1:0] A_is_late_arriving, B;
input [N-1:0] C, D;
output [N-1:0] Z;
reg [N-1:0] Z;

always @(A_is_late_arriving or B or C or D)
begin
    if (A_is_late_arriving < 24 - B)
        Z = C;
    else
        Z = D;
    end
endmodule
```

---

## *Carry-in Speedup*

---

### *Original Design*

```
module carry(A, B, Cin_is_late_arriving, Z);
parameter      N = 8;
input  [N-1:0] A, B;
input          Cin_is_late_arriving;
output [N-1:0] Z;
reg      [N-1:0] Z;

    always @(A or B or Cin_is_late_arriving)
begin
    Z = A + B + Cin_is_late_arriving;
end
endmodule
```

---

## Improved Design

```
module carry(A, B, Cin_is_late_arriving, Z);
parameter      N = 8;
input  [N-1:0] A, B;
input      Cin_is_late_arriving;
output [N-1:0] Z;
reg  [N-1:0] Z;

    always @(A or B or Cin_is_late_arriving)
begin
    if (Cin_is_late_arriving)
        Z = A + B + 1;
    else
        Z = A + B;
end
endmodule
```

common subexpression sharing

---

## *Eliminating Common Subexpressions Reducing Area*

---

### *Original Design*

```
module expressions(A, B, Q, R, S, C1, C2, C3, Z);
parameter      N = 8;
input  [N-1:0] A, B;
input  [N-1:0] Q, R, S;
input  [N-1:0] C1, C2, C3;
output [N-1:0] Z;
reg    [N-1:0] Z;

    always @(A or B or Q or R or S or C1 or C2 or C3)
begin
    if (C1 > A + B + Q)
        Z = R - S;
    if (C2 > A + B + R)
        Z = S - Q;
    if (C3 > A + B + S)
        Z = Q - R;
end
endmodule
```

---

## *Improved Design*

```
module expressions(A, B, Q, R, S, C1, C2, C3, Z);
parameter      N = 8;
input  [N-1:0] A, B;
input  [N-1:0] Q, R, S;
input  [N-1:0] C1, C2, C3;
output [N-1:0] Z;
reg    [N-1:0] Z;

    reg [N-1:0] temp;
    always @(A or B)
    begin
        temp = A + B;
    end

    always @(Q or R or S or C1 or C2 or C3 or temp)
    begin
        if (C1 > temp + Q)
            Z = R - S;
        if (C2 > temp + R)
            Z = S - Q;
        if (C3 > temp + S)
            Z = Q - R;
    end
endmodule
```

---

*Linear Structures*  
*Reduce XOR function*

---

*Original Design*

```
module xor_chain(A, Z);
parameter      N = 7;
input  [N-1:0] A;
output      Z;
reg        Z;

    reg      result;
    integer  I;

    always @(A or result)
    begin
        result = A[N-1];
        for (I=N-2; I>=0; I=I-1)
            begin
                result = result ^ A[I];
            end
        Z = result;
    end
endmodule
```

---

## Improved Design

```
module xor_tree(A, Z);
parameter      N = 7;
input  [N-1:0] A;
output      Z;
reg        Z;

`define logN log2N(N)

integer      I, J, K, NUM;
reg [N-1:0] temp, result;

always @(A)
begin
temp[N-1:0] = A[N-1:0];
NUM = N;
for (K=`logN-1; K>=0; K=K-1)
begin
J = (NUM+1)/2;
J = J-1;

if (even(NUM))
for (I=NUM-1; I>=0; I=I-2)
begin
result[J] = temp[I] ^ temp[I-1];
J = J-1;
end
else
begin
for (I=NUM-1; I>=1; I=I-2)
begin
result[J] = temp[I] ^ temp[I-1];
J = J-1;
end
result[0] = temp[0];
end
temp[N-1:0] = result[N-1:0];
NUM = (NUM+1)/2;
end
Z = result[0];
end
endmodule
```

---

## *Linear Structures*

### *MUXes*

---

### *Original Design*

```
module mux_chain(data, sel, Z);
parameter      N = 9;
input  [N-1:0] data;
input  [N-2:0] sel;
output      Z;
reg        Z;

    integer    I;

    always @(sel or data)
    begin
        Z = data[N-1];
        for (I=N-2; I>=0; I=I-1)
        begin
            if (sel[I])
                Z = data[I];
        end
    end
endmodule
```



---

## Improved Design

```
module mux_tree(data, sel, Z);
parameter      N = 9;
input  [N-1:0] data;
input  [N-2:0] sel;
output      Z;
reg        Z;

`define logN log2N(N)

    integer      I, J, K, S;
    integer      DEPTH, SEL_LEN, DATA_LEN;

    reg [N-1:0] i_data, result, i_sel, temp_sel;

    always @(sel or data)
    begin
        i_data[N-1:0] = data[N-1:0];
        i_sel[N-2:0] = sel[N-2:0];
        i_sel[N-1] = 1'b0;

        DATA_LEN = N;

        for (DEPTH=`logN-1; DEPTH>=0; DEPTH=DEPTH-1)
        begin
            SEL_LEN = (DATA_LEN+1)/2;
            S = SEL_LEN-1;
            J = (DATA_LEN+1)/2;
            J = J-1;

            if (even(DATA_LEN))
                for (I=DATA_LEN-1; I>=1; I=I-2)
                begin
                    result[J] = mux_2_1(i_sel[I-1],
                                         {i_data[I], i_data[I-1]});
                    temp_sel[S] = {(i_sel[I-1], i_sel[I])};
                    J = J-1; S = S-1;
                end
            else
                begin
                    for (I=DATA_LEN-1; I>=2; I=I-2)
                    begin
                        result[J] = mux_2_1(i_sel[I-1],
                                             {i_data[I], i_data[I-1]});
                        temp_sel[S] = {(i_sel[I-1], i_sel[I])};
                        J = J-1; S = S-1;
                    end
                    result[0] = i_data[0];
                    temp_sel[0] = i_sel[0];
                end
            i_data[N-1:0] = result[N-1:0];
            i_sel[N-1:0] = temp_sel[N-1:0];
            DATA_LEN = (DATA_LEN+1)/2;
        end
        Z = result[0];
    end
endmodule
```