 
 
 

Systematic Design of Analog CMOS Circuits Using g_m/I_D -Based Lookup Tables

Claudio TALARICO

Systematic Design of Analog CMOS Circuits Using g_m/I_D -based Lookup Tables



Research Projects: TIA


 


Table 4 Performance comparison of state-of-the-art CMOS TIAs

Spec.	[3]	[4]	[9]	[14]	[2]	This work
Gain (dBΩ)	66	66.02	94.96	69.8	72	78.34
BW (GHz)	2.1	22	0.0018	1	2.4	2.21
Cin (pF)	0.5	0.5	2	0.5	0.5	0.5
Input ref. noise (pA/√Hz)	10	22	0.065	4.5	18.12	11.91
P_{DISS} (mW)	7.2	75	0.436	4.62	20.57	13.5
FOM (Ω *GHz/mW)	581.95	586.7	231.19	668.9	464.4	1352
Process (μ m)	0.18	0.09	0.18	0.18	0.18	0.18
Supply voltage (V)	1.8	1.2	1.8	3.3	1.8	1.8

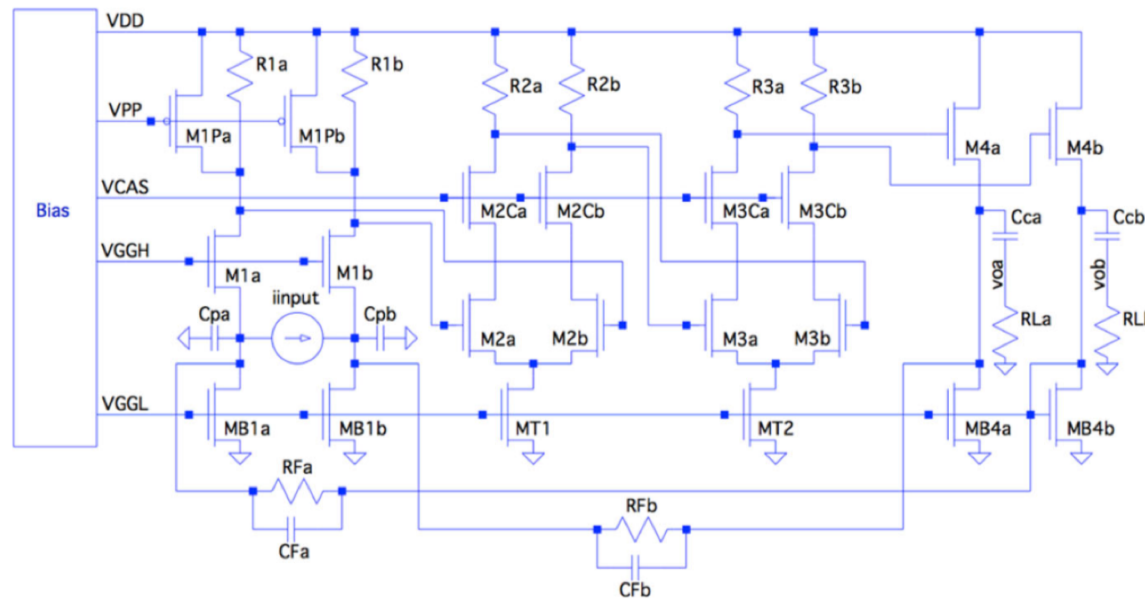

Research Projects: Mixer


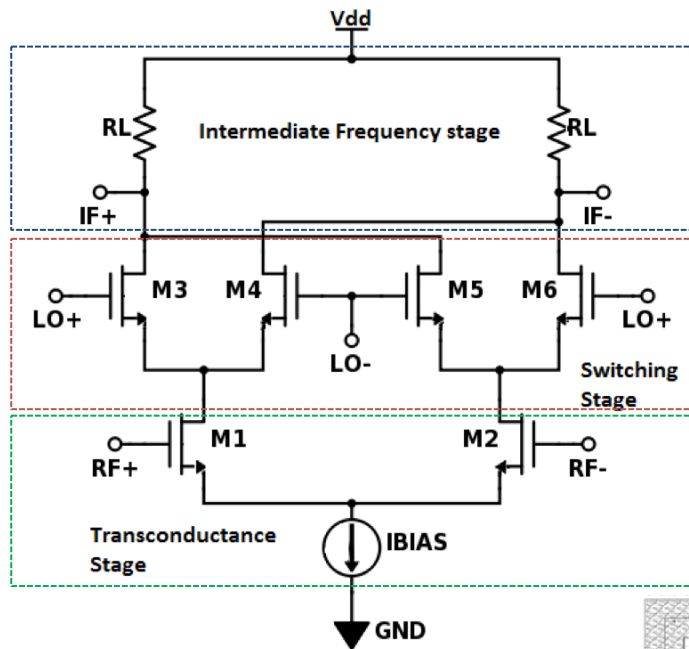


TABLE I. REPORTED PERFORMANCE OF CMOS GILBERT MIXERS

Ref.	CMOS Tech.	Gain [dB]	IIP3 [dBm]	NF Av. [dB]	P _{DC} [mW]	FOM
[4]	0.13 um	8	-3	11.2	5.57	0.12
[9]	0.18 um	10	4	10	10	0.16
[10]	0.13 um	8.95	-2.2	11.4	3.7	0.16
[11]	0.13 um	21	-1.8	15.7	18.3	0.06
[12]	0.18 um	13.5	-3.25	21.22	7.2	0.06
This Work	0.13 um	11.24	-3.1	11.6	2.1	0.32

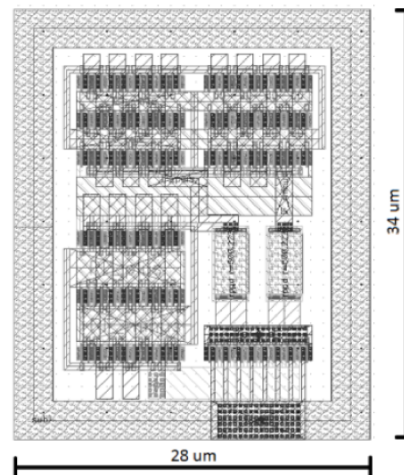The performance metrics indicated refers to the core of the mixer



$$FOM = \frac{CG_{[dB]} \cdot IIP3_{[mW]}}{NF_{[dB]} P_{DC[mW]}}$$

Research Projects: Distributed LNA for UWB

 


Fig. 1 Architecture of a UWB system

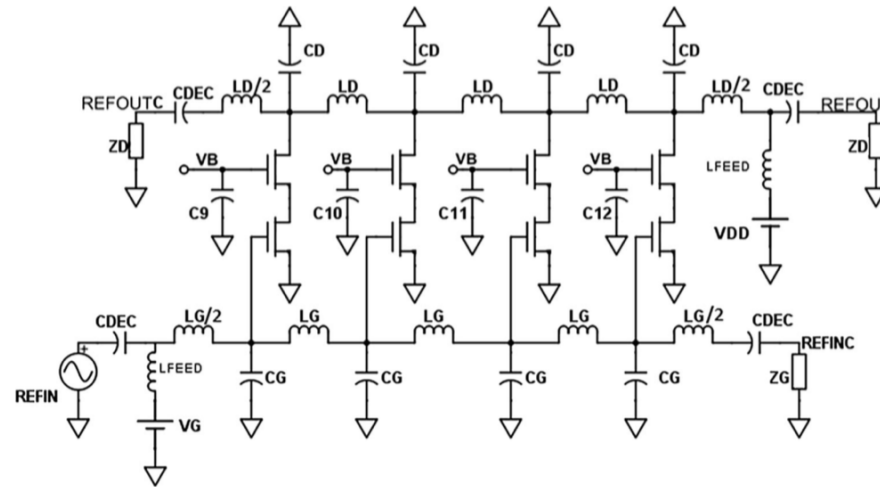



Fig. 2 Architecture of a conventional four stages distributed amplifier

$$FOM_{[GHz/mW \cdot mm^2]} = \frac{\alpha_{[dB]} \cdot BW_{[GHz]}}{NF_{[dB]} P_{DC[mW]} Area_{[mm^2]}}$$

$$\alpha_{[dB]} = 10 \cdot \log_{10} \{ |S_{21}|^2 \cdot [(1 - |S_{11}|^2) \cdot (1 - |S_{22}|^2)] \}$$

TABLE II. REPORTED PERFORMANCE OF CMOS DAS FOR UWB SYSTEMS

Reference	Technology	BW [GHz]	Gain [dB]	S11/S22 [dB]	NF average [dB]	Power [mW]	Area (mm ²)	FOM [GHz/mW·mm ²]
[2]	0.13 um CMOS	3-9.4	12	<-7 / <-8	3.3	30	0.82	0.28
[8] (HG mode)	0.13 um CMOS	3-10	20.4	<-10 / <-10	3.29	37.8	0.88	1.26
[8] (LG mode)	0.13 um CMOS	3-10	11	<-10 / <-10	4.25	6.86	0.88	1.71
[9]	0.13 um CMOS	3-10	15	<-12 / <-15	3.34	26	0.43	2.89
[10]	0.13 um CMOS	2.2-9	9.8	<-10 / <-9.2	4.25	30	0.68	0.28
[11]	0.18 um CMOS	3-10	18	<-10 / <-9	6	54	2.2	0.15
This Work	0.13 um CMOS	3-10	11	<-16 / <-18	2.65	26	0.75	1.61

 


Motivation

- The square-law MOS model is plagued by several limitations


$$I_D = \frac{1}{2} \mu C_{ox} \frac{W}{L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$

 - Modern MOSFETs are impaired by mobility degradation effects
- In moderate inversion with gate overdrive voltages below 150mV, the square law model is grossly inaccurate
- In weak inversion, the current flows by diffusion (like in a BJT) and the square-law model must be replaced with an exponential relationship



Simulations (nMOS, 5 $\mu\text{m}/0.18 \mu\text{m}$, $V_{DS}=1.8\text{V}$)

 
- The transistor does not abruptly turn off at V_T
- The current is not perfectly quadratic with V_{OV} ($=V_{GS}-V_T$)
- The current does not scale perfectly with $1/L$
- The threshold voltage V_T of the device changes with L



The square law model fails miserably for low V_{GS}


- The square law equation is adequate only for “strongly inverted” devices (that is for moderately-large V_{OV})

Currents on a Log Scale

 

A more design friendly perspective



Transconductance Efficiency

 

In weak inversion: $g_m = \frac{1}{n} \cdot \frac{I_D}{V_{th}}$

In moderate inversion: ???

  
In strong inversion: $g_m = \frac{2I_D}{V_{OV}}$




Weak Inversion (Subthreshold) Operation

- Physics governed by a “gated diode” model
- The amount of electrons injected into a given point of the body depends on the potential present at that given point

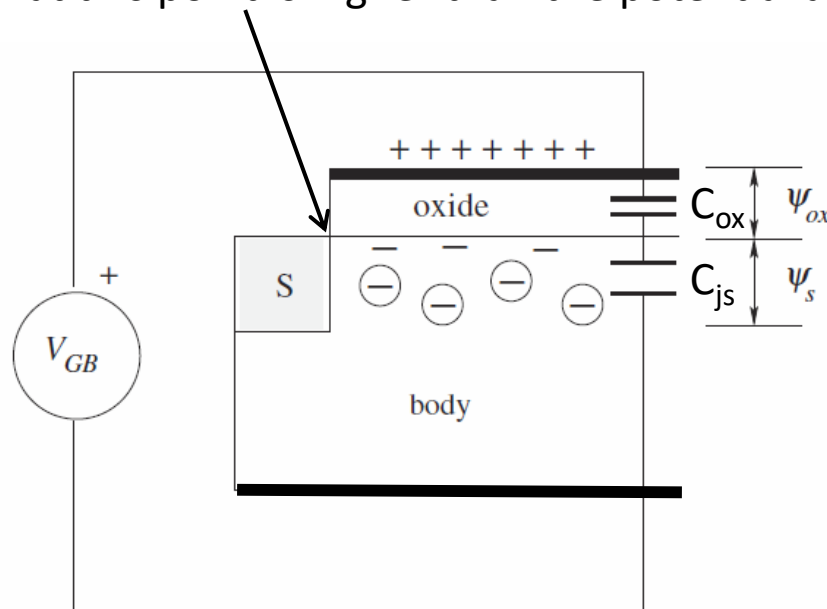Potential at this point is higher than the potential at any other body/source point




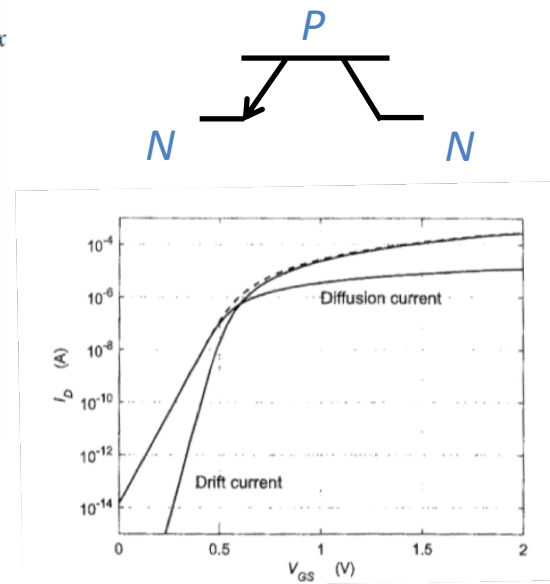D.L. Pulfrey, Understanding Modern Transistors and Diodes, Cambridge University Press, 2010.



Total drain current dashed line

Resulting Diffusion Current

 

$$I_D = qAD_n \frac{n_p(0) - n_p(L)}{L}$$

$$I_D = \frac{1}{L} qAD_n n_{p0} e^{\frac{\psi_s}{V_{th}}} (1 - e^{-\frac{V_{DS}}{V_{th}}})$$

- The current grows exponentially with ψ_s
- The current becomes independent of V_{DS} for $V_{DS} > 3V_{th}$ (78mV)

Capacitive Divider

$$\frac{d\psi_s}{dV_{GS}} = \frac{C_{ox}}{C_{js} + C_{ox}} = \frac{1}{n}$$

- n is called “subthreshold factor” or “nonideality factor”
- $n \cong 1.45$ for an NMOS device in our technology
- After including this relationship between ψ_s and V_{GS} and after a few additional manipulations, the final expression for the drain current becomes:


$$I_D = \frac{W}{L} I_{D0} e^{\frac{V_{GS}-V_t}{nV_{th}}} \left(1 - e^{-\frac{V_{DS}}{V_{th}}}\right)$$

where I_{D0} depends on technology ($I_{D0} \cong 0.43\mu\text{A}$ for an NMOS device in our technology)

In summary ...

- Modern MOSFETs are complicated !
- The behavior of a MOS in saturation can be roughly categorized according to the channel's inversion level: weak, moderate and strong inversion
- The bottom line is that there is no modeling expression that is simple enough for hand analysis and sufficiently accurate to match real world device behavior

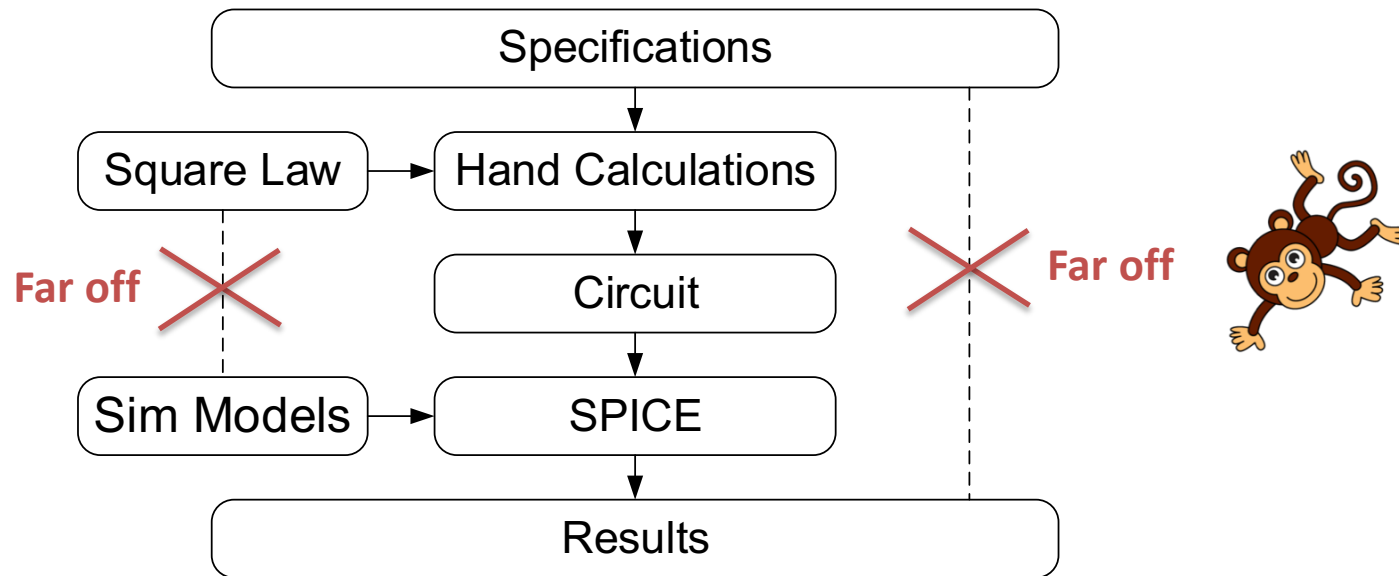Typical Analog circuits design flow based on square law hand calculations and SPICE simulation



- The complexity of the transistor model preclude the derivation of simple closed form analytical expressions
- Design process takes multiple iterations and “hand” tweaking of the transistor sizing before converging toward a working circuit

Technology centric vs. Design centric FOMs

- Most of the parameters in the square-law model are technology centric

$$I_D = \frac{1}{2} \mu C_{ox} \frac{W}{L} (V_{OV})^2 (1 + \lambda V_{DS})$$

$$V_{OV} \doteq V_{GS} - V_T$$

- It is hard to link technology parameters to the design requirements (gain, bandwidth, input and output impedances, noise)

By the way what are μC_{ox} , lambda and V_T for our technology ?

```
* 0.18um CMOS models (nominal process)
.MODEL nmos nmos (
+acm      = 3          hdif    = 0.32e-6      LEVEL   = 49
+ CAPOP = 39
+VERSION = 3.1        TNOM    = 27          TOX     = 4.1E-9
+XJ      = 1E-7       NCH    = 2.3549E17    VTH0    = 0.3618397
+K1      = 0.5916053  K2    = 3.225139E-3    K3      = 1E-3
+K3B     = 2.3938862  W0    = 1E-7          NLX     = 1.776268E-7
+DVT0W   = 0          DVT1W  = 0            DVT2W   = 0
+DVT0    = 1.3127368 DVT1   = 0.3876801    DVT2    = 0.0238708
+U0      = 256.74093  UA    = -1.585658E-9   UB      = 2.528203E-18
+UC      = 5.182125E-11 VSAT   = 1.003268E5    A0      = 1.981392
+AGS     = 0.4347252  B0    = 4.989266E-7    B1      = 5E-6
+KETA    = -9.888408E-3 A1    = 6.164533E-4    A2      = 0.9388917
+PRWG    = 0.5        PRWB   = -0.2
+WR      = 1          WINT   = 0
+XL      = 0          XW    = -1E-8          LINT    = 1.617316E-8
+DWB     = 9.111767E-9 VOFF   = -0.0854824   DWG     = -5.383413E-9
+CIT     = 0          CDSC   = 2.4E-4        NFACTOR = 2.2420572
+CDSCB   = 0          ETA0   = 2.981159E-3   CDSCD   = 0
+DSUB    = 0.0159753 PCLM   = 0.7245546    ETAB    = 9.289544E-6
+PDIBLC2 = 2.543351E-3 PDIBLCB = -0.1         PDIBLC1 = 0.1568183
+PSCBE1  = 8E10       PSCBE2 = 1.876443E-9   DROUT   = 0.7445011
+DELTA   = 0.01       MOBMOD = 1            PVAG    = 7.200284E-3
+PRT     = 0          UTE    = -1.5          KT1     = -0.11
+KT1L    = 0          KT2    = 0.022         UA1     = 4.31E-9
+UB1     = -7.61E-18  UC1    = -5.6E-11     AT      = 3.3E4
+WL      = 0          WLN    = 1            WW      = 0
+WWN     = 1          WWL    = 0            LL      = 0
+LLN     = 1          LW     = 0            LWN     = 1
+LWL     = 0          CAPMOD = 2            XPART   = 1
+CGD0    = 4.91E-10  CGSO   = 4.91E-10     CGB0    = 1E-12
+CJ      = 9.652028E-4 PB      = 0.8          MJ      = 0.3836899
+CJ5W    = 2.326465E-10 PBSW   = 0.8          MJSW   = 0.1253131
+CF      = 0          PVTH0  = -7.714081E-4  PRDSW   = -2.5827257
+PK2     = 9.619963E-4 WKETA  = -1.060423E-4   LKETA   = -5.373522E-3
+PU0     = 4.5760891  PUA    = 1.469028E-14 PUB     = 1.783193E-23
+PVSAT   = 1.19774E3 PETA0  = 9.968409E-5  PKETA   = -2.51194E-3
+nlev    = 3          kf     = 0.5e-25)
```

This is a 110-parameter
BSIM3v3 SPICE model:
 $\mu C_{ox} \triangleq KP$ and lambda
are nowhere to be found

Transistor Figures of Merit for Design

- Transconductance efficiency
 - Want large g_m , for as little current as possible

$$\frac{g_m}{I_D}$$

Square Law

$$= \frac{2}{V_{OV}}$$

- Transit frequency
 - Want large g_m , without large C_{gg}

$$\frac{g_m}{C_{gg}}$$

$$\approx \frac{3}{2} \frac{\mu V_{OV}}{L^2}$$


- Intrinsic gain
 - Want large g_m , but no g_{ds}

$$\frac{g_m}{g_{ds}}$$

$$\approx \frac{2}{\lambda V_{OV}}$$

Design Tradeoffs

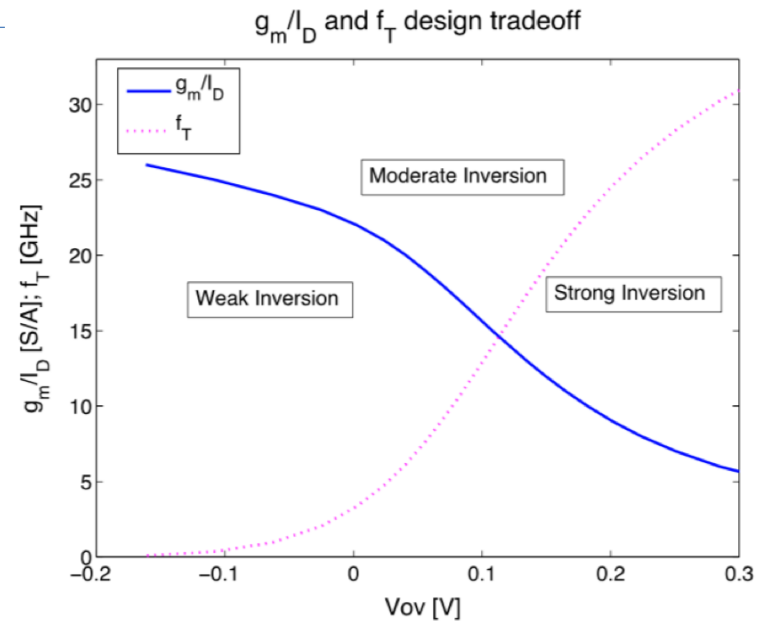Plot of g_m/I_D and f_T at different levels of inversion V_{ov} for an nMOS transistor with channel length $L = 0.18 \mu\text{m}$



Transconductance efficiency

Low g_m/I_D

High g_m/I_D

Strong inversion

Weak inversion

Poor power efficiency

Good power efficiency

Low output voltage range

High output voltage range

High transient frequency


Low transient frequency

Small transistor

Large transistor

Table 1 Transistor's properties at different levels of transconductance efficiency

Product of g_m/I_D and f_T

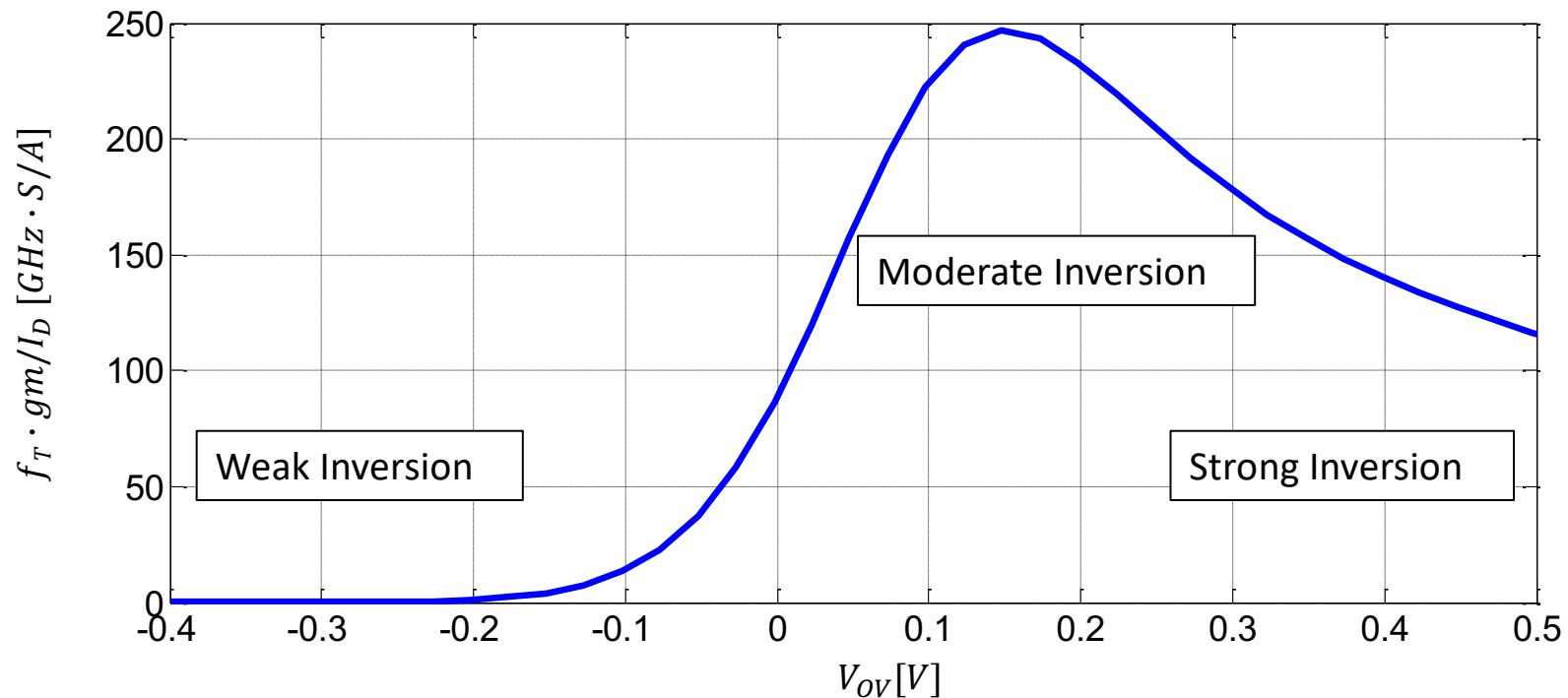

- Interestingly, the product of g_m/I_D and f_T peaks in moderate inversion
 - For our $0.18 \mu\text{m}$ technology it peaks at around $g_m/I_D \approx 13 \text{ S/A}$
- Operating the transistor in moderate inversion makes sense when we value speed and power efficiency equally
 - Not always the case, it depends on the application

Product of g_m/I_D and f_T for varying L


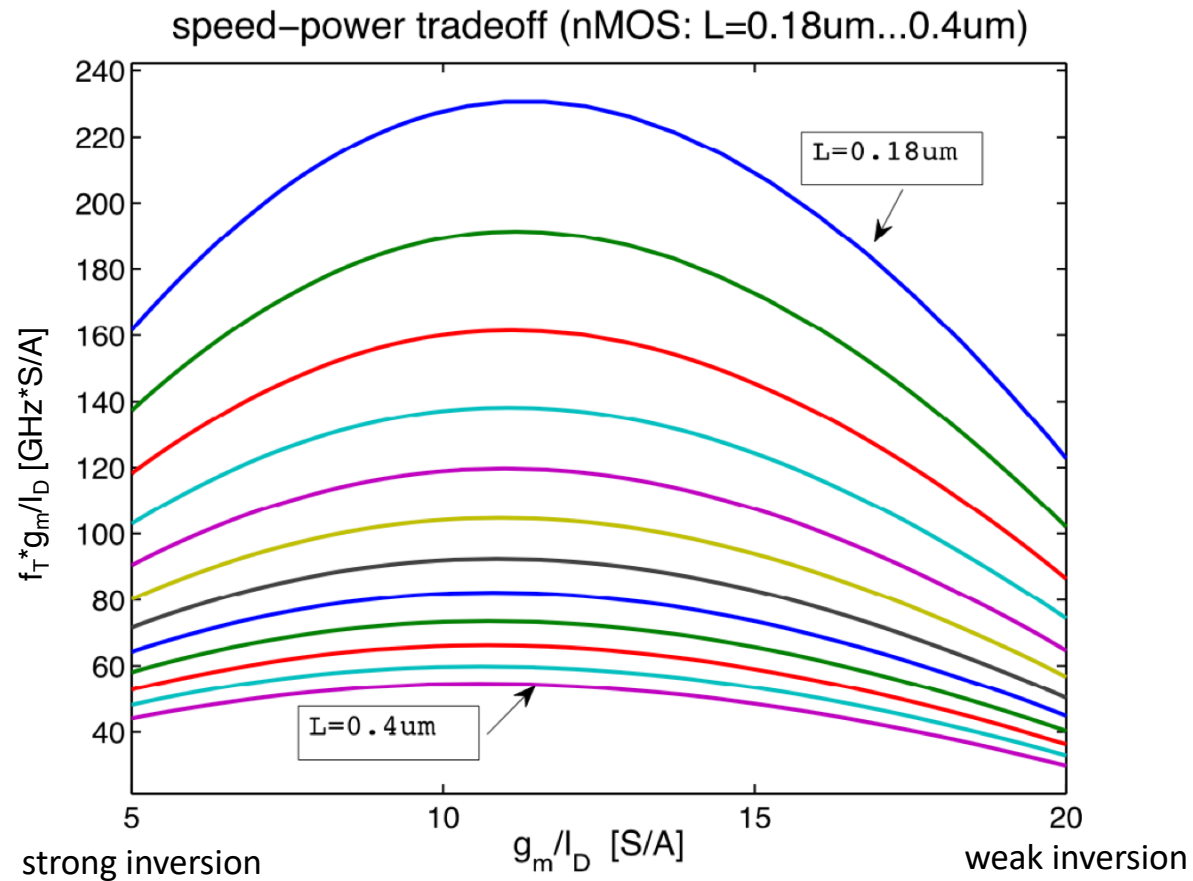


Fig. 1 Relationship between $f_T g_m / I_D$ and g_m / I_D for nMOS transistors with channel length L varying from 0.18 to 0.4 μm

Systematic Design of Analog CMOS Circuits Using g_m/I_D -based Methodology

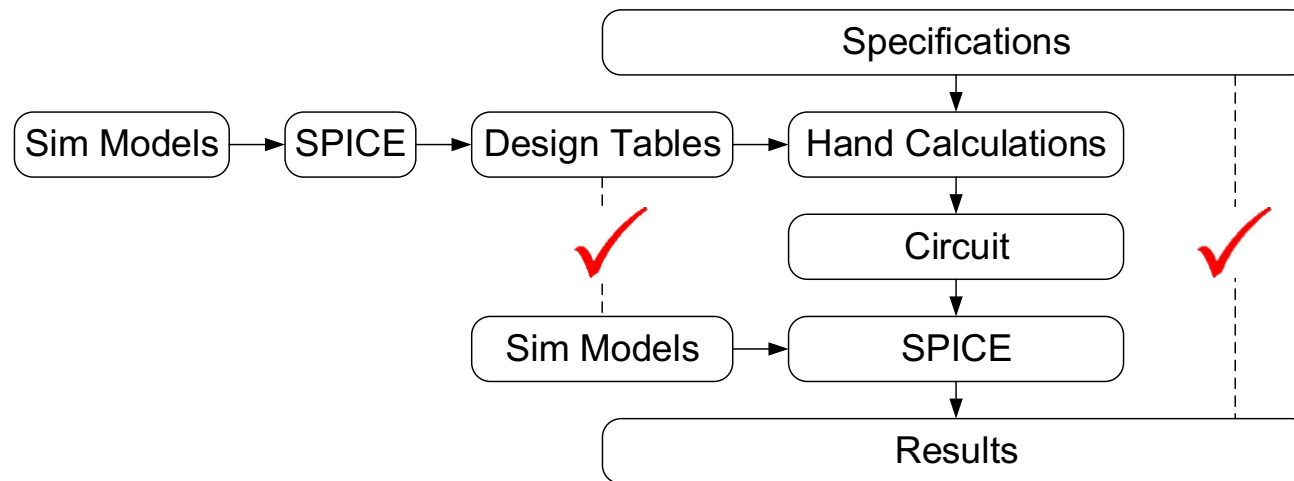- Goal
 - Maintain a systematic design methodology in the absence of a set of useful compact MOS equations
- Strategy
 - Design using look-up tables or charts



- Use pre-computed SPICE data in hand calculations


Starting Point:

g_m/I_D -Centric Technology Characterization

- Tabulate the figures of merit considering g_m/I_D as an index, over a reasonable range of g_m/I_D and channel lengths
 - Transit frequency (f_T)
 - Intrinsic gain (g_m/g_{ds})
- Also tabulate relative estimates of capacitances
 C_{gd}/C_{gg} and C_{dd}/C_{gg}
- Note, that all the FOMs are (to first order) independent of device width
- So, in order to compute device widths, we need one more table that links g_m/I_D and current density I_D/W

g_m/I_D -Centric Technology Characterization

- Obtain tables of device characteristics through a DC sweep of the transistor
 - Measure transistor .op parameters at each point of the sweep
 - g_m , I_D , C_{gg} , g_{ds} , etc.
 - Repeat the sweep for different lengths
 - 180nm, 200nm, 3 μ m
- Simple version: sweep V_{GS} with V_{DS} held fixed at $V_{DS} = V_{DD}/2$
 - The figures of merit and I_D/W don't vary too much with V_{DS}
- Advanced version: sweep also V_{DS} and V_{BS}
 - Captures the back-gate effect due to V_{BS}
 - Threshold Voltage shift
 - Often using “low/medium/high” V_{DS} charts is good enough

 

Simulation Data in MATLAB

```
% data stored in /home/ee406/matlab
>> load 180nch.mat
>> nch
nch =
    ID: [4-D double]
    VT: [4-D double]
    GM: [4-D double]
    GMB: [4-D double]
    GDS: [4-D double]
    CGG: [4-D double]
    CGS: [4-D double]
    CGD: [4-D double]
    CGB: [4-D double]
    CDD: [4-D double]
    CSS: [4-D double]
    INFO: 'GU ee406 models, 180nm CMOS, BSIM3'
    VGS: [73x1 double]
    VDS: [73x1 double]
    VSB: [11x1 double]
    L: [32x1 double]
    W: 5.0000e-06
    NFING: 1
>> size(nch.ID)
ans =
    32    73    73    11
```

Four-dimensional arrays


$$I_D(L, V_{GS}, V_{DS}, V_S)$$

$$V_t(L, V_{GS}, V_{DS}, V_S)$$


$$g_m(L, V_{GS}, V_{DS}, V_S)$$

...


Transit Frequency ($f_T = g_m / C_{gg}$)

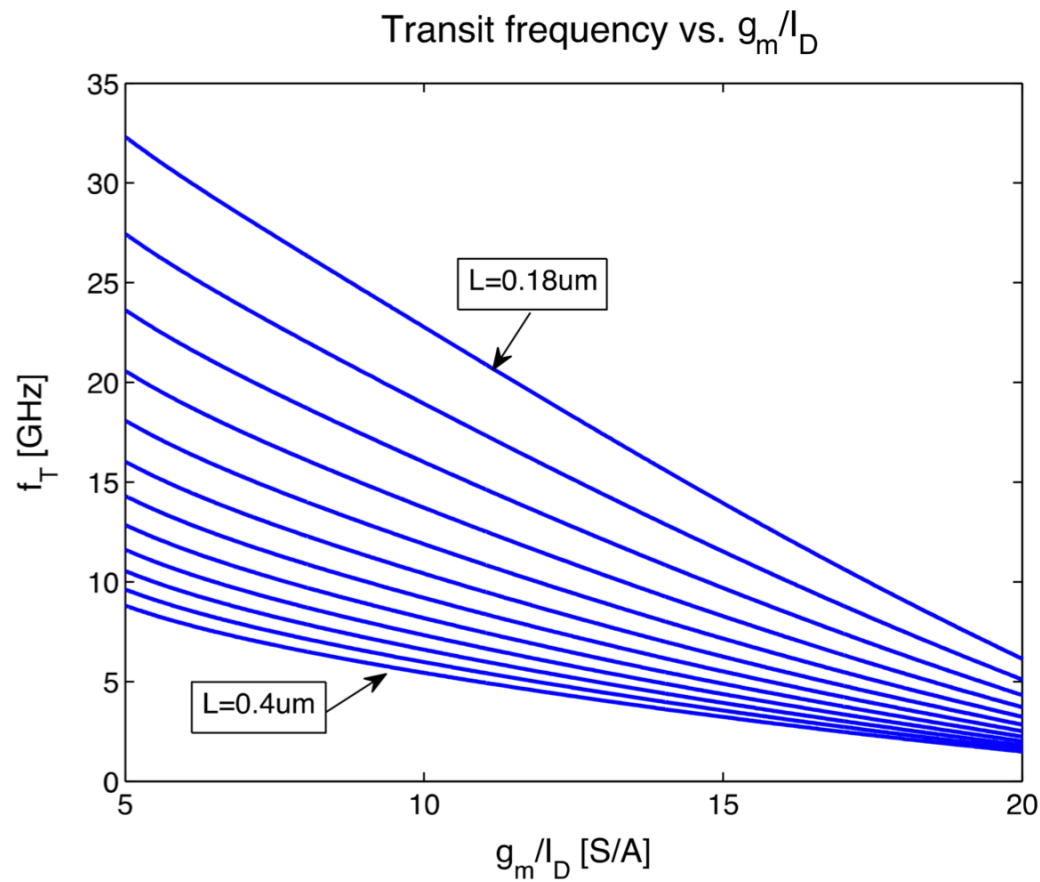


Intrinsic Gain (g_m/g_{ds})

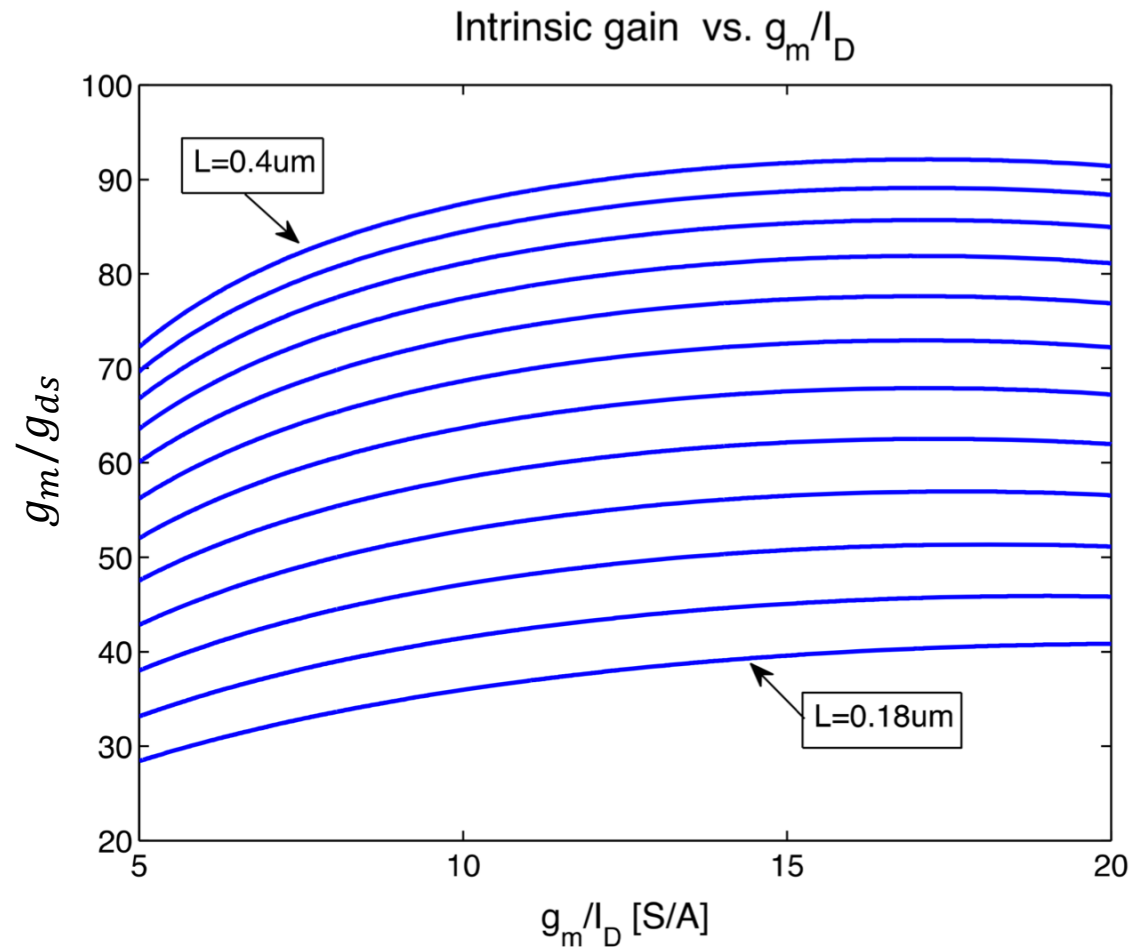

Current Density ($J_D = I_D/W$)

 


V_{DS} Dependence

 

- V_{DS} dependence is relatively weak
- Typically it is OK to work with data generated for $V_{DD}/2$

Capacitances

 

- Again, it's usually OK to work with estimates taken at $V_{DS}=V_{DD}/2$


$$C_{gg} = C_{gs} + C_{gd} + C_{gb}$$

$$C_{dd} = C_{gd} + C_{db}$$



$$C_{ss} = C_{gs} + C_{sb}$$

Capacitances – Length Dependence

 NMOS, $g_m/I_D = 10\text{S/A}$, $V_{DS} = 0.9\text{V}$



Design in a Nutshell

  


- Choose length L such that the circuit has 'enough' gain
- Choose the inversion level according to the proper tradeoff between speed (f_T) and transconductance efficiency (g_m/I_D) for the given circuit
- The inversion level is fully determined by the gate overdrive V_{OV}
 - But, V_{OV} is not a very interesting parameter outside the square law framework; not much can be computed from V_{OV}


Eliminating V_{OV}

- But, ... the inversion level is also fully defined by g_m/I_D so there is no need to know V_{OV}


$$\frac{g_m}{I_D} = \frac{2}{V_{OV}}$$

 

Reality Check

 

computed as
 $2/(g_m/I_D)$ values

 


The SPICE model data confirms that $2/(g_m/I_D)$ is a good estimate for the minimum reasonable V_{DS}

A Generic Design Optimization Flow

Complicated circuits have *many* degrees of freedom and objectives

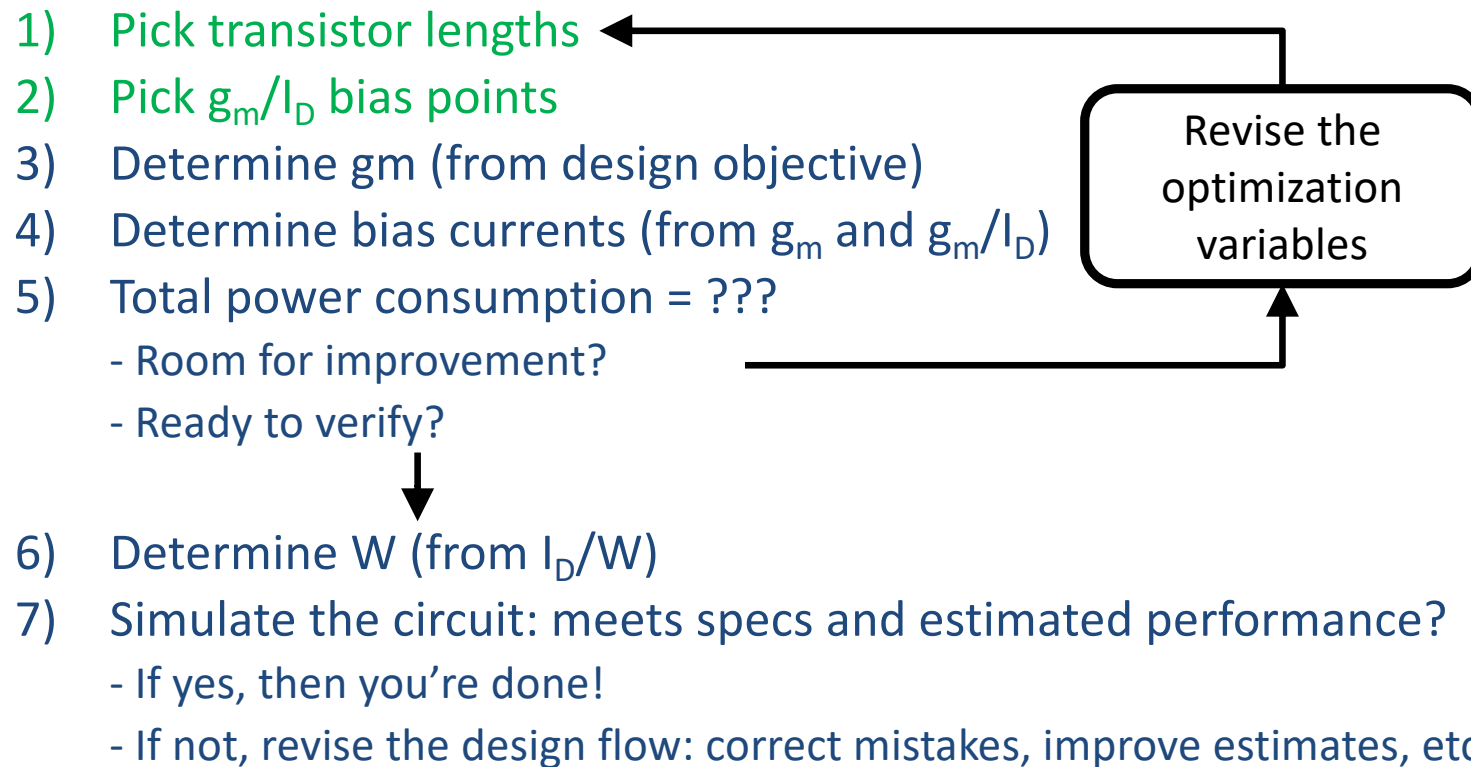- Usually we must make some **heuristic** choices up front
- Charts and lookup tables help you iterate through possible designs rapidly



TIA for Fiber Optic Receiver

 


Fig. 2 Typical optical communication (OC) system

TIA specifications:

- 0.18 μ m CMOS technology,
- closed-loop transimpedance gain of 73 dB Ω
- 0.5 pF photodiode
- 250 Ω -load,
- Total current budget up to 16mA
- input referred current noise PSD up to 160×10^{-24} A²/Hz
- Optimize for gain, speed and power consumption

$$\text{FOM} = \frac{\text{GBW}}{P_{\text{DISS}}}$$

Performance metric	Analysis	Simulation	l% Relative errorl
Gain (dB Ω)	73.06	78.34	6.74
$f_{3\text{ db}}$ (GHz)	2.4	2.21	8.6
Input ref. noise (pA/ $\sqrt{\text{Hz}}$)	11.99	11.91	0.67
Power dissipated (mW)	14.40	13.5	6.67
Phase margin (degrees)	47.48	45.19	5.07

TIA for Fiber Optic Receiver

 


Fig. 4 TIA topology (CG = common gate, CS = common source, SF = source follower)


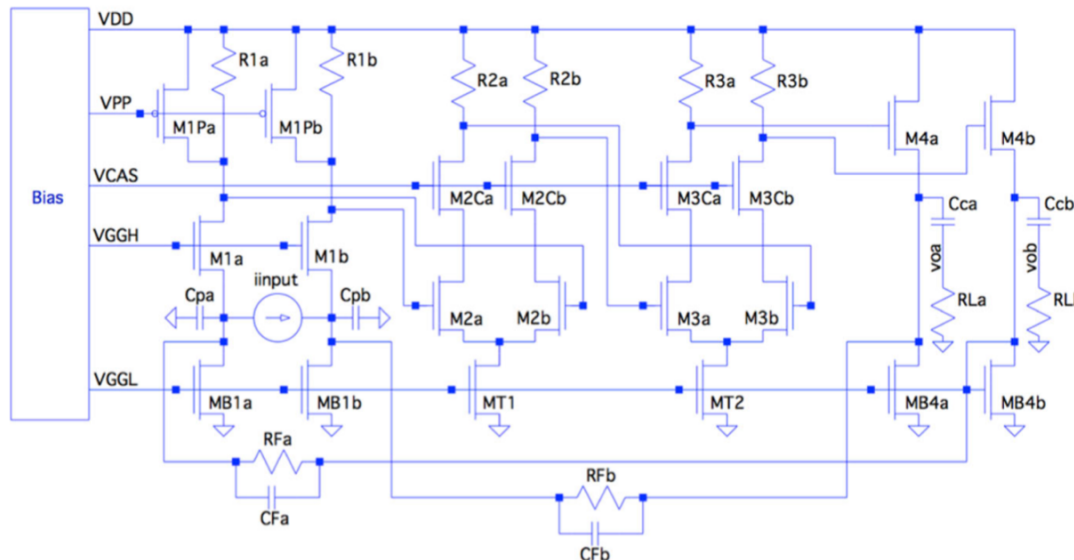


Fig. 5 TIA schematic

Fig. 6 TIA's biasing circuit

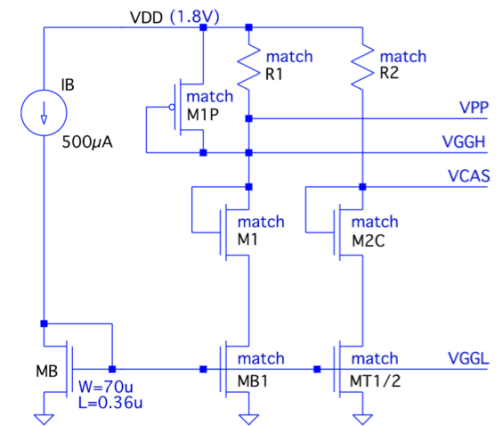

TIA for Fiber Optic Receiver

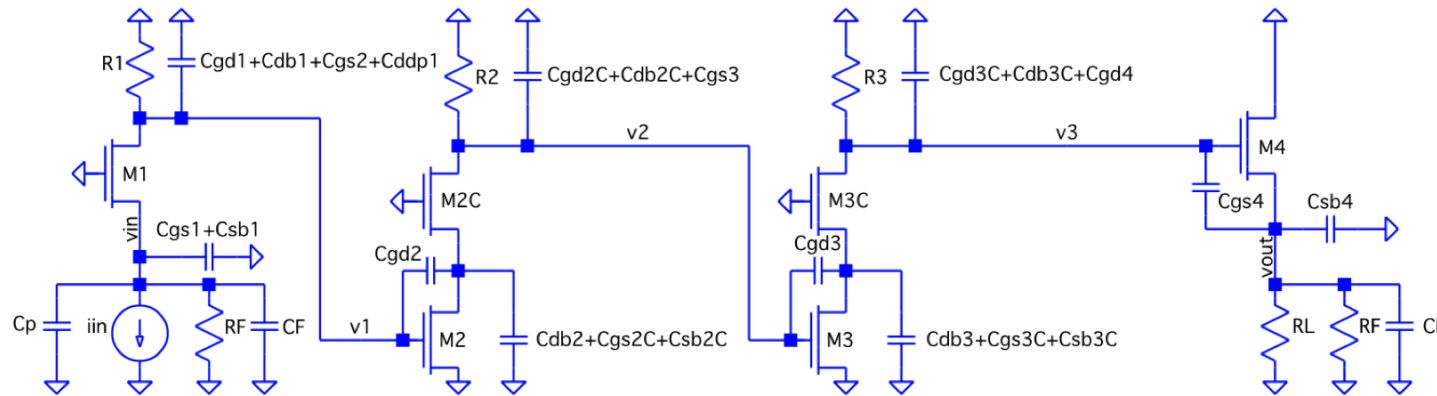


Fig. 7 TIA AC half circuit with feedback loading and relevant capacitances

Loop gain: $T_0 = a_0 f_0$

Closed Loop Trans-impedance gain: $A_0 = \frac{v_{out,diff}}{i_{input}} \approx \frac{2a_0}{1 + T_0}$ $i_{input} = i_{in}/2$ and $v_{out,diff} = v_{oa} - v_{ob}$

Bandwidth (ZVTC): $f_{-3dB} \approx \frac{1 + T_0}{2\pi \cdot \sum v_i \tau_i}$

Input referred current noise PSD: $\frac{\overline{i_{noise}^2}}{\Delta f} \approx \frac{1}{2} \cdot \left(\frac{4KT}{R_F} + 4KT\gamma_n g_{mB1} + \frac{4KTR_1}{A_{CG}^2} + 4KT\gamma_p g_{m1P} \frac{R_1^2}{A_{CG}^2} \right)$

TIA for Fiber Optic Receiver

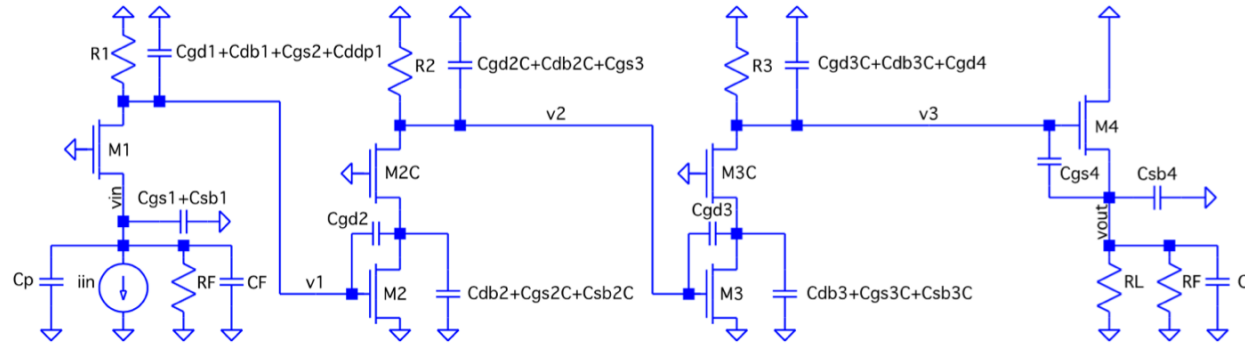


Fig. 7 TIA AC half circuit with feedback loading and relevant capacitances

TC at the CG input: $\tau_{in} \approx C_{in} \cdot \left(R_F \parallel \frac{1}{g_{m1}^*} \right)$ where $C_{in} = C_P + C_F + C_{gs1} + C_{sb1} + C_{ddp1}$ and $C_{ddp1} = C_{gdp1} + C_{dbp1}$

TC at the CG output: $\tau_2 \approx R_1 C_2$ where $C_2 = C_{gd1} + C_{db1} + C_{gs2} + C_{gd2}(1 + g_{m2}/g_{m2C}^*)$

TC at the source of M2C: $\tau_{2C} \approx \frac{1}{g_{m2C}^*} C_{2C}$ where $C_{2C} = C_{db2} + C_{gs2C} + C_{sb2C}$


TCs at the first CS output: $\tau_3 \approx R_2 C_3$ and $\tau_{3m} \approx C_{gd3} \cdot \left(R_2 + \frac{1}{g_{m3C}^*} + g_{m3} \frac{R_2}{g_{m3C}^*} \right)$

TC at the source of M3C: $\tau_{3C} \approx \frac{1}{g_{m3C}^*} C_{3C}$ where $C_{3C} = C_{db3} + C_{gs3} + C_{sb3C}$

TC at the CD input: $\tau_{4in} \approx R_2 C_{4in}$ and $\tau_{4m} \approx C_{gs4} \frac{R_3 + R_{Lp}}{g_{m4} R_{Lp} + 1}$ where $C_{4in} = C_{db2C} + C_{gd2C} + C_{gs3}$

TC at the CD output: $\tau_{4out} \approx R_{Lp} \cdot (C_F + C_{sb4})$

Design Optimization Framework

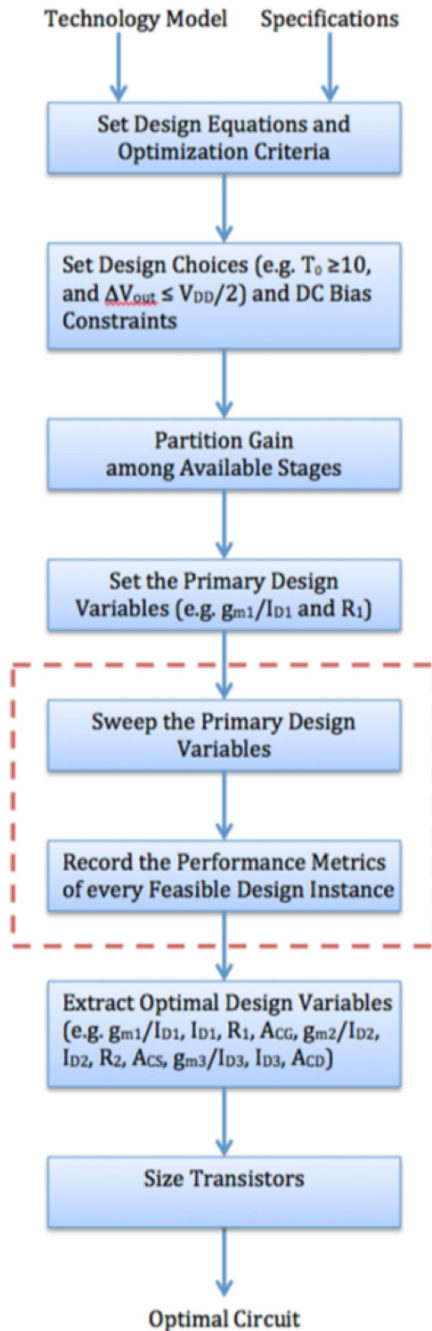

1. Set the loop gain T_0 to an appropriate value ($T_0 \geq 10$) and derive R_F based on the design objectives ($A_0 \geq 73 \text{ dB}\Omega$).
2. Set g_m/I_D for the transistor M_4 (source follower) to allow max output signal swing (that is $V_{IN4} = V_{DD}/2$) and compute the corresponding transient frequency f_T . Select an appropriate value of bias current based on C_{gg4} such that the time constants associated with the source follower are not dominant. Estimate the parasitic capacitances and compute the resulting gain A_{CD} of the source follower.

$$C_{gg4} = \frac{g_{m4}}{2\pi f_{T4}}$$

$$I_{D4} = \frac{g_{m4}}{g_{m4}/I_{D4}}$$


 


Fig. 10 Source follower design optimization: C_{gg} capacitance versus g_m/I_D and gain A_{CD}

Design Optimization Framework

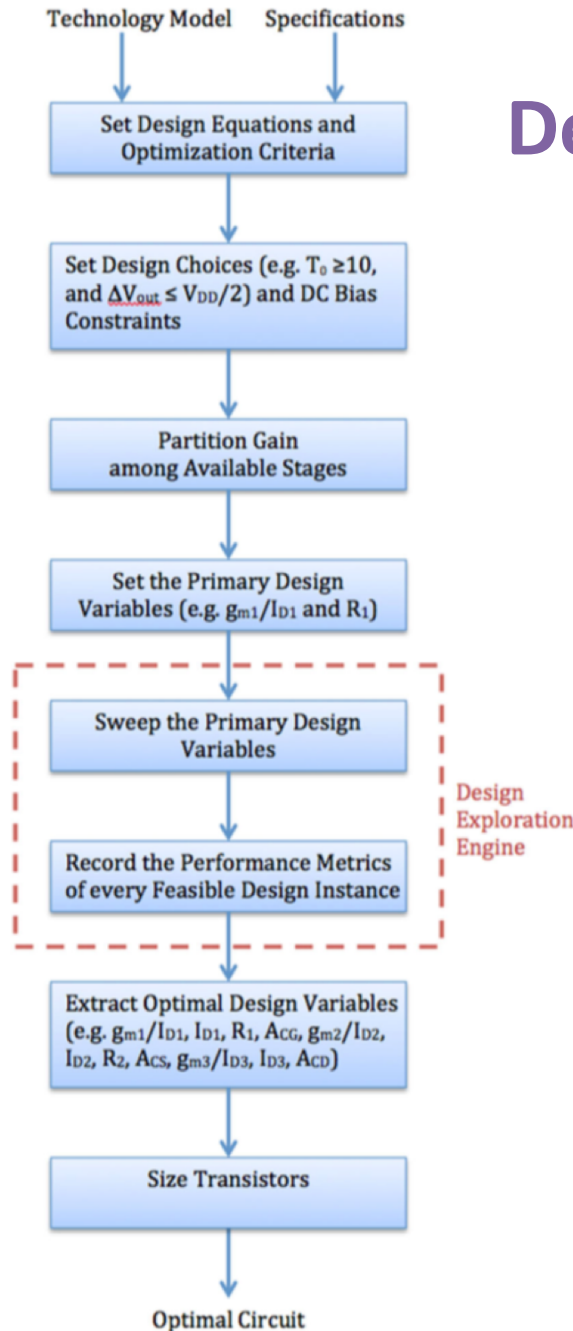

- Partition the amount of gain needed to meet specification between the common source and the common gate:

$$A_{CS}A_{CG} = \frac{a_0}{A_{CD}} \quad (16)$$

An excessive value of A_{CS} causes a strong miller effect at the intermediate node between the transistors M_2 and M_{2C} and results in a non optimal value of the dominant time constant τ_2 . Similarly, an excessive value of A_{CG} implies an excessive value of R_1 and results in a suboptimal value of the dominant time constant τ_2 . Appropriate values of A_{CS} and A_{CG} are in the following ranges:

$$1 \leq A_{CS} \leq 50 \text{ and } \frac{a_0}{A_{CD}A_{CSmax}} \leq A_{CG} \leq \frac{a_0}{A_{CD}} \quad (17)$$


- Set g_m/I_D of transistor M_1 and the value of R_1 as the primary design variables. The values of g_m/I_{D1} and R_1 set the value of A_{CG} . The value of A_{CG} set the value of A_{CS} and therefore the value of g_{m2}/I_{D2} , R_2 , g_{m3}/I_{D3} and R_3 .
- Sweep g_m/I_{D1} from weak inversion region ($g_m/I_D = 25 \text{ S/A}$) to strong inversion region ($g_m/I_D = 5 \text{ S/A}$) and R_1 from A_{CG_min} to A_{CG_max} . Register the performance metrics of every feasible design in the explored space. Design feasibility and the current bias for the CG and CS are determined by the bias constraints.
- Determine g_m/I_{D1} , I_{D1} , R_1 , A_{CG} , g_{m2}/I_{D2} , I_{D2} , R_2 , R_3 , g_{m3}/I_{D3} , I_{D3} , A_{CS} , and A_{CD} for the TIA design that achieves the best bandwidth.
- Finally, determine transistor widths from g_m/I_D , the calculated I_D , and the current density (I_D/W) look-up tables

Results


Table 4 Performance comparison of state-of-the-art CMOS TIAs

Spec.	[3]	[4]	[9]	[14]	[2]	This work
Gain (dBΩ)	66	66.02	94.96	69.8	72	78.34
BW (GHz)	2.1	22	0.0018	1	2.4	2.21
Cin (pF)	0.5	0.5	2	0.5	0.5	0.5
Input ref. noise (pA/√Hz)	10	22	0.065	4.5	18.12	11.91
P_{DISS} (mW)	7.2	75	0.436	4.62	20.57	13.5
FOM (Ω*GHz/mW)	581.95	586.7	231.19	668.9	464.4	1352
Process (μm)	0.18	0.09	0.18	0.18	0.18	0.18
Supply voltage (V)	1.8	1.2	1.8	3.3	1.8	1.8


TIA Frequency Response

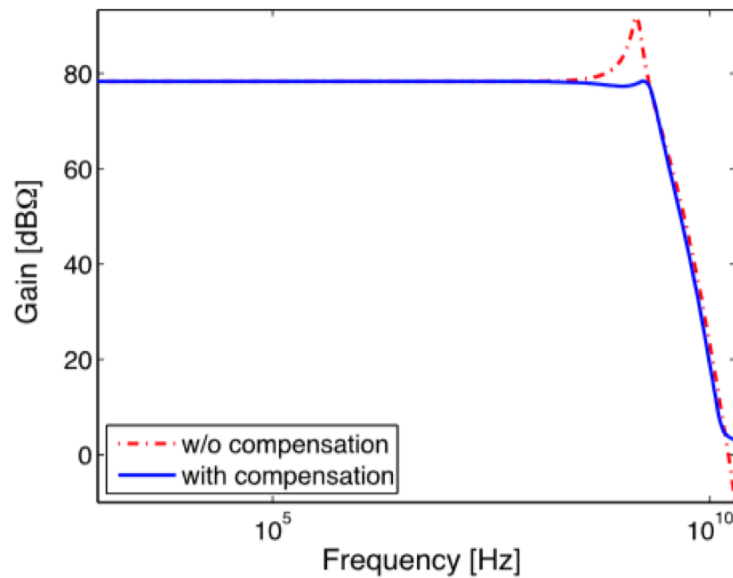

Root Locus w/o compensation

 

Gilbert Cell Mixer

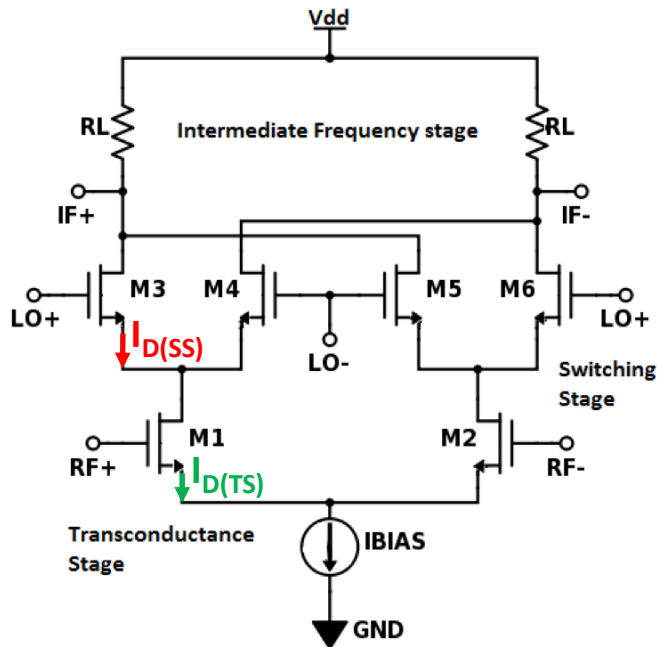

Specifications:

- A conversion gain greater than 10 dB
- DC-power consumption lower than 3 mW
- A resistive load of 500 Ω
- A target third-order intercept (IIP3) > -5 dBm

Topology Main Benefits:



- Simple
- Good port-to-port isolation
- Low even-order harmonic distortion

Topology Drawback:



The cell is composed of a stack of three MOS transistors, so it requires large voltage headroom to keep the transistors biased in saturation, and it results in a large DC-power consumption

$$A_v \cong \left(\frac{2}{\pi}\right) g_m R_L \quad g_m = \sqrt{\frac{2KP_n W I_D}{L}}$$
  
$$I_{BIAS} = 2 \times I_{D(TS)} \quad I_{D(SS)} = 2 \times I_{D(TS)}$$



Optimization Framework

  

Optimization Framework


 


TABLE I. REPORTED PERFORMANCE OF CMOS GILBERT MIXERS

Ref.	CMOS Tech.	Gain [dB]	IIP3 [dBm]	NF Av. [dB]	P _{DC} [mW]	FOM
[4]	0.13 μm	8	-3	11.2	5.57	0.12
[9]	0.18 μm	10	4	10	10	0.16
[10]	0.13 μm	8.95	-2.2	11.4	3.7	0.16
[11]	0.13 μm	21	-1.8	15.7	18.3	0.06
[12]	0.18 μm	13.5	-3.25	21.22	7.2	0.06
This Work	0.13 μm	11.24	-3.1	11.6	2.1	0.32

The performance metrics indicated refers to the core of the mixer

Optimization Framework

 

$$FOM = \frac{CG_{[dB]} \cdot IIP3_{[mW]}}{NF_{[dB]} P_{DC}[mW]}$$

Gilbert Cell: Framework

1. Given the target gain and the load resistance specifications, use (1) to derive the value of g_m ;
2. Once the value of g_m has been set, sweep g_m/I_D (that is the inversion level of the transistors) in the range 5÷25, and let the framework computes the corresponding current levels $I_{D(SS)}$ and $I_{D(TS)}$;
3. Exploiting the lookup table of the current density (I_D/W), computes the values of $W_{(SS)}$ and $W_{(TS)}$ for all inversion levels explored. Set the channel length L to the minimum value of 130nm to maximize speed[5];
4. Perform systematic DC analysis of the mixer by independently varying the g_m/I_D ratio for the TS and SS. For each bias point computes the DC-power consumption of the mixer.
5. For each solution checks that the circuit is correctly biased (that is all transistors operates in saturation) and compares the DC-power consumption with the design specification. Discard any unfeasible solution.
6. For each solution left from the previous step, compute the conversion gain of the mixer. Discard any further solution that exhibit a conversion gain lower than the design specifications.
7. Repeat the previous step for the noise figure and the third-order intercept of the system.
8. Explores the pruned solutions space and extract the optimal bias point, that is the bias point that allows to achieve the best tradeoff among the performance metrics of the mixer.


 


Fig. 4 FOM versus $g_m/I_{D(TS)}$ and $g_m/I_{D(SS)}$ ratios.

$$FOM = \frac{CG_{[dB]} \cdot IIP3_{[mW]}}{NF_{[dB]} P_{DC}[mW]}$$

UWB LNA Distributed Amplifier

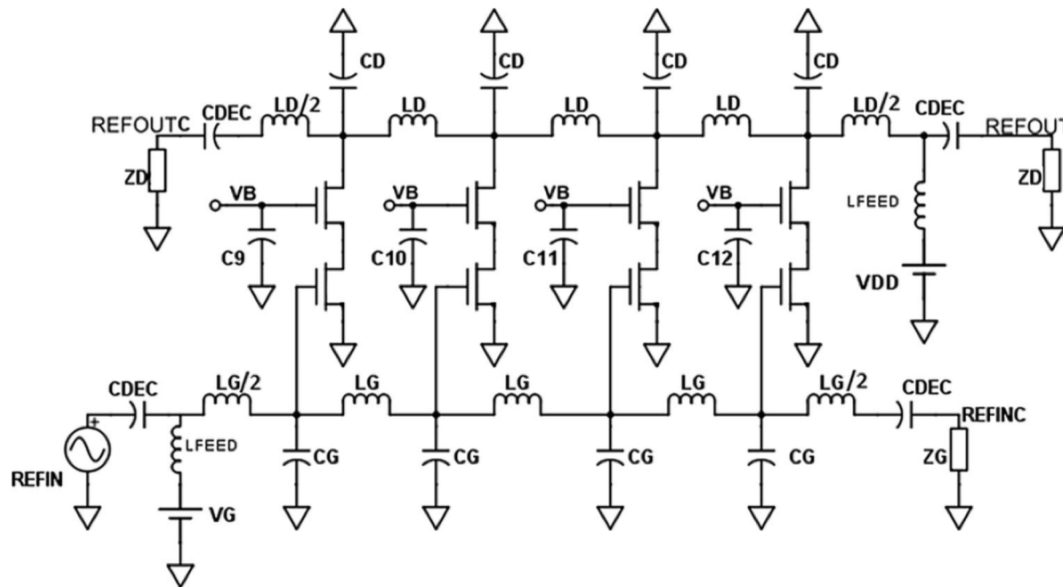

Theoretical Gain:

$$G = \frac{Ng_m Z_0}{2}$$

Upper Bound:

$$N_{opt} = \frac{\ln(A_D/A_G)}{A_D - A_G}$$

Synchronism of propagation:

$$L_G C_{GG} \approx L_D C_{DD}$$


Symmetry of characteristic impedance

$$Z_G = \sqrt{\frac{L_G}{C_G}} = Z_D = \sqrt{\frac{L_D}{C_D}}$$

Bandwidth:

$$BW \cong \min\left(\frac{1}{\pi} \sqrt{\frac{1}{C_{GG} L_G}}, \frac{1}{\pi} \sqrt{\frac{1}{C_{DD} L_D}}\right)$$

UWB Framework

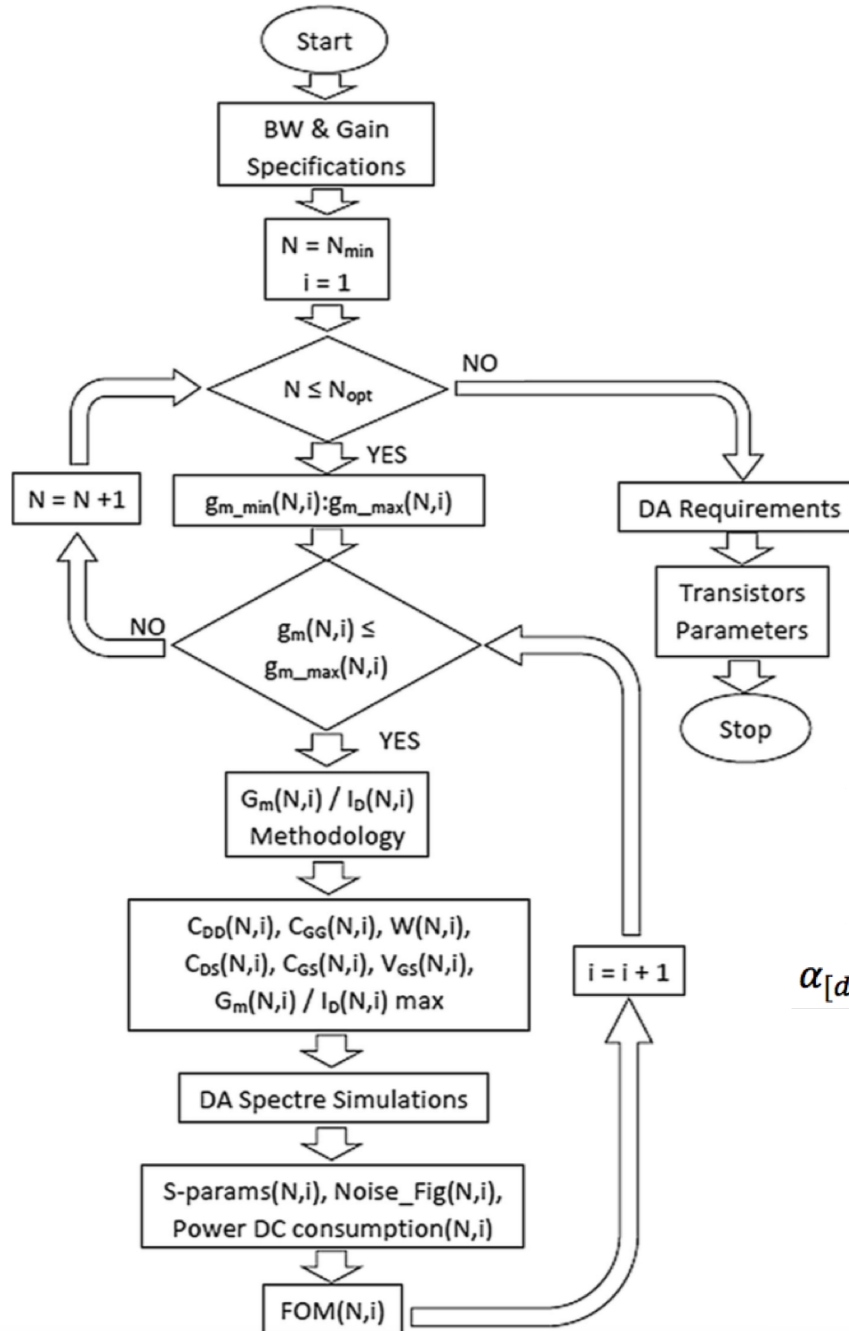

$$FOM_{[GHz/mW \cdot mm^2]} = \frac{\alpha_{[dB]} \cdot BW_{[GHz]}}{NF_{[dB]} P_{DC[mW]} Area[mm^2]}$$

$$\alpha_{[dB]} = 10 \cdot \log_{10} \{ |S_{21}|^2 \cdot [(1 - |S_{11}|^2) \cdot (1 - |S_{22}|^2)] \}$$