

# **First and Second Order Circuits**


**Claudio Talarico, Gonzaga University  
Spring 2015**

# Capacitors and Inductors

- intuition: bucket of charge

$$q = Cv \rightarrow i = C \frac{dv}{dt}$$

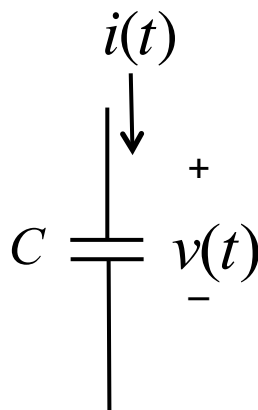
- Resist change of voltage
- DC open circuit
- Store voltage (charge)
- Energy stored =  $0.5 C v(t)^2$



- intuition: water hose

$$\lambda = Li \rightarrow v = L \frac{di}{dt}$$

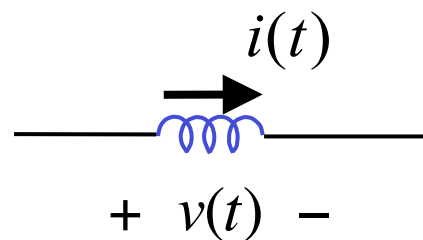- Resist change of current
- DC short circuit
- Store current (magnetic flux)
- Energy stored =  $0.5 L i(t)^2$



# Characterization of an LTI system's behavior


---

- Techniques commonly used to characterize an LTI system:

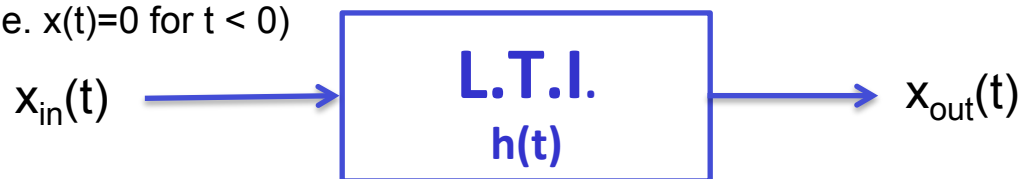1. Observe the response of the system when excited by a step input (time domain response)

Assumption:

$x_{in}(t)$  is causal (i.e.  $x(t)=0$  for  $t < 0$ )



$$x_{out} = \int_{0-}^t x_{in}(\tau) h(t - \tau) d\tau \equiv x_{in}(t) * h(t)$$

2. Observe the response of the system when excited by sinusoidal inputs (frequency response)

$$X_{out}(s) = X_{in}(s) \cdot H(s)$$

# Frequency Response

---

- The merit of frequency-domain analysis is that it is easier than time domain analysis:

$$L[x(t)] = \int_{0-}^{\infty} e^{-st} x(t) dt = X(s) \quad \longleftarrow \quad \begin{array}{l} \text{One sided Laplace Transform} \\ \text{(assumption: } x(t) \text{ is causal or is made} \\ \text{causal by multiplying it by } u(t)) \end{array}$$

- The transfer function of any of the LTI circuits we consider
  - Are rational with  $m \leq n$
  - Are real valued coefficients  $a_j$  and  $b_i$
  - Have poles and zeros that are either real or complex conjugated
  - Furthermore, if the system is stable
    - All denominator coefficients are positive
    - The real part of all poles are negative

$$\begin{aligned} H(s) &= \frac{a_0 + a_1 s + \dots + a_m s^m}{1 + b_1 s + \dots + b_n s^n} = K \frac{(s + \omega_{z1}) \dots (s + \omega_{zm})}{(s + \omega_{p1}) \dots (s + \omega_{pn})} = \\ &= K \frac{(s - z_1) \dots (s - z_m)}{(s - p_1) \dots (s - p_n)} \quad \text{with } K \equiv \frac{a_m}{b_n} \quad \longleftarrow \quad \begin{array}{l} \text{root form} \\ \text{"mathematicians" style} \end{array} \end{aligned}$$


# Frequency Response

$$H(s) = a_0 \frac{\left(1 + \frac{s}{\omega_{z1}}\right) \dots \left(1 + \frac{s}{\omega_{zm}}\right)}{\left(1 + \frac{s}{\omega_{p1}}\right) \dots \left(1 + \frac{s}{\omega_{pn}}\right)} = a_0 \frac{\left(1 - \frac{s}{z_1}\right) \dots \left(1 - \frac{s}{z_m}\right)}{\left(1 - \frac{s}{p_1}\right) \dots \left(1 - \frac{s}{p_n}\right)} \quad \leftarrow \text{“EE” style}$$

**NOTE :**

$p_i = -\omega_{pi}$  (*poles*)

$z_i = -\omega_{zi}$  (*zeros*)

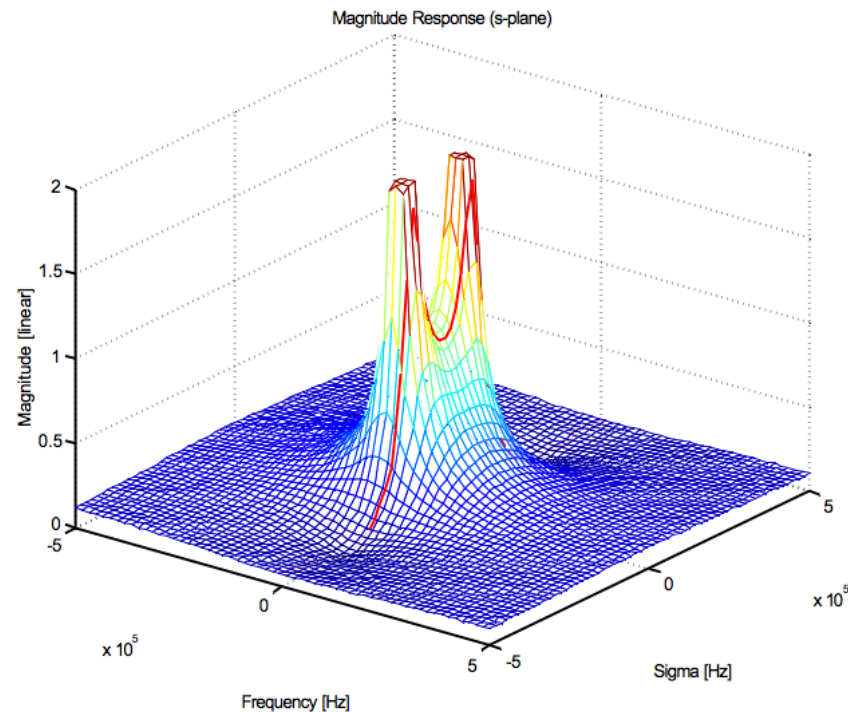

# Magnitude and Phase (1)

- When an LTI system is excited with a sinusoid the output is a sinusoid of the same frequency. The magnitude of the output is equal to the input magnitude multiplied by the magnitude response ( $|H(j\omega_{in})|$ ). The phase difference between the output and input sinusoid is equal to the phase response ( $\phi = \text{phase}[H(j\omega_{in})]$ )


$$x_{in}(t) = A_{in} \cos(\omega t) = A_{in} \frac{e^{j\omega t} + e^{-j\omega t}}{2}$$

$\updownarrow \mathcal{F}$

$$X_{in}(j\omega) = \mathcal{F}[x_{in}(t)]$$

$$H(j\omega) = |H(j\omega)| e^{j\omega t_0}$$
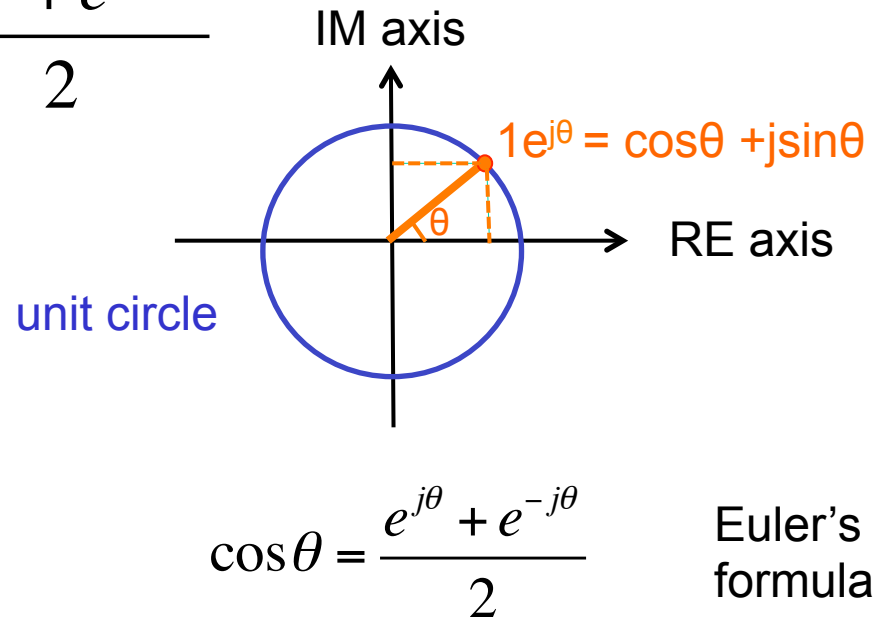
$$X_{out}(j\omega) = X_{in}(j\omega) \cdot H(j\omega)$$



## Magnitude and Phase (2)

---

$$X_{out}(j\omega) = X_{in}(j\omega) \cdot H(j\omega) = X_{in}(j\omega) \cdot |H(j\omega)| \cdot e^{j\omega t_0}$$

$$\mathcal{F}^{-1} \updownarrow$$

Time Shift Property:  
 $\mathcal{F}[x(t-t_0)] = X(f) e^{-j2\pi f t_0}$

$$\begin{aligned} x_{out}(t) &= |H(j\omega_{in})| x_{in}(t + t_0) = \\ &= A_{in} |H(j\omega_{in})| \cos[\omega(t + t_0)] = \\ &= A_{in} |H(j\omega_{in})| \cos(\omega t + \omega t_0) \end{aligned}$$

# First order circuits

---

- A first order transfer function has a first order denominator

$$H(s) = \frac{A_0}{1 + \frac{s}{\omega_p}}$$

First order low pass transfer function.  
This is the most commonly encountered transfer function in electronic circuits

$$H(s) = A_0 \frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{\omega_p}}$$

General first order transfer function.



# Step Response of first order circuits (1)

---

- Case 1: First order low pass transfer function

$$H(s) = \frac{A_0}{1 + \frac{s}{\omega_p}}$$

$$x_{in}(t) = A_{in} \cdot u(t) \quad \Leftrightarrow \quad X_{in}(s) = \frac{A_{in}}{s}$$

$$X_{out}(s) = \frac{A_{in}}{s} \frac{A_0}{1 + \frac{s}{\omega_p}} = A_{in} A_0 \left[ \frac{1}{s} - \frac{1}{s + \omega_p} \right]$$



$$x_{out}(t) = A_{in} A_0 u(t) \left[ 1 - e^{-t/\tau} \right] \quad \text{with } \tau = 1 / \omega_p$$

## Step Response of first order circuits (2)

---

- Case 2: General first order transfer function

$$H(s) = A_0 \frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{\omega_p}}$$

$$x_{in}(t) = A_{in} \cdot u(t) \quad \Leftrightarrow \quad X_{in}(s) = \frac{A_{in}}{s}$$

$$X_{out}(s) = \frac{A_{in} A_0}{s} \frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{\omega_p}}$$

$\Updownarrow$

$$x_{out}(t) = A_{in} A_0 u(t) \left[ 1 - \left( 1 - \frac{\omega_p}{\omega_z} \right) e^{-t/\tau} \right] \quad \text{where } \tau = 1 / \omega_p$$

## Step Response of first order circuits (3)

---

- Notice  $x_{out}(t)$  “short term” and “long term” behavior

$$x_{out}(0+) = A_{in} A_0 \frac{\omega_p}{\omega_z}$$

$$x_{out}(\infty) = A_{in} A_0$$

- The short term and long term behavior can also be verified using the Laplace transform

$$x_{out}(0+) = \lim_{s \rightarrow \infty} s \cdot X_{out}(s) = \lim_{s \rightarrow \infty} s \cancel{\frac{A_{in}}{s}} \cdot H(s) = A_{in} A_0 \frac{\omega_p}{\omega_z}$$

$$x_{out}(\infty) = \lim_{s \rightarrow 0} s \cdot X_{out}(s) = \lim_{s \rightarrow 0} s \cancel{\frac{A_{in}}{s}} \cdot H(s) = A_{in} A_0$$


# Equation for step response to any first order circuit

---

$$x_{out}(t) = \underbrace{x_{out}(\infty)}_{\text{Steady response}} - \underbrace{[x_{out}(\infty) - x_{out}(0+)] \cdot e^{-t/\tau}}_{\text{Transitory response}} \quad \text{where } \tau = 1 / \omega_p$$

## Example #1

---

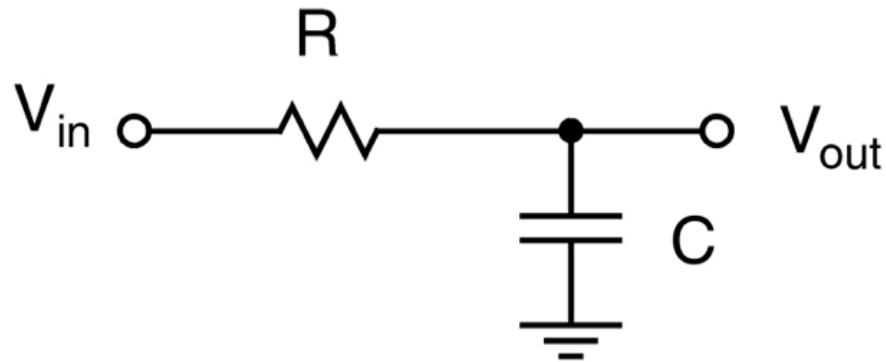

- $R = 1K\Omega$ ,  $C = 1\mu F$ .
- Input is a 0.5V step at time 0

Source: Carusone, Johns and Martin


---

$$H(s) = \frac{1}{1 + sRC}$$

$$\tau = RC = 1\mu s \Leftrightarrow \omega_p = \frac{1}{\tau} = 1Mrad / s \Leftrightarrow f_{-3dB} = \frac{\omega_p}{2\pi} \cong 159KHz$$

$$V_{out}(t) = 0.5 \cdot (1 - e^{-t/\tau}) u(t)$$

## Example #2 (1)

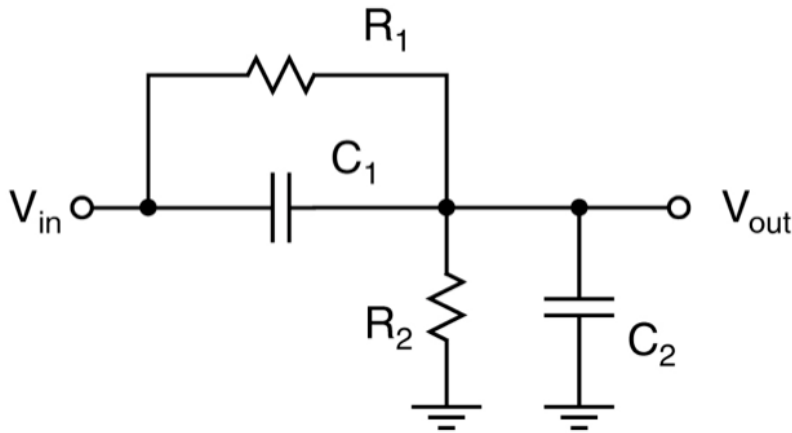

- $R_1 = 2\text{K}\Omega$ ,  $R_2 = 10\text{K}\Omega$
- $C_1 = 5\text{pF}$ ,  $C_2 = 10\text{pF}$
- Input is a 2V step at time 0

Source: Carusone, Johns and Martin

$$H(s \rightarrow 0) = \frac{R_2}{R_1 + R_2} \equiv A_0; \quad H(s \rightarrow \infty) = \frac{C_1}{C_1 + C_2} \equiv A_\infty$$


$$\tau_p = (R_1 \parallel R_2) \cdot (C_1 \parallel C_2) = \frac{R_1 R_2}{R_1 + R_2} (C_1 + C_2)$$

$$H(s) = \frac{R_2}{R_1 + R_2} \cdot \left[ \frac{1 + sR_1C_1}{1 + s \frac{R_1 R_2}{R_1 + R_2} (C_1 + C_2)} \right] \quad \leftarrow \text{By inspection}$$

$$\tau_z = R_1 C_1$$
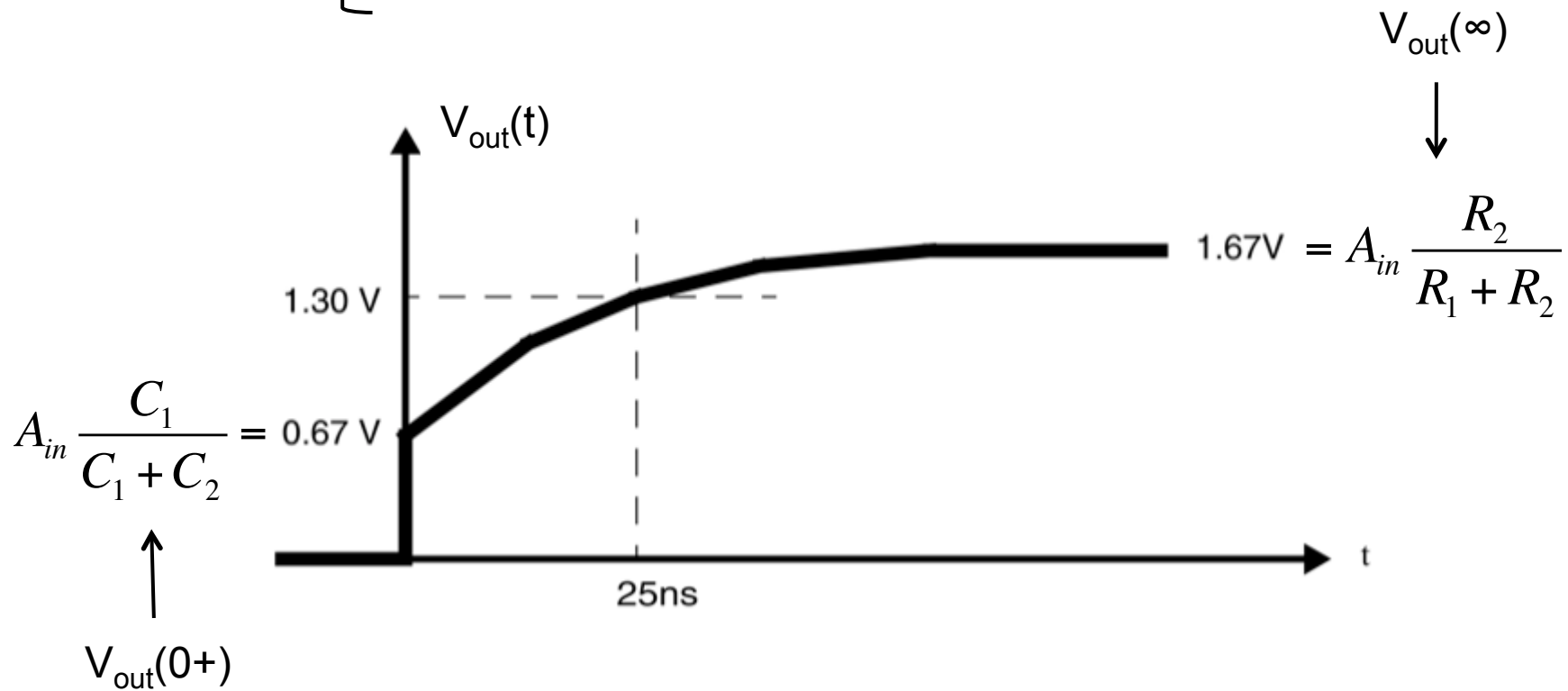
## Example #2 (2)

$$V_{out}(t) = \begin{cases} V_{out}(0+) + [V_{out}(\infty) - V_{out}(0+) \cdot (1 - e^{-t/\tau_p})] & \text{for } t > 0 \\ 0 & \text{for } t \leq 0 \end{cases}$$



## Example #3

---

- Consider an amplifier having a small signal transfer function approximately given by

$$A(s) = \frac{A_0}{1 + \frac{s}{\omega_p}}$$

- $A_0 = 1 \times 10^5$
- $\omega_p = 1 \times 10^3 \text{ rad/s}$

- Find approx. unity gain BW and phase shift at the unity gain frequency
- 

since  $A_0 \gg 1$ :

$$A(s) \approx \frac{A_0}{\frac{s}{\omega_p}} = \frac{A_0 \omega_p}{s} \iff A(j\omega) \approx \frac{A_0 \omega_p}{j\omega}$$

$$\left| \frac{A_0 \omega_p}{j\omega_u} \right| = 1 \Rightarrow \omega_u \cong A_0 \omega_p \quad \text{Phase}[A(j\omega_u)] \approx \text{Phase}\left[ \frac{A_0 \omega_p}{j\omega_u} \right] = -90^\circ$$



## Second-order low pass Transfer Function

---

$$H(s) = \frac{a_0}{1 + b_1 s + b_2 s^2} = \frac{a_0}{1 + \frac{s}{\omega_0 Q} + \frac{s^2}{\omega_0^2}}$$

$$b_1 \equiv \frac{1}{\omega_0 Q}; \quad b_2 \equiv \frac{1}{\omega_0^2}$$

- Interesting cases:

- Poles are real
  - one of the poles is dominant
- Poles are complex

$$\longrightarrow \omega_{3dB} \cong \frac{1}{b_1} \quad \left( b_1 = \sum \tau_j \right)$$

# Poles Location

- Roots of the denominator of the transfer function:  $1 + \frac{s}{\omega_0 Q} + \frac{s^2}{\omega_0^2} = 0$


- Complex Conjugate poles  
(overshooting in step response)

for  $Q > 0.5 \Rightarrow p_{1,2} = -\frac{\omega_0}{2Q} \left(1 \mp j\sqrt{4Q^2 - 1}\right) = -\omega_R \mp j\omega_I$

- For  $Q = 0.707$  ( $\Phi = 45^\circ$ ), the  $-3\text{dB}$  frequency is  $\omega_0$   
(Maximally Flat Magnitude or Butterworth Response)
- For  $Q > 0.707$  the frequency response has peaking

- Real poles (no overshoot in the step response)

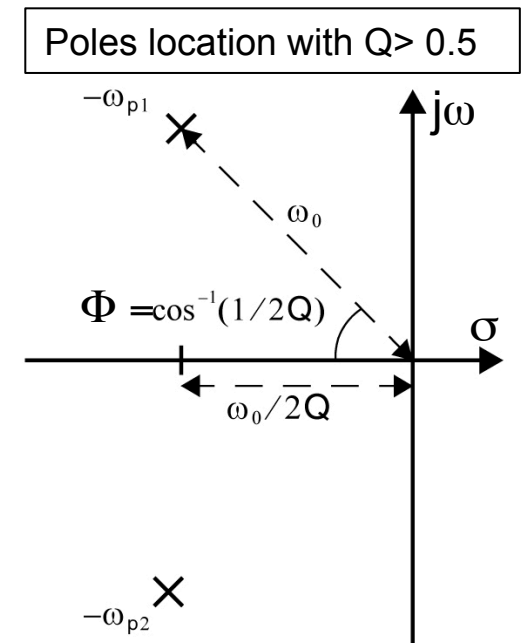
for  $Q \leq 0.5 \Rightarrow p_{1,2} = -\frac{\omega_0}{2Q} \left(1 \mp \sqrt{1 - 4Q^2}\right)$




Source:  
Carusone
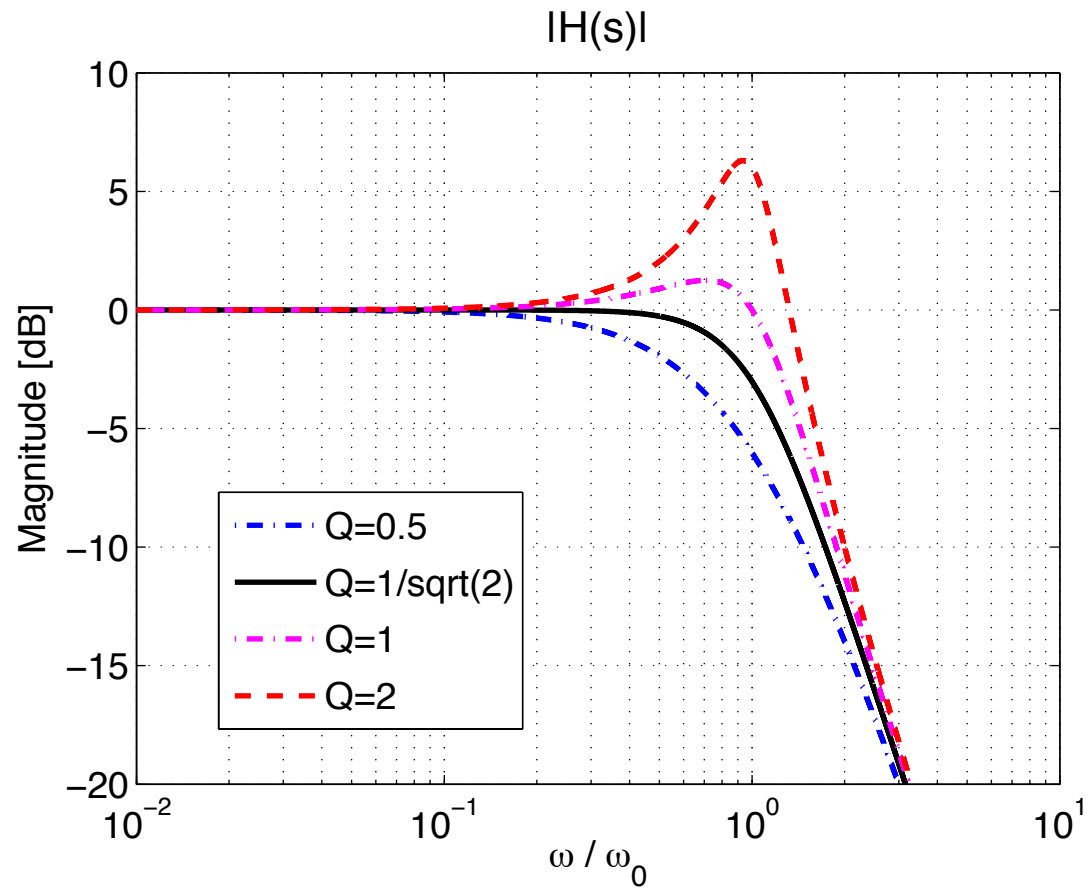
# Frequency Response

$$H(s) = \frac{1}{1 + \frac{s}{\omega_0 Q} + \frac{s^2}{\omega_0^2}}$$



# Step Response

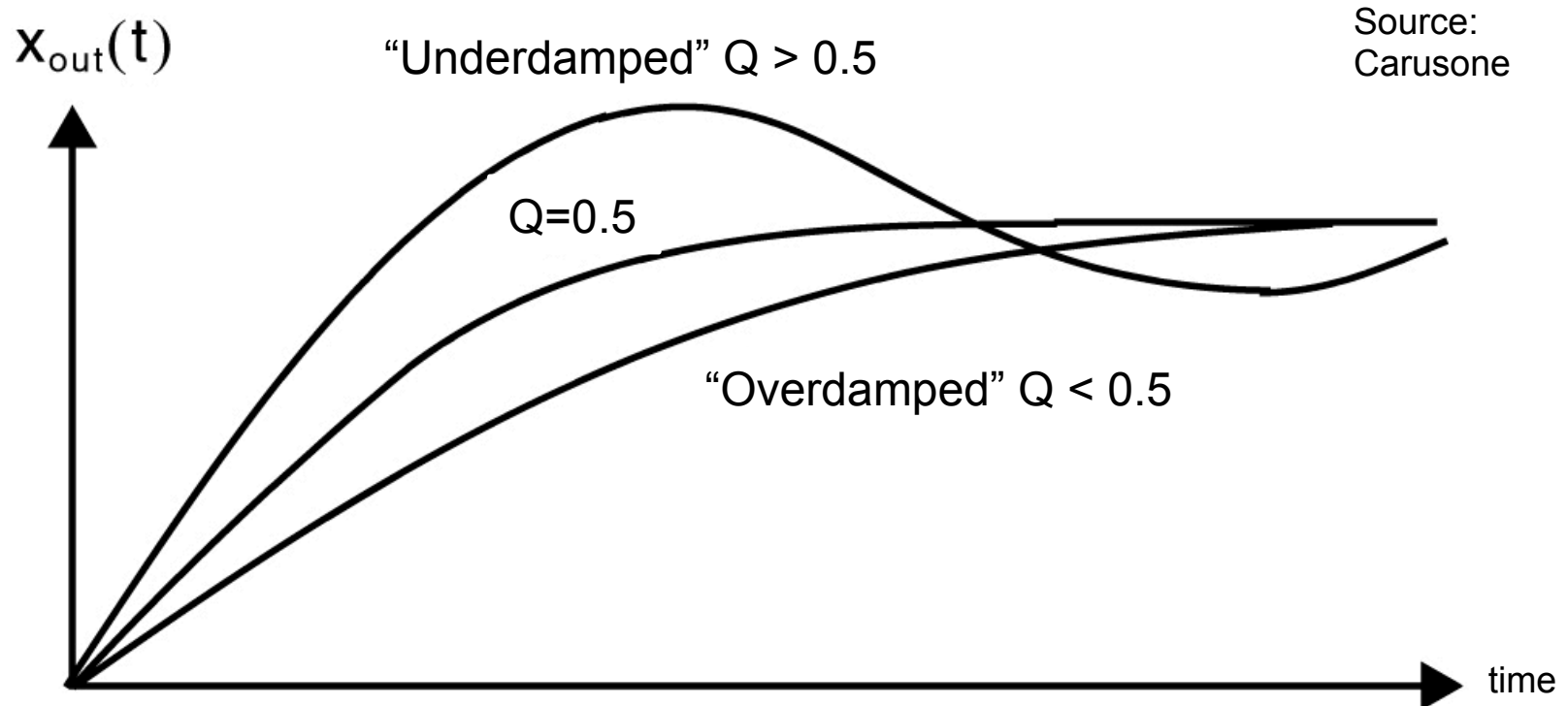

- Ringing for  $Q > 0.5$
- The case  $Q=0.5$  is called maximally damped response (fastest settling without any overshoot)

## Widely- Spaced Real Poles

---

$$H(s) = \frac{a_0}{1 + b_1 s + b_2 s^2} = \frac{a_0}{1 + \frac{s}{\omega_0 Q} + \frac{s^2}{\omega_0^2}} \quad b_1 \equiv \frac{1}{\omega_0 Q}; \quad b_2 \equiv \frac{1}{\omega_0^2}$$

Real poles occurs when  $Q \leq 0.5$ :

$$\text{for } Q \leq 0.5 \Rightarrow p_{1,2} = -\frac{\omega_0}{2Q} \left( 1 \mp \sqrt{1 - 4Q^2} \right)$$

Real poles widely-spaced (that is one of the poles is dominant) implies:

$$p_1 \equiv -\frac{\omega_0}{2Q} - \frac{\omega_0}{2Q} \sqrt{1 - 4Q^2} \ll p_2 \equiv -\frac{\omega_0}{2Q} + \frac{\omega_0}{2Q} \sqrt{1 - 4Q^2}$$

$\Updownarrow$

$$0 \ll 2\sqrt{1 - 4Q^2} \Leftrightarrow 0 \ll \sqrt{1 - 4Q^2} \Leftrightarrow 0 \ll 1 - 4Q^2 \Leftrightarrow Q^2 \ll \frac{1}{4} \Leftrightarrow \frac{b_2}{b_1^2} \ll \frac{1}{4}$$

## Widely-Spaced Real Poles

---

$$H(s) = \frac{a_0}{1 + b_1 s + b_2 s^2} = \frac{a_0}{\left(1 - \frac{s}{p_1}\right) \cdot \left(1 - \frac{s}{p_2}\right)} = \frac{a_0}{1 - \frac{s}{p_1} - \frac{s}{p_2} + \frac{s^2}{p_1 p_2}} \cong \frac{a_0}{1 - \frac{s}{p_1} + \frac{s^2}{p_1 p_2}}$$

$$\Rightarrow p_1 \cong -\frac{1}{b_1} \quad p_2 \cong \frac{1}{p_1 b_2} = -\frac{b_1}{b_2}$$


This means that in order to estimate the -3dB bandwidth of the circuit, all we need to know is  $b_1$  !

$$H(s) \cong \frac{a_0}{1 - \frac{s}{p_1}} \Rightarrow \omega_{-3dB} \cong |p_1| \cong \frac{1}{b_1}$$

ZVTC method:  $b_1 = \sum \tau_j \Rightarrow \omega_{-3dB} \cong \frac{1}{b_1} = \frac{1}{\sum \tau_j}$

## Example: Series RLC circuit (1)

---

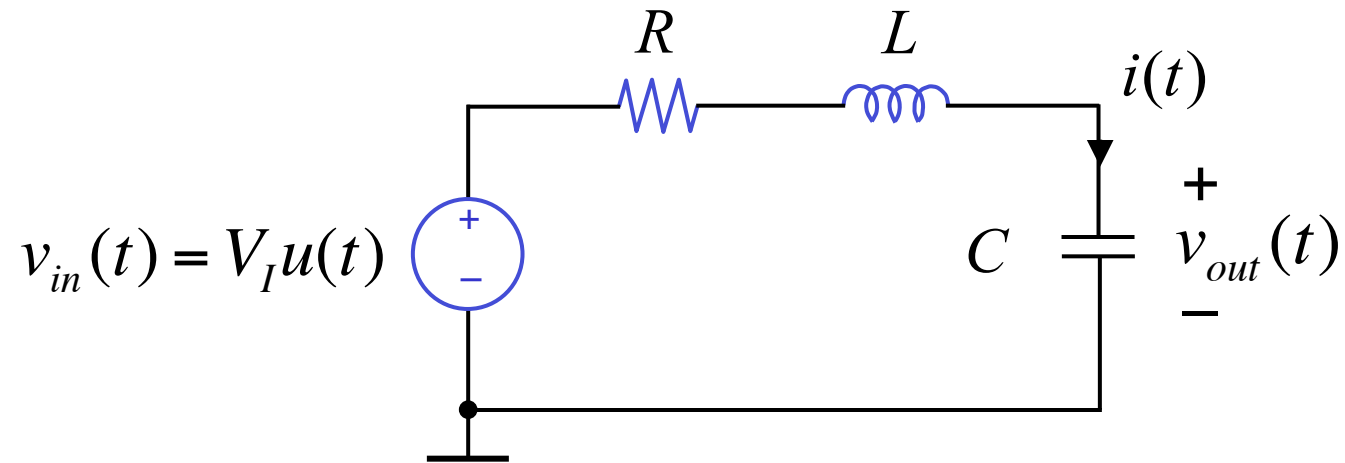

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{\frac{1}{sC}}{R + sL + \frac{1}{sC}} = \frac{1}{1 + sRC + s^2 LC} \equiv \frac{1}{1 + \frac{s}{\omega_0 Q} + \frac{s^2}{\omega_0^2}}$$

$$\omega_0^2 = \frac{1}{LC}; \quad Q = \frac{1}{\omega_0 RC} = \frac{\sqrt{L/C}}{R} \equiv \frac{Z_0}{R}$$

## Example - Series RLC: Poles location (2)

---

$$1 + \frac{s}{\omega_0 Q} + \frac{s^2}{\omega_0^2} = 0 \Leftrightarrow s^2 + s \cdot \frac{\omega_0}{Q} + \omega_0^2 = 0 \Leftrightarrow s_{1,2} = \frac{-\frac{\omega_0}{Q} \mp \sqrt{\left(\frac{\omega_0}{Q}\right)^2 - 4\omega_0^2}}{2} \Leftrightarrow$$
$$\Leftrightarrow s_{1,2} = -\underbrace{\frac{\omega_0}{2Q}}_{\alpha} \left(1 \mp \sqrt{1 - 4Q^2}\right) \rightarrow \frac{\omega_0}{2Q} \equiv \alpha$$

- Two possible cases:
  - For  $Q \leq \frac{1}{2}$  real poles:

$$s_{1,2} = -\frac{\omega_0}{2Q} \left(1 \mp \sqrt{1 - 4Q^2}\right) \equiv -\alpha \left(1 \mp \sqrt{1 - 4Q^2}\right)$$

- For  $Q > \frac{1}{2}$  complex poles

$$s_{1,2} = -\frac{\omega_0}{2Q} \left(1 \mp j\sqrt{4Q^2 - 1}\right) \equiv -\alpha \left(1 \mp j\sqrt{4Q^2 - 1}\right)$$



## Example – series RLC

---

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{\frac{1}{sC}}{R + sL + \frac{1}{sC}} = \frac{1}{1 + sRC + s^2LC} \equiv \frac{1}{1 + s\frac{Q}{\omega_0} + \frac{s^2}{\omega_0^2}}$$

$$\omega_0^2 = \frac{1}{LC}; \quad Q = \frac{1}{\omega_0 RC} = \frac{\sqrt{L/C}}{R} \equiv \frac{Z_0}{R}; \quad \frac{\omega_0}{2Q} \equiv \alpha$$



$$C = \frac{1}{L \cdot \omega_0^2}; \quad L = \frac{1}{C \cdot \omega_0^2}$$

$$Q = \frac{1}{RC\omega_0} = \frac{L}{R} \cdot \frac{1}{\omega_0}$$

$$\alpha = \frac{\omega_0}{2Q} = \frac{R}{2L}$$

## Example – series RLC

$$s^2 + s \cdot \frac{\omega_0}{Q} + \omega_0^2 = 0 \Leftrightarrow s^2 + s \cdot 2\alpha + \omega_0^2 = 0 \Leftrightarrow s_{1,2} = -\alpha \mp \sqrt{\alpha^2 - \omega_0^2}$$

– For  $Q \leq \frac{1}{2}$  real poles:


$$s_{1,2} = -\alpha \mp \sqrt{\alpha^2 - \omega_0^2} \quad \left( \text{for } \frac{\omega_0}{\alpha} \ll 1 \text{ the poles are widely spaced} \right)$$

– For  $Q > \frac{1}{2}$  complex poles

$$s_{1,2} = -\alpha \mp j\sqrt{\omega_0^2 - \alpha^2} = -\alpha \mp j\omega_n$$


$\omega_n$  = natural (damped) frequency

$\omega_0$  = resonant frequency

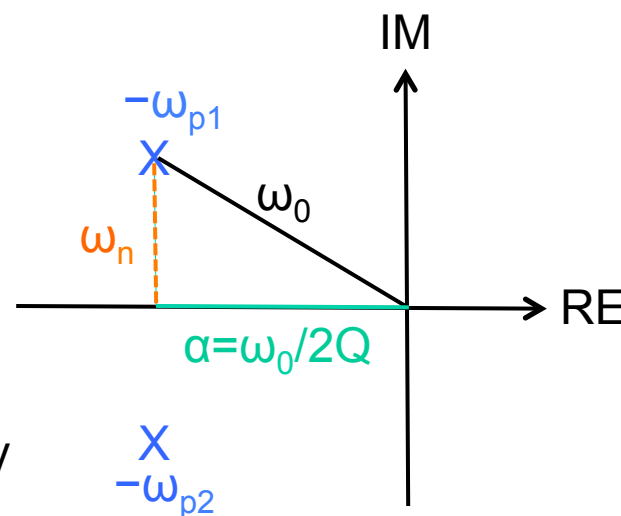

## Example – series RLC: Step response

---

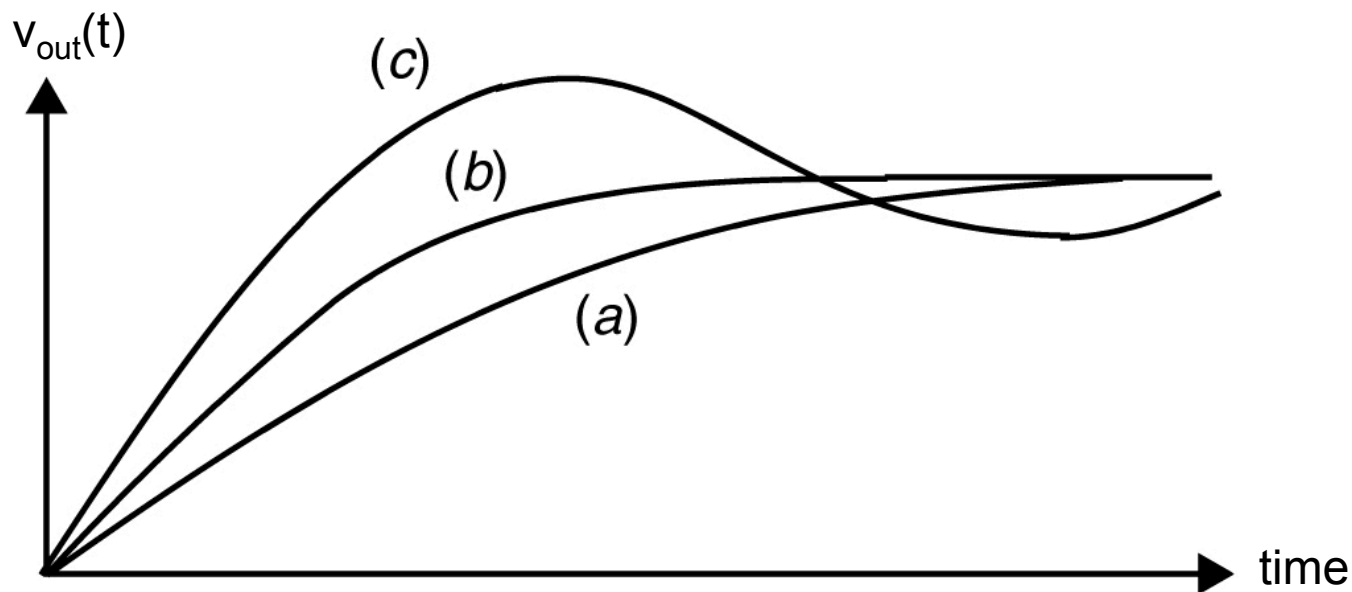

(a) Overdamped  $Q < 0.5$       ( $\alpha > \omega_0 \Leftrightarrow \zeta \equiv \alpha / \omega_0 > 1$ )

(b) Critically damped  $Q=0.5$       ( $\alpha = \omega_0 \Leftrightarrow \zeta \equiv \alpha / \omega_0 = 1$ )

(c) Underdamped  $Q > 0.5$       ( $\alpha < \omega_0 \Leftrightarrow \zeta \equiv \alpha / \omega_0 < 1$ )       $\omega_n$  = ringing frequency

$\alpha$  = damping factor (rate of decay)

$\omega_0$  = resonance frequency

$\zeta$  = Damping ratio

## Example – RLC series: Quality Factor Q

---

For a system under sinusoidal excitation at a frequency  $\omega$ , the most fundamental definition for Q is:

$$Q = \omega \frac{\text{energy stored}}{\text{average power dissipated}} \quad \longleftarrow \text{dimensionless}$$

At the resonant frequency  $\omega_0$ , the current through the network is simply  $V_{in}/R$ . Energy in such a network sloshes back and forth between the inductance and the inductor, with a constant sum. The peak inductor current at resonance is  $I_{pk} = V_{pk}/R$ , so the energy stored by the network can be computed as:

$$E_{stored} = \frac{1}{2} L \cdot I_{pk}^2$$

The average power dissipated in the resistor at resonance is:  $P_{avg} = \frac{1}{2} R \cdot I_{pk}^2$


$$Q = \omega_0 \frac{E_{stored}}{P_{avg}} = \frac{1}{\sqrt{LC}} \cdot \frac{L}{R} = \frac{\sqrt{L/C}}{R} = \frac{Z_0}{R}$$

$Z_0$  = Characteristic impedance of the network

At resonance  $|Z_C| = |Z_L| = \omega_0 L = (\omega_0 C)^{-1} = \sqrt{L/C} \equiv Z_0$
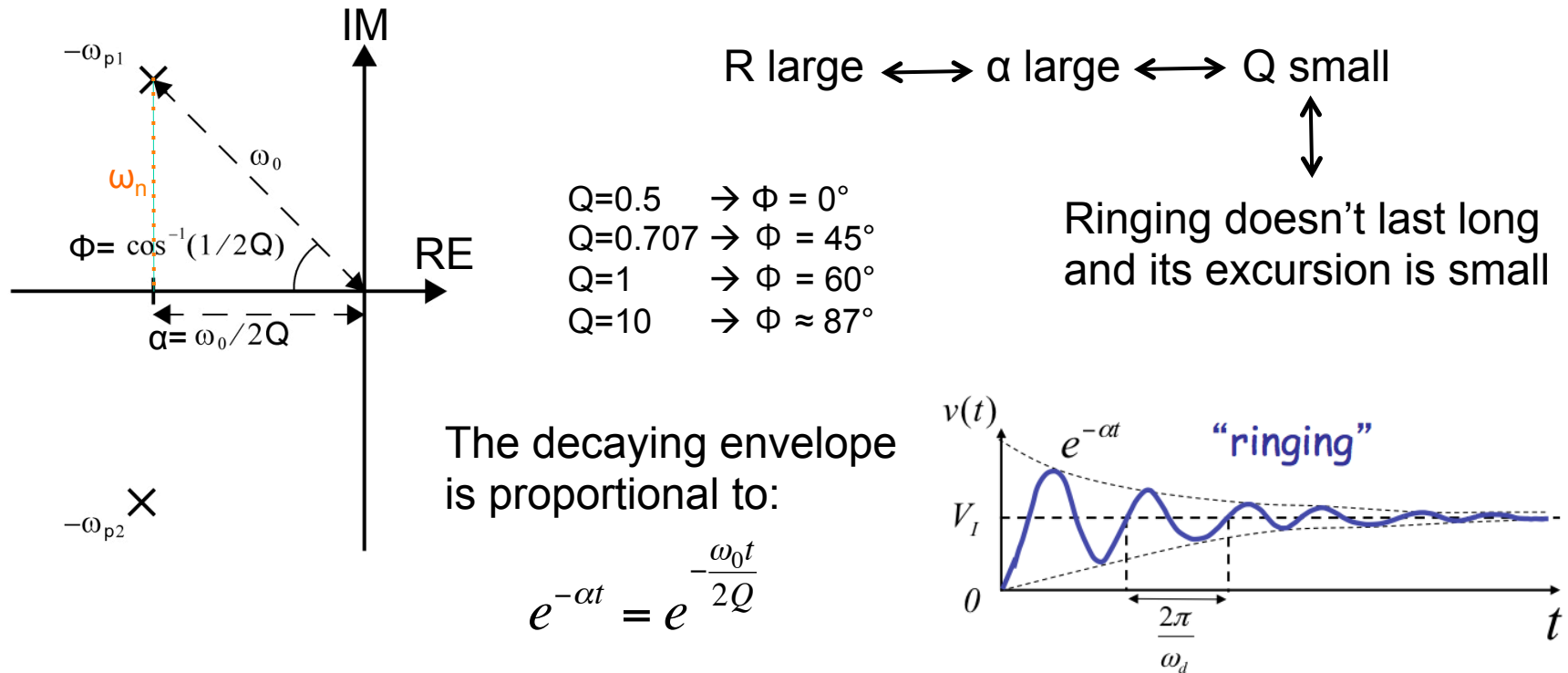
## Example – series RLC: Ringing and Q

Since Q is a measure of the rate of energy loss, one expect a higher Q to be associated with more persistent ringing than a lower Q.




Rule of thumb: Q is roughly equal to the number of cycles of ringing.

Frequency of the ringing oscillations:  $1/f_n = T_n = 2\pi/\omega_n$
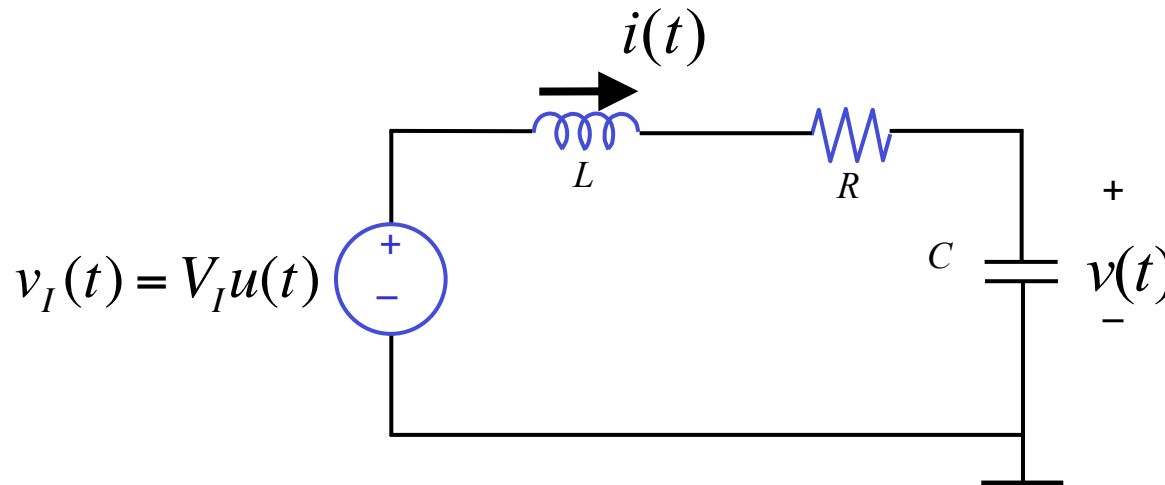
## Example – RLC series by intuition (1)

- We can predict the behavior of the circuit without solving pages of differential equations or Laplace transforms. All we need to know is the characteristics equation (denominator of  $H(s)$ ) and the initial conditions




Assume the values of  $R, L, C$  are such that  $\omega_0 > \alpha$  (underdamping).

Initial conditions:  
 $i(0) = -I_0$   
 $v(0) = +V_0$

- The voltage across the capacitor cannot jump:  $v(0+) = v(0) = +V_0$
- The current through the inductor cannot jump:  $i(0+) = i(0) = -I_0$
- The output voltage starts at  $V_0$ , it ends at  $v(\infty) = V_I$  and it rings about  $Q$  times before settling at  $V_I$
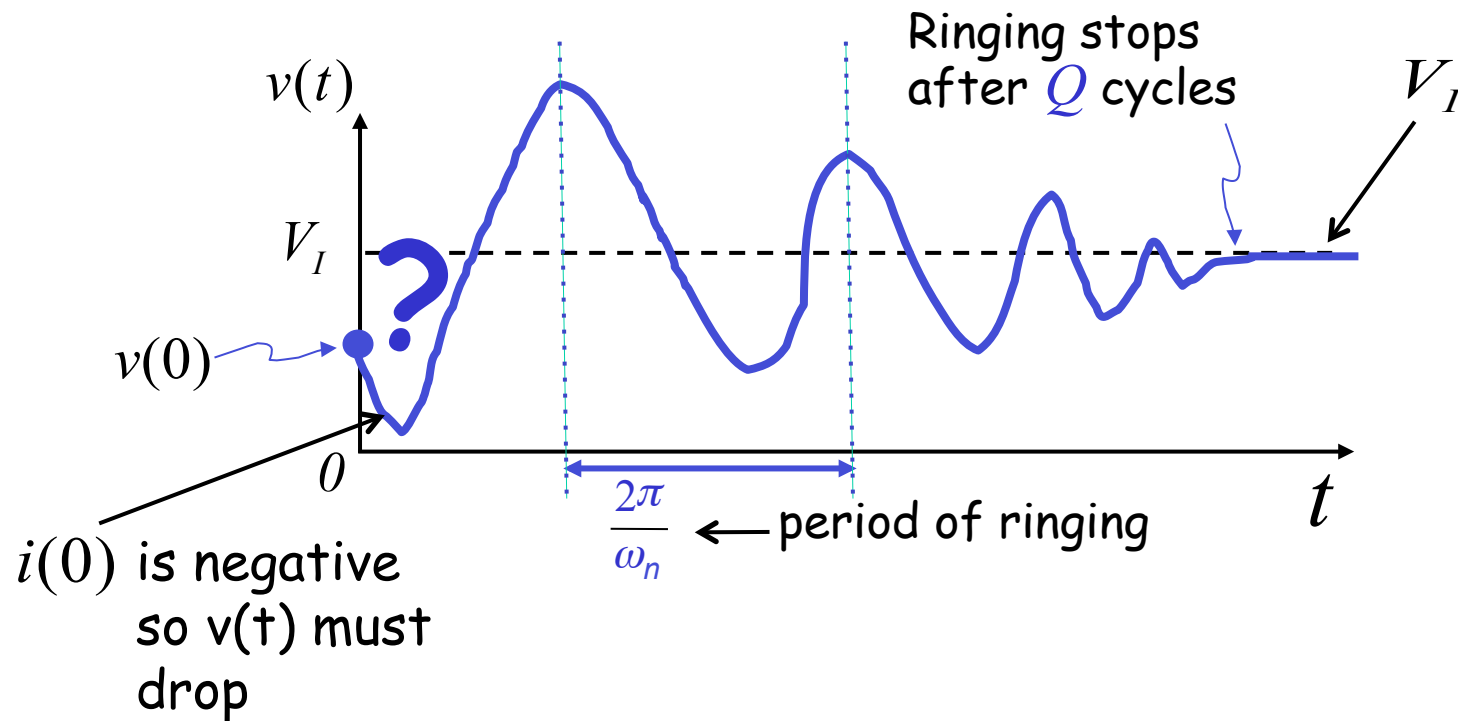
## Example – RLC series using intuition (2)

- The only question left is to decide if  $v(t)$  will start off shooting down or up ?
- But, ... we know that  $i(0+)$  is negative  $\rightarrow$  this means the current flows from the capacitor toward the inductor  $\rightarrow$  which means the capacitor must be discharging  $\rightarrow$  the voltage across the capacitor must be dropping



## Example – RLC series using intuition (3)

---

- In practice for the under damped case it useful to compute two parameters
  - Overshoot
  - Settling time

$$OS = \exp\left(\frac{-\pi}{\omega_n} \alpha\right) \quad \longleftarrow \quad \text{Normalized overshoot = \% overshoot w.r.t. final value}$$

$$t_s \cong -\frac{1}{\alpha} \ln\left(\varepsilon \frac{\omega_n}{\omega_0}\right) \quad \varepsilon \text{ is the \% error that we are willing to tolerate w.r.t. the ideal final value}$$



# First order vs. Second order circuits Behavior

---

- First order circuits introduce exponential behavior
- Second order circuits introduce sinusoidal and exponential behavior combined
- Fortunately we will not need to go on analyzing 3<sup>rd</sup>, 4<sup>th</sup>, 5<sup>th</sup> and so on circuits because they are not going to introduce fundamentally new behavior