

# CMOS Digital Circuits

- Types of Digital Circuits

## Combinational

The value of the outputs at any time  $t$  depends only on the combination of the values applied at the inputs at time  $t$  (the system has no memory)

## Sequential

The value of the outputs at any time  $t$  depends not only on the values applied at the inputs at time  $t$ , but also on the past sequence of inputs that have been applied (the system has memory)

# Logic values and noise margins


 


Figure 1-2

Logic values and noise margins.

# MOS Transistors


- Four terminals: gate, source, drain, body (= bulk)

 

**FIG 1.8** nMOS transistor (a) and pMOS transistor (b)

# Silicon Lattice



- Transistors are built on a silicon substrate
- Silicon is a semiconductor (Group IV material)
- Forms crystal lattice with bonds to four neighbors

 

**FIG 1.6** Silicon lattice and dopant atoms
  
# Dopant atoms




- Pure silicon has no free carriers and conducts poorly.
- Adding dopants increases the conductivity
- Group V: extra electron (n-type)
- Group III: missing electron, called hole (p-type)



# Types of Transistor

- Bipolar Junction Transistor (BJT)
  - NPN and PNP transistors
  - Small current into very thin base layer controls large current between emitter and collector
  - Base currents limit integration density
- MOS Field Effect Transistor (MOSFET)
  - NMOS and PMOS FETs
  - Voltage applied to insulated gate controls current between source and drain
  - Low power allows very high integration

# MOS Transistor symbols

  
 


(a)

(b)

# N-MOSFET operation (1)


- Body is commonly tied to ground (0 V)
- When the gate is at a “low” voltage:
  - P-type body is at low voltage
  - Source-body and drain-body diodes are OFF
  - No current flows, transistor is OFF

  

**FIG 1.7** p-n junction diode structure and symbol

 
# N-MOSFET operation (2)

- When the gate is at a “high” voltage:
  - Positive charge on gate of MOS capacitor
  - Negative charge attracted to body
  - channel under gate gets “inverted” to n-type
  - Now current **can** flow through n-type silicon from source through channel to drain, transistor is ON


 
# P-MOSFET operation

- Similar BUT **doping and voltages are reversed**
- Body tied to "high" voltage ( $V_{DD}$ )
- Gate "low": transistor ON
- Gate "high": transistor OFF
- Bubble indicates inverted behavior




# What does high and low voltage really mean ?

- Power Supply Voltage:
  - GND = 0 V
  - In 1980's,  $V_{DD} = 5V$
  - $V_{DD}$  has decreased in modern processes
  - High  $V_{DD}$  would damage modern tiny transistors
  - Lower  $V_{DD}$  saves power
  - $V_{DD} = 3.3, 2.5, 1.8, 1.5, 1.2, 1.0, \dots$

# MOSFETs as SWITCHES


- We can model MOS transistors as controlled switches
- Voltage at gate controls current path from source to drain

 


**FIG 1.9** Transistor symbols and switch-level models

# CMOS Inverter (= NOT gate)

Table 1.1 Inverter truth table	
A	Y
0	1
1	0

 

(a)

 

(b)

**FIG 1.10** Inverter schematic (a) and symbol (b)  $Y = \overline{A}$


# CMOS Technology

- CMOS technology uses both nMOS and pMOS transistors
- The transistors are arranged in a structure formed by two complementary networks
  - Pull-up network is complement of pull-down network
  - Parallel  $\rightarrow$  Series
  - Series  $\rightarrow$  Parallel

# CMOS Logic NAND

**Table 1.2** NAND gate truth table

A	B	pull-down network	pull-up network	Y
0	0	OFF	ON	1
0	1	OFF	ON	1
1	0	OFF	ON	1
1	1	ON	OFF	0

 

(a)




(b)

**FIG 1.11** 2-input NAND gate schematic (a) and symbol (b)  $Y = \overline{A \cdot B}$

# CMOS Logic NOR

**Table 1.4** NOR gate truth table

<i>A</i>	<i>B</i>	<i>Y</i>
0	0	1
0	1	0
1	0	0
1	1	0

 


(a)



(b)

**FIG 1.15** 2-input NOR gate schematic (a) and symbol (b)  $Y = \overline{A + B}$

# CMOS logic gates (a.k.a. Static CMOS)

 

- Pull-up network is complement of pull-down
- Parallel  $\rightarrow$  Series
- Series  $\rightarrow$  Parallel


**FIG 1.13** General logic gate using pull-up and pull-down networks

<b>Table 1.3</b> Output states of CMOS logic gate		
	<b>pull-up OFF</b>	<b>pull-up ON</b>
<b>pull-down OFF</b>	Z	1
<b>pull-down ON</b>	0	crowbarred (X)


# Compound gates

- Example:  $\overline{(A + B + C)} * D$

A	B	C	D	Y
-	-	-	0	1
0	0	0	-	1
1	-	-	1	0
-	1	-	1	0
-	-	1	1	0

 

# Compound gates

 


**FIG 1.18** CMOS compound gate for function  $Y = \overline{(A + B + C)} \cdot D$

# How good is the output signal ?

- **Strength** of signal
  - How close the signal approximate ideal voltage source
- $V_{DD}$  and GND rails are the strongest 1 and 0
- nMOS and pMOS are not ideal switches
  - pMOS passes strong 1 , but degraded (weak) 0
  - nMOS passes strong 0. but degraded (weak) 1
- **THUS:**
  - nMOS are best for the pull-down network
  - pMOS are best for the pull-up network

# The Pass Transistor


- Transistors used as switches

 

**FIG 1.19** Pass transistor strong and degraded outputs

# The Transmission Gate

- Pass transistors produce degraded outputs
- Transmission gates pass both 0 and 1 well

 


**FIG 1.20** Transmission gate

# Static CMOS gates are fully restoring

- In static CMOS, the nMOS transistors only need to pass 0's and the pMOS only pass 1's, so the output is always strongly driven and the levels are never degraded
- This is called a fully restoring logic gate

# Static CMOS is inherently inverting

- CMOS single stage gates must be inverting
- For building non inverting functions we need multiple stages

 

**FIG 1.21** Bad noninverting buffer

# Tristate Buffer


- A tristate buffer produce Z when not enabled



A	EN	Y
0	0	Z
0	1	0
1	0	Z
1	1	1

**FIG 1.24** Tristate buffer symbol

# Non restoring tristate

 


**FIG 1.25** Transmission gate

- Transmission gate acts as tristate buffer
  - It takes only 2 transistors
  - **BUT** is nonrestoring  
A is passed to Y as it is  
(thus, Y is not always a strong 0 or 1)


# Tristate inverter

- Tristate inverter produces restored output
- For a non inverting tristate add an inverter in front

 

**FIG 1.26** Tristate inverter



# Designing a 2:1 mux

 

D0	D1	S	Y
0	-	0	0
1	-	0	1
-	0	1	0
-	1	1	1

# 2:1 mux - gate level approach


$$Y = D0 * \bar{S} + D1 * S$$

  


- How many transistors are needed ?  
**Too Many !!!** (20 transistors)
 
# 2:1 mux – TG approach

- We need only 4 transistors (6 to be honest)




BUT it is non restoring and it has another issue called charge sharing

 

**FIG 1.27** Transmission gate multiplexer


# inverting mux

 

**FIG 1.28** Inverting multiplexer

# D Latch


- When  $CLK = 1$ , latch is *transparent*
  - D flows through to Q like a buffer
- When  $CLK = 0$ , the latch is *opaque*
  - Q holds its old value independent of D
- a.k.a. *transparent latch* or *level-sensitive latch*

 

**FIG 1.30** CMOS positive-level-sensitive D latch

# D Latch Design and Operation



Multiplexer chooses D or hold Q

 

**FIG 1.30** CMOS positive-level-sensitive D latch

# D Flip Flop






- When CLK rises, D is copied to Q
- At all other times, Q holds its value
- a.k.a. *positive edge-triggered flip-flop, master-slave flip-flop*

  

**FIG 1.31** CMOS positive-edge-triggered D flip-flop

# D Flip Flop Design and Operation

- Built from master and slave D Latches

     

**FIG 1.31** CMOS positive-edge-triggered D flip-flop