

Getting Started with HSPICE

Topics

- Starting HSPICE
- Netlist file structure
- HSPICE output files
- Using components, sources and subcircuits to construct a netlist
- HSPICE analysis types
- Simulation controls and options

Starting HSPICE

- 32-bits
 - Unix only:
 - hspice design.sp > design.lis
 - Unix and Windows:
 - hspice –i design.sp –o design.lis
- 64-bits
 - Unix only:
 - hspice64 design.sp > design.lis
 - hspice –i design.sp –o design.lis

The output list file

- .lis contains results of
 - .PRINT
 - .OP
 - .OPTIONS

Files and suffixes

HSPICE Input	
Input netlist	.sp
Model libraries	.inc, .lib
HSPICE Output	
Run Status	.st0
Output listing	.lis
Analysis data, transient	.tr# (e.g. .tr0)
Analysis data, dc	.sw# (e.g. .sw0)
Analysis data, ac	.ac# (e.g. .ac0)
FFT Analysis data	.ft# (e.g. .ft0)
Measure output	.m*# (e.g. .mt0)
Waveform Viewer Input	
All analysis data and measure output	


Netlist Structure

Title	First line is always the title
Comment character	* - comment for a line \$ - comment after a command
Options	.option post
Print/Probe/Analysis	.print v(d) i(rl) .probe v(g) .tran .1n 5n
Initial Conditions	.ic v(b) = 0 \$ input state
Sources	Vg g 0 pulse 0 1 0 0.15 0.15 0.42 * example of a voltage source
Circuit Description	MN d g gnd n nmos RL vdd d 1K
Models	.model n nmos level = 49 + vto = 1 tox = 7n * '+' continuation character
End	.end \$ terminates the simulation


Netlist structure

- A netlist consists of one main file and one or more optional added files
- Some commands can be used to structure the netlist:
 - Add a file to your netlist
 - . INCLUDE 'filename'
 - Add a library to the netlist
 - . LIB 'filename' libname
 - Assign a parameter value
 - . PARAM res=1
 - . PARAM res2='res+1'
 - R1 n1 n2 'res2'
 - Alter the netlist or parameters and run more simulations
 - . ALTER
 - . DATA
- Elements in a netlist are order independent
 - For Parameters and Options the last definition is used


Netlist Topologies to avoid

 


No voltage loops

 


No dangling nodes

 


Every node must have a DC path to ground

 

No stacked current sources

 

 No ideal voltage source in closed inductor loop



No ideal current source in closed capacitor loop

Node Naming Conventions

- Node Names:
 - Can be up to 1024 characters
 - Either names or numbers (e.g. n1, 33, in1, 100)
 - Numbers: 1 to 9999999999999999 (1 to 1e16)
 - Leading zeros in node names are ignored
 - Can begin with these characters: # _ ! %
 - 0 is ALWAYS ground
 - Global vs. local
 - Do not begin with a “/”
 - May contain:
 - + - * / : ; \$ # . [] ! < > _ %
 - May NOT contain: () , = ' <space>
 - Ground may be either 0, GND, !GND or GROUND

Element Naming Conventions

- Element Names:
 - Names must begin with an alphabetic character, but thereafter can contain numbers and the following characters:
! # \$ % * + - / < > [] _
 - Names can be up to 1024 characters long
 - Names are not case sensitive
 - Element instances begin with the element key letter
 - Subcircuit instance names begin with X

Parameter Naming Conventions

- Parameter Names:
 - Follow the name syntax rules except that names must begin with an alphabetic character
 - The other characters must be either a number, or one of these characters:
! # \$ % [] _

Units and Scale factors

- Element units:
 - R - ohm
 - C - Farad
 - L - Henry
- Technology Scaling:
 - SCALE and SCALM
 - ALL lengths and widths are in METERS
- Common conversion factors
 - MIL(S) = 25.4e-6
 - FT = .3048 (METERS)
 - DB = 20log10
- Scale Factors
 - A = 1e-18
 - F = 1e-15
 - P = 1e-12
 - N = 1e-9
 - U = 1e-6
 - M = 1e-3
 - K = 1e3
 - MEG = X = 1e6
 - G = 1e9
 - T = 1e12

Circuit Elements


- Passive components
 - R, C, L, etc.
- Sources
 - Independent sources
 - DC, AC, TRAN (pulse, pwl, pattern, pseudo random bit stream, sin, AM, exp, single frequency frequency modulated), Mixed, Digital
 - Dependent sources
 - G (voltage controlled current source), E (voltage controlled voltage source), F (current controlled voltage source), H (current controlled current source)
- Active Elements
 - D, M, Q, J (need a .MODEL)

Subcircuits

- Subcircuit definition syntax:
`.SUBCKT subnam n1 n2 [n3 n4 ...] [parnam=val ...]`
 - **subnam** – Reference name for the subcircuit model call
 - **n1, n2 ...** - Node numbers for external reference
 - Any element nodes appearing in the subcircuit, but not included in this list, are strictly local, EXCEPT
 - Ground node (0)
 - Nodes assigned using BULK (MOSFET) or SUBSTRATE (BJT)
 - Nodes assigned using the **.GLOBAL** statement
 - **parnam=val** - A parameter name set to a value
 - For use only in the subcircuit
 - Overridden by an assignment in the subcircuit call or by a value set in a **.PARAM** statement that is external to the subcircuit

Subcircuit Example

- Inverter Example

 

Output Variables:

```
.PRINT I(X1.M1)
.PRINT V(X1.99)
.PRINT V(1) $ IN and OUT replaced by nodes 1 and 2, respectively
.PRINT TRAN ISUB(X1.IN) $ PRINT subcircuit pin current
```

Analysis Types

- DC Operating Point
- DC Analysis
- AC Analysis
- Transient Analysis
- Temperature Analysis

Output Commands

- .PROBE:
 - Save output variables in analysis data file without additional output in the output listing file
 - With option probe, can limit *.tr# file size
- .PRINT:
 - Numeric analysis results printed to output listing file
- .MEASURE:
 - Print numeric results of measured electrical specifications for specified analysis

Examples:

.PROBE tran v(4) i(vin) par('v(out)/v(in)')

.PRINT AC VM(4,2) VP(8,3) VR(7) Ii(R1)

→ .PRINT LX8(m1)

→ Print the drain-source conductance of element m1

Limiting the size of the output data

- Specifying analysis data format:
 - .OPTION POST —————> Generate binary output waveform files
- Limiting the size of the analysis data file:
 - .OPTION PROBE
 - ALL nodes plotted by default
 - Limit data in analysis data file to that specified in .PRINT and .PROBE statements
 - .OPTION INTERP
 - Limit the number of points stored to step size specified in .TRAN statement
 - Pre-interpolates the output to the interval specified on the .TRAN statement

Limiting the size of the output data

- Summary:

Netlist Input File, *.sp	Waveform File, *.tr0
.option post	→ All nodes and points
.option post probe	→ Fewer nodes
.option post interp	→ Fewer points per node

Output Variables

- Five Groups of Output Variables:
 - DC and transient analysis
 - Displays individual nodal voltages, branch currents, element power dissipation
 - AC analysis
 - Displays imaginary and real components of nodal voltage, branch current
 - Displays phase and impedance parameters
 - Element templates
 - Displays element specific nodal voltages, branch currents, element parameters, and the derivatives of element voltage, current, or charge
 - .MEASURE
 - Displays user-defined variables as specified in the .MEASURE statement
 - Parametric statements
 - Displays mathematically, user-defined expressions operating on nodal voltages, etc

Output Variables: Examples

- DC and Transient output examples:
 - Standard form is $V(\text{node})$ or $I(\text{element})$
 - v(1)**
 - Voltage at node 1
 - i(Rin)**
 - Current through R_{in} (direction of I is n1 to n2)
 - v(1,2)**
 - Voltage between node 1 and node 2 (differential)
 - Complex addressing
 - i1(xinv1.m3)**
 - Drain current of transistor m3 in subcircuit inv1

Output Variables: Examples

- DC and Transient output examples (cont.)

p(rload)

– Power dissipated in rload at point of analysis

p(m1)

– Power dissipated in transistor m1 at point of analysis

Power

– Total power dissipation output at point of analysis

v(x3.5)

– Voltage at INTERNAL node 5 of subckt x3

par('p(x1.m1)+p(x2.m2)')

– Sum of power in m1 of x1 and m2 of x2

i3(2:q2)

– Emitter current of q2 in second subcircuit called

Output Variables: Examples

- AC analysis output examples:

`vi(2)`

– Imaginary voltage component at node 2

`ip1(q4)`

– The phase of the collector current in q4

`vdb(2,8)`

– The voltage ratio between node 2 and 8 in decibels

`vp(4,6)`

– The arctangent [$vi(4,6)/vr(4,6)$]

`vp(6)`

– Phase at node 6

ACOUT option (1/2)

- ACOUT controls the AC output calculation method, for the difference in values of magnitude, phase, and decibels:
 - ACOUT = 1 (default) selects HSPICE method, which calculates the difference of the magnitudes of the values
 - Real and imaginary
 - $VR(N1, N2) = \text{REAL}[V(N1, 0)] - \text{REAL}[V(N2, 0)]$
 - $VI(N1, N2) = \text{IMAG}[V(N1, 0)] - \text{IMAG}[V(N2, 0)]$
 - Magnitude
 - $VM(N1, 0) = [VR(N1, 0)^2 + VI(N1, 0)^2]^{0.5}$
 - $VM(N2, 0) = [VR(N2, 0)^2 + VI(N2, 0)^2]^{0.5}$
 - $VM(N1, N2) = VM(N1, 0) - VM(N2, 0)$
 - Phase
 - $VP(N1, 0) = \text{ARCTAN}[VI(N1, 0) / VR(N1, 0)]$
 - $VP(N2, 0) = \text{ARCTAN}[VI(N2, 0) / VR(N2, 0)]$
 - $VP(N1, N2) = VP(N1, 0) - VP(N2, 0)$
 - Decibel
 - $VDB(N1, N2) = 20 \cdot \text{LOG10}(VM(N1, 0) / VM(N2, 0))$

ACOUT option (2/2)

Berkeley SPICE method

- ACOUT = 0 selects SPICE method, which calculates the magnitude of differences
- Real and imaginary

$$VR(N1, N2) = \text{REAL}[V(N1, 0) - V(N2, 0)]$$

$$VI(N1, N2) = \text{IMAG}[V(N1, 0) - V(N2, 0)]$$

- Magnitude

$$VM(N1, N2) = [VR(N1, N2)^2 + VI(N1, N2)^2]^{0.5}$$

- Phase

$$VP(N1, N2) = \text{ARCTAN}[VI(N1, N2) / VR(N1, N2)]$$

- Decibel

$$VDB(N1, N2) = 20 \cdot \text{LOG10}[VM(N1, N2)]$$

ACOUT Example

```
.option ACOUT=1
v1 1 0 ac .5
v2 0 2 ac .5
r1 1 0 1k
r2 2 0 1k
.print ac Vm(1) vm(2) vm(1,2) vp(1,2)
```

- output:
0.5 0.5 0 180
- If we change to .option ACOUT=0 then
0.5 0.5 1 0

Output Variables: Element Templates

- Element Templates:
 - Display element specific nodal voltages, branch currents, element parameters and the derivatives of element voltage, current, and charge

Examples:

- `.print tran lv16(m3)`
- Prints the effective drain conductance ($1/r_{deff}$)

There are over hundred element templates: check documentation

Output variables: .MEASURE

- .MEASURE
 - Prints user-defined electrical specifications of a circuit
 - Used extensively in optimization
 - Has seven fundamental measurement modes, each with its own form:
 - Rise, fall, and delay
 - Average, RMS, min, max, and P-P
 - Find - When
 - Equation evaluation
 - Derivative evaluation
 - Integral evaluation
 - Relative error

.MEASURE Examples

- Measure delay from 2nd rising edge of node 1 to 2nd falling edge of node 2:

```
.MEAS TRAN TDELAY TRIG V(1) VAL=2.5 TD=10ns RISE=2  
+ TARG V(2) VAL=2.5 FALL=2
```

- Measure the average voltage of node 10 between 10ns and 55ns:

```
.MEAS TRAN avgval AVG V(10) From=10ns To=55ns
```

- Measure the time of the 5th rise of node "osc_out" at 2.5v and report as "r5":

```
.MEAS TRAN r5 WHEN V(osc_out)=2.5v RISE=5
```

- Measure v(out) when v(in)=40m, then store and print variable "result":

```
.MEAS TRAN result FIND v(out) WHEN v(in)=40m
```

- Make a calculation on previously measured values:

```
.MEAS TRAN my_result PARAM='(result/avgval)'
```

Output variables: Parametric Output

Parametric Variables are waveform vectors

- Parametric Output Variables:

- . PRINT tran PAR('algebraic expression')
 - . PRINT tran out_var=PAR('algebraic expression')

Examples:

- . PRINT dc conductance=PAR('i(m1)/v(22)')
 - . PROBE tran PAR('log10(i(xff4.m1))')
 - . PRINT tran vds=PAR(vds) vgs=PAR(vgs)

Commonly used .OPTIONS

See the Command Reference for a complete list of options

<u>Listing</u>	<u>Output</u>	<u>Model</u>	<u>Transient</u>
ACCT	CAPTAB	SCALE	<u>Accuracy</u>
BRIEF	DCCAP	SEARCH	RUNLVL
INGOLD	UNWRAP	TNOM	ACCURATE
LIST			
NODE	<u>Error</u>	<u>MOSFETs</u>	<u>Efficiency</u>
NOMOD	BADCHR	SCALM	AUTOSTOP
NUMDGT	DIAGNOSTIC	WL	NOELCK
OPTLST			NOTOP
<u>Interface</u>	<u>Convergence</u>	<u>DC Matrix</u>	<u>Time Step</u>
ARTIST	CONVERGE	ITL1	DELMAX
PSF	DV		METHOD
CSDF	GMIN		
POST	GMINDC		
PROBE	GRAMP		

General Listing Options

.option LIST

- Prints a list of netlist elements, node connections and, parameter values
- Prints effective sizes of elements and key values
- Useful in diagnosing topology-related problems

.option NODE

- Prints a node connection table
- The nodal cross-reference table lists each node and all the elements connected to it
- Useful in diagnosing topology related non-convergence problems

.option ACCT

- Reports job accounting and runtime statistics at the end of the output listing
- Useful in observing simulation efficiency

.option OPTS

- Reports settings of all .OPTIONS in the listing file

More listing file options

- Simulation listing can get large:
- .OPTION nomod
 suppress the printout of model parameters
- .OPTION BRIEF
 suppress the printout of the netlist
- But ... if you have troubles, remove the nomod and brief options so you can see all information

More listing file options

`.option INGOLD=value`

- Controls the format of numbers in printouts
 - 0 – engineering format (default)
 - 1 – mix of fixed and exponential format
 - 2 – exponential format

`.option NUMDGT=value`

- Number of significant digits printed for output variables
 - Range is between 1 to 10
 - Defaults is 4

Output Control Options

- POST (syntax: .OPTION POST)
Save simulation results for a waveform viewer
- PROBE (syntax: .OPTION PROBE)
Limit the waveforms generated
- POSTTOP
 - Limits data written to waveform file to top-level nodes only
- Syntax
.OPTION POSTTOP
- POSTLVL
 - Limits data written to waveform file that only a specified level of nodes signals will be saved
- Syntax
.OPTION POSTLVL=*n*
 - *n*=1 top level only
 - *n*=0 all levels, i.e., POSTLVL option is turned off

Netlist Options (1/2)

- GLOBAL SCALE
 - Scale element geometric instance parameters whose default unit is meters.
- SYNTAX

.option scale=value

Example:

```
.option scale=1e-6
M1 Vdd 10 20 0 mymodel L=1u w=1u    $ L=1e-12, W=1e-12
M2 Vdd 10 20 0 mymodel L=1 w=1        $ L=1e-6, W=1e-6
C1 Vdd 10 capmod L=0.1 W=0.1         $ L=1e-7, W=1e-7
R1 20 0 resmod L=1 W=1                $ L=1e-6, W=1e-6
```

Netlist Options (2/2)

- LOCAL SCALE
 - Scale passive device values

Examples:

```
R1 1 0 1k scale=10      $ R1=10K  
C1 5 0 1u scale=10      $ C1=10u  
L1 10 0 1u scale=10     $ L1=10u
```

Model Options (1/2)

- GLOBAL SCALM
 - Affects model parameters with units in METERS
 - Scales active devices (MOSFETs, diodes, JFETs etc.)
 - Passive devices are not affected by scalm
 - Local scalm takes precedence over global
 `.option scalm`
- SYNTAX:
`.option scalm=value`

Example:

```
.option scalm=1e-6
```

Model Options (2/2)

- LOCAL SCALM
 - Affects model parameters with the units of meters

Example:

```
M1 Vdd 10 20 0 mymodel L=1u w=1u
.model mymodel nmos scalm=1e-6 level=2
+ tox=1e-1 kp=2.0e-5
```

- Only model parameters tox will be scaled
`tox=1e-7`
- L and W will not be affected

Options for Simulation Efficiency

.option AUTOSTOP

- Stops a transient analysis in HSPICE after calculating all TRIG-TARG, FIND-WHEN, and FROM-TO measure functions
 - Special interest when testing corners

.option NOELCK

- Bypasses element checking to reduce pre-processing time

.option NOTOP

- Suppresses topology checks to increase the speed for pre-processing

NOT RECOMMENDED !!!

Circuit Simulation with SPICE

SPICE Simulation

- Introduction to SPICE
- DC Analysis
- Transient Analysis
- Subcircuits
- Optimization
- Power Measurement
- Design Corners

Introduction

- **S**imulation **P**rogram with **I**ntegrated **C**ircuit **E**mphasis
 - Developed in 1970's at Berkeley
 - Many versions are available
 - HSPICE is a robust commercial industry standard
 - Has many enhancements that we will use
- Written in FORTRAN for punch-card machines
 - Circuits elements are called *cards*
 - Complete description is called a SPICE *deck*


Writing SPICE Decks

- Writing a SPICE deck is like writing a program
 - Plan: sketch schematic on paper or in editor
 - Whenever possible, “modify” existing decks
 - Code: strive for clarity
 - Start with name, date, purpose
 - Comment, comment, comment ...
 - Drive the tool (avoid SPICE monkeying):
 - Predict what results should be
 - Compare with actual
 - *Garbage In, Garbage Out!*

Example: A simple RC circuit

```
* rc.sp
* Created David.Harris@hmc.edu - 2/2/03,
* Modified ctalarico@ewu.edu - 9/17/11
* Find the response of RC circuit to rising input
*-----
* Parameters and models
*-----
.option post brief nomod
*-----
* Simulation netlist
*-----
Vin in      gnd  pwl  0ps 0 100ps 0 150ps 1.0 1ns 1.0
R1 in      out  2k
C1 out      gnd  100f
*-----
* Analysis
*-----
.tran 20ps 1ns
.plot v(in) v(out)
.end
```

Result (Graphical)

 

Sources (for digital design)

- DC Source

```
vdd vdd gnd 2.5
```

- Piecewise Linear Source


```
PWL t1 v1 t2 v2 ...
```

```
Vin in gnd pwl 0ps 0 100ps 0 150ps 1.0 1ns 1.0
```

- Pulsed Source

```
Vck clk gnd PULSE 0 1.0 0ps 100ps 100ps 300ps 800ps
```

```
PULSE v1 v2 td tr pw per
```

 

SPICE Elements

Letter	Element
R	Resistor
C	Capacitor
L	Inductor
K	Mutual Inductor
V	Independent voltage source
I	Independent current source
M	MOSFET
D	Diode
Q	Bipolar transistor
W	Lossy transmission line
X	Subcircuit
E	Voltage-controlled voltage source
G	Voltage-controlled current source
H	Current-controlled voltage source
F	Current-controlled current source

SPICE Units

Letter	Unit	Magnitude
a	atto	10^{-18}
f	femto	10^{-15}
p	pico	10^{-12}
n	nano	10^{-9}
u	micro	10^{-6}
m	milli	10^{-3}
k	kilo	10^3
x or meg	mega	10^6
g	giga	10^9

- Example:
100 femtoFarad capacitor = 100fF = 100f = $100e-15$

DC Analysis

```
* mosiv.sp
* nMOS I-V Characteristics


*-----
* Parameters and models
*-----

.include '../mosistsmc180/mosistsmc180.sp'
.temp 70
.option post brief nomod
*-----
* Simulation netlist
*-----



*nmos
Vgs g gnd 0
Vds d gnd 0
M1 d g gnd gnd NMOS W=360n L=180n

*-----
* Analysis
*-----

.dc Vds 0 1.8 0.05 SWEEP Vgs 0 1.8 0.2
.probe i(m1)
.end
```

 

nMOS I-V Characteristics (Result)

  

MOSFET Elements

M element for MOSFET

Mname drain gate source body type


- + W=<width> L=<length>
- + AS=<area source> AD = <area drain>
- + PS=<perimeter source> PD=<perimeter drain>

Transient Analysis

```
* inv.sp
*-----
* Parameters and models
*-----
.param SUPPLY=1.8
.option scale=90n
.include '../mosistsmc180/mosistsmc180.sp'
.temp 70
.option post brief nomod

*-----
* Simulation netlist
*-----
Vdd vdd gnd 'SUPPLY'
Vin a gnd DC 0 PULSE 0 'SUPPLY' 50ps 1ps 1ps 99ps 200ps
M1 y a gnd gnd NMOS W=4 L=2
+ AS=20 PS=18 AD=20 PD=18
M2 y a vdd vdd PMOS W=8 L=2
+ AS=40 PS=26 AD=40 PD=26

 *-----
* Analysis
*-----
.tran 0.1ps 250ps
.end
```





$\lambda=90\text{n}$

$W=360\text{n}; L=180\text{n}$

$W=720\text{n}; L=180\text{n}$

Transient Analysis Results

  - Unloaded inverter with fast edges
 - Overshoot



MOSFET Junction Capacitances



 
 




FIGURE 2.22 Substrate to diffusion diodes in CMOS circuits

 

 Area and Side Wall Perimeter of the diffusion regions


  
```
M1 y a gnd gnd NMOS W='N' L=2
+ AS='N*5' PS='2*N+10' AD='N*5' PD='2*N+10'
M2 y a vdd vdd PMOS W='P' L=2
+ AS='P*5' PS='2*P+10' AD='P*5' PD='2*P+10'
.ends.subckt inv a y N=4 P=8
```




Make sure to check MOS model LEVEL and ACM

Don't forget we
are using .SCALE

$$AD = AS = W \times D; PD = PS = 2W + 2D$$


$$AD = AS = 5W\lambda^2; PD = PS = (2W + 10)\lambda$$

MOSFET Capacitances

 


C_{gc} modeled through C_{gs} and C_{gd}


C_{cb} modeled through C_{gb}

 



Inverter Delay Calculation (1/3)

 

 C_{sb} shorted, C_{gb} negligible
What about C_{gd} ?



Inverter Delay Calculation (2/3)

  


$$C_{out} = C_{dbn1} + C_{dbp1} + C_{wire} + C_{gsn2} + C_{gsp2}$$

Before the step voltage is applied, $V_A=0$, N_1 is OFF, P_1 is ON and $V_B=V_{DD}$.

After the step, N_1 turns ON and it is initially in saturation ($V_{ds1}=V_{DD} > V_{gs1}-V_t=V_{DD}-V_t$) and later as V_B drops below $V_{DD}-V_t$ it enters linear region.

$$-I_{dn1} = C_{out} \frac{dV_B}{dt}$$

Delay Calculations (3/3)

 

C_{sb} shorted, C_{gb} negligible.

What about C_{gd} ?


 
 




FIG 2.14 Capacitances of an MOS transistor

$$C_{gd} = C_{gdP1} + C_{gdN1}$$

$$C_{gs} = C_{gsp1} + C_{gsn1}$$

 

Bootstrapping (Miller Effect)

  


$$A_v = \frac{V_{out}}{V_{in}}$$

$$C'_{gd} = C_{gd}(1 - A_V)$$

$$C''_{gd} = C_{gd} \left(1 - \frac{1}{A_V}\right)$$

Factors affecting delay ? (1/3)

- Output capacitance


 


$$C_{\text{out}} = C_{\text{dbn}1} + C_{\text{dbp}1} + C_{\text{wire}} + C_{\text{gsn}2} + C_{\text{gsp}2}$$

Factors affecting delay ? (2/3)

- Slope of the input waveform
(a.k.a. input slew rate)

  As the gate voltage changes so does the capacitance (the transistors go through different operating modes, before turning fully ON or OFF)



Factors affecting delay ? (3/3)

- Bootstrapping
the effect of C_{gd} on gate capacitance is effectively doubled

 
 
 


FIGURE 4.28 The effect of bootstrapping on inverter delay and waveform shape

more on Bootstrapping ...

- The extra capacitance has greater effect when connected between input and output (feedback) as compared to when it is connected between input and ground.
- Because C_{gd} is fairly small, bootstrapping is only a mild annoyance in digital circuits.
- However if the inverter is biased in its linear region near $VDD/2$ the C_{gd} is multiplied by the large gain of the inverter (this is of major importance in analog circuits)

Other factors affecting delay ...


- Arrival time at multiple-input gates
- Velocity saturation
- Supply voltage dependence
- Gate-to-source (rather than gate to gnd) capacitance
- We'll see the details later ...

Subcircuits


- Declare common elements as subcircuits

```
.subckt inv a y N=4 P=8
M1 y a gnd gnd NMOS W='N' L=2
+ AS='N*5' PS='2*N+10' AD='N*5' PD='2*N+10'
M2 y a vdd vdd PMOS W='P' L=2
+ AS='P*5' PS='2*P+10' AD='P*5' PD='2*P+10'
.ends
```

 - Example: Fanout-of-4 Inverter Delay
 - Reuse inv
 - Shaping
 - Loading



FO4 inverter delay

 

X1	a	b	inv	N=4	P=8	*shape input waveform
X2	b	c	inv	N=16	P=32	*reshape input waveform
X3	c	d	inv	N=64	P=128	*DUT
X4	d	e	inv	N=256	P=512	*load
X5	e	f	inv	N=1024	P=2048	*slow down switching rate of e

FO4 inverter delay

```

* fo4.sp
* David_Harris@hmc.edu 2/16/05
* Modified C. Talarico 9/30/11
• Delay (typ) of FO4 inverter in TSMC 180nm process

***** Parameters and models
.param SUPPLY=1.8
.param H=4
.option scale=90n
.include '../mosistsmc180/mosistsmc180.sp'
.option post nomod brief

***** Subcircuits
.global vdd gnd

.subckt inv a y N=4 P=8
M1      y      a      gnd      gnd      nmos      W='N'      L=2
+ AS='N*5'  PS='2*N+10' AD='N*5'  PD='2*N+10'
M2      y      a      vdd      vdd      pmos      W='P'      L=2
+ AS='P*5'  PS='2*P+10' AD='P*5'  PD='2*P+10'
.ends


***** Simulation netlist
Vdd      vdd      gnd      'SUPPLY'
Vin      a      gnd      PULSE    0 'SUPPLY' 0ps 20ps 20ps 220ps 480ps
X1      a      b      inv      * shape input waveform
X2      b      c      inv      M='H'      * reshape input waveform
X3      c      d      inv      M='H**2'   * device under test
X4      d      e      inv      M='H**3'   * load
x5      e      f      inv      M='H**4'   * load on load

***** Analysis and Measurements
*.tran 1ps 500ps
.measure tpdr                      * rising propagation delay
+    TRIG v(c) VAL='SUPPLY/2' FALL=1
+    TARG v(d)           VAL='SUPPLY/2' RISE=1
.measure tpdf                      * falling propagation delay
+    TRIG v(c)           VAL='SUPPLY/2' RISE=1
+    TARG v(d)           VAL='SUPPLY/2' FALL=1
.measure tpd param='(tpdr+tpdf)/2'   * average propagation delay
.measure trise                      * rise time
+    TRIG v(d)           VAL='0.2*SUPPLY' RISE=1
+    TARG v(d)           VAL='0.8*SUPPLY' RISE=1
.measure tfall                      * fall time
+    TRIG v(d)           VAL='0.8*SUPPLY' FALL=1
+    TARG v(d)           VAL='0.2*SUPPLY' FALL=1
.end

```

FIGURE 8.10 FO4 SPICE deck

FO4 inverter delay

 

Optimization

- HSPICE can automatically adjust parameters
 - Seek value that optimizes some measurement
- Example: Best P/N ratio
 - We've assumed 2:1 gives equal rise/fall delays
 - But we see rise is actually slower than fall
 - What P/N ratio gives equal delays?
- Strategies
 - (1) run a bunch of simulations with different P size
 - (2) let HSPICE optimizer do it for us

Optimization

P/N ratio

```

* fo4opt.sp
* David_Harris@hmc.edu 2/2/03
* Modified C. Talarico 9/30/11
* P/N ratio for equal rise/fall delay (typ)

***** Parameters and models
.option accurate
.param SUPPLY=1.8
.param H=4
.option scale=90n nomod brief
.include '../mosistsmc180/mosistsmc180.sp'
***** Subcircuits
.global vdd gnd
.subckt inv a y N=4 P=8
M1      y      a      gnd      gnd      NMOS      W='N'      L=2
+ AS='N*5'  PS='2*N+10' AD='N*5'  PD='2*N+10'
M2      y      a      vdd      vdd      PMOS      W='P'      L=2
+ AS='P*5'  PS='2*P+10' AD='P*5'  PD='2*P+10'
.ends
***** Simulation netlist
Vdd    vdd    gnd    'SUPPLY'
Vin    a      gnd    PULSE   0 'SUPPLY' 0ps 20ps 20ps 220ps 480ps
X1     a      b      inv     P='P1'      * shape input waveform
X2     b      c      inv     P='P1'      M=4      * reshape input waveform
X3     c      d      inv     P='P1'      M=16     * device under test
X4     d      e      inv     P='P1'      M=64     * load
X5     e      f      inv     P='P1'      M=256    * load on load
***** Optimization setup
.param P1=optrange(8,4,16)          * search from 4 to 16, guess 8
.model optmod opt itropt=30         * maximum of 30 iterations
.measure bestratio param='P1/4'     * compute best P/N ratio
***** Stimulus
*.tran 0.1ps 480ps SWEEP OPTIMIZE=optrange RESULTS=diff MODEL=optmod
*.tran 0.1ps 280ps SWEEP OPTIMIZE=optrange RESULTS=tpd MODEL=optmod
.measure tpdr                      * rising propagation delay
+      TRIG v(c)      VAL='SUPPLY/2' FALL=1
+      TARG v(d)      VAL='SUPPLY/2' RISE=1
.measure tpdf                      * falling propagation delay
+      TRIG v(c)      VAL='SUPPLY/2' RISE=1
+      TARG v(d)      VAL='SUPPLY/2' FALL=1
.measure tpd param='(tpdr+tpdf)/2' goal=0 * average prop delay
.measure diff param='tpdr-tpdf' goal = 0 * diff between delays
.end

```

Optimization Results

Best P/N ratio for lowest average delay is 1:1

```
.TITLE '* fo4opt.sp'
Index    p1      bestratio   tpdr       tpdf      tpd       diff      temper   alter#
1.0000  4.0000  1.0000    9.163e-11  5.860e-11  7.511e-11  3.303e-11  25.0000  1
```

Best P/N ratio for equal rise and fall delay is $\approx 2.84:1$

```
.TITLE '* fo4opt.sp'
index    p1      bestratio   tpdr       tpdf      tpd       diff      temper   alter#
6.0000  11.3522 2.8381    8.271e-11  8.270e-11  8.270e-11  2.192e-15  25.0000  1
```

Design Corners

- It is important to simulate circuits in multiple design corners to verify the correct operation of the circuit across variations in device characteristics (process variations) and environmental conditions (supply and temperature variations)

Design Corners

```
* Corner.sp
* Step response of unloaded unit inverter across
* design corners

***** Parameters and models
.options scale=90nm
.param SUP=1.8 *must be set before calling lib
.lib '../mosistsmc180/opConditions.lib' TT
.option post nomod brief

***** Simulation Netlist
Vdd vdd gnd 'SUPPLY'
Vin a gnd PULSE 0 'SUPPLY' 25ps 0ps 0ps 95ps 200ps
Mn y a gnd gnd NMOS W=4 L=2
+ AS=20 PS=18 AD=20 PD=18
Mp y a vdd vdd PMOS W=8 L=2
+ AS=40 PS=26 AD=40 PD=26

***** Analysis
.tran 0.1ps 250ps
.alter
.lib '../mosistsmc180/opConditions.lib' FF
.alter
.lib '../mosistsmc180/opConditions.lib' SS
.end
```

Design Corners

```
* opConditions.lib
* Example of OPCONDITIONS library

* TT: Typical nMOS, pMOS, voltage, temperature
.lib TT
.temp 70
.param SUPPLY='SUP'
.include 'modelsTT.sp'
.endl


* SS: Slow nMOS, pMOS, low voltage, high temperature
.lib SS
.temp 125
.param SUPPLY='0.9 * SUP'
.include 'modelsSS.sp'
.endl

* FF: Fast nMOS, pMOS, high voltage, low temperature
.lib FF
.temp 0
.param SUPPLY='1.1 * SUP'
.include 'modelsFF.sp'
.endl

* and so on ...
```

Design Corners

TT
FF
SS

 

Power Measurements

- HSPICE can measure power
 - Instantaneous $P(t)$
 - or average P over some interval

```
.print P(vdd)
.measure pwr AVG P(vdd) FROM=0ns TO=10ns
.measure charge INTEGRAL I(Vdd) FROM=0ns TO=10ns
.measure energy param='charge*SUPPLY'
```

Power Measurements

- Power in single gate
 - Connect to separate V_{DD} supply
 - When the input of a “logic gate” switches, it delivers power to the supply through the gate-to-source capacitances. Be careful to differentiate this input power from the power drawn by the “logic gate” discharging its internal and load capacitance