

NodeVr Example (Problem 4.4-5)

>> NodeVr

Enter Network Elements

Element 1: Vs, 1, 0, 12


Element 2: R1, 1, 2, 2

Element 3: R2, 2, 0, 2

Element 4: Is, 0, 2, 1

Element 5: CCVS, 1, 2, 3, R2

Element 6:

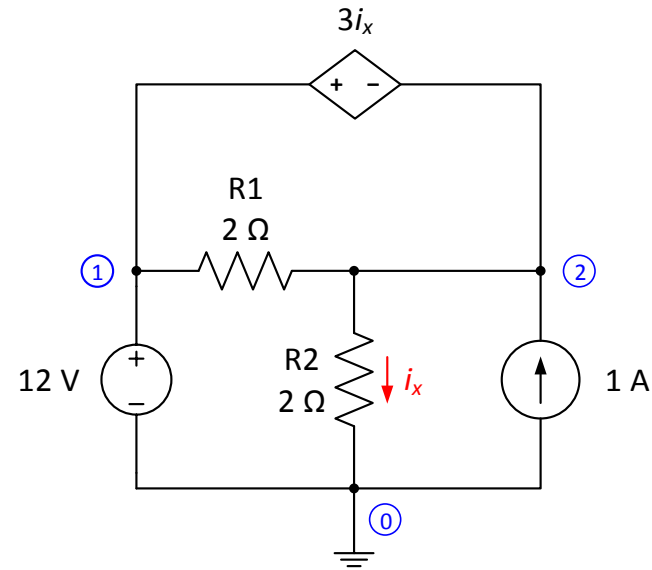

NODE VOLTAGES

Node	Voltage
0	Reference
1	12.000 V
2	4.800 V

SOURCES

Element	Value	NodeA	NodeB	Control	Voltage	Current	P supplied	
Vs	12.000 V	1	0		12.000 V	-1.400 A	16.800 W	
Is	1.000 A	0	2		-4.800 V	1.000 A	4.800 W	
CCVS	3.000 Ω	1	2	R2	7.200 V	-2.200 A	15.840 W	
							-----	37.440 W

PASSIVE ELEMENTS

Element	Value	NodeA	NodeB	Voltage	Current	P absorbed	
R1	2.000 Ω	1	2	7.200 V	3.600 A	25.920 W	
R2	2.000 Ω	2	0	4.800 V	2.400 A	11.520 W	
						-----	37.440 W

>> A

A =

0.5000	-0.5000	1.0000	0	1.0000	0
-0.5000	1.0000	0	-1.0000	-1.0000	0
1.0000	0	0	0	0	0
0	0	0	1.0000	0	0
1.0000	-1.0000	0	0	0	-3.0000
0	-0.5000	0	0	0	1.0000

>> B

B =

0
0
12
1
0
0

>> X

X =

12.0000
4.8000
-1.4000
1.0000
-2.2000
2.4000