

common source amplifier

- SPICE simulation

$$A_{v0} = 4.7 \text{ V/V}$$

$$f_{3dB} = 31.52 \text{ MHz}$$

$$I_D = I_B = 500 \mu\text{A}$$



$$V_{GS} = 1.39 \text{ V}$$

$$V_{th} = 0.5 \text{ V}$$

$$G_m = 1.12 \text{ mS}$$

$$G_{ds} = 40 \mu\text{S}$$
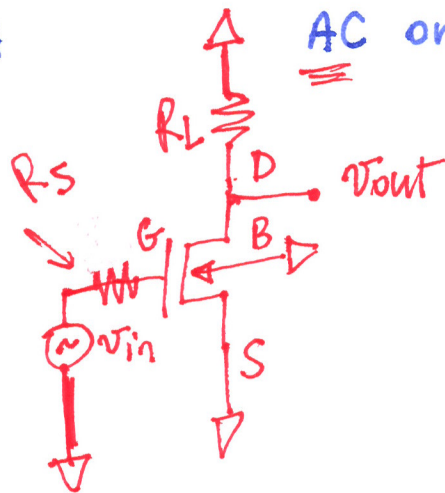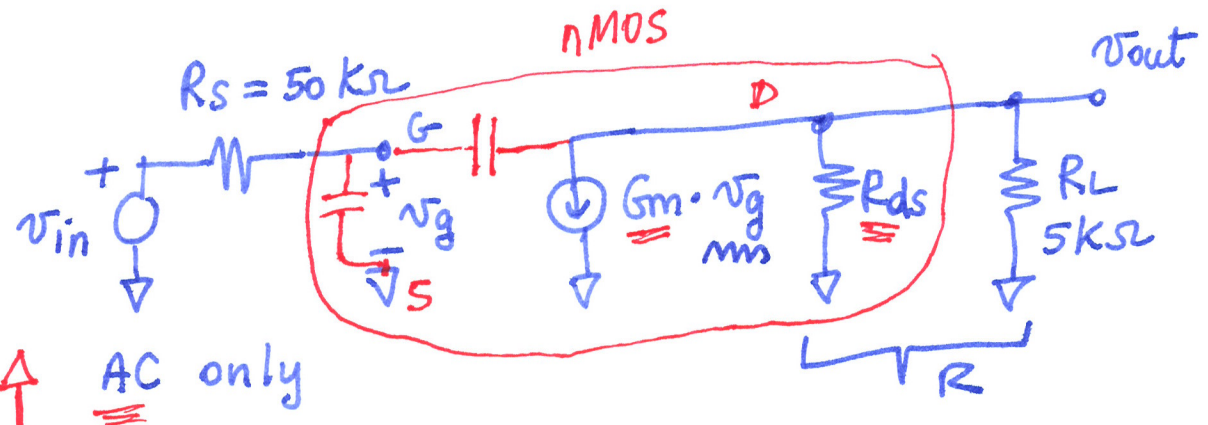
$$(R_{ds} = \frac{1}{G_{ds}} = 25 \text{ k}\Omega)$$



$$G_m = \frac{2I_D}{V_{GS} - V_{th}} \approx 1.12 \text{ mS}$$

$$G_{ds} \approx 1 \cdot I_D \approx 50 \mu\text{S}$$

$$R_{ds} = \frac{1}{G_{ds}} \approx 20 \text{ k}\Omega$$

$$A_{v0} = \left| \frac{v_{out}}{v_{in}} \right| = G_m \cdot R = 1.12 \text{ mS} \cdot 4 \text{ k}\Omega = 4.48 \text{ V/V}$$

