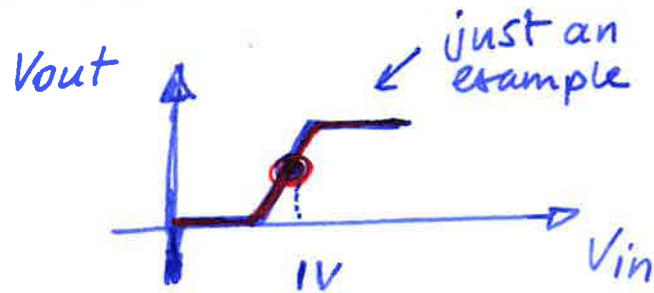


Example #6 - .TF simulation command


DC Transfer function



assuming input is voltage and output is voltage



op. amp based non-inverting ampl.

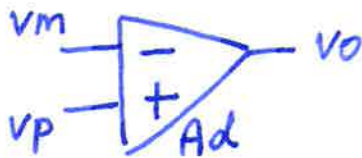

$$V_o = A_d (V_p - V_m)$$


$$A_d \rightarrow \infty$$


$$(V_p - V_m) \rightarrow 0$$

$$V_p - V_m \rightarrow 0$$



$$V_p = V_m$$

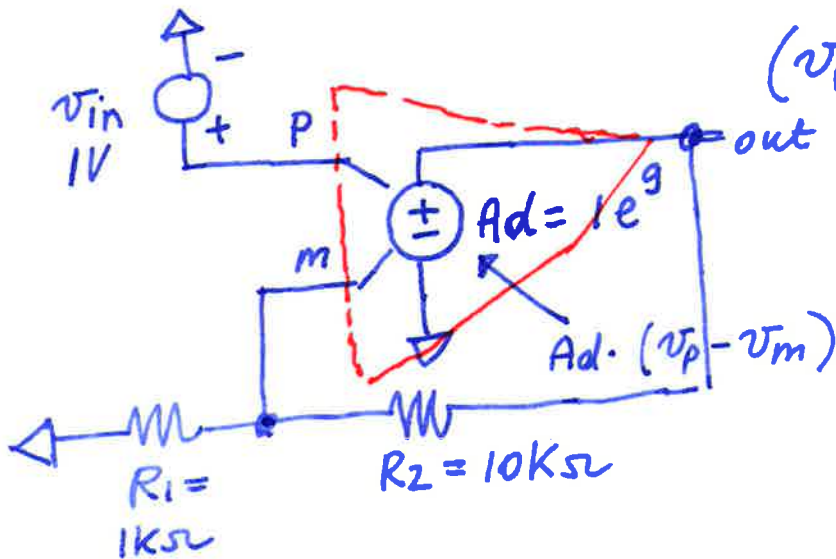

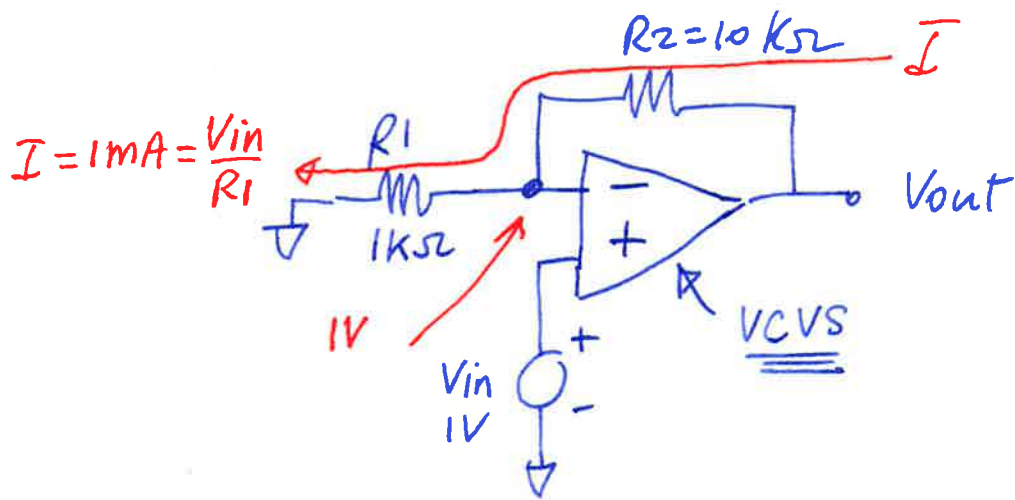

$$V_{out} - V_m = R_2 \cdot I$$

$$\downarrow$$

$$V_{out} - V_{in} = R_2 \cdot I$$

$$\downarrow$$


$$V_{out} - V_{in} = R_2 \cdot \frac{V_{in}}{R_1}$$

$$\downarrow$$



$$V_{out} = V_{in} \left(1 + \frac{R_2}{R_1} \right)$$

$$\downarrow$$
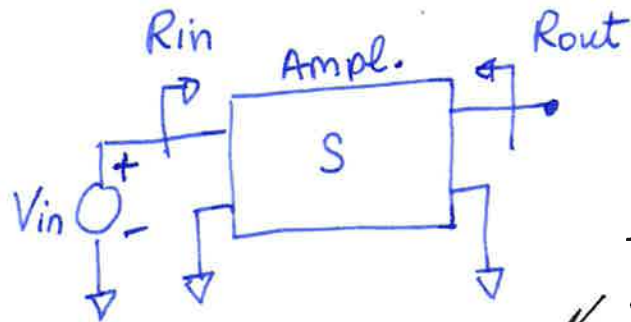
$$\frac{V_{out}}{V_{in}} = \left(1 + \frac{R_2}{R_1} \right) = 11$$



This ~~is~~ must be a short

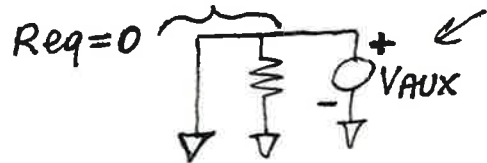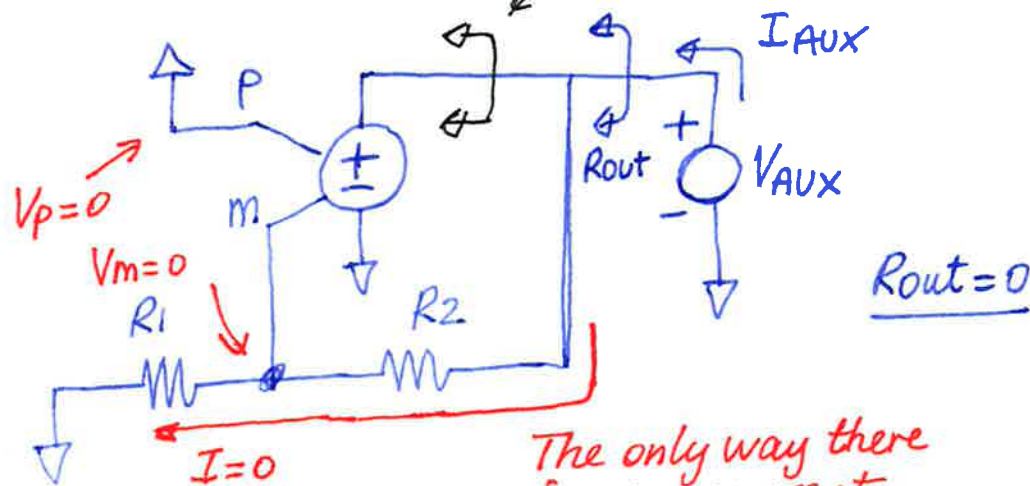

The only way there is no current flowing through R_1 and R_2 is if I_{AUX} is "shunted" by a short

$$\frac{V_{out}}{V_{in}} = 11 = A_{vamp.} \neq A_d$$

$$R_{in} = \infty \Omega$$

$$R_{out} = 0$$