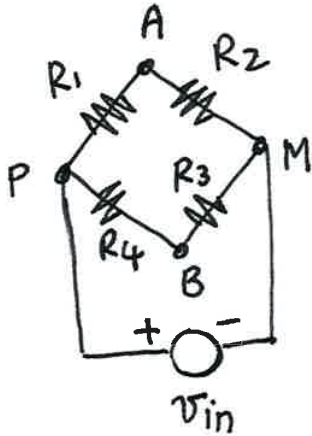


SYSTEMS OF EQUATIONS



WHEATSTONE BRIDGE

$$v_{in} = 1V$$

$$R_1 = 1k\Omega$$


$$R_2 = 4k\Omega$$

$$R_3 = 10k\Omega$$

$$R_4 = \frac{10}{4} k\Omega = 2.5k\Omega$$

$$i_t, i_b$$

$$v_1, v_2, v_3, v_4$$

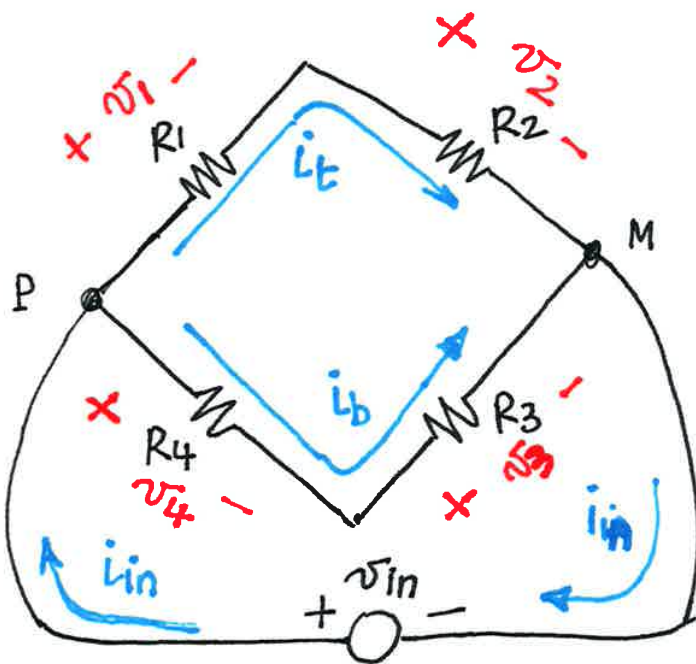

$$\begin{cases} v_{in} = R_3 i_b + R_4 i_b \\ v_{in} = R_1 i_t + R_2 i_t \end{cases}$$

↓

$$\begin{cases} v_{in} = (R_3 + R_4) \cdot i_b \\ v_{in} = (R_1 + R_2) \cdot i_t \end{cases}$$

$$i_b = \frac{v_{in}}{R_3 + R_4} = \frac{1V}{12.5K} = 0.08mA$$

$$i_t = \frac{V_{in}}{R_1 + R_2} = \frac{1V}{5K} = 0.2 \text{ mA} \quad i_b = 0.08 \text{ mA}$$

$$i_{in} = i_t + i_b = 0.28 \text{ mA}$$

$$\underbrace{R_1 + R_2}_{R_t} = R_t = 5K\Omega$$

$$\underbrace{R_3 + R_4}_{R_b} = R_b = 12.5K\Omega$$

$$V_1 = i_t \cdot R_1 = 0.2 \text{ V} \quad \left. \vphantom{V_1} \right\}$$

$$V_2 = i_t \cdot R_2 = 0.8 \text{ V} \quad \left. \vphantom{V_2} \right\}$$

$$V_3 = i_b \cdot R_3 = 0.8 \text{ V} \quad \left. \vphantom{V_3} \right\}$$

$$V_4 = i_b \cdot R_4 = 0.2 \text{ V} \quad \left. \vphantom{V_4} \right\}$$

$$\begin{cases} V_{in} = 5K \cdot i_t \\ V_{in} = 12.5K \cdot i_b \end{cases} \rightarrow \begin{cases} V_{in} = 5K \cdot i_t + 0 \cdot i_b \\ V_{in} = 0 \cdot i_t + 12.5K \cdot i_b \end{cases}$$


$$\rightarrow \begin{cases} 1 = 5K \cdot i_t + 0 \cdot i_b \\ 1 = 0 \cdot i_t + 12.5K \cdot i_b \end{cases} \quad \begin{matrix} b = A \cdot x \\ \uparrow \quad \uparrow \quad \uparrow \end{matrix}$$

$$\begin{bmatrix} 1 \\ 1 \end{bmatrix}_b = \begin{bmatrix} 5K & 0 \\ 0 & 12.5K \end{bmatrix}_A \begin{bmatrix} i_t \\ i_b \end{bmatrix}_x$$

$$\rightarrow x = A \setminus b$$

$$0.2 \text{ mA} = i_t$$

$$0.08 \text{ mA} = i_b$$

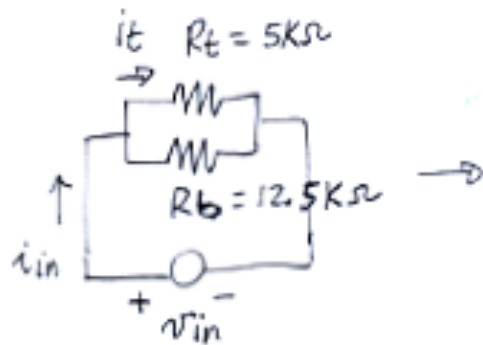


$$R_t \parallel R_b = R_{in} = \frac{R_t \cdot R_b}{R_t + R_b}$$

$$i_{in} = \frac{v_{in}}{R_{in}} = 0.28 \text{ mA}$$

$$i_t = \frac{i_{in}}{R_t + R_b} \cdot R_b \approx 0.2 \text{ mA}$$

$$i_b = i_{in} - i_t = 0.28 - 0.2 = 0.08 \text{ mA}$$

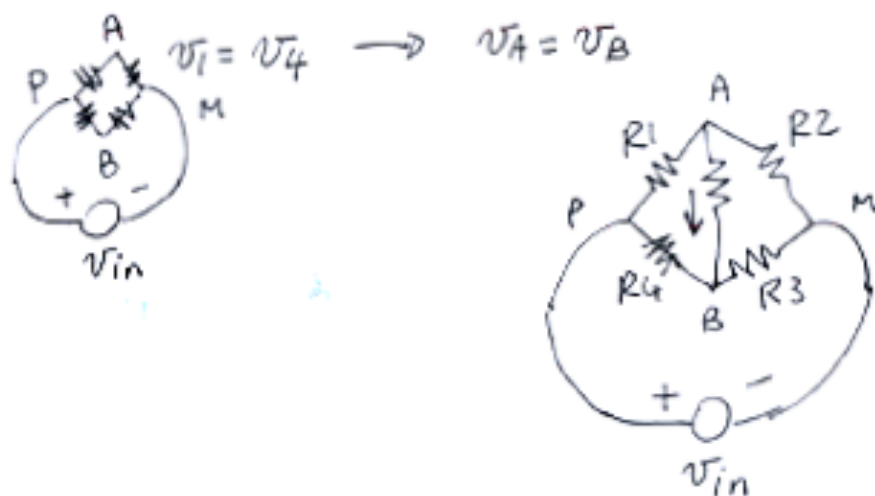- Let's try to gather some insight about the circuit



$$v_1 = v_4 \rightarrow v_A = v_B$$

$$v_1 = v_4$$



$$v_3 = v_2$$

$$v_3 = v_{in} - v_4$$

$$v_2 = v_{in} - v_1$$

$$v_1 = R_1 \cdot i_t = v_4 = R_4 \cdot i_b \rightarrow i_b = \frac{R_1}{R_4} \cdot i_t$$


$$v_3 = R_3 \cdot i_b = v_2 = R_2 \cdot i_t$$



$$R_3 \cdot \frac{R_1}{R_4} \cdot i_t = R_2 \cdot i_t \rightarrow$$

$$R_3 R_1 = R_2 R_4$$



BALANCED WHEAT.
BRIDGE

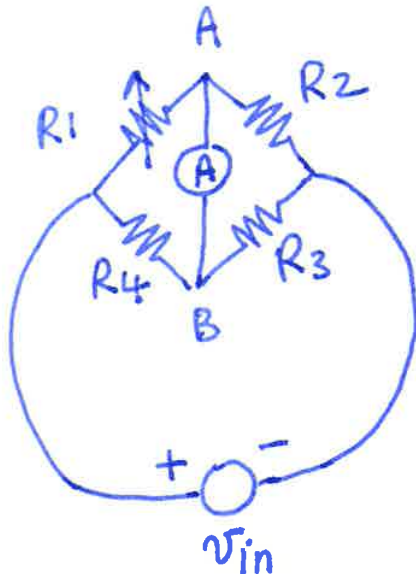

$$R_1 R_3 = R_2 R_4$$

$$R_3 = \frac{R_2 R_4}{R_1}$$

AMPLIFIER

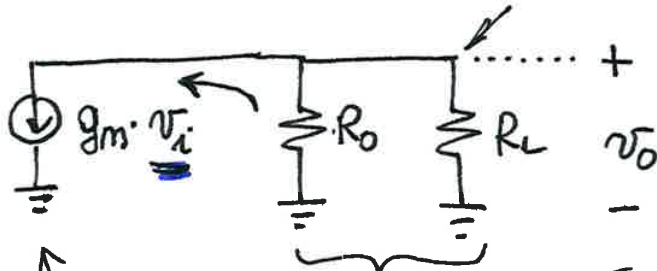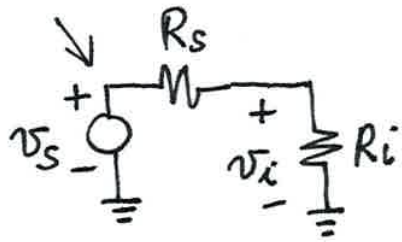

AMPLIFIER

$$\frac{v_o}{v_s} = ? = A_v$$

dependent current source controlled voltage

$$v_i = \frac{v_s}{R_s + R_i} \cdot R_i$$


$$R = R_o \parallel R_L$$


$$v_o = -g_m \cdot v_i \cdot R = -g_m \cdot v_i \cdot \frac{R_o R_L}{R_o + R_L}$$

$$A_v = \frac{v_o}{v_s} = -g_m \frac{R_o R_L}{R_o + R_L} \cdot \frac{R_i}{R_s + R_i}$$

for $R_o \rightarrow \infty$ $A_v \approx -g_m R_L \cdot \frac{R_i}{R_s + R_i}$

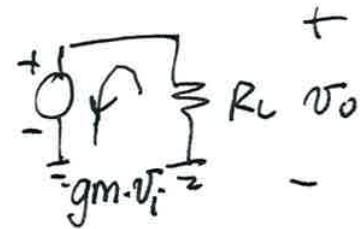$R_o \rightarrow \infty$ means ($R_o \gg R_L$)
in practice



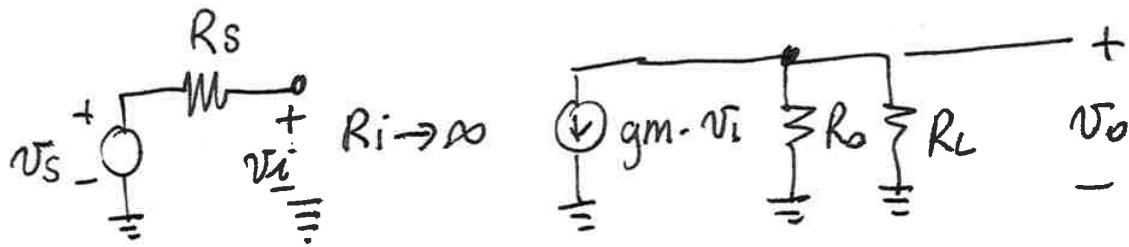

$$v_i = v_s \rightarrow A_v = -g_m \frac{R_L R_o}{R_L + R_o} \cdot \frac{R_i}{R_s + R_i} \approx -g_m \frac{R_L R_o}{R_L + R_o}$$

\uparrow
 $R_i \rightarrow \infty$

$R_i \rightarrow \infty$: in practice
 $R_i \gg R_s$