

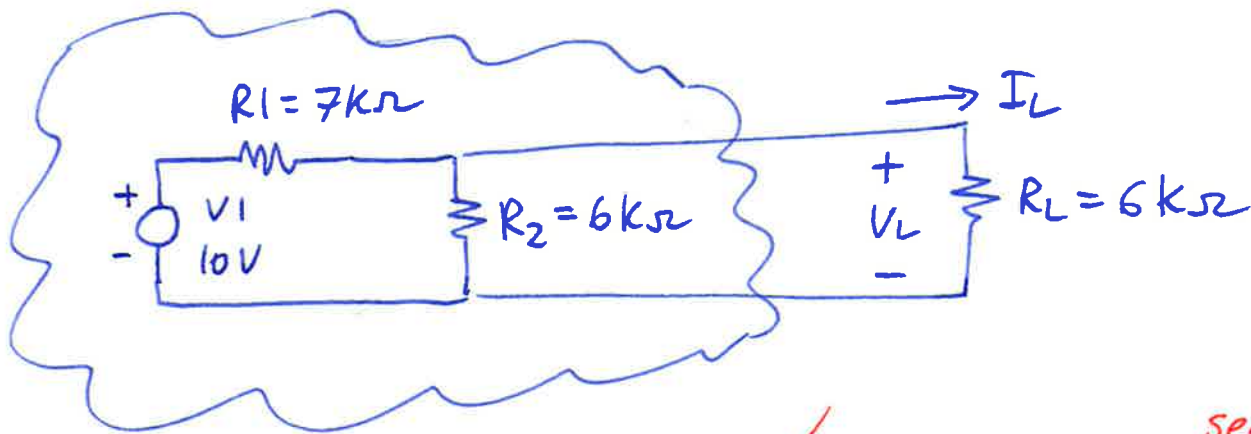
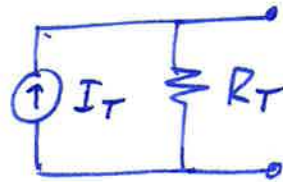
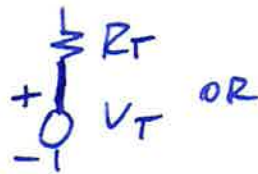



THEVENIN AND NORTON TRANSFORMATIONS

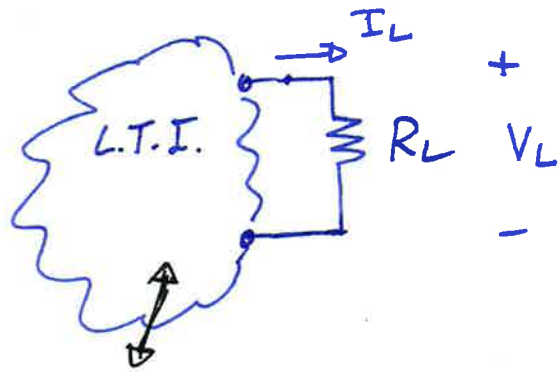

First attempt

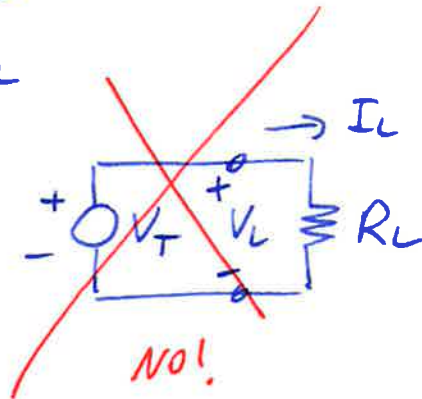


second attempt

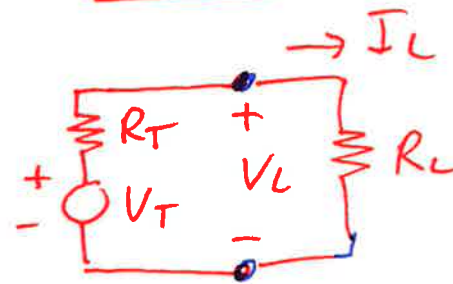

→ 2 cases (extremes)


• $R_L = \infty$

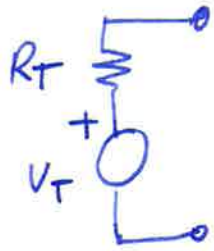

$$V_{open} = V_T$$


$$I_L = 0$$

• $R_L = 0$

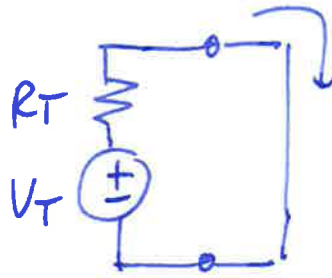

$$I_{short} = \frac{V_T}{R_T}$$

$$V_L = 0$$

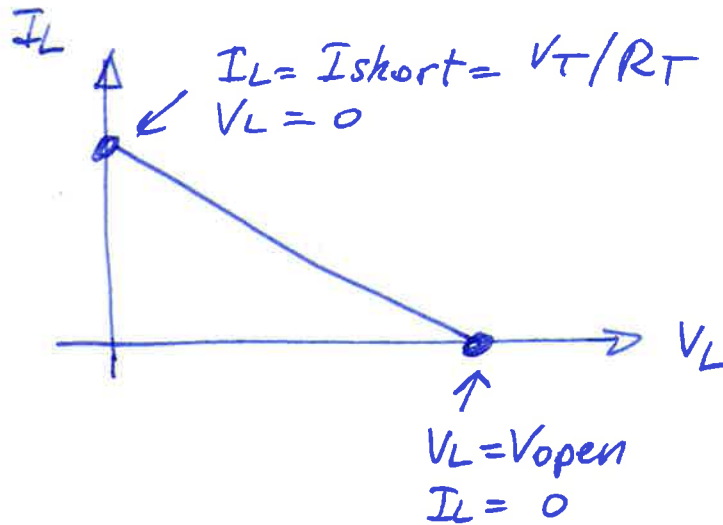

straight line between two points:


$$I_L - \frac{V_T}{R_T} = -\frac{1}{R_T} \cdot V_L$$

↓


$$I_L = -\frac{1}{R_T} V_L + \frac{V_T}{R_T}$$

$$(y = m \cdot x + n)$$

back to the example:

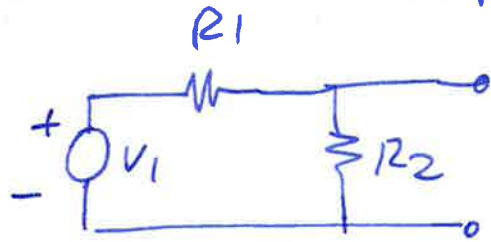

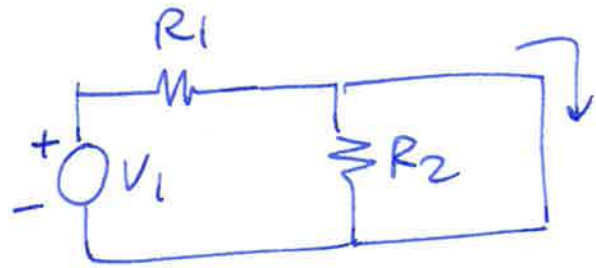
$$V_T = V_{open} = \frac{V_1}{R_1 + R_2} \cdot R_2 = 4.62 \text{ V}$$





$$I_{short} = \frac{V_T}{R_T} = \frac{V_1}{R_1} = \frac{10 \text{ V}}{7 \text{ k}\Omega} \approx 1.43 \text{ mA}$$

$$R_T = \frac{V_T}{I_{short}} = \frac{4.62 \text{ V}}{1.43 \text{ mA}} \approx 3.23 \text{ k}\Omega$$


Thevenin/Norton Transf. rules

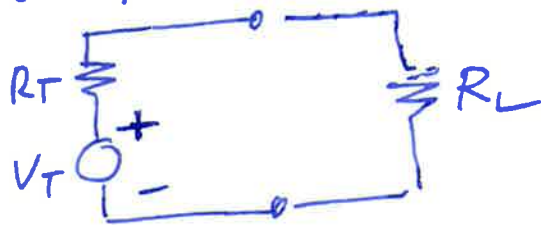


→ remove R_L to find out V_T

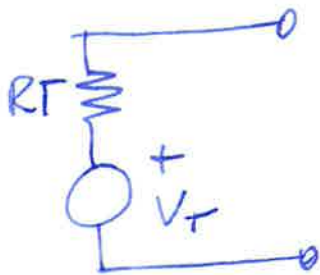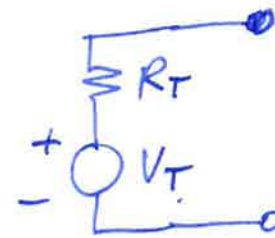

→ remove V_T and apply test voltage

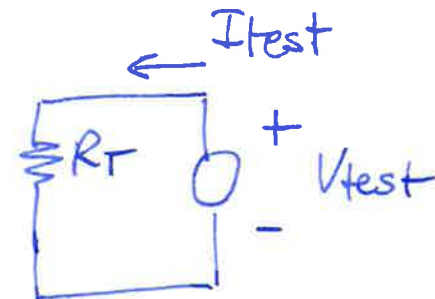

$$\frac{V_{test}}{I_{test}} = R_T$$

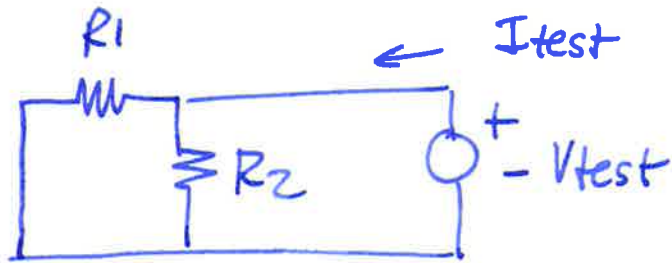

$V=0 \rightarrow$ replace indep. voltage source short

$I=0 \rightarrow$ replace indep. current source open

$$\frac{V_{test}}{I_{test}} = R_T = R_1 \parallel R_2 =$$

$$= 7k\Omega \parallel 6k\Omega \approx 3.23k\Omega$$

same as using ~~multimeter~~ a multimeter in a lab.
(shutdown the supply of the board)