 


# Gm over ID Methodology

## Design Optimization Example (CS with active load)

source: Drew Hall (Stanford University, 2011)



### 1. Objectives

- Illustrate the use of the gm/Id design methodology
- Design of a common source amplifier with a PMOS load
- Discuss biasing without relying on a voltage source


### 2. Specifications

- 0.18 $\mu$ m CMOS Technology
- $V_{DD} = 1.8V$
- $A_v = 30$  dB
- $P_{diss} = 2$  mW (neglecting bias)
- $C_L = 500$  fF
- Ratio of gm/ID of NMOS to PMOS must be 2 (for noise considerations)
- **Maximize the BW**

**Disclaimer:** This circuit would need feedback to properly set the output voltage. This ONLY works in simulation where we can control the offset! It is meant to illustrate the design process only.
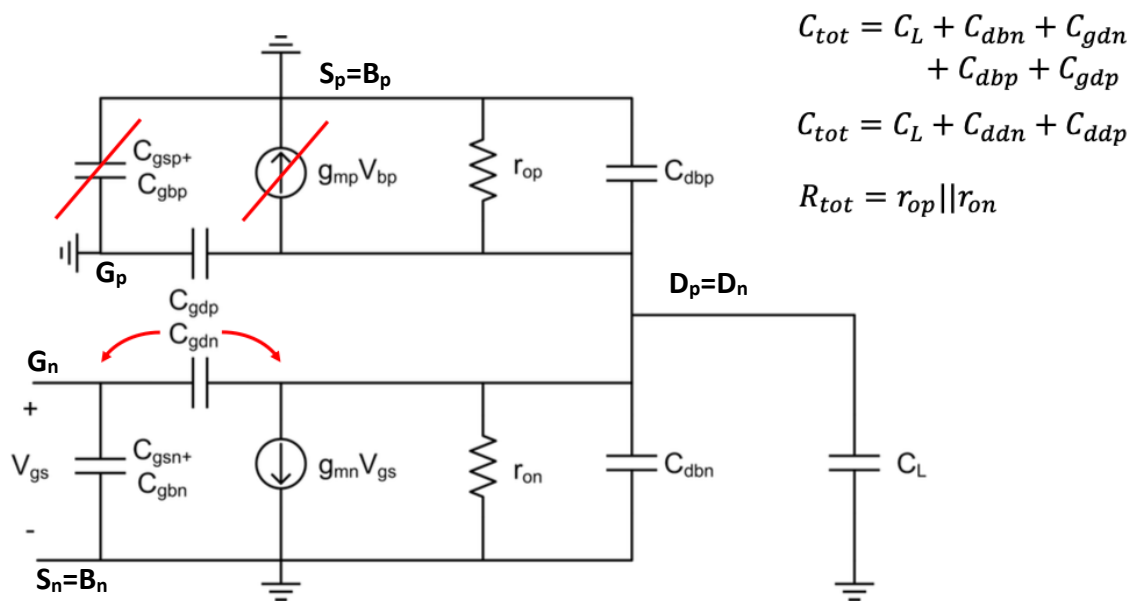
## Design – Small Signal Model

- Sketch out small signal model for transistors in the signal path
- The small signal circuit has a single pole at the output node (use Miller effect for  $C_{gdn}$ )



## Design Equations

- Small signal gain:

$$|A_v(0)| = g_{mn} R_{tot}$$

$$R_{tot} = r_{op} || r_{on}$$

- Small signal bandwidth:

$$BW = \frac{1}{2\pi} \frac{1}{R_{tot} C_{tot}}$$

↓  
Rewrite with  
primary gm/id  
design variables

$$R_{tot} = \frac{1}{\frac{1}{g_{mn} r_{on}} + \frac{1}{g_{mp} r_{op}}}$$

- Power consumption:

$$P_{wr} = V_{dd} I_d$$

- Area:

$$Area = W_p L_p + W_n L_n$$

## Design Flow

- 1) Calculate  $I_D$  from power specification
- 2) Calculate  $g_{mn}$  and  $g_{mp}$
- 3) Lookup  $r_{on}$
- 4) Calculate necessary  $r_{op}$  and find appropriate  $L_p$
- 5) Lookup  $I_D/W$  and size NMOS and PMOS transistors
- 6) Lookup  $f_t$  and calculate intrinsic capacitances
- 7) Calculate extrinsic capacitances
- 8) Calculate BW

### NOTE:

More than one design flow exists, this one comes from choosing  $g_m/I_{Dn}$  and  $L_n$  as the primary design variables

## MATLAB Design script

### Design\_CS\_PMOS\_Load\_Sweep.m

```
%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%
% original script:
% Drew Hall
% EE 214 (Winter 2011)
% 18 Jan 2011
%
% Design a common source amplifier with a PMOS load using the gm/id design
% methodology.
%
% modified script:
% Claudio Talarico
% EE406 9fall 2021)
% adapted to use toolkit v.2_3
%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%
clearvars;
close all;
clear all;
clc;

format short eng;

% Constraints
Pwr = 2e-3;           % Power dissipation [Watts]
Av_dB = 30;          % Gain [dB]      (Maximum 35 with this arch)
C_L = 500e-15;       % Load capacitance [Farads]
Vdd = 1.8;           % Supply Voltage [Volts]
k = 1/2;             % Ratio of (gm/id_p) / (gm/id_n);
```

```

% Primary Design Variables
gmid_n = (5:1:24);
Ln = (0.18:0.02:0.5); % REMEBBER: units of L are expressed in um

Area = zeros(length(gmid_n), length(Ln));
BW = zeros(length(gmid_n), length(Ln));

% Design a bunch of different amplifiers
for i = 1:length(gmid_n)
    for j = 1:length(Ln)
        [Area(i,j), BW(i,j)] = ...
            CS_PMOS_Load_function(Pwr, Av_dB, C_L, ...
                Vdd, k, gmid_n(i), Ln(j));
    end
end

% Plot
[X,Y] = meshgrid(Ln, gmid_n);

h = figure;
set(h, 'Name', 'Bandwidth', 'NumberTitle', 'off')
set(h, 'Position', [100 100 900 500]);
axes('LineWidth', 1.5, 'FontWeight', 'bold', 'FontSize', 10);
hold on;
set(gca, 'FontName', 'Arial Narrow', 'FontWeight', 'bold');
xlabel('L_n [\num]', 'FontSize', 12, 'FontWeight', 'bold');
ylabel('Gm/Id_n [S/A]', 'FontSize', 12, 'FontWeight', 'bold');
title('BW [MHz]', 'FontSize', 14, 'FontWeight', 'bold');

surf(X,Y, BW ./ 1e6);
colormap(jet);
view([0 90]);
xlim([Ln(1), Ln(end)]);
colorbar;

% Save the figure
set(gcf, 'Units', 'inches');
set(gcf, 'Position', [1 1 9 6]);
set(gcf, 'PaperPositionMode', 'auto');
print(h, '-dtiff', '-r150', sprintf('Plots_BW_%.0fdB_%.1fmW.tif', ...
    Av_dB, Pwr.*1e3));

% Find the best design
[BW_max, idx_max] = max(BW(:));
gmid_nmax = Y(idx_max);
Ln_max = X(idx_max);

[Area_max, BW_max, Wn_max, Ln_max, Wp_max, Lp_max] = ...
    CS_PMOS_Load_function(Pwr, Av_dB, C_L, Vdd, k, gmid_nmax, Ln_max);

% Print the results
disp(sprintf('\nDesign Summary of maximum BW'));
disp(sprintf('-----'));
disp(sprintf('BW = %.3f MHz\tArea = %.3f um^2', BW_max ./1e6, Area_max));
disp(sprintf('Wn = %.3f um\t\tWp = %.3f um', Wn_max, Wp_max));
disp(sprintf('Ln = %.3f um\t\tLp = %.3f um', Ln_max, Lp_max));

```

## CS\_PMOS\_Load\_function.m

```
%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%
% original script:
% Drew Hall
% EE 214 (Winter 2011)
% 18 Jan 2011
%
% Design of common source amplifier with PMOS load using the gm/id design
% methodology.
%
% modified script:
% Claudio Talarico
% EE406 (Fall 2021)
% Adapted to use toolkit v.2_3
% 08 Aug. 2021
%
%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%
function [Area, BW, Wn, Ln, Wp, Lp] = CS_PMOS_Load_function(Pwr, Av_dB, C_L, Vdd, k,
gm_id_n, Ln)

% path to lookup functions and technology files
addpath('/usr/class/gmidLUTs;/usr/class/gmidTECHs')

% Load technology files
load('180nch.mat');
load('180pch.mat');

%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%
% Calculations
%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%

Av = 10^(Av_dB/20);
id = Pwr/Vdd;      % Use all the available current

% Calculate the transconductances
gm_n = gm_id_n*id;
gm_id_p = gm_id_n * k;
gm_p = gm_id_p*id;

% Calculate the length of each transistor based on the gain
R = Av / gm_n;
ro_n = look_up(nch, 'GM_GDS', 'GM_ID', gm_id_n, 'L', Ln) / gm_n;
ro_p_min = 1*R*ro_n/(ro_n-R);

gm_gds_p_min = gm_p*ro_p_min;

gm_gds_vec = look_up(pch, 'GM_GDS', 'GM_ID', gm_id_p, 'L', pch.L);
M = gm_gds_vec >= gm_gds_p_min;

% if there is no length satisfying ro_p_min we must set Lp to NaN
if(~M)
    Lp = NaN;
else
    Lp = min(pch.L(M)); % minimum length satisfying ro_p_min
end

% Check to see if we cannot achieve this gain regardless of sizing
if(ro_p_min < 0 || isnan(Lp))
    Area = -inf; BW = -inf; Wn = 0; Ln = 0; Wp = 0; Lp = 0;
    return;
end

ro_p = look_up(pch, 'GM_GDS', 'GM_ID', gm_id_p, 'L', Lp) / gm_p;
```

```

% Size the transistors
Wn = id / look_up(nch, 'ID_W', 'GM_ID', gmid_n, 'L', Ln);
Wp = id / look_up(pch, 'ID_W', 'GM_ID', gmid_p, 'L', Lp);

% Calculate the capacitances
wT_n = look_up(nch, 'GM_CGG', 'GM_ID', gmid_n, 'L', Ln);
Cgg_n = gm_n / wT_n;
wT_p = look_up(pch, 'GM_CGG', 'GM_ID', gmid_p, 'L', Lp);
Cgg_p = gm_p / wT_p;

% since we already know the transistors width
Cdd_n = Wn*look_up(nch, 'CDD_W', 'GM_ID', gmid_n, 'L', Ln);
Cdd_p = Wp*look_up(pch, 'CDD_W', 'GM_ID', gmid_p, 'L', Lp);
Cgs_n = Wn*look_up(nch, 'CGS_W', 'GM_ID', gmid_n, 'L', Ln);
Cgs_p = Wp*look_up(pch, 'CGS_W', 'GM_ID', gmid_p, 'L', Lp);
Cgd_n = Wn*look_up(nch, 'CGD_W', 'GM_ID', gmid_n, 'L', Ln);
Cgd_p = Wp*look_up(pch, 'CGD_W', 'GM_ID', gmid_p, 'L', Lp);

% alternatively, if we didn't know the width we could have used the
% following syntax:
% This is just for sake of showing off different syntax options :-))

% Cdd_Cgg_n = look_up(nch, 'CDD_CGG', 'GM_ID', gmid_n, 'L', Ln);
% Cdd_n = Cdd_Cgg_n*Cgg_n
% Cdd_Cgg_p = look_up(pch, 'CDD_CGG', 'GM_ID', gmid_p, 'L', Lp);
% Cdd_p = Cdd_Cgg_p*Cgg_p
% Cgd_Cgg_n = look_up(nch, 'CGD_CGG', 'GM_ID', gmid_n, 'L', Ln);
% Cgd_n = Cgd_Cgg_n*Cgg_n
% Cgs_n = Cgg_n - Cgd_n
% Cgd_Cgg_p = look_up(pch, 'CGD_CGG', 'GM_ID', gmid_p, 'L', Lp);
% Cgd_p = Cgd_Cgg_p*Cgg_p
% Cgs_p = Cgg_p - Cgd_p
% Cdb_n = Cdd_n - Cgd_n
% Cdb_p = Cdd_p - Cgd_p

% Compute the total capacitance at the output node [F]
Ctot = C_L + Cdd_n + Cdd_p; % Total capacitance at output node [F]

%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%
% Metrics
%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%
Area = Wn*Ln + Wp*Lp; % [um^2]
BW = 1/(2*pi) * 1/(R*Ctot); % [Hz]

return


```

# Design Script result

**Spec:** *Power = 2mW, DC gain = 30dB*

Design Summary of maximum BW

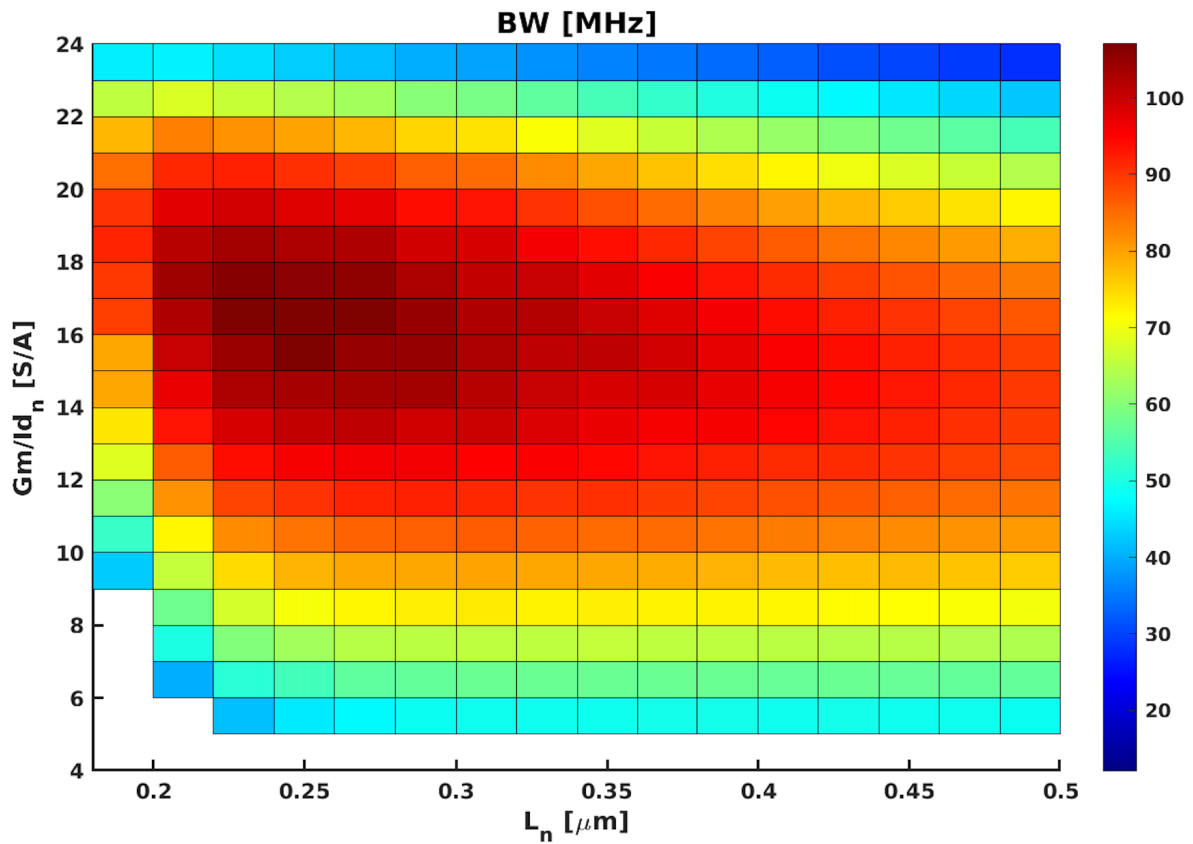BW = 107.160 MHz      Area = 58.914  $\mu\text{m}^2$   
Wn = 147.984  $\mu\text{m}$       Wp = 109.824  $\mu\text{m}$   
Ln = 0.220  $\mu\text{m}$       Lp = 0.240  $\mu\text{m}$







## SPICE Netlist

```
** file: cs_activeload.sp
*
.netrc
.option nomod noascii
.option compat      * HSPICE model and netlist compatibility
.option POST_VERSION=9601 post=1 * HSPICE database format
.option aex         * save measurements in .aex file

.include /usr/class/models/ee214_hspice.mod

.param Wp=110u Lp=0.24u Wn=148u Ln=0.22u id=1.1m

.temp 27

* circuit
mpb1 bp bp vdd vdd pch W='Wp' L='Lp'
mpb2 bn bp vdd vdd pch W='Wp' L='Lp'
mnb1 bn bn 0 0 nch W='Wn' L='Ln'
Cbp1 bp vdd 100u
Cbn1 bn 0 100u


mp out bp vdd vdd pch W='Wp' L='Lp'
mn out in 0 0 nch W='Wn' L='Ln'
CL out 0 500f

vdd vdd 0 DC 1.8
vin in bn AC 1 DC 0
ib bp 0 'id'

* Analysis
.op
.AC dec 1000 10K 10G
.PZ v(out)

* plots and measurements
.probe AC v(out)
.defwave v_out=vm(out)
.extract ac label=gain_db max(vdb(out))
.extract ac label=f3db 'crossing(vdb(out), gain_db-3)'

.end
```

 

## .OP Simulation (vs. calculated)



	Simulated					Calculated	%Error
	MPB1	MPB2	MNB1	MP	MN		
MODEL	PCH	PCH	NCH	PCH	NCH		
ID	-1.1000E-03	-1.2122E-03	1.2122E-03	-1.2122E-03	1.2122E-03	1.1mA, 1.1mA	+10.2%
VGS	-7.0462E-01	-7.0462E-01	5.9125E-01	-7.0462E-01	5.9125E-01		
VDS	-7.0462E-01	-1.2087E+00	5.9125E-01	-1.2087E+00	5.9125E-01		
VTH	-4.7330E-01	-4.7110E-01	4.8196E-01	-4.7110E-01	4.8196E-01		
VDSAT	-2.0134E-01	-2.0303E-01	9.7884E-02	-2.0303E-01	9.7884E-02		
GM	8.7809E-03	9.3811E-03	1.8861E-02	9.3811E-03	1.8861E-02	8.9mS, 17.8mS	+ 5.9%
GDS	2.5377E-04	2.0211E-04	3.9114E-04	2.0211E-04	3.9114E-04	213.53uS, 347.63uS	+12.5%
Cdd	1.5492E-13	1.4621E-13	1.7900E-13	1.4621E-13	1.7900E-13	155.07fF, 180.16fF,	-5.71%
Cgg	2.8449E-13	2.8445E-13	3.3935E-13	2.8445E-13	3.3935E-13		
Cgd	-7.1863E-14	-7.1833E-14	-7.1576E-14	-7.1833E-14	-7.1576E-14		
Cgs	-2.0556E-13	-2.0538E-13	-2.4911E-13	-2.0538E-13	-2.4911E-13		
Region	Saturation	saturation	Saturation	saturation	saturation		
VTH_D	2.3133E-01	2.3353E-01	1.0930E-01	2.3353E-01	1.0930E-01		

## .PZ Simulation (vs. calculated)

Simulated			Calculated	%Error
POLES	REAL PART	IMAGINARY PART		
1	-1.137972e+08	-0.000000e+00	106.93MHz	+6.42%
ZEROS	REAL PART	IMAGINARY PART		
1	4.089441e+10	-0.000000e+00		

## .AC Simulation (vs. calculated)


Simulated	Calculated	%Error
TEMPERATURE = 2.7000E+01 Celsius		
gain_db = 3.0042E+01	30 dB	+0.14%
f3db = 1.1353E+08	106.93MHz	+6.17%

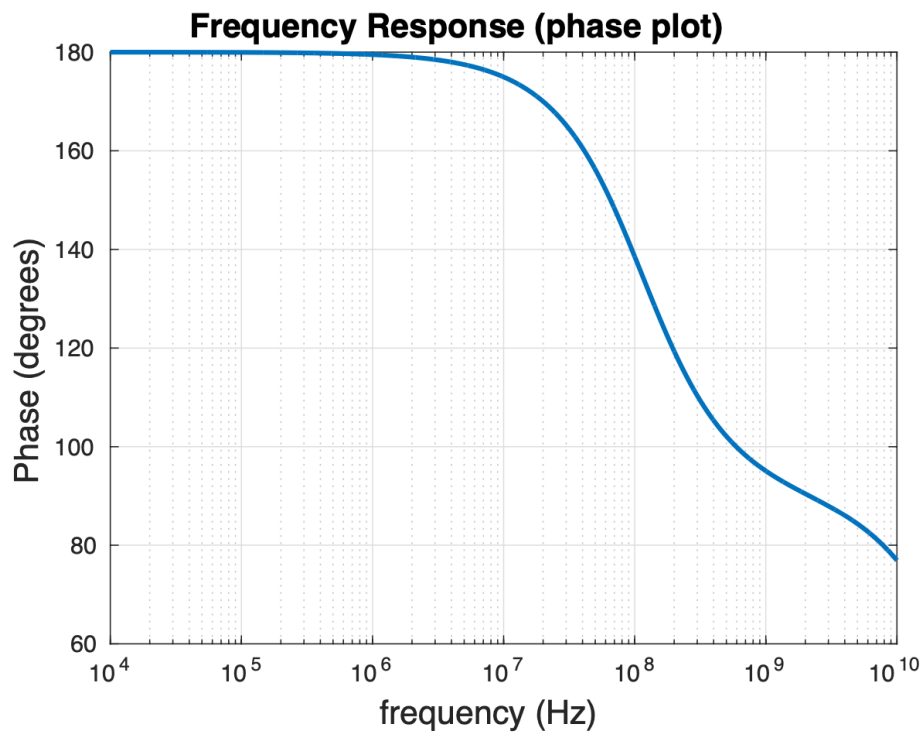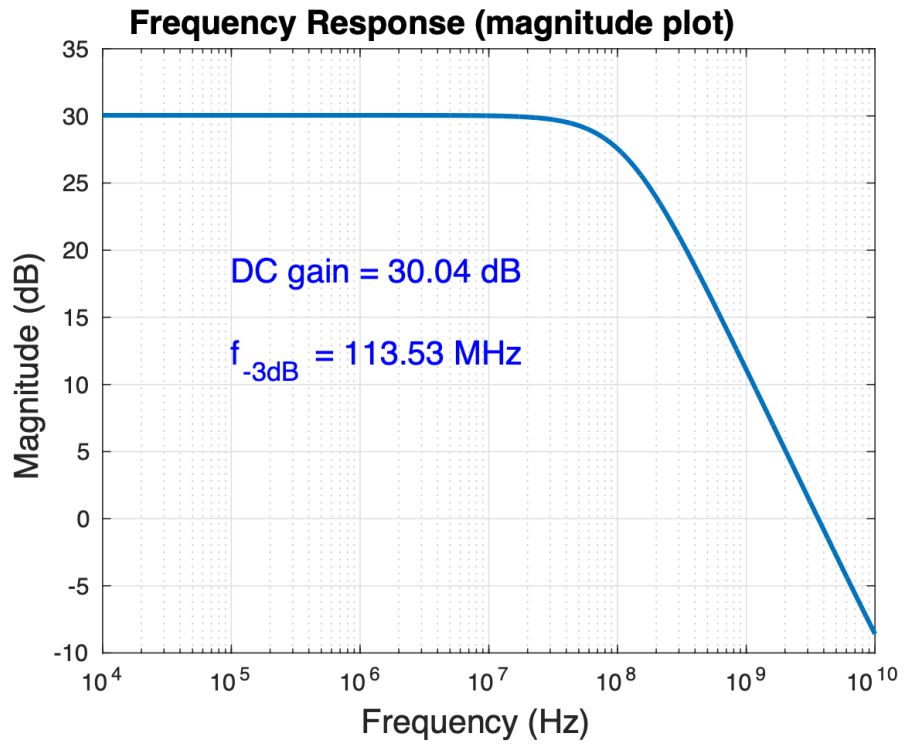

## Observations

- Using the gm/id design methodology, we can easily hit our design target without resorting to spice monkeying
- If we want, we can resolve the small (~10%) discrepancies through “educated” tweaking
  - i.e, we know what knobs to adjust and what to expect, we do not do random tweaking (monkeying!)
  - the simulated current was about 10.2% higher than expected. This resulted in our  $g_m$  also being slightly higher. Ultimately, this happened because of the  $V_{ds}$  dependence in our current mirror. Mbp1 had exactly 1.1 mA whereas mbp2 had 1.21mA.

	MPB1	MPB2	MNB1	MP	MN
MODEL	PCH	PCH	NCH	PCH	NCH
ID	1.1000E-03	-1.2122E-03	1.2122E-03	-1.2122E-03	1.2122E-03
VGS	-7.0462E-01	-7.0462E-01	5.9125E-01	-7.0462E-01	5.9125E-01
VDS	7.0462E-01	-1.2087E+00	5.9125E-01	-1.2087E+00	5.9125E-01
Region	Saturation	saturation	Saturation	saturation	saturation

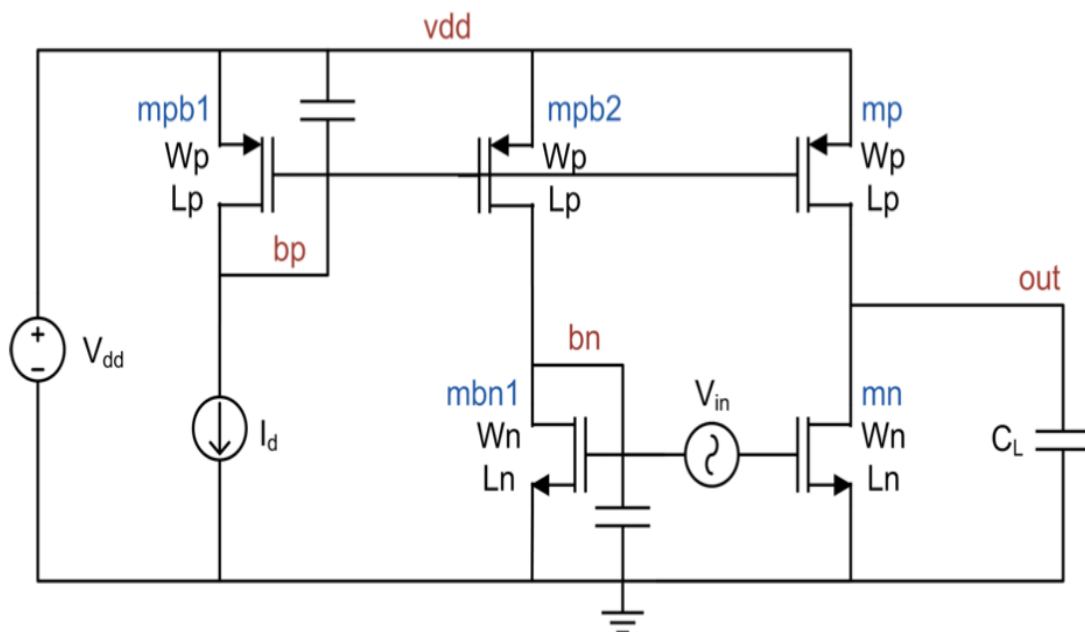


## Design Space Exploration: increased power budget to 20 mW and left gain unchanged to 30 dB

**Spec:** *Power = 20mW, DC gain = 30dB*

-----  
Design Summary of maximum BW  
-----

BW = 283.757 MHz	Area = 303.344 $\mu\text{m}^2$
Wn = 671.476 $\mu\text{m}$	Wp = 463.188 $\mu\text{m}$
Ln = 0.300 $\mu\text{m}$	Lp = 0.220 $\mu\text{m}$

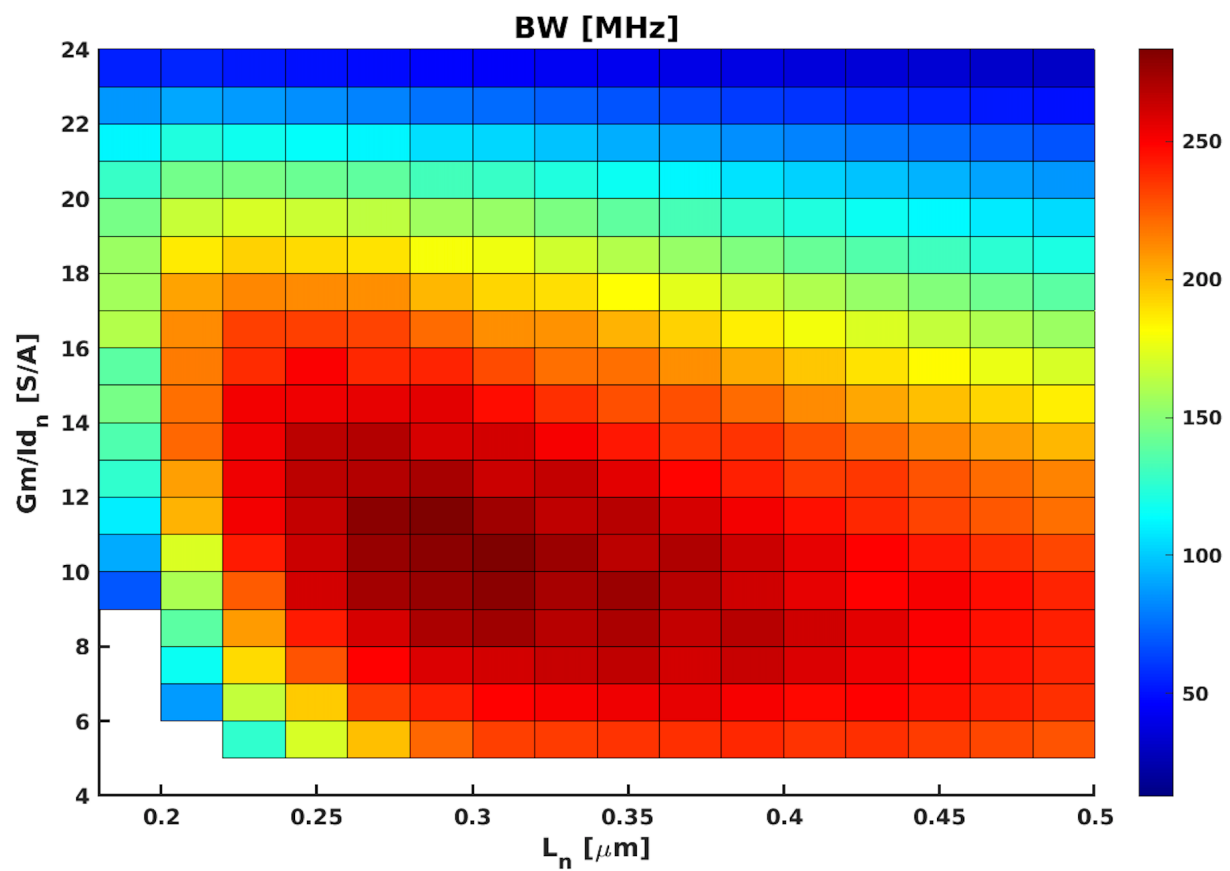


## Design Space Exploration: increased power budget to 20 mW and reduced gain to 10 dB

**Spec:** *Power = 20mW, DC gain = 10dB*

-----  
Design Summary of maximum BW  
-----

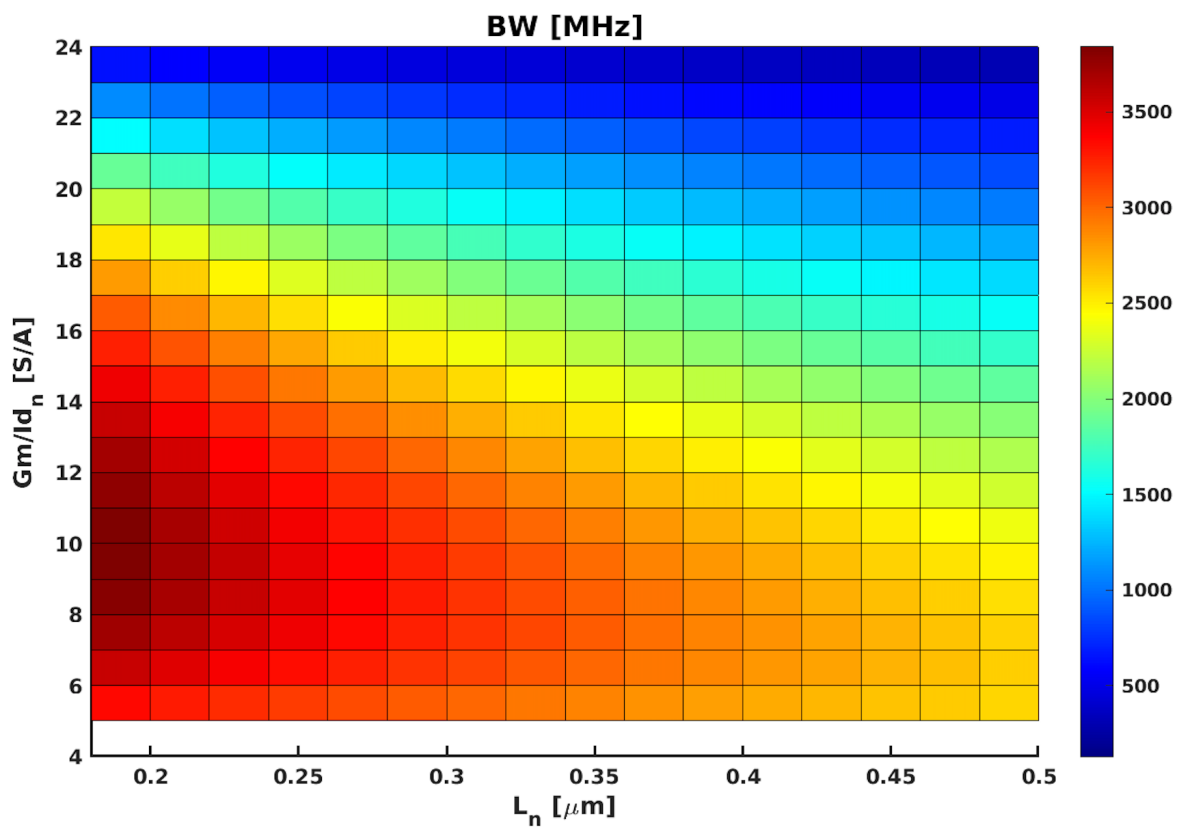BW = 3844.287 MHz      Area = 111.139  $\mu\text{m}^2$   
Wn = 318.590  $\mu\text{m}$       Wp = 298.850  $\mu\text{m}$   
Ln = 0.180  $\mu\text{m}$       Lp = 0.180  $\mu\text{m}$




## Design Space Exploration: increased power budget to 20 mW and increased gain to 34 dB

**Spec:** *Power = 20mW, DC gain = 34dB*

-----  
Design Summary of maximum BW  
-----

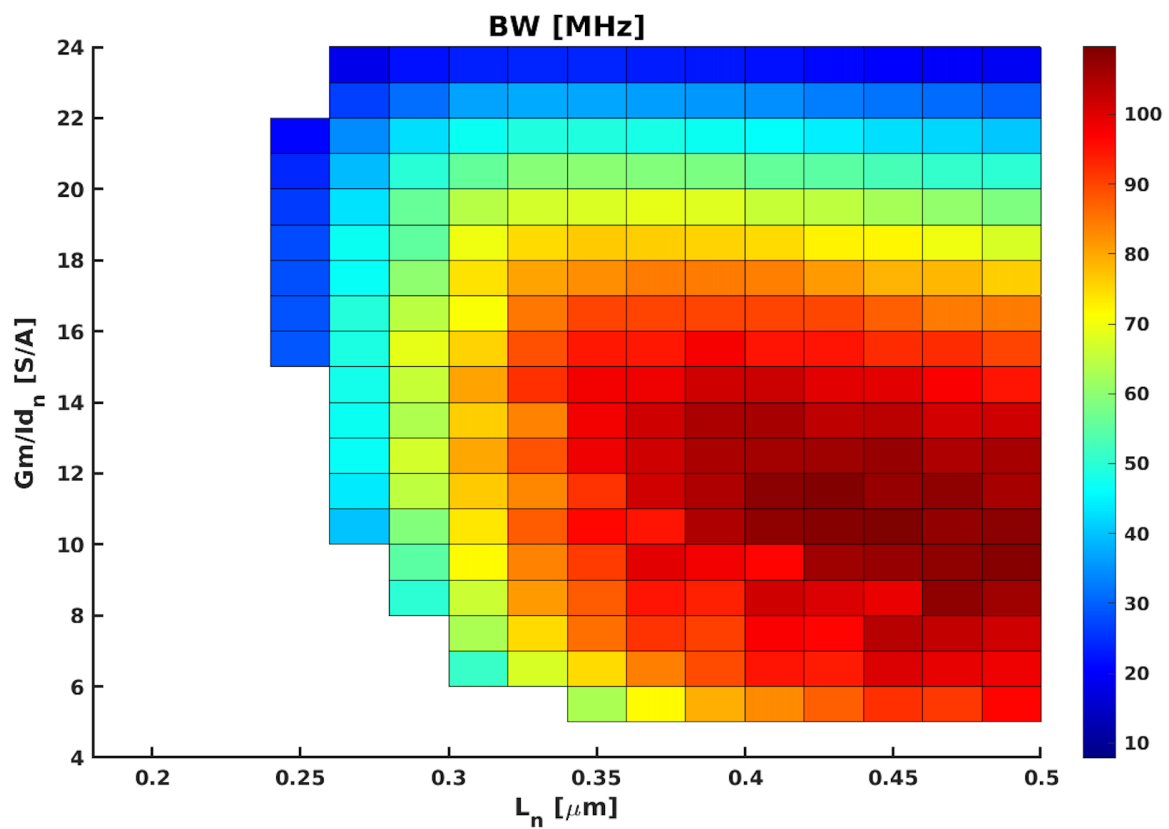BW = 109.743 MHz      Area = 886.469  $\mu\text{m}^2$   
Wn = 1011.829  $\mu\text{m}$       Wp = 1050.628  $\mu\text{m}$   
Ln = 0.440  $\mu\text{m}$       Lp = 0.420  $\mu\text{m}$



## Design of Common Source with PMOS Load– Summary

- Using the precomputed lookup tables and the gm/id design methodology, we created an optimization script for a common source with a PMOS load
- In this example, we optimized for maximum BW, but we could easily have optimized for any other parameter (area, power, some weighted combination, etc.)
- gm/id is a powerful design tool that serves as an enabler for deep submicron processes where short channel effects make the square law equation useless for design
- Note: It is important to realize the limitations of the gm/id design methodology! It assumes a small signal model of the device (ie: it assumes the devices can be linearized around some operating point). It has limitations when designing mixers, power amplifiers, switches, etc.

## MATLAB script for design analysis and simulation plots

```
% C. Talarico
% File: cs_analysis_and_plots.m

clearvars; close all; clc;

%-----%
% Simulation Results %
%-----%
addpath('/usr/local/MATLAB/HspiceToolbox');
x = loadsig('./spiceout_cs_activeload/cs_activeload.ac0')
lssig(x)

freq = evalsig(x, 'HERTZ');
vout = evalsig(x, 'v_out');
mag = abs(vout);
magdb = 20*log10(mag);
phase = (180/pi)*unwrap(angle(vout));

gain = max(magdb)
f3db = 1e-6*interp1(magdb, freq, magdb(1)-3, 'spline')

% Plots
figure(1);
semilogx(freq, magdb, 'linewidth', 2);
grid;
```



```

xlabel('Frequency (Hz)', 'fontsize',14);
ylabel('Magnitude (dB)', 'fontsize', 14);
title('Frequency Response (magnitude plot)', 'fontsize', 14)
% annotate the plot
str1 = sprintf('DC gain = %.2f dB\n', gain);
str2 = sprintf('f_{-3dB} = %.2f MHz', f3db);
str = {str1, str2};
text(1e5,15, str, 'color', 'b', 'fontsize', 14);

figure(2)
semilogx(freq, phase, 'linewidth',2);
grid;
xlabel('frequency (Hz)', 'fontsize',14);
ylabel('Phase (degrees)', 'fontsize',14);
title('Frequency Response (phase plot)', 'fontsize',14);

print(figure(1), '-dpasc', 'Plot_CS_activeload.ps');
print(figure(2), '-append', '-dpasc', 'Plot_CS_activeload.ps');

%-----%
%   Calculations   %
%-----%
addpath('/usr/class/gmidLUTs', '/usr/class/gmidTECHs');
load('180nch.mat');
load ('180pch.mat');

Pwr = 2e-3;           % Power dissipation [Watts]
Av_dB = 30;          % Gain [dB]           (Maximum 35 with this arch)
C_L = 500e-15;       % Load capacitance [Farads]
Vdd = 1.8;           % Supply Voltage [Volts]

Ln = 0.220           % um
Wn = 148
Lp = 0.240
Wp = 110

Id = Pwr/Vdd
Av = 10^(Av_dB/20)
JD_n = Id/Wn;
JD_p = Id/Wp;
gmid_n = look_up(nch, 'GM_ID', 'ID_W', JD_n, 'L', Ln)
gm_n = gmid_n*Id
gmid_p = look_up(pch, 'GM_ID', 'ID_W', JD_p, 'L', Lp)
gm_p = gmid_p*Id
gmgds_n = look_up(nch, 'GM_GDS', 'GM_ID', gmid_n, 'L', Ln)
gds_n = gm_n/gmgds_n
gmgds_p = look_up(pch, 'GM_GDS', 'GM_ID', gmid_p, 'L', Lp)
gds_p = gm_p/gmgds_p

Rtot = 1/(gds_n + gds_p)
Cdd_n = Wn*look_up(nch, 'CDD_W', 'GM_ID', gmid_n, 'L', Ln)
Cdd_p = Wp*look_up(pch, 'CDD_W', 'GM_ID', gmid_p, 'L', Lp)
Ctot = C_L + Cdd_n + Cdd_p

BW = 1/(2*pi*Rtot*Ctot)

```

### Simulated Results

-----  
gain = 30.0416 (dB)  
f3db = 113.5282 (MHz)

### Calculated Results

-----  
Ln = 0.2200 (um)  
Wn = 148 (um)  
Lp = 0.2400 (um)  
Wp = 110 (um)  
Id = 0.0011 (A)  
Av = 31.6228 (V/V)  
gmid\_n = 16.0028 (S/A)  
gm\_n = 0.0178 (S)  
gmid\_p = 8.0083 (S/A)  
gm\_p = 0.0089 (S)  
gmgds\_n = 51.1487 (S)  
gds\_n = 3.4763e-04 (S)  
gmgds\_p = 41.6721 (S)  
gds\_p = 2.1353e-04 (S)  
Rtot = 1.7820e+03 (ohm)  
Cdd\_n = 1.8016e-13 (Farad)  
Cdd\_p = 1.5507e-13 (Farad)  
Ctot = 8.3523e-13 (Farad)  
BW = 1.0693e+08 (Hz)

## A faster MATLAB implementation of the Design script

The “original” MATLAB implementation of the design script ( `Design_CS_PMOS_Load_Sweep.m` + `CS_PMOS_Load_function.m` ) takes about 913 seconds of run time.

“Recoding” the script allows to reduce the run time to about 26 seconds (about 35x):

### `cs_activeLoad_pm.m`

```
% gm/id design of Common Source with PMOS Load
% Patrick Munar
% adapted from Drew Hall (Stanford)
% Gonzaga University
% July 30th, 2021
% file: cs_activeLoad_pm.m

tic

clearvars;
close all;

addpath('/usr/class/gmidLUTs;/usr/class/gmidTECHs');

% Load transistor data
load 180nch.mat;
load 180pch.mat;

nmos = nch;
pmos = pch;

% Design Specifications
VDD = 1.8;           % Voltage source [V]
AV0_dB = 30;        % Gain in [dB]
AV0 = 10^(AV0_dB/20); % Gain in [V/V]
CL = 500*1e-15;     % Load capacitance [fF]
P = 2*1e-3;         % Power dissipated [mW]
Ratio = 1/2;        % ratio between gm_IDp : gm_IDn

% Design Choices
Ln = [0.18:0.02:0.5]; % NMOS transistor length [um]
gm_IDn = [5:1:24];    % NMOS inversion levels [S/A]

% Assumptions and Equations:
% Use small-signal model to derive expressions for BW, Gain, and total
% resistance/capacitance

% Calculating remaining component values based on assumptions and equations
ID = P/VDD; % Drain current [mA]

% Pre-allocation of variables for efficiency
Area = zeros(length(gm_IDn),length(Ln));
BW = zeros(length(gm_IDn),length(Ln));
Lp = zeros(1,length(Ln));
```

```

Wn          = zeros(length(gm_IDn),length(Ln));
Wp          = zeros(length(gm_IDn),length(Ln));
BW_max     = 0;

% Determining other parameters via lookup tables
for i = 1:length(gm_IDn)
    for j = 1:length(Ln)
        % Determine NMOS and PMOS transconductance and inversion levels
        gmn = gm_IDn(i)*ID;          % NMOS transconductance [S]
        gm_IDp = gm_IDn(i)*Ratio;    % PMOS inversion levels [S/A]
        gmp = gm_IDp*ID;            % PMOS transconductance [S]
        RT = AV0/gmn;                % Total resistance [kohms]

        % Determine minimum and sample PMOS intrinsic gain
        ron = look_up(nmos, 'GM_GDS', 'GM_ID', gm_IDn(i), 'L', Ln(j))/gmn;
        % NMOS output resistance [kohms]
        rop_min = (RT*ron)/(ron-RT);
        % PMOS output resistance [kohms]
        gmrop_min = gmp*rop_min;
        % PMOS intrinsic gain
        gmrop_ref = look_up(pmos, 'GM_GDS', 'GM_ID', gm_IDp, 'L', pmos.L);
        % Reference PMOS intrinsic gain

        % Checks if the samples are greater than or equal to the minimum
        % PMOS intrinsic gain
        gmrop_test = gmrop_min <= gmrop_ref;

        % Assigns appropriate PMOS length
        for k = 1:length(gmrop_test)
            if (gmrop_test(k) == true)
                Lp(j) = min(pch.L(k));
                break
            else
                Lp(j) = NaN;
            end
        end
    end

    % Checks if it is impossible to properly size the PMOS transistor
    if (rop_min < 0) || (isnan(Lp(j)))
        Area(i,j) = -inf;
        BW(i,j) = -inf;
        Wn(i,j) = 0;
        Wp(i,j) = 0;
        Lp(j) = 0;
        continue
    end

    rop = look_up(pmos, 'GM_GDS', 'GM_ID', gm_IDp, 'L', Lp(j))/gmp;
    %PMOS output resistance [kohms]

    % Size NMOS and PMOS transistors
    Wn(i,j) = ID/look_up(nmos, 'ID_W', 'GM_ID', gm_IDn(i), 'L', Ln(j));
    % NMOS transistor width [um]
    Wp(i,j) = ID/look_up(pmos, 'ID_W', 'GM_ID', gm_IDp, 'L', Lp(j));
    % PMOS transistor width [um]

```

```

% Calculate internal capacitances
CGGn = gmn/look_up(nmos, 'GM_CGG', 'GM_ID', gm_IDn(i), 'L', Ln(j));
% Total NMOS gate capacitance
CDDn = CGGn*look_up(nmos, 'CDD_CGG', 'GM_ID', gm_IDn(i), 'L', Ln(j));
% Total NMOS drain capacitance
CGGp = gmp/look_up(pmos, 'GM_CGG', 'GM_ID', gm_IDp, 'L', Lp(j));
% Total PMOS gate capacitance
CDDp = CGGp*look_up(pmos, 'CDD_CGG', 'GM_ID', gm_IDp, 'L', Lp(j));
% Total PMOS drain capacitance
CT = CL + CDDn + CDDp;
% Capacitance at the output node

% Calculate total transistor area and bandwidth
Area(i,j) = Wn(i,j)*Ln(j) + Wp(i,j)*Lp(j); % Transistor area [um]^2
BW(i,j) = 1/(2*pi*RT*CT); % Bandwidth [MHz]


% Determine optimum amplifier design
BW_test = BW(i,j);
if (BW_test > BW_max) % Updates variables if previous BW is exceeded
    BW_max = BW_test;
    Area_max = Area(i,j);
    Ln_max = Ln(j);
    Lp_max = Lp(j);
    Wn_max = Wn(i,j);
    Wp_max = Wp(i,j);
end
end
end

% Plot results
specifications = "Gain = " + AV0_dB + " dB, Power = " + P*1e3 + " mW";
figure('Name', 'CS Amplifier with PMOS Load', 'NumberTitle', 'off');
[X,Y] = meshgrid(Ln, gm_IDn);
surf(X,Y,BW*1e-6);
xlabel('NMOS Transistor Length [um]');
ylabel('Inversion Level [S/A]');
title('BW Optimization', specifications);
c = colorbar; c.Label.String = 'BW [MHz]';
colormap(jet);
view([0 90]);
xlim([Ln(1),Ln(end)]);

% Displaying results
fprintf('\nBW Optimization for CS Amplifier with PMOS Load\n')
fprintf('-----\n');
fprintf('Maximum Bandwidth: %3.2f [MHz]\n', BW_max*1e-6);
fprintf('Optimum Amplifier Area: %3.2f [um^2]\n', Area_max);
fprintf('-----\n');
fprintf('NMOS Dimensions (Ln x Wn): %1.3f [um] x %3.2f\n', Ln_max, Wn_max);
fprintf('PMOS Dimensions (Lp x Wp): %1.3f [um] x %3.2f\n', Lp_max, Wp_max);

toc

```

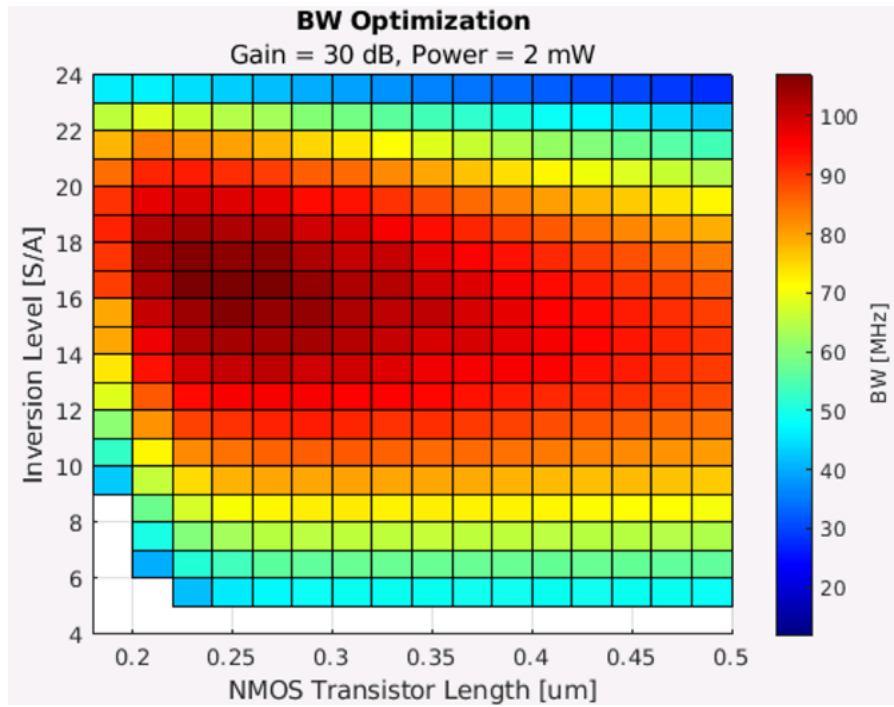


BW Optimization for CS Amplifier with PMOS Load

-----  
 Maximum Bandwidth: 107.16 [MHz]  
 Optimum Amplifier Area: 58.91 [um<sup>2</sup>]  
 -----

NMOS Dimensions (Ln x Wn): 0.220 [um] x 147.98 [um]  
 PMOS Dimensions (Lp x Wp): 0.240 [um] x 109.82 [um]  
 Elapsed time is 26.273401 seconds.

 If instead of using the technology files generated using HSPICE (180nch.mat and 180pch.mat) we use the technology files generated using ELDO (180nch\_e.mat, 180pch\_e.mat) the results obtained are slightly different (the % error on the estimated BW is about 0.4%)



BW Optimization for CS Amplifier with PMOS Load

-----  
Maximum Bandwidth: 106.75 [MHz]  
Optimum Amplifier Area: 60.98 [um<sup>2</sup>]  
-----  
NMOS Dimensions (Ln x Wn): 0.240 [um] x 163.35 [um]  
PMOS Dimensions (Lp x Wp): 0.220 [um] x 98.97 [um]  
Elapsed time is 23.705611 seconds.

## .OP Simulations

	HSPICE TECH FILES		ELDO TECH FILES	
	MP	MN	MP	MN
	<b>Lp=0.24, Wp=110u</b>	<b>Ln=0.22u, Wp=148u</b>	<b>Lp=0.22u, Wp=99u</b>	<b>Ln=0.24u, Wn=163u</b>
MODEL	PCH	NCH	PCH	NCH
ID	-1.2122E-03	1.2122E-03	-1.2244E-03	1.2244E-03
VGS	-7.0462E-01	5.9125E-01	-7.0982E-01	5.9109E-01
VDS	-1.2087E+00	5.9125E-01	-1.2089E+00	5.9109E-01
VTH	-4.7110E-01	4.8196E-01	-4.7677E-01	4.7836E-01
VDSAT	-2.0303E-01	9.7884E-02	-2.0297E-01	9.9923E-02
GM	9.3811E-03	1.8861E-02	9.4551E-03	1.8900E-02
GDS	2.0211E-04	3.9114E-04	2.2750E-04	3.5229E-04
Cdd	1.4621E-13	1.7900E-13	1.3166E-13	1.9725E-13
Cgg	2.8445E-13	3.3935E-13	2.4220E-13	3.9661E-13
Region	saturation	saturation	saturation	saturation
VTH_D	2.3353E-01	1.0930E-01	2.3305E-01	1.1273E-01

## .AC Simulations

	HSPICE TECH FILES	ELDO TECH FILES
TEMPERATURE	27 Celsius	27 Celsius
gain_db	3.00416E+01	3.0265E+01
f3db	1.135282E+08	1.1105E+08